

Basic Definitions:


Voltage: The potential difference btw. any two points in an electrical circuit.

Current: The amount of charge flow btw. any two connected points in a circuit.

Resistance: The amount of opposition to current flow.

Resistor: A circuit element causing resistance.

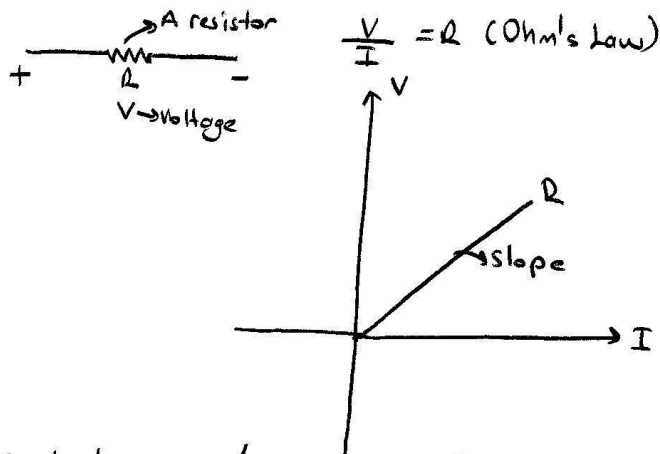Ohm's Law: The relation btw. the voltage drop resistor and current flow over the same resistor is a linear relation.



Conductance: $\frac{1}{\text{Resistance}}$ (siemens)

$R \rightarrow \text{Ohm}$


$I \rightarrow \text{Amper}$

$V \rightarrow \text{Volt}$

Simple Circuit Theorems


Kirchoff's Voltage Law (KVL):

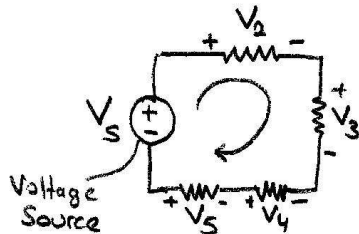The algebraic sum of all the voltage drops over closed planer circuit is 0.



Applying KVL:

$$-V_S + V_2 + V_3 - V_4 - V_5 = 0$$

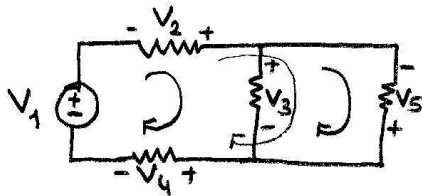

Applying KVL:

$$-V_1 - V_2 + V_3 + V_4 = 0 \quad \left. \begin{array}{l} \uparrow \\ \downarrow \end{array} \right\} \text{Same!}$$

$$V_1 + V_2 - V_3 - V_4 = 0$$


$$-V_3 - V_5 = 0 \Rightarrow V_3 = -V_5$$

$$-V_1 - V_2 - V_5 + V_4 = 0$$


Kirchoff's Current Law:

The sum of incoming currents to a point in a circuit is equal to the sum of outgoing currents from the same point.

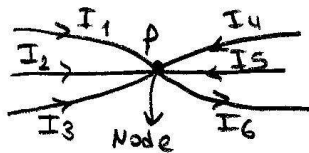Point (Node): Points where two or more circuit elements are connected to each other.



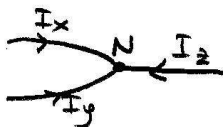
$$\underbrace{I_1 + I_2 + I_3}_{\text{incoming}} + I_4 + I_5 = \underbrace{I_6}_{\text{outgoing}}$$



$$I_x + I_y + I_z = 0$$

Series Connection of Resistors



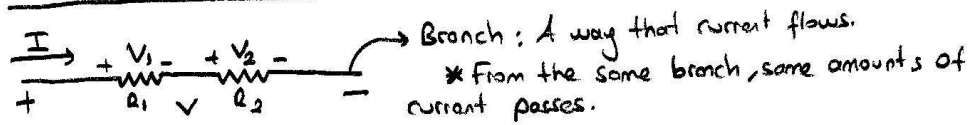


$$V = V_1 + V_2$$


$$R_T I = R_1 I + R_2 I$$

$$R_T = R_1 + R_2$$


Parallel Connection of Resistors

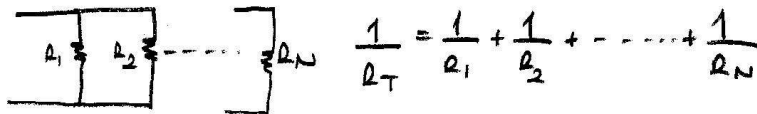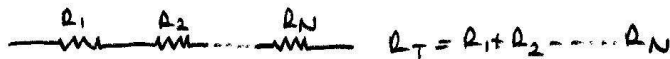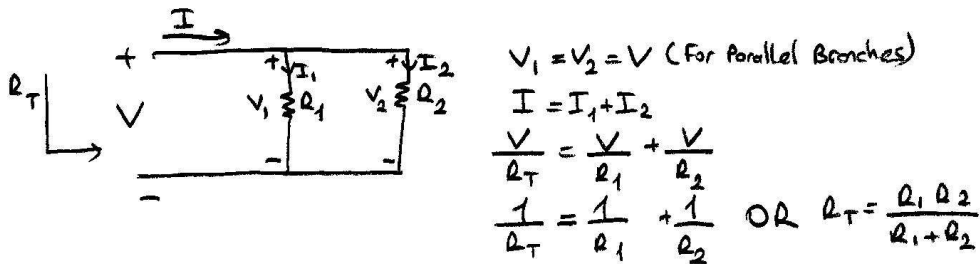




Voltage Division in Series Circuit

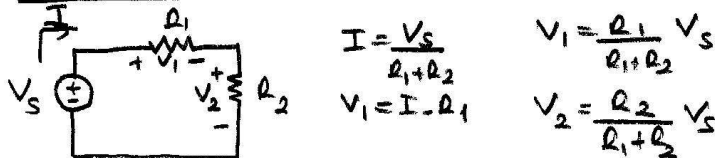

Current Division in Parallel Circuit

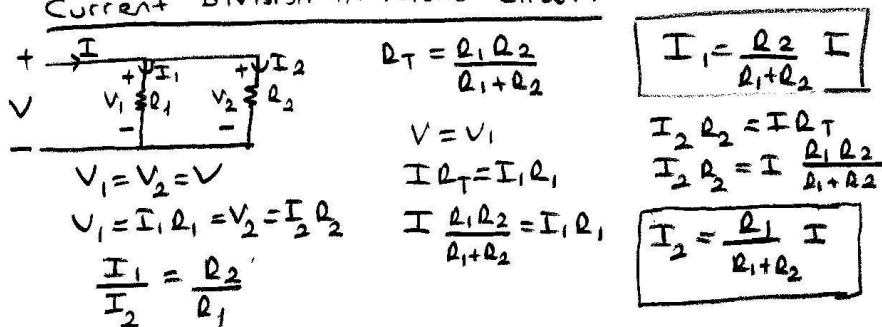

Node Voltage Method

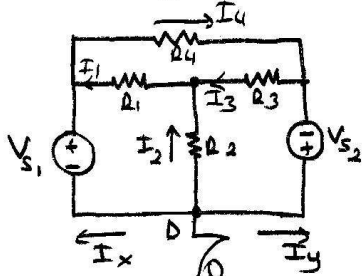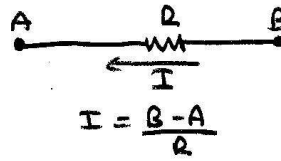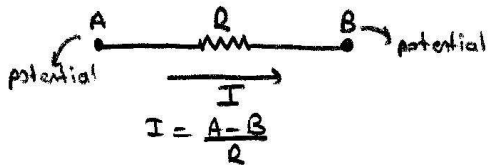

$$\begin{aligned} A-D &= V_{s1} & C-D &= -V_{s2} \\ A-D &= V_{s1} & C &= -V_{s2} \\ A &= V_{s1} \end{aligned}$$

- ① Assign voltage values to all the nodes
- ② Choose a node as the reference node
(Generally the nodes, which are close to the negative polarity of the sources are chosen) as the reference node
Reference Node = 0 Potential
- ③ If it's possible using the reference node determine potentials of other nodes.
A ✓ C ✓ D ✓
- ④ Assign currents to branches of the circuit.
- ⑤ Use KCL for the nodes where the potential is unknown.

$$I_2 + I_3 = I_1$$


$$\frac{D-B}{R_2} + \frac{C-B}{R_3} = \frac{B-A}{R_1} \quad \begin{aligned} D &= 0 \\ A &= V_{s1} \\ C &= -V_{s2} \end{aligned}$$

$$\boxed{\frac{-B}{R_2} + \frac{-V_{s2}-B}{R_3} = \frac{B-V_{s1}}{R_1}} \quad B \rightarrow \text{unknown (solve for B)}$$

$$I_x = I_2 - I_1 = \frac{A-C}{R_1} - \frac{B-A}{R_1}$$

$$I_y = I_3 - I_4 = \frac{C-B}{R_3} - \frac{A-C}{R_4}$$

Super Node

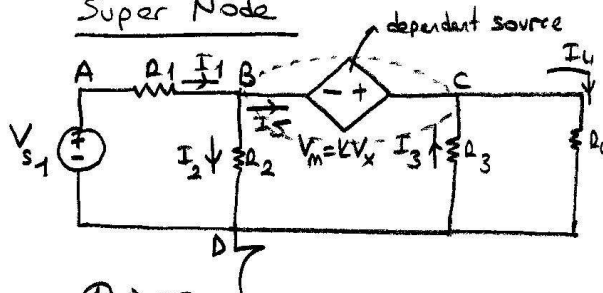

- ① $D=0$
- ② $A=V_{s1}$
 $V_m = KV_x$
- ③ $C-B = K(C-D)$
 $I_5 = I_1 - I_2 = I_4 - I_3$ (Super Node eq.)
 $I_1 + I_3 = I_2 + I_4$ (Some eq.)


If some voltage source exists btw. two nodes of a circuit that branch acts as super-node and node-voltage eq. is written accordingly.

$$I_1 + I_3 = I_2 + I_4$$

$$\textcircled{4} \frac{A-B}{R_1} + \frac{D-C}{R_2} = \frac{B-D}{R_2} + \frac{C-D}{R_4}$$

Mesh Current Method

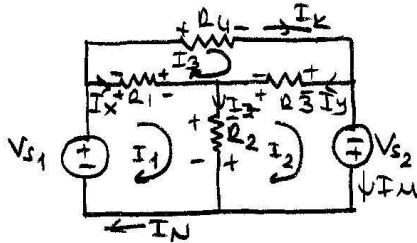Mesh: Directed current loop (clockwise direction)



loop current \neq branch current

- ① Assign mesh currents (loop currents) for all separate mesh.
- ② Determine polarity of circuit elements (except for the sources since they are directly) given according to mesh-current directions.
- ③ Use KVL to write voltage drops for each separate mesh.

$$\text{Mesh I} \rightarrow -V_{s1} + R_1(I_1 - I_3) + R_2(I_1 - I_2) = 0$$


$$\text{Mesh II} \rightarrow -V_{s2} + R_2(I_2 - I_1) + R_3(I_2 - I_3) = 0$$

$$\text{Mesh III} \rightarrow R_4 I_3 + R_3(I_3 - I_2) + R_1(I_3 - I_1) = 0$$


Solve for I_1, I_2, I_3 :

$I_u = I_2$	$I_x = I_1 - I_3$	branch currents
$I_w = I_1$	$I_y = I_2 - I_3$	
$I_k = I_3$	$I_z = I_1 - I_2$	

For Some Circuit

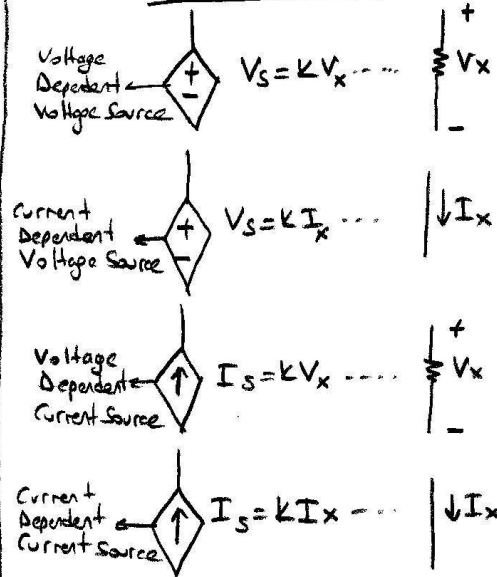

Super Mesh

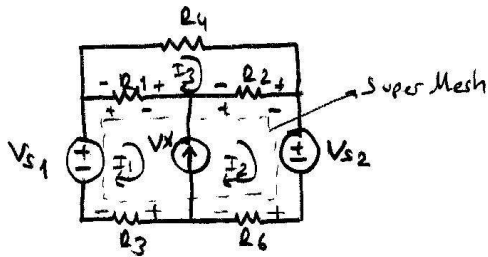

$$\text{Mesh I} \rightarrow -V_{s1} + R_1(I_1 - I_3) - V_x + R_3 I_1 = 0$$

$$\text{Mesh II} \rightarrow +V_{s2} + R_6(I_2) - V_x + R_2(I_2 - I_3) = 0$$

$$\text{Mesh III} \rightarrow R_4 I_3 + R_2(I_3 - I_2) + R_1(I_3 - I_1) = 0$$

Let's eliminate V_x using Mesh I and Mesh II:


Super Mesh Eq.

$$-V_{s1} + R_1(I_1 - I_3) + R_2(I_2 - I_3) + V_{s2} + R_6 I_2 + R_3 I_1 = 0$$

* If there exists a current source btw. two meshes, these two mesh behave a single mesh and a supermesh eq. is written as:

$$\boxed{I_s = I_2 - I_1} \quad **$$

Thevenin Equivalent Circuit

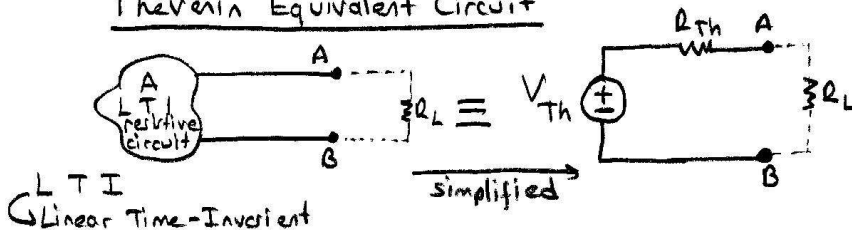


L T I
Linear Time-Invariant

V_{Th} = Open circuit voltage btw. A and B points

R_{Th} = Resistance btw A and B points.

For finding R_{Th}

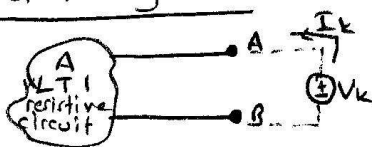


- 1 Kill all independent voltage-current sources.
* Killing voltage source \rightarrow Short that branch
* " " " " \rightarrow Open " "
- Put a source btw. A and B
Calculate the current " I_k "

$$R_{Th} = \frac{V_k}{I_k}$$

- 2 If no dependent source exist in the circuit, kill independent sources and then use series-parallel connection concepts of the resistors to find R_{Th} .


Norton Equivalent Circuit

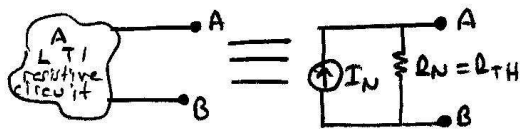

$I_N =$ short circuit current btw. A-B

$R_N = R_{Th} \begin{cases} \rightarrow R_{Thermin} \\ \rightarrow R_{Norton} \end{cases}$
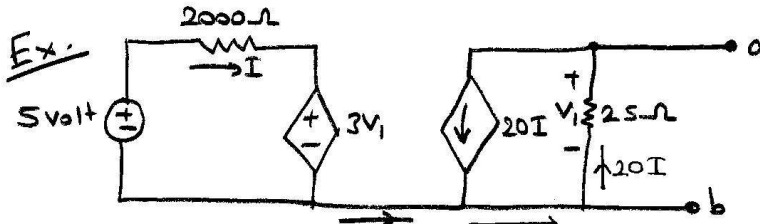
$$\textcircled{2} R_N = R_{Th} = \frac{V_{Th}}{I_N}$$



Find the equivalent circuit btw. a and b.

Solution

For $V_{Th} = V_{ob}$ (When a-b is open)

$$I = I + I_x$$

$$I_x = 0 \checkmark$$

$$5 = I \cdot 2000 + 3V_1$$

$$V_1 = -25 \times 20I$$


$$\boxed{V_1 = -500I}$$

$$V_{Th} = V_{ob} = V_1$$

$$I = \frac{1}{100} \text{ Amp}$$

$$V_1 = -5 \text{ Volt}$$

$$V_{Th} = V_1 = -5 \text{ Volt}$$

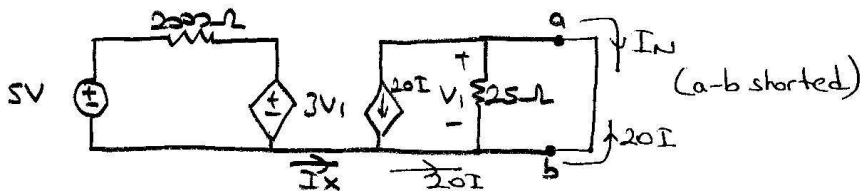

To Find I_N

$$I = I + I_x$$

$$I_x = 0$$

$$V_1 = V_a - V_b = V_{ob} = 0$$


$$V_1 = 0 \rightarrow 3V_1 = 0$$

$$I = \frac{5 - 3V_1}{2000} = \frac{1}{400} \text{ Amp}$$

$$I_x = \frac{V_1}{25} = \frac{0}{25} = 0$$

$$I_N = -20I = -20 \cdot \left(\frac{1}{400}\right) = -\frac{1}{20} \text{ A}$$
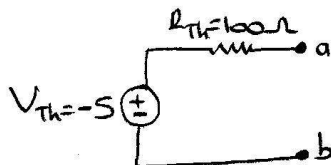
$$R_{Th} = R_N = \frac{V_{Th}}{I_N} = \frac{-5}{-1/20} = 100 \Omega$$



Thermin equivalent circuit