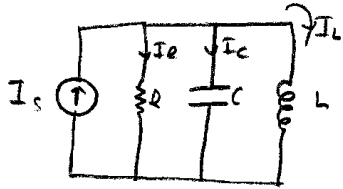


25.09.2010

Step Input ($I_s(t) = u(t)$)



$$\frac{d^2 V_C}{dt^2} + 2 \frac{dV_C}{dt} + \omega_0^2 V_C = \frac{1}{C} \frac{dI_s}{dt} = \frac{1}{C} \delta(t)$$

$$V_C(0^-) = 0$$

$$\frac{d^2 I_L}{dt^2} + 2 \frac{dI_L}{dt} + \omega_0^2 I_L = \omega_0^2 I_s = \omega_0^2 u(t)$$

$$I_L(0^-) = 0$$

$$\begin{aligned} \frac{dV_C}{dt}(0) &= -\frac{V_C(0)}{RC} - \frac{I_L(0)}{C} + \frac{I_s(0)}{C} \\ &= -\frac{0}{RC} - \frac{0}{C} + \frac{0}{C} = 0 \end{aligned}$$

$$\frac{dI_L}{dt}(0) = \frac{V_C(0)}{L} = 0$$

$t > 0$

$$\frac{dV_C}{dt} = -\frac{1}{RC} V_C - \frac{1}{C} I_L + \frac{1}{C} I_s$$

$$\int_{V_C(0^-)}^{V_C(0^+)} dV_C = -\frac{1}{RC} \int_{0^-}^{0^+} V_C(t') dt' - \frac{1}{C} \int_{0^-}^{0^+} I_L(t') dt' + \frac{1}{C} \int_{0^-}^{0^+} \underbrace{I_s(t')}_{u(t)} dt'$$

$$V_C(0^+) - V_C(0^-) = \underbrace{0}_{0} - \underbrace{0}_{0} + \underbrace{0}_{0} = 0$$

$$\frac{dI_L}{dt} = \frac{V_C}{L}$$

$$\int_{I_L(0^-)}^{I_L(0^+)} dI_L = \frac{1}{L} \int_{0^-}^{0^+} V_C(t') dt'$$

$$I_L(0^+) - I_L(0^-) = 0 \Rightarrow I_L(0^+) = I_L(0^-) = 0$$

$$\frac{dI_L}{dt}(0^+) = \frac{V_C(0^+)}{L} = \frac{0}{L} = 0$$

$$\begin{aligned} \frac{dV_C}{dt}(0^+) &= -\frac{1}{RC} V_C(0^+) - \frac{1}{C} I_L(0^+) + \frac{1}{C} I_S(0^+) \\ &= 0 - 0 + \frac{1}{C} \end{aligned}$$

$$\boxed{\frac{dV_C}{dt}(0^+) = \frac{1}{C}}$$

$t > 0$

$$\frac{d^2 V_C}{dt^2} + 2\alpha \frac{dV_C}{dt} + \omega_0^2 V_C = 0$$

$$V_C(0^+) = 0 \quad \frac{dV_C}{dt}(0^+) = \frac{1}{C}$$

$$\frac{d^2 I_L}{dt^2} + 2\alpha \frac{dI_L}{dt} + \omega_0^2 I_L = \omega_0^2$$

$$I_L(0^+) = 0 \quad \frac{dI_L}{dt}(0^+) = 0$$

$$2\alpha = \frac{1}{RC} \quad \omega_0^2 = \frac{1}{LC}$$

For I_L

Assume overdamped $\rightarrow s_{1,2}$ real, different, negative

① $I_{Lp} = K$ (constant) $I_{Cp} \rightarrow$ particular solution

$$\frac{d^2}{dt^2} \underbrace{K + 2d \frac{d}{dt} K + \omega_0^2 K = \omega_0^2 K = \omega_0^2 K}$$

$$\omega_0^2 K = \omega_0^2 K \implies K = 1$$

② $s^2 + 2d s + \omega_0^2 = 0$ (char eq)

$\xrightarrow{s=1,2 \text{ solution}}$
 $I_{LH} = B_1 e^{s_1 t} + B_2 e^{s_2 t}$

③ $I_L(t) = I_{Cp} + I_{CH}$

$$I_L(t) = 1 + B_1 e^{s_1 t} + B_2 e^{s_2 t}$$

④ $I_L(0^+) = 0 = 1 + B_1 + B_2$

$$\frac{dI_L}{dt}(0^+) = 0 = s_1 B_1 + s_2 B_2$$

$$B_1 = \frac{s_2}{s_1 - s_2}, \quad B_2 = \frac{s_1}{s_2 - s_1}$$

$$L \frac{dI_L}{dt} = V_C = L \left[\frac{d}{dt} \left[1 + \frac{s_2}{s_1 - s_2} e^{s_1 t} + \frac{s_1}{s_2 - s_1} e^{s_2 t} \right] \right]$$

$$= L \left[\frac{s_1 s_2}{s_1 - s_2} e^{s_1 t} + \frac{s_1 s_2}{s_2 - s_1} e^{s_2 t} \right]$$

$$s_1 s_2 = \omega_0^2 = \frac{1}{LC}$$


$$= L \left[\frac{1}{LC} \frac{1}{s_1 - s_2} e^{s_1 t} + \frac{1}{LC} \frac{1}{s_2 - s_1} e^{s_2 t} \right]$$

$$V_C(t) = \left[\frac{1}{L} \frac{1}{(s_1 - s_2)} e^{s_1 t} + \frac{1}{L(s_2 - s_1)} e^{s_2 t} \right]$$

$$\lim_{t \rightarrow \infty} V_C(t) = 0 \text{ (at steady-state } V_C(t) \rightarrow 0)$$

$$\lim_{t \rightarrow \infty} I_L(t) = 1 \text{ (at steady state } I_L(t) \rightarrow 1)$$

Impulse Response ($I_S(t) = \delta(t)$)

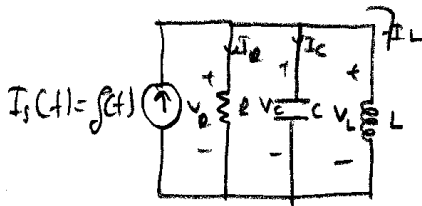

$$\frac{d^2 V_C}{dt^2} + 2\omega \frac{dV_C}{dt} + \omega_0^2 V_C = \frac{1}{C} \frac{d}{dt} \delta(t)$$

$$V_C(0) = 0$$

$$\frac{d^2 I_L}{dt^2} + 2\omega \frac{dI_L}{dt} + \omega_0^2 I_L = \omega_0^2 \underbrace{I_S(t)}_{\delta(t)}$$

$$I_L(0) = I_0$$

$$\begin{aligned} \frac{dV_C}{dt}(0) &= -\frac{1}{RC} V_C(0) - \frac{1}{C} I_L(0) + \frac{1}{C} I_S(0) \\ &= -\frac{V_0}{RC} - \frac{I_0}{C} + \frac{1}{C} \cdot 0 \end{aligned}$$

$$\frac{dV_C}{dt}(0) = -\frac{V_0}{RC} - \frac{I_0}{C}$$

$$\frac{dI_L}{dt}(0) = \frac{V_C(0)}{L} = \frac{V_0}{L}$$

$t > 0$

$$\frac{dV_C}{dt} = -\frac{1}{RC} V_C - \frac{1}{C} I_L + \frac{1}{C} I_S$$

$$\int_{V_C(0)}^{V_C(0^+)} dV_C = -\frac{1}{RC} \int_{0^-}^{0^+} V_C(t) dt - \frac{1}{C} \int_{0^-}^{0^+} I_L(t) dt + \frac{1}{C} \int_{0^-}^{0^+} \frac{I_S(t)}{\delta(t)} dt$$

$$V_C(0^+) - V_C(0) = 0 - 0 + \frac{1}{C} \cdot 1 = \frac{1}{C}$$

$$V_C(0^+) = V_C(0) + \frac{1}{C}$$

$$V_C(0^+) = V_0 + \frac{1}{C}$$

$$\frac{dI_L}{dt} = \frac{V_c}{L}$$

$$\int_{I_L(t_0^-)}^{I_L(t_0^+)} dI_L = \frac{1}{L} \int_{0^-}^{0^+} V_c(t') dt'$$

$$I_L(t_0^+) - I_L(t_0^-) = 0$$


$$I_L(t_0^+) = I_L(t_0^-) = I_0$$

$$\frac{dI_L}{dt}(t_0^+) = \frac{V_c(t_0^+)}{L} = \frac{V_0 + \frac{1}{c}}{L} = \frac{V_0}{L} + \frac{1}{Lc}$$

$$\frac{dV_c}{dt}(t_0^+) = -\frac{1}{Rc} V_c(t_0^+) - \frac{1}{c} I_L(t_0^+) + \frac{1}{c} \underbrace{I_s(t_0^+)}_{\delta(t)}$$

$$= -\frac{1}{Rc} \left(V_0 + \frac{1}{c} \right) - \frac{1}{c} I_0 + 0$$
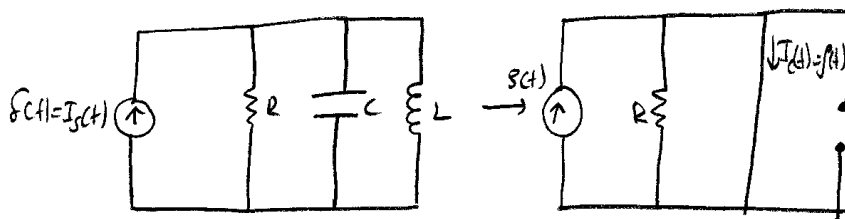
$$= -\frac{V_0}{Rc} - \frac{I_0}{c} - \frac{1}{c^2 R}$$



$$I_c(t) = \delta(t)$$

$$C \frac{dV_c}{dt} = I_c(t) = \delta(t)$$

$$\int_{V_c(t_0^-)}^{V_c(t_0^+)} dV_c = \frac{1}{C} \int_{0^-}^{0^+} I_c(t') dt'$$

$$V_c(t_0^+) - V_c(t_0^-) = \frac{1}{C} \cdot 1$$

$$V_c(t_0^+) - \frac{V_0}{c} = \frac{1}{C}$$

$$V_c(t_0^+) = V_0 + \frac{1}{C}$$

$t > 0$

$$\frac{d^2 V_c}{dt^2} + 2\alpha \frac{dV_c}{dt} + \omega_0^2 V_c = 0$$

$$V_c(0^+) = V_0 + \frac{1}{C} \quad \frac{dV_c}{dt}(0^+) = -\frac{V_0}{RC} - \frac{I_0}{C} - \frac{1}{RC^2}$$

$$\frac{d^2 I_L}{dt^2} + 2\alpha \frac{dI_L}{dt} + \omega_0^2 I_L = 0$$

$$I_L(0^+) = I_0 \quad \frac{dI_L}{dt}(0^+) = \frac{V_0}{L} + \frac{1}{LC}$$

Let $V_0 = 0, I_0 = 0$

s_1, s_2 real, negative, different (overdamped)

① $I_{LP} = 0$

② $I_{LH} = \beta_1 e^{s_1 t} + \beta_2 e^{s_2 t}$

③ $I_L = I_{LH} + I_{LP} = \beta_1 e^{s_1 t} + \beta_2 e^{s_2 t}$

④ $I_L(0^+) = 0 = \beta_1 + \beta_2$

$$\frac{dI_L}{dt}(0^+) = \frac{1}{LC} = s_1 \beta_1 + s_2 \beta_2 = \omega_0^2$$

$$\beta_1 = \frac{\omega_0^2}{s_1 - s_2}, \quad \beta_2 = \frac{\omega_0^2}{s_2 - s_1}$$

$$L \frac{dI_L}{dt} = V_c \Rightarrow L \left[\frac{d}{dt} \left[\frac{\omega_0^2}{s_1 - s_2} e^{s_1 t} + \frac{\omega_0^2}{s_2 - s_1} e^{s_2 t} \right] \right]$$

$$V_c = L \left[\frac{s_1 \omega_0^2 e^{s_1 t}}{s_1 - s_2} + \frac{s_2 \omega_0^2 e^{s_2 t}}{s_2 - s_1} \right]$$
$$= \left[\frac{1}{C} \frac{s_1}{s_1 - s_2} e^{s_1 t} + \frac{s_2}{C(s_2 - s_1)} e^{s_2 t} \right]$$


if $V_0 \neq 0$ $I_0 \neq 0$

$$I_L(0^+) = I_0 = B_1 + B_2$$

$$\frac{dI_L}{dt}(0^+) = \frac{V_0}{L} + \frac{1}{LC} = s_1 B_1 + s_2 B_2 \quad \text{HW!!!}$$

* Note that, the zero-state unit step response is the time derivative of zero-state ramp response AND zero-state impulse response is the time derivative of zero-state unit step response.

Series RLC

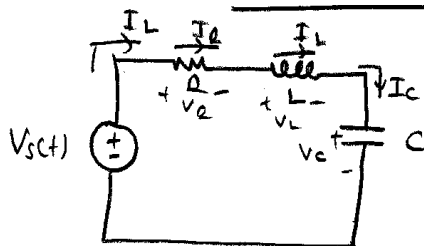

$$V_C(t_0) = V_0$$

$$I_L(t_0) = I_0$$

$$I_R = I_L = I_C$$

$$I_C = C \frac{dV_C}{dt} = I_L \Rightarrow \boxed{\frac{dV_C}{dt} = \frac{I_L}{C}} \quad (1)$$

$$V_S(t) = V_R + V_L + V_C$$

$$V_S(t) = I_L R + L \frac{dI_L}{dt} + V_C$$

$$V_S(t) = I_L R + L \frac{dI_L}{dt} + V_C$$

$$\frac{dI_L}{dt} = -\frac{1}{L} V_C - \frac{R}{L} I_L + \frac{V_S}{L}$$

$$R = \frac{1}{G} \Rightarrow \boxed{\frac{dI_L}{dt} = -\frac{1}{L} V_C - \frac{1}{LG} I_L + \frac{V_S}{L}} \quad (2)$$

$G \rightarrow$ conductance

$$\frac{d}{dt} \begin{bmatrix} V_C \\ I_L \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{1}{LG} \end{bmatrix} \begin{bmatrix} V_C \\ I_L \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} V_S$$

$$V_C(t_0) = V_0$$

$$I_L(t_0) = I_0$$

\Rightarrow

Take derivative of ① put ② inside:

$$= \frac{d^2 V_c}{dt^2} = \frac{1}{C} \frac{dI_L}{dt} = \frac{1}{C} \left[-\frac{1}{L} V_c - \frac{1}{L C} I_L + \frac{1}{L} V_s \right]$$

$$= \frac{d^2 V_c}{dt^2} = -\frac{1}{L C} V_c - \frac{1}{L C} \underbrace{I_L}_{\frac{C dV_c}{dt}} + \frac{1}{L C} V_s$$

$$= \boxed{\frac{d^2 V_c}{dt^2} + \frac{1}{L C} \frac{dV_c}{dt} + \frac{1}{L C} V_c = \frac{1}{L C} V_s}$$

$$V_c(t_0) = V_0$$

$$\frac{dV_c}{dt}(t_0) = \frac{I_L(t_0)}{C} = \frac{I_0}{C}$$

Take derivative of ② put ① inside:

$$\frac{d^2 I_L}{dt^2} = -\frac{1}{L} \underbrace{\left(\frac{dV_c}{dt} \right)}_{\frac{I_L}{C}} - \frac{1}{L C} \frac{dI_L}{dt} + \frac{1}{L} \frac{dV_s}{dt}$$


$$\frac{d^2 I_L}{dt^2} + \frac{1}{L C} \frac{dI_L}{dt} + \frac{1}{L C} I_L = \frac{1}{L} \frac{dV_s}{dt}$$

$$I_L(t_0) = I_0 \quad \frac{dI_L}{dt}(t_0) = -\frac{1}{L} V_c(t_0) - \frac{1}{L C} I_L(t_0) + \frac{1}{L} V_s(t_0)$$

$$= -\frac{V_0}{L} - \frac{I_0}{L C} + \frac{V_s(t_0)}{L}$$

$$\frac{1}{L C} = \frac{R}{L} = 2\alpha \quad \alpha: \text{damping ratio}$$
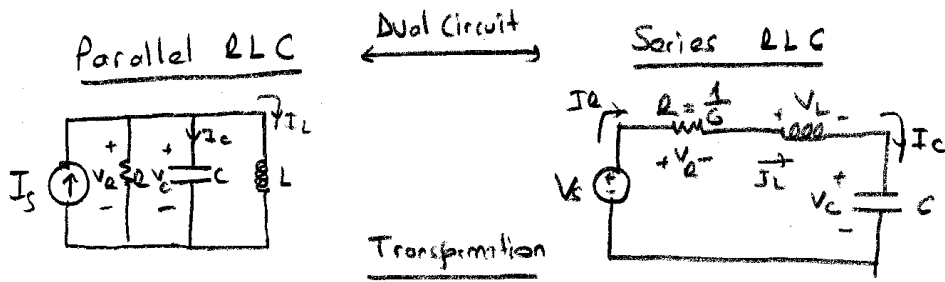
$$\frac{1}{L C} = \omega_0^2 \quad \omega_0: \text{resonance frequency}$$



parallel \longleftrightarrow series

$I_s \longleftrightarrow V_s$

$R \longleftrightarrow G$

$L \longleftrightarrow C$

$C \longleftrightarrow L$


$I_L \longleftrightarrow V_C$

$V_C \longleftrightarrow I_L$

$V_o \longleftrightarrow I_o$

$I_o \longleftrightarrow V_o$

Ex.

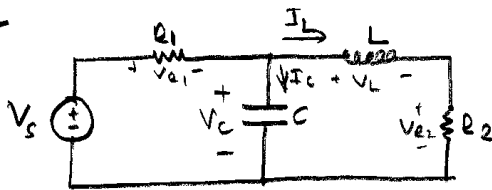

$$V_C(0) = V_o$$

$$I_L(0) = I_o$$

Solution.

$$V_s = V_{R_1} + V_C$$

$$V_s = R_1 [I_L + I_C] + V_C$$

$$V_s = R_1 I_L + R_1 C \frac{dV_C}{dt} + V_C$$

$$\textcircled{1} \quad \frac{dV_C}{dt} = \frac{V_s}{R_1 C} - \frac{1}{C} I_L - \frac{V_C}{R_1 C}$$

$$V_C = V_L + V_{R_2}$$

$$V_C = L \frac{dI_L}{dt} + R_2 I_L$$

$$\textcircled{2} \quad \frac{dI_L}{dt} = \frac{1}{L} V_C - \frac{R_2}{L} I_L$$

$$\frac{d}{dt} \begin{bmatrix} V_C \\ I_L \end{bmatrix} = \begin{bmatrix} -\frac{1}{R_1 C} & -\frac{1}{C} \\ \frac{1}{L} & -\frac{R_2}{L} \end{bmatrix} \begin{bmatrix} V_C \\ I_L \end{bmatrix} + \begin{bmatrix} \frac{1}{R_1 C} \\ 0 \end{bmatrix} V_s$$

\implies

Take derivative of ① put ② inside:

$$\frac{d^2 V_c}{dt^2} = -\frac{1}{R_1 C} \frac{dV_c}{dt} - \frac{1}{C} \frac{dI_L}{dt} + \frac{1}{R_1 C} \frac{dV_s}{dt}$$

$$\frac{d^2 V_c}{dt^2} + \frac{1}{R_1 C} \frac{dV_c}{dt} = -\frac{1}{C} \left[\frac{1}{L} V_c - \frac{R_2}{L} I_L \right] + \frac{1}{R_1 C} \frac{dV_s}{dt}$$

$$\frac{d^2 V_c}{dt^2} + \frac{1}{R_1 C} \frac{dV_c}{dt} + \frac{1}{LC} V_c = \frac{R_2}{LC} I_L + \frac{1}{R_1 C} \frac{dV_s}{dt}$$

$$I_L = \frac{V_s}{R_1} - C \frac{dV_c}{dt} - \frac{V_c}{R_1}$$

$$\frac{d^2 V_c}{dt^2} + \frac{1}{R_1 C} \frac{dV_c}{dt} + \frac{1}{LC} V_c = \frac{R_2}{R_1 LC} V_s - \frac{R_2}{L} \frac{dV_c}{dt} - \frac{R_2}{R_1 LC} V_c + \frac{1}{R_1 C} \frac{dV_s}{dt}$$

$$\boxed{\frac{d^2 V_c}{dt^2} + \left(\frac{1}{R_1 C} + \frac{R_2}{L} \right) \frac{dV_c}{dt} + \left(\frac{1}{LC} + \frac{R_2}{R_1 LC} \right) V_c = \frac{R_2}{R_1 LC} V_s + \frac{1}{R_1 C} \frac{dV_s}{dt}}$$

$$V_c(\bar{0}) = V_0, \quad \frac{dV_c}{dt}(\bar{0}) = \frac{V_s(\bar{0})}{R_1 C} - \frac{1}{C} I_L(\bar{0}) - \frac{V_c(\bar{0})}{R_1}$$

Take derivative of ② put ① inside:

$$\frac{d^2 I_L}{dt^2} = \frac{1}{L} \frac{dV_c}{dt} - \frac{R_2}{L} \frac{dI_L}{dt}$$

$$\frac{d^2 I_L}{dt^2} + \frac{R_2}{L} \frac{dI_L}{dt} = \frac{1}{L} \left[\frac{V_s}{R_1 C} - \frac{1}{C} I_L - \frac{V_c}{R_1 C} \right]$$

$$\frac{d^2 I_L}{dt^2} + \frac{R_2}{L} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{V_s}{LR_1 C} - \frac{V_c}{LR_1 C} + L \frac{dI_L}{dt} + R_2 I_L$$

$$\frac{d^2 I_L}{dt^2} + \frac{R_2}{L} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{V_s}{LR_1 C} - \frac{1}{LR_1 C} \left[L \frac{dI_L}{dt} + R_2 I_L \right]$$

$$\boxed{\frac{d^2 I_L}{dt^2} + \left(\frac{R_2}{L} + \frac{1}{R_1 C} \right) \frac{dI_L}{dt} + \left(\frac{1}{LC} + \frac{R_2}{R_1 LC} \right) I_L = \frac{V_s}{LR_1 C}}$$

$$I_L(\bar{0}) = I_0, \quad \frac{dI_L}{dt}(\bar{0}) = \frac{1}{L} V_c(\bar{0}) - \frac{R_2}{L} I_L(\bar{0}) = \frac{V_0}{L} - \frac{R_2 I_0}{L}$$

==>

If $v_s(t) = \delta(t)$ find initial condition changes.

$$\frac{dI_L}{dt} = \frac{1}{L} v_c - \frac{R_2}{L} I_L$$

$$\int_{I_L(\bar{0})}^{I_L(0^+)} dI_L = \frac{1}{L} \int_{0^-}^{0^+} v_c(t') dt' - \frac{R_2}{L} \int_{0^-}^{0^+} I_L(t') dt'$$

$$I_L(0^+) - I_L(0^-) = 0 - 0$$

$$\boxed{I_L(0^+) = I_L(0^-) = I_0}$$

$$\frac{dv_c}{dt} = -\frac{1}{R_1 C} v_c - \frac{1}{C} I_L + \frac{1}{R_1 C} v_s(t)$$

$$\int_{v_c(\bar{0})}^{v_c(0^+)} dv_c = \frac{-1}{R_1 C} \int_{0^-}^{0^+} v_c(t') dt' - \frac{1}{C} \int_{0^-}^{0^+} I_L(t') dt' + \frac{1}{R_1 C} \int_{0^-}^{0^+} v_s(t') dt'$$

$$v_c(0^+) - v_c(0^-) = 0 + \frac{1}{R_1 C}$$

$$v_c(0^+) = v_c(0^-) + \frac{1}{R_1 C} = V_0 + \frac{1}{R_1 C}$$

$$\frac{dI_L}{dt}(0^+) = \frac{1}{L} v_c(0^+) - \frac{R_2}{L} I_L(0^+) = \frac{1}{L} \left(V_0 + \frac{1}{R_1 C} \right) - \frac{R_2}{L} I_0 = \frac{V_0}{L} + \frac{1}{L R_1 C} - \frac{R_2 I_0}{L}$$

$$\frac{dv_c}{dt}(0^+) = -\frac{1}{R_1 C} v_c(0^+) - \frac{1}{C} I_L(0^+) + \frac{1}{R_1 C} v_s(0^+) = -\frac{R_2 I_0}{L}$$

$$= -\frac{1}{R_1 C} \left[V_0 + \frac{1}{R_1 C} \right] - \frac{1}{C} I_0 + 0$$

$$= -\frac{V_0}{R_1 C} - \frac{I_0}{C} - \frac{1}{R_1^2 C^2}$$

\Rightarrow

$$\frac{dV_c}{dt} = -\frac{1}{R_1 C} V_c - \frac{1}{C} I_L + \frac{1}{R_1 C} V_s(t)$$

$\frac{d^2 V_c}{dt^2}$

$$2d = \left(\frac{1}{R_1 C} + \frac{R_2}{L} \right)$$


$$\omega_0^2 = \frac{1}{LC} + \frac{R_2}{R_1 LC}$$

$\rightarrow > 0$

$$\frac{d^2 V_c}{dt^2} + 2d \frac{dV_c}{dt} + \omega_0^2 V_c = 0$$

$$\frac{d^2 I_L}{dt^2} + 2d \frac{dI_L}{dt} + \omega_0^2 I_L = 0$$

Switching

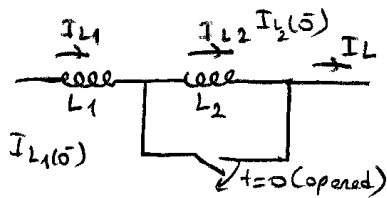


$\phi(0^-) = \phi(0^+) \rightarrow$ flux is preserved

$$I_{L1}(0^-) L_1 + I_{L2}(0^-) L_2 = (L_1 + L_2) I_L(0^+)$$

$$I_L(0^+) = \frac{I_{L1}(0^-) L_1 + I_{L2}(0^-) L_2}{L_1 + L_2}$$

$E(0^-) > E(0^+) \text{ HW.}$

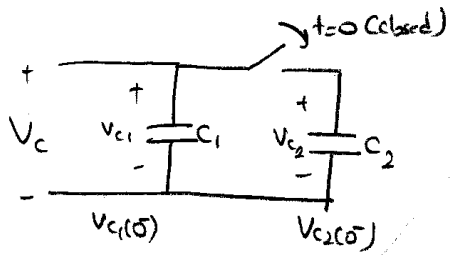

$$\rightarrow V_{c1}(\bar{0})C_1 + V_{c2}(\bar{0})C_2 = (C_1 + C_2)V_c(\bar{0}')$$

$$V_c(\bar{0}') = \frac{V_{c1}(\bar{0})C_1 + V_{c2}(\bar{0})C_2}{C_1 + C_2}$$

$$E(\bar{0}) > E(\bar{0}')$$

$Q(\bar{0}) = Q(\bar{0}')$
charge is preserved