
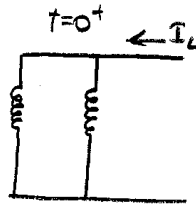


27.07.2010

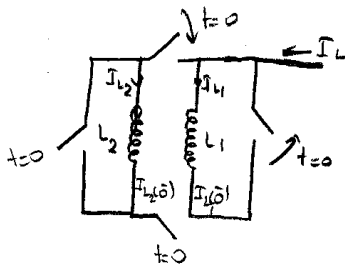

$$I_2(0^+) = I_2(0^-)$$

$$I_1(0^+) = I_1(0^-)$$


$$L_{total} = \frac{L_1 L_2}{L_1 + L_2}$$

$E_{initial} > E_{final}$

$$\frac{1}{2} L_1 I_1^2(0^-) + \frac{1}{2} L_2 I_2^2(0^-) \geq \frac{1}{2} \left(\frac{L_1 L_2}{L_1 + L_2} \right) [I_1(0^+) + I_2(0^+)]^2$$


$$I_L(0^+) = I_1(0^+) + I_2(0^+)$$

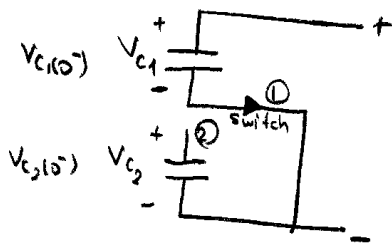if I_{L_2} is reversed $\Rightarrow I_L(0^+) = I_1(0^+) - I_2(0^+)$




at $t=0$ switch is brought to position 2 from position 1

when $t=0^+$

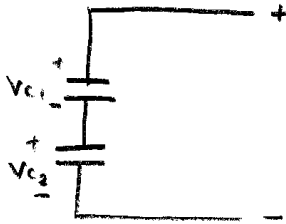

$E_{initial} \geq E_{final}$

esti final sorusu 2008-2009

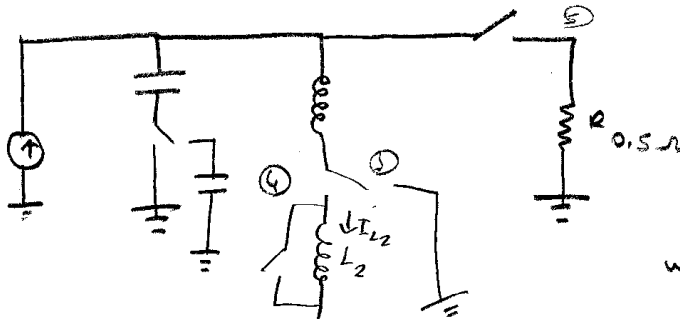

$0 < t < 10 \pi$
 $S_1 \rightarrow 1$
 $S_2 \rightarrow 3$
 $S_3 \rightarrow \text{closed}$
 $S_4 \rightarrow \dots$
 when $t > 10 \pi$
 $S_1 \rightarrow 2$
 $S_2 \rightarrow 4$
 $S_3, S_4 \rightarrow \text{open}$

Find $I_{L_1}(t) > 0$

Hint = w $0 < t < 10 \pi$

$I_{L_1 p} = K t^2 e^{-t}$ where $I_{L_1 p}$ is the particular solution for I_{L_1}

$C_1 = C_2 = 1 \text{ F}$

$L_1 = L_2 = 1 \text{ H}$


$V_{C_1}(0) = 0 \text{ V}$

$V_{C_2}(0) = 2 \text{ V}$

$I_{L_2}(0) = 2 \text{ A}$

$I_{L_1}(0) = 0 \text{ A}$

$I_S(t) = e^{-t}$

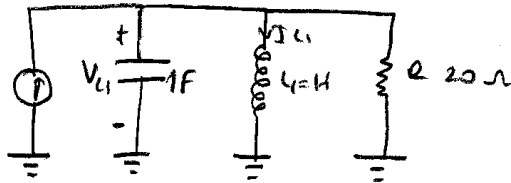

$V_{C_2}(10\pi^-) = V_{C_2}(0)$

$I_{L_2}(10\pi^-) = I_{L_2}(0)$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC_1} \frac{dV_C}{dt} + \frac{1}{LC_1} V_C = \frac{1}{C_1} \frac{dI_S}{dt}$$

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC_1} \frac{dI_L}{dt} + \frac{1}{LC_1} I_L = \frac{1}{LC_1} I_S(t)$$

$V_{C_1}(0) = 0$

$I_{L_1}(0) = 0$

$$\frac{I_{L_1}(0)}{dt} = \frac{V_{C_1}(0)}{L} = 0$$

$\frac{d^2 I_{L_1}}{dt^2} + 2 \frac{dI_{L_1}}{dt} + I_{L_1} = e^{-t}$ put $I_{L_1 p}$ in diff-eqn.

$$\frac{d^2}{dt^2} (k + t^2 e^{-t}) + 2 \frac{d}{dt} (k + t^2 e^{-t}) + (k + t^2 e^{-t}) = e^{-t}$$

$$k [2(e^{-t} - t e^{-t}) - (2 + e^{-t} - t^2 e^{-t})] + 2k [2t e^{-t} - t^2 e^{-t}] + k + t^2 e^{-t} = t e^{-t}$$

$$k = \frac{1}{2}$$

$$I_{L,p} = \frac{1}{2} t^2 e^{-t} \quad (0 < t < 10\pi)$$

② char eqn.

$$s^2 + 2s + 1 = 0 \quad \text{critically damped}$$

$$s_{1,2} = -1$$

$$I_{L,h} = A_1 e^{-t} + A_2 t e^{-t}$$

$$\text{we know that } I_{sc}(t) = e^{-t}, \text{ so } I_{L,p} = k + t^2 e^{-t}$$

$$\textcircled{3} \quad I_L = I_{L,p} + I_{L,h} = \frac{1}{2} + t^2 e^{-t} + A_1 e^{-t} + A_2 t e^{-t}$$

for A_1

$$I_L(0) = 0 = A_1 \quad \frac{dI_L(0)}{dt} = 0 = \frac{V_L(0)}{L}$$

$$\left. \frac{d}{dt} \left(\frac{1}{2} t^2 e^{-t} + A_2 t e^{-t} \right) \right|_{t=0} = 0$$

$$A_2 = 0$$

when $0 < t < 10$

$$I_L(t) = \frac{1}{2} t^2 e^{-t}$$

$$V_L = V_{c1} = L \frac{dI_L}{dt} = 1 \left[\frac{d}{dt} \left[\frac{1}{2} t^2 e^{-t} \right] \right]$$

$$V_{c1} = \frac{1}{2} [2t e^{-t} - t^2 e^{-t}]$$

=)

$$0 < t < 210\pi$$

$$I_L = \frac{1}{2} t^2 e^{-t} \quad V_{C1} = \frac{1}{2} [2t e^{-t} - t^2 e^{-t}]$$

$$I_L(10\pi^-) = \frac{1}{2} (10\pi)^2 e^{-10\pi} \approx 0$$


$$V_{C1}(10\pi^-) = \frac{1}{2} [2(10\pi) e^{-10\pi} - (10\pi)^2 e^{-10\pi}] \approx 0$$

$$e^{-x} \approx 0 \text{ when } x > 5 \text{ (approximation)}$$

$$I_L(10\pi^-) \approx 0$$

$$V_{C1}(10\pi^-) \approx 0$$

when $t = 10\pi$

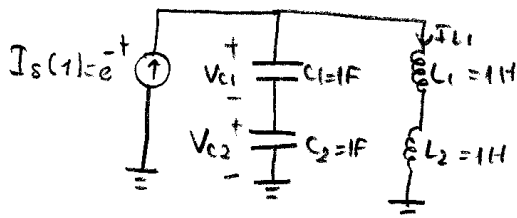

$$V_C(10\pi^+) = V_{C1}(10\pi^-) + V_{C2}(10\pi^-)$$

$$0 + 1$$

$$V_C(10\pi^+) = 1$$

$$\phi_{L1}(10\pi^+) = \phi_{L2}(10\pi^+)$$


$$L_1 I_{L1}(10\pi^+) + L_2 I_{L2}(10\pi^+) = (L_1 + L_2) I_L(10\pi^+)$$

$$1 \times 0 + 1 \times 2 = (1+1) I_L(10\pi^+)$$

$$I_L(10\pi^+) = 1 \text{ Ampers}$$

$$C_T = \frac{C_1 C_2}{C_1 + C_2} \quad L_T = L_1 + L_2 = 2 \text{ Henry}$$

$$= \frac{1}{2} \text{ Farad}$$

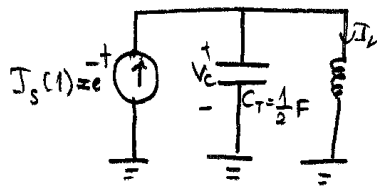

$$V_C(10\pi^+) = 1 \text{ Volt}$$

$$L_T = 2 \text{ H}$$

$$V_C(10\pi^+) = 1 \text{ Volt}$$

$$I_L(10\pi^+) = I_L(10\pi^-) = 1 \text{ Ampere}$$

$$\frac{d^2 I_L}{dt^2} + \frac{1}{2C_T} \frac{dI_L}{dt} + \frac{1}{L_T C_T} I_L = \frac{1}{L_T C_T} I_S(t)$$

$$\frac{d^2 I_L}{dt^2} + I_L = I_S(t)$$

$$I_L(10\pi^+) = 1 \text{ A}$$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{2C_T} \frac{dV_C}{dt} + \frac{1}{L_T C_T} V_C = \frac{1}{C_T} \frac{d}{dt} I_S(t)$$

$$V_C(10\pi^+) = 1 \text{ Volt}$$

$$\frac{d^2 V_C}{dt^2} + V_C = 2 \frac{d}{dt} e^{-t} = -2e^{-t}$$

$$\frac{dI_L}{dt}(10\pi^+) = \frac{V_C(10\pi^+)}{L_T} = \frac{1}{2}$$

$$s^2 + 1 = 0 \quad s_{1/2} = \pm j \rightarrow \text{natural frequencies} \rightarrow s_1 \neq -1$$

$$\textcircled{1} I_{L,p} = I_{L,p} = M e^{-t}$$

(particular solution is similar to input when $t > 10\pi$)

$$\frac{d^2}{dt^2} I_L + I_L = e^{-t}$$

$$\frac{d^2}{dt^2} (M e^{-t}) + M e^{-t} = e^{-t}$$

$$2M e^{-t} = e^{-t} \quad M = \frac{1}{2}$$

$s_2 \neq -1$
(dynamic hysteresis)

$$S_{1,2} = \bar{T} \int$$

$$I_{Lh} = A_1 \cos(t) + A_2 \sin(t)$$

$$I_L = I_{cp} + I_{ch}$$

$$I_L = \frac{1}{2} e^{-t} + A_1 \cos(t) + A_2 \sin(t)$$

$$I_L(10\pi^+) = 1 \text{ Amper} = \frac{1}{2} e^{-10\pi} + A_1 \cos(10\pi) + A_2 \sin(10\pi)$$

$$1 = 0 + A_1 + A_2 \Rightarrow A_1 = 1$$

$$\left. \frac{dI_L}{dt} \right|_{t=10\pi^+} = \frac{1}{2}$$

$$\frac{dI_L}{dt} = -\frac{1}{2} e^{-t} - A_1 \sin(t) + A_2 \cos(t)$$


$$\left. \frac{dI_L}{dt} \right|_{t=10\pi^+} = -\frac{1}{2} e^{-10\pi} - \sin(10\pi) + A_2 \cos(10\pi)$$

$$\frac{1}{2} = 0 - 0 + A_2$$

$$A_2 = \frac{1}{2}$$

$$I_L(t) = \frac{1}{2} e^{-t} + \cos(t) + \frac{1}{2} \sin(t)$$
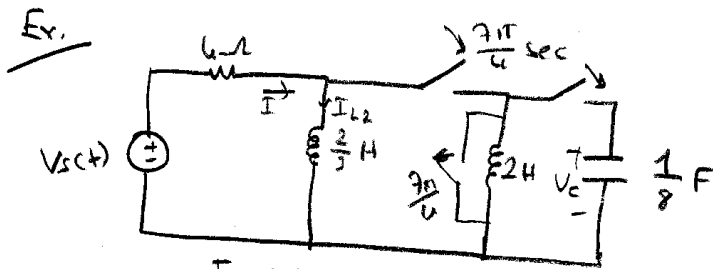
$$I_L = \begin{cases} \frac{1}{2} t^2 e^{-t} & 0 \leq t < 10\pi \\ \frac{1}{2} e^{-t} (\cos(t) + \sin(t)) & t > 10\pi \end{cases}$$




$$I_{L_1}(0) = 0 \text{ A}$$

$$I_{L_2}(0) = 0 \text{ A}$$

$$V_C(0) = 3 \text{ V}$$

$$e^{-x} \approx 0 \quad x \gg 5$$

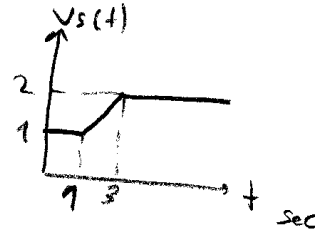


Soln.

$$V_C\left(\frac{7\pi}{4}\right) = V_C(0) \quad \checkmark$$


$$I_{L_1}\left(\frac{7\pi}{4}\right) = I_{L_1}(0) \quad \checkmark$$

$$0 < t < \frac{7\pi}{4}$$

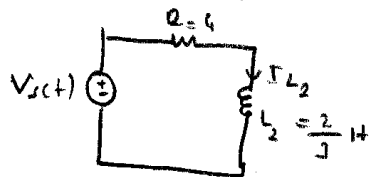

$$I_{L_2}(0) = 0 \text{ A} //$$

when $0 < t < 1$ $V_s(t) = t$

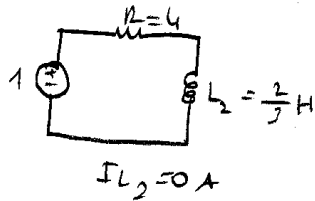

$$V_s = V_R + V_{L_2}$$

$$V_s = R I_{L_2} + L_2 \frac{dI_{L_2}}{dt}$$

$$1 = 4 I_{L_2} + \frac{2}{3} \frac{dI_{L_2}}{dt}$$

\Rightarrow

$$\frac{dI_{L2}}{dt} + 6I_{L2} = \frac{3}{2}$$

$$\textcircled{1} I_{L2p} = k$$

$$\frac{d}{dt} k + 6k = \frac{3}{2} \quad k = \frac{1}{4}$$

$$\textcircled{2} I_{L2h} = M e^{-6t} \quad \left[\begin{array}{l} s + 6 = 0 \text{ char eq} \\ s = -6 \text{ nat-freq} \end{array} \right]$$

$$\textcircled{3} I_{L2} = I_{L2p} + I_{L2h}$$


$$I_{L2} = \frac{1}{4} + M e^{-6t}$$

$$I_{L2}(0) = 0 = \frac{1}{4} + M e^{-0} \Rightarrow M = -\frac{1}{4}$$

$$I_{L2} = \frac{1}{4} - \frac{1}{4} e^{-6t} \quad \text{when } t=1 \quad I_{L2}(1) = \frac{1}{4} - \frac{1}{4} e^{-6} \approx \frac{1}{4}$$

when $1 < t < 3$


$V_s(t)$

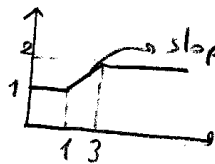

$$\frac{1}{2} = \frac{V_s(t) - 2}{t - 3}$$

$$\frac{1}{2} (t - 3) + 2 = V_s(t)$$

$$\frac{1}{2} t + \frac{1}{2} = V_s(t)$$

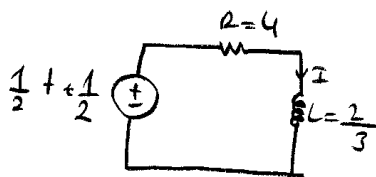

$$\frac{1}{2} t + \frac{1}{2} = V_R + V_L$$

$$\frac{1}{2} t + \frac{1}{2} = 4I_{L2} + \frac{2}{3} \frac{dI_{L2}}{dt}$$

$$\frac{3t}{4} + \frac{3}{4} = 6I_{L2} + \frac{dI_{L2}}{dt}$$

$$I_{L2}(1) = \frac{1}{4}$$

$$I_{L_2 p}(t) = A + B$$

$$\frac{d}{dt}(A + B) + 6(A + B) = \frac{3t}{4} + \frac{3}{4}$$

$$A + 6A + 6B = \frac{3t}{4} + \frac{3}{4}$$

$$6A - \frac{3}{4} \quad A + 6B = \frac{3}{4}$$

$$A = \frac{1}{8} \quad \frac{1}{8} + 6B = \frac{3}{4} \rightarrow 6B = \frac{5}{8} \quad B = \frac{5}{48}$$

$$I_{L_2 p} = \frac{1}{8}t + \frac{5}{48}$$

$$I_{L_2 h}(t) = \mu_1 e^{-t}$$

$$= \mu_1 e^{-(t-1)}$$

$$I_{L_2} = I_{L_2 h} + I_{L_2 p}$$

$$= \mu_1 e^{-(t-1)} + \frac{1}{8}t + \frac{5}{48}$$

$$I_{L_2}(1) = \mu_1 + \frac{1}{8} + \frac{5}{48}$$

$$\frac{1}{4} = \mu_1 + \frac{11}{48}$$

$$\mu_1 = \frac{1}{48}$$

$$1 < t < 3$$


$$I_{L_2}(t) = \frac{1}{48} e^{-(t-1)} + \frac{1}{8}t + \frac{5}{48}$$

$$I_{L_2}(3) = \frac{1}{48} e^{-6(3-1)} + \frac{2}{8} + \frac{5}{48}$$

$$I_{L_2}(3) \approx \frac{23}{48}$$

⇒
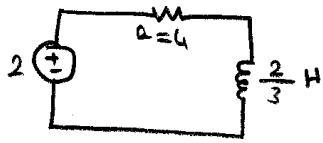
$$3 < t < \frac{7\pi}{4} \rightarrow U_S(t) = 2$$



$$2 = V_R + V_{L_2}$$

$$2 = I_{L_2} \cdot 4 + \frac{2}{3} \frac{dI_{L_2}}{dt}$$

$$3 = \frac{dI_{L_2}}{dt} + 6I_{L_2} \quad I_{L_2}(3) = \frac{23}{48}$$

$$\textcircled{1} I_{L_2 p} = K$$

$$\frac{d}{dt} K + 6K = 3$$

$$K = 1/2$$

$$\textcircled{2} I_{L_2 h} = N_1 e^{-6(t-3)}$$

$$\textcircled{3} I_{L_2} = I_{L_2 p} + I_{L_2 h}$$

$$= \frac{1}{2} + N_1 e^{-6(t-3)}$$

$$I_{L_2}(3) = \frac{1}{2} + N_1 = \frac{23}{48} \Rightarrow N_1 = \frac{-1}{48}$$


$$I_{L_2} = \frac{1}{2} - \frac{1}{48} e^{-6(t-3)}$$

$$I_{L_2} \left(\frac{7\pi}{4} \right) = \frac{1}{2} - \frac{1}{48} e^{-6 \left(\frac{7\pi}{4} - 3 \right)}$$

$$\approx \frac{1}{2}$$


\Rightarrow

$t) \frac{7\pi}{4}$

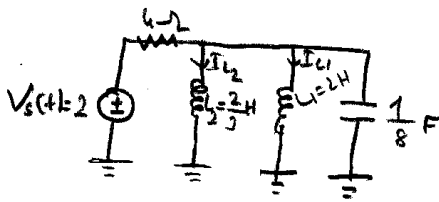

$$V_c\left(\frac{7\pi}{4}\right) = V_c\left(\frac{7\pi}{4}\right) = V_c(0) = 3$$
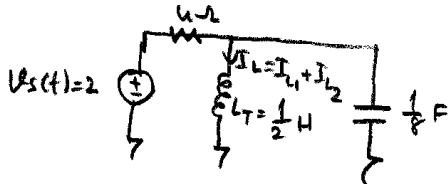
$$L_T = \frac{L_1 L_2}{L_1 + L_2} = \frac{2 \times 2}{2 + 2} = \frac{1}{2} \text{ H}$$



$$I_L\left(\frac{7\pi}{4}\right) = I_{L_1}\left(\frac{7\pi}{4}\right) + I_{L_2}\left(\frac{7\pi}{4}\right)$$

$$0 + \frac{1}{2} = \frac{1}{2} \text{ A}$$

$$V_c\left(\frac{7\pi}{4}\right) = 3 \text{ V}$$

$$V_s = V_R + V_c$$

$$2 = (I_L + I_c)R + V_c$$

$$2 = (I_L + \frac{1}{8} \frac{dV_c}{dt})R + V_c$$

$$\frac{dV_c}{dt} = 4 - 8I_L - 2V_c$$

$$V_c\left(\frac{7\pi}{4}\right) = 3 \text{ V}$$

$$\frac{1}{2} \frac{dI_L}{dt} = V_L \quad \left[\frac{dI_L}{dt} = 2V_c \right]$$

$$I_L\left(\frac{7\pi}{4}\right) = \frac{1}{2} \text{ A}$$

$$\frac{dV_c}{dt^2} = 0 - 8 \frac{dI_L}{dt} - 2 \frac{dV_c}{dt}$$

$$\frac{d^2 V_c}{dt^2} + 2 \frac{dV_c}{dt} + 16V_c = 0$$

\Rightarrow

$$\frac{d^2 I_L}{dt^2} = 2 \frac{dV_C}{dt}$$

$$\frac{d^2 I_L}{dt^2} = 2 [4 - 8I_L - 2V_C]$$

$$\begin{aligned} \frac{d^2 I_L}{dt^2} + 16I_L &= 8 - 4V_C \\ &= 8 - \frac{2dI_L}{dt} \end{aligned}$$

$$\boxed{\frac{d^2 I_L}{dt^2} + 2 \frac{dI_L}{dt} + 16I_L = 8}$$

$$I_L \left(\frac{3\pi}{4} \right) = \frac{1}{2} \quad V_C \left(\frac{3\pi}{4} \right) = 3V$$

→ Find $I_{Lp} = X$

$$\frac{d^2}{dt^2} X + 2 \frac{d}{dt} X + 16X = 8$$

$$16X = 8 \quad X = \frac{1}{2}$$

$$s^2 + 2s + 16 = 0 \rightarrow s_{1,2} = \frac{-2 \pm \sqrt{4 - 64}}{2} = \frac{-2 \pm \sqrt{-60}}{2}$$

$$s_{1,2} = -1 \pm j\sqrt{15}$$

$$\begin{aligned} I_L(t) &= I_{Lp} + I_{Lh} \\ &= \frac{1}{2} + e^{-(t - \frac{3\pi}{4})} \left[A_1 \cos \left[\sqrt{15} \left(t - \frac{3\pi}{4} \right) \right] + A_2 \sin \left[\sqrt{15} \left(t - \frac{3\pi}{4} \right) \right] \right] \end{aligned}$$

$$I_L \left(\frac{3\pi}{4} \right) = \frac{1}{2} = \frac{1}{2} + 1 \left[A_1 \cos 0 + A_2 \sin 0 \right]$$

$$I_L(t) = \frac{1}{2} + e^{-(t - \frac{3\pi}{4})} A_2 \sin(\sqrt{15}(t - \frac{3\pi}{4}))$$

$$L_T \frac{dI_L}{dt} = V_C$$

$$\frac{dI_L}{dt} = \frac{V_C}{L_T}$$

$$\left. \frac{dI_L}{dt} \right|_{t = \frac{3\pi}{4}} = \frac{V_C \left(\frac{3\pi}{4} \right)}{1/2} = \frac{3}{1/2} = 6$$


⇒

$$\frac{dI_L}{dt} = 0 - e^{-(t-\frac{3\pi}{4})} \cdot A_2 \sin(\sqrt{15}(t-\frac{3\pi}{4})) + e^{-(t-\frac{3\pi}{4})} A_2 \sqrt{15} \cos(\sqrt{15}(t-\frac{3\pi}{4}))$$

$$\left. \frac{dI_L}{dt} \right|_{t=\frac{3\pi}{4}} = 0 + A_2 \sqrt{15} = 6$$

$$A_2 = \frac{6}{\sqrt{15}}$$
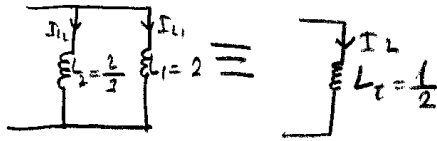
$$I_2(t) = \frac{1}{2} + \frac{6}{\sqrt{15}} e^{-(t-\frac{3\pi}{4})} \sin(\sqrt{15}(t-\frac{3\pi}{4}))$$



$$I_2 = I_L \times \frac{L_1}{L_1 + L_2}$$

$$= I_L \frac{2}{2 + \frac{1}{2}}$$

$$= I_L \frac{6}{8}$$

$$I_1 = I_L \times \frac{L_2}{L_1 + L_2}$$

$$I_1 = I_L \times \frac{\frac{1}{2}}{2 + \frac{1}{2}} = I_L \frac{2}{8}$$

$$I_2 = \frac{3}{4} \left[\frac{1}{2} + \frac{6}{\sqrt{15}} e^{-(t-\frac{3\pi}{4})} \sin(\sqrt{15}(t-\frac{3\pi}{4})) \right]$$

$$I_{L_2} = \begin{cases} \frac{1}{4} - \frac{1}{4} e^{-6t} & 0 < t \leq 1 \\ \frac{t}{48} + \frac{5}{68} \frac{t}{48} e^{-6(t-1)} & 1 < t \leq 3 \\ \frac{1}{2} - \frac{1}{48} e^{-6(t-3)} & 3 < t < \frac{3\pi}{4} \\ \frac{3}{4} \left[\frac{1}{2} + \frac{6}{\sqrt{15}} e^{-(t-\frac{3\pi}{4})} \sin(\sqrt{15}(t-\frac{3\pi}{4})) \right] & t > \frac{3\pi}{4} \end{cases}$$