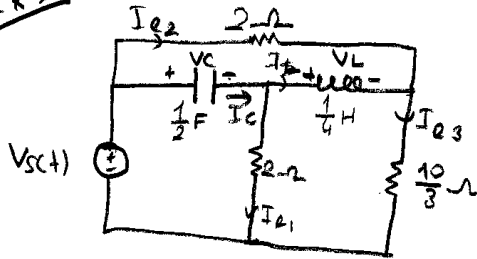


28.07.2010

Ex.



Soln.

$$I_c = I_L + I_{L1}$$

$$\frac{1}{2} \frac{dV_C}{dt} = I_L + \frac{V_s - V_C}{2}$$

$$* \frac{dV_C}{dt} = V_s + 2I_L - V_C$$

$$V_C(0) = 3V$$

$$I_L(0) = 5A$$

a) Find diff. eqn for V_C and I_L ,

b) If $V_s(t) = u(t)$ find Initial condition

$$V_C(0) = ? \quad I_L(0) = ? \quad \frac{dV_C(0)}{dt} = ?$$

$$\frac{dI_L(0)}{dt} = ?$$

$$\frac{dV_C(0)}{dt} = ?$$

$$\frac{dI_L(0)}{dt} = ?$$

$$I_{L2} = I_L + I_{L1}$$

$$\frac{V_s - V_C - V_L}{\frac{10}{3}} = I_L + \frac{V_C + V_L}{2}$$

$$I_L + \frac{V_C}{2} + \frac{1}{4} \frac{dI_L}{dt} = \frac{3}{10} V_s - \frac{3}{10} V_C - \frac{3}{10} \frac{dI_L}{dt}$$

$$\left(\frac{1}{4} + \frac{3}{10}\right) \frac{dI_L}{dt} = \frac{3}{10} V_s - \left(\frac{1}{2} + \frac{3}{10}\right) V_C - I_L$$

$$\frac{1}{5} \frac{dI_L}{dt} = \frac{3}{10} V_s - \frac{4}{5} V_C - I_L$$

$$* * \frac{dI_L}{dt} = \frac{3}{2} V_s - 4V_C - 5I_L$$

$\frac{d}{dt} *$, put $**$ inside:

$$\frac{d^2 V_C}{dt^2} = \frac{dV_s}{dt} + 2 \frac{dI_L}{dt} - \frac{dV_C}{dt}$$

$$\frac{d^2 V_C}{dt^2} + \frac{dV_C}{dt} = \frac{dV_s}{dt} + 2 \left(\frac{3}{2} V_s - 4V_C - 5I_L \right)$$

$$\frac{d^2 V_C}{dt^2} + \frac{dV_C}{dt} + 8V_C = \frac{dV_s}{dt} + 3V_s - 10I_L$$

$$= \frac{dV_s}{dt} + 3V_s - \left(\frac{5dV_C}{dt} + 5V_C - 5V_s \right)$$

$$\frac{d^2 V_C}{dt^2} + \frac{6dV_C}{dt} + 13V_C = \frac{dV_s}{dt} + 8V_s$$

$$V_C(0) = ? \quad \frac{dV_C(0)}{dt} = V_s(0) + 2I_L(0) - V_C(0)$$

$$= V_s(0) + 2 \times 5 - 3 = V_s(0) + 7 \implies 7$$

$$\frac{d^2 I_L}{dt^2} = \frac{3}{2} \frac{dV_S}{dt} - 4 \frac{dV_C}{dt} - 5 \frac{dI_L}{dt}$$

$$\frac{d^2 I_L}{dt^2} + 5 \frac{dI_L}{dt} = \frac{3}{2} \frac{dV_S}{dt} - 4 (V_S + 2I_L - V_C)$$

$$\frac{d^2 I_L}{dt^2} + 5 \frac{dI_L}{dt} \stackrel{\text{PFI}}{=} \frac{3}{2} \frac{dV_S}{dt} - 4V_S + 4V_C \quad \leftarrow \quad 4V_C = \frac{3}{2} V_S - 5I_L - \frac{dI_L}{dt}$$

$$\frac{d^2 I_L}{dt^2} + 5 \frac{dI_L}{dt} + 4I_L = \frac{3}{2} \frac{dV_S}{dt} - 4V_S + \frac{3}{2} V_S - 5I_L - \frac{dI_L}{dt}$$

$$\boxed{\frac{d^2 I_L}{dt^2} + 6 \frac{dI_L}{dt} + 13 I_L = \frac{3}{2} \frac{dV_S}{dt} - \frac{5}{2} V_S}$$

$$I_L(0) = 5$$

$$\frac{dI_L}{dt}(0) = \frac{3}{2} V_S(0) - 4V_C(0) - 5I_L(0)$$

$$= \frac{3}{2} V_S(0) - 4 \times 7 - 5 \times 5$$

$$= \frac{3}{2} V_C(0) - 37$$

b)

$$\frac{dV_C}{dt}(0) = V_S(0) + 7 = 0(0) + 7 = 7$$

$$\frac{dI_L}{dt}(0^-) = \frac{3}{2} V_S(0) - 37$$

$$= \frac{3}{2} \times 0 - 37 = -37$$

$$\int_{I_L(0)}^{I_L(0^+)} dI_L = \frac{3}{2} \int_{0^-}^{0^+} V_S(t') dt' - 4 \int_{0^-}^{0^+} V_C(t') dt' - 5 \int_{0^-}^{0^+} I_L(t') dt'$$

$$I_L(0^+) - I_L(0) = 0 - 0 - 0 \Rightarrow \boxed{I_L(0^+) = I_L(0) = -37}$$

$$\int_{V_C(0)}^{V_C(0^+)} dV_C = \int_{0^-}^{0^+} V_S(t') dt' - 2 \int_{0^-}^{0^+} I_L(t') dt' - \int_{0^-}^{0^+} V_C(t') dt'$$

$$V_C(0^+) - V_C(0) = 0 + 0 - 0$$

$$\boxed{V_C(0^+) = V_C(0) = 7}$$

\Rightarrow

$$\frac{dI_L}{dt}(0^+) = \frac{1}{2} \frac{dV_s(0^+)}{dt} - (uV_c(0^+) - SI_L(0^+))$$

$$= \frac{2}{2} - (4 \times 3 - 5 \times 5) = \frac{-71}{2}$$

$$\frac{dV_c}{dt}(0^+) = V_s(0^+) + 2I_L(0^+) - V_c(0^+)$$

$$= 1 + 2 \times 5 - 3 = 8$$

$$t > 0 \rightarrow u(t) = 1 \quad \frac{du(t)}{dt} = 0 \quad \text{when } t > 0$$

$$\frac{d^2 V_c}{dt^2} + \frac{6dV_c}{dt} + 13V_c = 8V_s + \frac{dV_s}{dt} = 8$$

$$V_c(0^+) = 3V \quad \frac{dV_c}{dt}(0^+) = 8$$

$$\frac{d^2 I_L}{dt^2} + \frac{6dI_L}{dt} + 13I_L = -\frac{5}{2}V_s + \frac{1}{2} \frac{dV_s}{dt}$$

$$= -\frac{5}{2}$$

$$I_L(0^+) = 5 \quad \frac{dI_L}{dt}(0^+) = -\frac{7}{2}$$

$$\text{char eqn} = s^2 + 6s + 13$$

$$s_{1,2} = \frac{-6 \pm \sqrt{36-52}}{2} = \frac{-6 \pm 4j}{2} = -3 \pm 2j$$

For I_L

$$\textcircled{1} I_{LP} = K$$

$$\frac{d^2 K}{dt^2} + \frac{6dK}{dt} + 13K = \frac{-5}{2}$$

$$K = -\frac{5}{26}$$

$$I_L = -\frac{5}{26} + e^{-3t} [k_1 \cos(2t) + k_2 \sin(2t)]$$

$$I_L(0^+) = 5, \quad \frac{dI_L}{dt}(0^+) = -\frac{7}{2} \quad \text{H.W.}$$

For V_c


$$V_c p = u \frac{d^2 u}{dt^2} + 6 \frac{d}{dt} u + 13u = 8$$

$$u = \frac{8}{13}$$

$$V_c(t) = \frac{8}{13} + e^{-3t} [A_1 \cos(4t) + A_2 \sin(4t)]$$

$$V_c(0^+) = 3 \quad \frac{dV_c}{dt}(0^+) = 8$$

Ex.

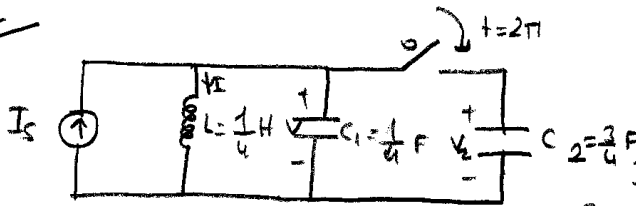

$$I(0) = 0 \text{ A} \quad V_c(0) = 0 \text{ A}$$

$$V_2(0) = \frac{4}{3} \text{ V}$$


$$I_s(t) = 1 \text{ A}$$

Switch open when $0 < t < 2\pi$
and closed when $t > 2\pi$

Find $V_c(t)$, $I(t)$ when $t > 0$

Soln

$$0 < t < 2\pi$$

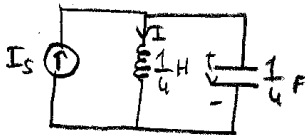

$$I_s = I + I_{C_1}$$

$$I_s = I + C_1 \frac{dV}{dt}$$

$$I_s = I + \frac{1}{4} \frac{dV}{dt}$$

$$\frac{dV}{dt} = 4I_s - 4I$$

$$\frac{dV}{dt} = 4 - 4I$$

$$V = L \frac{dI}{dt}$$

$$V = \frac{1}{4} \frac{dI}{dt} \Rightarrow \frac{dI}{dt} = 4V$$

⇒

$\frac{d}{dt}$ **, put ** inside ;

$$\frac{d^2 I}{dt^2} = 4 \frac{dV}{dt} = 4(4 - 4I)$$

$$\boxed{\frac{d^2 I}{dt^2} + 16I = 16}$$

$$I(0) = 0, \frac{dI}{dt}(0) = 4V(0) = 0$$

$\frac{d}{dt}$ **, put * inside ;

$$\frac{d^2 V}{dt^2} = -4 \frac{dI}{dt} = -4(4V)$$

$$\boxed{\frac{d^2 V}{dt^2} + 16V = 0}$$

$$V(0) = 0, \frac{dV}{dt}(0) = 4 - 4I(0) = 4$$

Solve for I

$$I_p = k$$

$$\frac{d^2}{dt^2} k + 16k = 16$$

$$k = 1$$

$$\text{Char eq } s^2 + 16 = 0 \Rightarrow s_{1,2} = \pm 4j$$

$$I(t) = \underbrace{I_p}_{1} + I_h$$

$$= 1 + A_1 \cos(4t) + A_2 \sin(4t)$$

$$I(0) = 0 = 1 + A_1 \Rightarrow A_1 = -1, \quad \frac{dI}{dt}(0) = 0$$

$$\frac{dI}{dt} = 0 - 4A_1 \sin(4t) + 4A_2 \cos(4t)$$

$$\frac{dI}{dt}(0) = 4A_2 = 0 \Rightarrow A_2 = 0$$

$$\boxed{I(t) = 1 - \cos(4t)}$$

Solve for V

$$L \frac{dI}{dt} = V$$

$$\frac{1}{4} \frac{d}{dt} [1 - \cos(4t)] = V$$

$$V = \frac{1}{4} [0 + 4 \sin(4t)] = \sin 4t$$


$$\boxed{V = \sin(4t)}$$

$$t = 2\pi^-$$

$$V(2\pi^-) = 0$$

$$I(2\pi^-) = 1 - \cos(8\pi) = 0$$

$2\pi < t$ (switch closed)

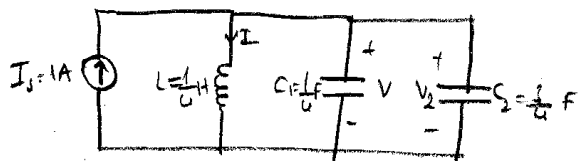

$$Q(2\pi^-) = Q(2\pi^+) \\ \text{(preserve charge amount)}$$


$$V_2(2\pi) = V_2(0) = \frac{4}{3}$$

$$C_1 V(2\pi^-) + C_2 V_2(2\pi^-) = (C_1 + C_2) V(2\pi^+)$$


$$\frac{1}{4} \times 0 + \frac{3}{4} \times \frac{4}{3} = \left(\frac{1}{4} + \frac{3}{4}\right) V(2\pi^+)$$

$$V(2\pi^+) = 1 V$$

$$I(2\pi^+) = I(2\pi^-) = 0 A$$

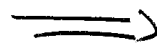

New equivalent circuit

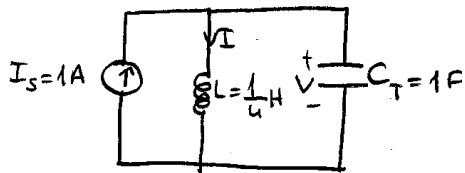

$$I(2\pi^+) = 0 \quad V(2\pi^+) = 1V$$

$t > 2\pi$

$$\frac{d^2V}{dt^2} + \frac{1}{C_T L} V = \frac{1}{C_T} \frac{dI_s}{dt}$$

$$\boxed{\frac{d^2V}{dt^2} + 4V = 0}$$

$$\frac{d^2I}{dt^2} + \frac{1}{C_T L} I = \frac{1}{C_T L} I_s$$

$$\boxed{\frac{d^2I}{dt^2} + 4I = 4}$$

$$I(2\pi^+) = 1A$$

$$\frac{dI}{dt}(2\pi^+) = \frac{V(2\pi^+)}{L} = \frac{1}{1/4} = 4$$

$$V(2\pi^+) = 1V$$

$$\frac{dV}{dt}(2\pi^+) = \frac{I_s(2\pi) - I(2\pi^+)}{C_T} = \frac{1 - 0}{1} = 1$$

For I

$$I_p = M$$

$$\frac{d^2}{dt^2} M + 4M = 4 \rightarrow M = 1$$

$$s^2 + 4 = 0 \rightarrow B_{1,2} = \pm 2j$$

$$I(t) = I_p + I_h$$

$$= 1 + A_1 \cos(2t) + A_2 \sin(2t)$$

$$I(2\pi^+) = 0 = 1 + A_1 \cos(4\pi^+) + A_2 \sin(4\pi^+)$$

$$0 = 1 + A_1 + 0 \quad \boxed{A_1 = -1}$$

$$\frac{dI}{dt}(2\pi^+) = 4$$

$$\frac{dI}{dt} = -2A_1 \sin(2t) + 2A_2 \cos(2t)$$

$$\frac{dI}{dt}(2\pi^+) = 2A_2 = 4$$

$$\boxed{A_2 = 2}$$

$t > 2\pi$

$$\boxed{I(t) = 1 - \cos(2t) + 2\sin(2t)}$$

$$L \frac{dI}{dt} = V(t)$$

$$V = -2\sin(2t) + 4\cos(2t)$$

$$\boxed{V(t) = -\frac{1}{2}\sin(2t) + \cos(2t)}$$


$$\text{Result } \leq 0.2 + 2.2\pi \Rightarrow v(t) = \sin(4t)$$

$$I(t) = 1 - \cos(4t)$$


$$+ > 2\pi \Rightarrow v(t) = -\frac{1}{2} \sin(2t) + \cos(2t)$$

$$I(t) = -\frac{1}{2} \sin(2t) + \cos(2t)$$

Ex.

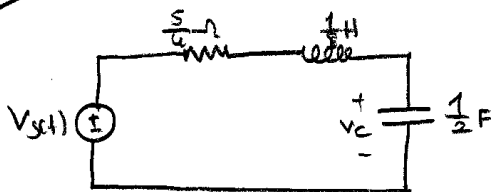
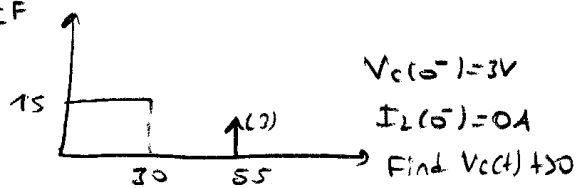
$$v_s(t) = 15 [u(t) - u(t-30)] + 3\delta(t-55)$$



$$v_c(0^-) = 3V$$

$$i_L(0^-) = 0A$$

Find $v_c(t) + 30$

Soln.

1st Method

* Let $q(t)$ be unit step zero-state response

input	output	initial condition
$v_s(t)$	$\rightarrow q(t)$	$v_c(0^-) = 0, i_L(0^-) = 0$

** Let $h(t)$ be impulse zero-state response

input	output	initial condition
$\delta(t)$	$\rightarrow h(t)$	$v_c(0^-) = 0, i_L(0^-) = 0$

*** Let $v_{zi}(t)$ be the zero input response

(no input $v_s(t) = 0$, but $v_c(0^-) = -3, i_L(0^-) = 0$)

$$v_c(t) = 15 \left[q(t)u(t) - q(t-30)u(t-30) + 3h(t-55)u(t-55) \right] + v_{zi}(t)$$

2nd Method

Inspect the input in different regions.

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{\frac{1}{2} \times \frac{1}{8}} = 16 \quad \alpha = \frac{R}{2L} = \frac{5}{2 \times \frac{1}{8}} = 5$$

\Rightarrow

$$\frac{d^2 V_C}{dt^2} + 2d \frac{dV_C}{dt} + \omega_0^2 V_C = \omega_0^2 V_S$$

$$\frac{d^2 I_L}{dt^2} + 2d \frac{dI_L}{dt} + \omega_0^2 I_L = \frac{1}{L} \frac{dV_S}{dt}$$

$$0 < t < 30 \Rightarrow V_S(t) = 15u(t)$$

$$\frac{dV_C}{dt} = \frac{I_L}{C}, \quad \frac{dI_L}{dt} = \frac{V_S}{L} - \frac{V_C}{L} - \frac{I_L R}{L}$$

$$V_C(0^-) = 3, \quad I_L(0^-) = 0$$

$$\frac{dV_C}{dt}(0^-) = \frac{I_L(0^-)}{C} = 0$$

$$\begin{aligned} \frac{dI_L}{dt}(0^-) &= \frac{15u(0^-)}{L} - \frac{V_C(0^-)}{L} - \frac{I_L(0^-) R}{L} \\ &= 0 - \frac{3}{\frac{1}{8}} - 0 = -24 \end{aligned}$$

$$\int_{V_C(0^-)}^{V_C(t^+)} dV_C = \frac{1}{C} \int_{0^-}^{0^+} I_L(t') dt'$$

$$V_C(0^+) - V_C(0^-) = 0$$

$$I_{L(0^+)} = I_{L(0^-)} = 0$$

$$\int_{I_L(0^-)}^{I_L(0^+)} dI_L = \frac{1}{L} \int_{0^-}^{0^+} \underbrace{V_S(t')}_{15u(t')} dt' - \frac{1}{L} \int_{0^-}^{0^+} V_C(t') dt' - \frac{R}{L} \int_{0^-}^{0^+} I_L(t') dt'$$

$$I_L(0^+) - I_L(0^-) = 0 - 0 - 0$$

$$I_L(0^+) = I_L(0^-) = 0$$

$$\frac{dV_C}{dt}(0^+) = \frac{I_L(0^+)}{C} = 0$$

$$\begin{aligned} \frac{dI_L}{dt}(0^+) &= \frac{V_S(0^+)}{L} - \frac{V_C(0^+)}{L} - \frac{I_L(0^+) R}{L} \\ &= \frac{15}{\frac{1}{8}} - \frac{3}{\frac{1}{8}} - \frac{0}{\frac{1}{8}} = 96 \end{aligned}$$

02+230

$$\frac{d^2 V_c}{dt^2} + \underbrace{2d}_{10} \frac{dV_c}{dt} + \underbrace{\omega_0^2}_{16} V_c = \underbrace{\omega_0^2}_{16} V_s = 240$$

$$V_c(0^+) = 3 \quad \frac{dV_c}{dt}(0^+) = 0$$

$$\frac{d^2 I_L}{dt^2} + 10 \frac{dI_L}{dt} + 16 I_L = 8 \frac{dV_s}{dt} = 0$$

$$I_L(0^+) = 0 \quad \frac{dI_L}{dt}(0^+) = 96$$

For V_c

$$V_{cp} = K$$

$$\frac{d^2}{dt^2} K + 10 \frac{d}{dt} K + 16 K = 16 \times 15$$

$$K = 15$$

$$s^2 + 10s + 16 = 0 \Rightarrow s_{1,2} = -2, -8$$

$$V_c(t) = V_{cp} + V_{ch}$$

$$= 15 + A_1 e^{-2t} + A_2 e^{-8t}$$

$$V_c(0^+) = 3 = 15 + A_1 + A_2$$

$$A_1 + A_2 = -12$$

$$\frac{dV_c}{dt}(0^+) = 0 = -2A_1 - 8A_2$$

$$A_1 + A_2 = -12$$

$$-2A_1 - 8A_2 = 0$$

$$A_2 = 4$$

$$A_1 = -16$$

$$V_c(t) = 15 - 16e^{-2t} + 4e^{-8t}$$

$$C \frac{dV_c}{dt} = I_L = \frac{1}{2} \left[\frac{d}{dt} (15 - 16e^{-2t} + 4e^{-8t}) \right]$$

$$= \frac{1}{2} [0 + 32e^{-2t} - 32e^{-8t}]$$

$$= 16e^{-2t} - 16e^{-8t}$$

$$V_c(0^+) \cong 15$$

$$I_L(0^+) = 0$$

$$\Rightarrow$$

302 + 255

$$\frac{dV_c}{dt}(35) = \frac{I_L(35)}{C} = 0$$

$$\begin{aligned} \frac{dI_L}{dt}(35) &= \frac{V_s(35)}{L} - \frac{V_c(35)}{L} - \frac{R}{L} I_L(35) \\ &= \frac{15}{1/8} - \frac{15}{1/8} - 0 = 0 \end{aligned}$$

$$\begin{aligned} \frac{dV_c}{dt} &= \frac{I_L}{L} \\ \int_{V_c(35)}^{V_c(30^+)} dV_c &= \frac{1}{L} \int_{I_L(35)}^{I_L(30^+)} I_L(t) dt \end{aligned}$$

$$V_c(30^+) = V_L(35) = 15$$

$$\begin{aligned} \frac{dI_L}{dt} &= \frac{V_s}{L} - \frac{V_c}{L} - \frac{R}{L} I_L \\ \int_{I_L(35)}^{I_L(30^+)} dI_L &= \frac{1}{L} \int_{35}^{30^+} V_c(t) dt - \frac{1}{L} \int_{35}^{30^+} V_c(t) dt - \frac{R}{L} \int_{35}^{30^+} I_L(t) dt \end{aligned}$$

$$I_L(30^+) - I_L(35) = 0 - 0 - 0$$

$$I_L(30^+) = I_L(35) = 0$$

$$\frac{dV_c}{dt}(30^+) = \frac{I_L(30^+)}{L} = 0$$

$$\begin{aligned} \frac{dI_L}{dt}(30^+) &= \frac{1}{L} V_s(30^+) - \frac{1}{L} V_c(30^+) - \frac{R}{L} I_L(30^+) \\ &= 0 - \frac{1}{1/8} 15 - 0 = -120 \end{aligned}$$

$$\frac{d^2V_c}{dt^2} + 10 \frac{dV_c}{dt} + 16V_c = 16 \times 0 = 0$$

$$V_c(30^+) = 15 \quad \frac{dV_c}{dt}(30^+) = 0$$

$$\frac{d^2I_L}{dt^2} + 10 \frac{dI_L}{dt} + 16I_L = \frac{1}{1/8} \frac{d}{dt} (-15 u(t-30))$$

$$= 8(-15 \delta(t-30))$$

$$= 0 \text{ when } t > 30 \implies$$

$$I_L(30^+) = 0 \quad \frac{dI_L}{dt}(30^+) = -120$$

for V_C :

$$V_C p = 0$$

$$s^2 + 10s + 16 = 0 \rightarrow s_{1,2} = -2, -8$$

$$V_C = V_{Cp} + V_{Ch} \\ = 0 + A_1 e^{-2(t-30)} + A_2 e^{-8(t-30)}$$

$$V_C(30^+) = 15 = A_1 + A_2$$

$$\frac{dV_C}{dt}(30^+) = 0 = -2A_1 - 8A_2$$

$$A_2 = -5$$

$$A_1 = 20$$

$$V_C(t) = 20e^{-2(t-30)} - 5e^{-8(t-30)}$$

$$\frac{dV_C}{dt} = I_L = \frac{1}{2} \left(\frac{d}{dt} (20e^{-2(t-30)} - 5e^{-8(t-30)}) \right) \\ = -20e^{-2(t-30)} + 20e^{-8(t-30)}$$

$$V_C(55^-) \approx 0 \quad I_L(55^-) \approx 0$$

$$\frac{dV_C}{dt}(55^-) \approx 0 \quad \frac{dI_L}{dt}(55^-) = 0$$

t > 55

$$\int_{V_C(55^-)}^{V_C(55^+)} dV_C = \frac{1}{C} \int_{55^-}^{55^+} I_C(t') dt'$$

$$V_C(55^+) - V_C(55^-) = 0 \Rightarrow V_C(55^+) = V_C(55^-) = 0$$

$$\int_{I_L(55^-)}^{I_L(55^+)} dI_L = \frac{1}{L} \int_{55^-}^{55^+} \frac{V_C(t')}{30(t')} dt' - \frac{1}{L} \int_{55^-}^{55^+} V_C(t') dt' - \frac{R}{L} \int_{55^-}^{55^+} I_L(t') dt'$$

$$I_L(55^+) - I_L(55^-) = \frac{1}{1/8} \times 3 = 24 \Rightarrow I_L(55^+) = 24$$

$$\frac{dV_C}{dt}(55^+) = \frac{I_L(55^+)}{C} = \frac{24}{1/2} = 48$$

$$\frac{dI_L}{dt}(55^+) = \frac{V_S(55^+)}{L} - \frac{V_C(55^+)}{L} - \frac{R}{L} I_L(55^+) \\ = 0 - 0 - \frac{5/4}{1/8} 24 = -240 \Rightarrow$$

$$t > 5.5 \quad (V_c(t) = 3 \delta(t-5) \rightarrow V_c(t) = 0 \quad t > 5.5)$$

$$\frac{d^2 V_c}{dt^2} + 10 \frac{dV_c}{dt} + 16V_c = 0$$

$$V_c(5.5^+) = 0 \quad \frac{dV_c}{dt}(5.5^+) = 4.8$$

$$V_{cp} = 0$$

$$s^2 + 10s + 16 = 0 \Rightarrow s_{1,2} = -2, -8$$

$$V_c = V_{cp} + V_{ch}$$

$$= 0 + k_1 e^{-2(t-5.5)} + k_2 e^{-8(t-5.5)}$$

$$V_c(5.5^+) = 0 = k_1 + k_2$$

$$\frac{dV_c}{dt}(5.5^+) = 4.8 = -2k_1 - 8k_2 \quad \begin{matrix} k_1 = 8 \\ k_2 = -8 \end{matrix}$$

$$V_c(t) = 8e^{-2(t-5.5)} - 8e^{-8(t-5.5)}$$

$$C \frac{dV_c}{dt} = I_L = \frac{1}{2} \left[\frac{d}{dt} (8e^{-2(t-5.5)} - 8e^{-8(t-5.5)}) \right]$$

$$I_L = -8e^{-2(t-5.5)} + 32e^{-8(t-5.5)}$$