

DIODES


31.07.2010

A circuit element that allows current flow in a single direction.



$$I = \begin{cases} 0, & V < 0 \text{ (open circuit)} \\ \text{full current}, & V = 0 \text{ (short circuit)} \end{cases}$$


Ex.

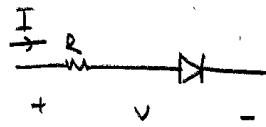


find I-V characteristic.

if $V < 0$ $I = 0$

if $V > 0$ $I = \frac{V}{R}$

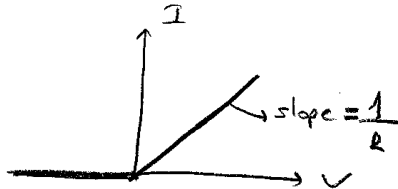


Ex.

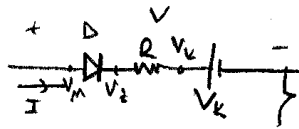


if I is passing $V = V_z = V_m > V_k$

if $V < V_k$, $I = 0$

if $V > V_k$, $I = \frac{V - V_k}{R}$

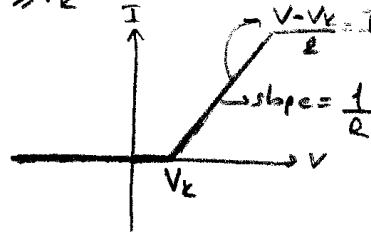


Ex.

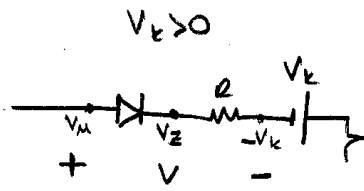


To observe current $V = V_m = V_k \geq -V_k$

if $V < -V_k$, $I = 0$

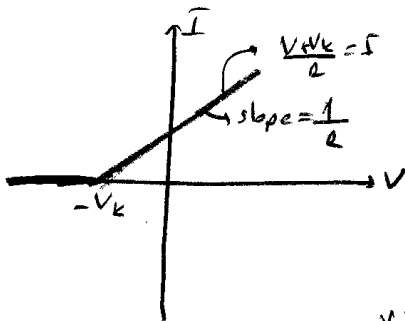if $V \geq -V_k$, $I = \frac{V - (-V_k)}{R} = \frac{V + V_k}{R}$



Ex.

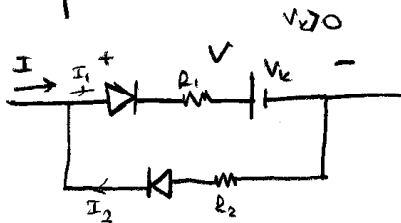

$I = I_1 - I_2$ $\begin{matrix} V = V_k \\ V = 0 \end{matrix}$ → important points

if $V > V_k$


$I_1 \checkmark$ $\Rightarrow I = I_1 = \frac{V - V_k}{R_1}$
 $I_2 \times$

if $0 < V < V_k$


$I_1 \times$ $\Rightarrow I = 0$
 $I_2 \times$

if $V < 0$

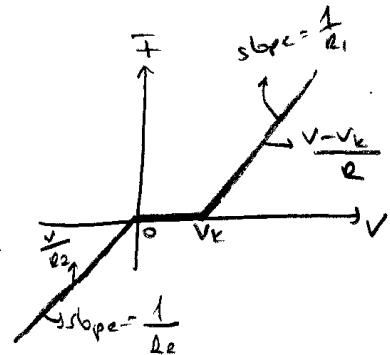$I_1 \times$ $\Rightarrow I = -I_2 = -\left[\frac{0 - V}{R_2}\right] = \frac{V}{R_2}$
 $I_2 \checkmark$



Ex.

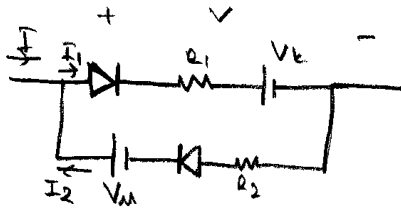

$$I = I_1 - I_2$$

important points
 $V = V_k$
 $V = V_M$

assume $V_M < V_k$

if $V > V_k$

$$I_1 \checkmark \quad I = I_1 = \frac{V - V_k}{R_1}$$

$$I_2 \times$$

if $V_M < V < V_k$

$$I_1 \times \quad I = 0$$


$$I_2 \times$$

if $V < V_M$


$$I_1 \times$$


$$I_2 \checkmark$$
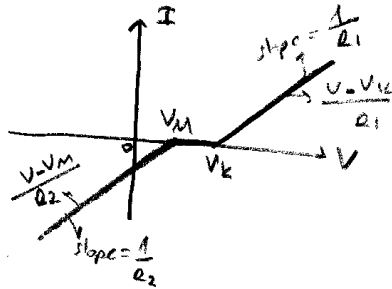
$$I = -I_2 = - \left[\frac{V_M - V}{R_2} \right] = \frac{V - V_M}{R_2}$$



if $V_M = V_k$

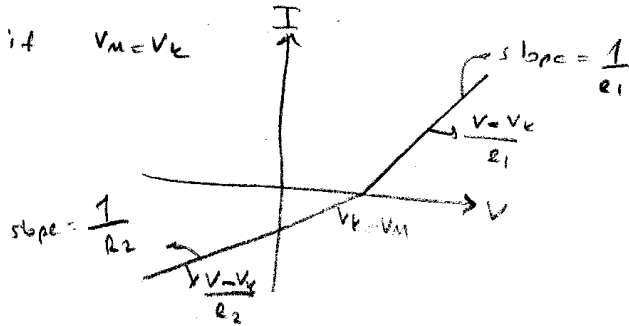

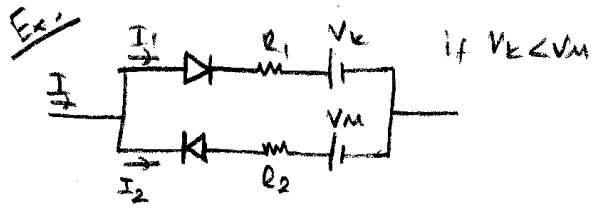

important points $V_M = V_k$

if $V > V_M$ $I_2 \times$ $\Rightarrow I = I_1 = \frac{V - V_k}{R_1}$
 $I_1 \checkmark$

if $V_k < V < V_M$

$I_1 \checkmark$

$I_2 \checkmark \Rightarrow I_1 = \frac{V - V_k}{R_1}, I_2 = \frac{V_M - V}{R_2}$


$I = I_1 - I_2 = \frac{V - V_k}{R_1} - \frac{V_M - V}{R_2}$


if $V < V_k$

$I_1 \times$

$I_2 = \frac{V_M - V}{R_2}$

$I = -I_2 = \frac{V - V_M}{R_2}$

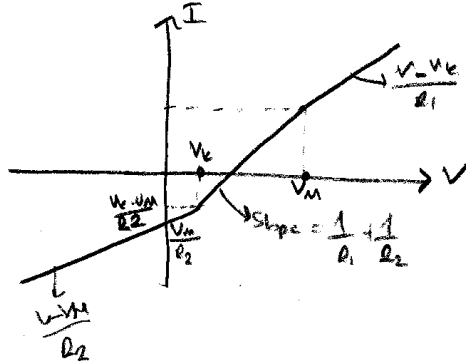

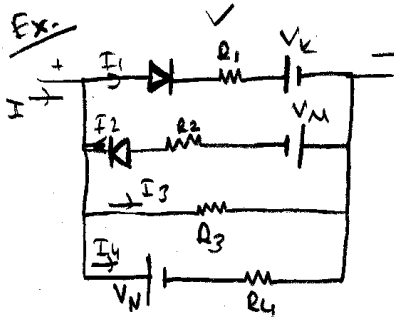

$$I = I_1 - I_2 + I_3 + I_4$$

always existing currents

$$I_3 = \frac{V}{R_3}$$

$$I_4 = \frac{V - V_n}{R_4}$$

if $-V_n \leq V < V_k$

$$I_2, I_1 \\ \times \quad \times$$

if $V > V_k$ I_1 exists

$$I_1 = \frac{V - V_k}{R_1} \quad I_2 \text{ not exists}$$

if $V < -V_n$

$$I_1 \times$$

$$I_2 = \frac{-V_n - V}{R_2}$$

if $V > V_k$

$$I = I_1 + I_3 + I_4 \quad I_2 \times$$

$$= \frac{V - V_k}{R_1} + \frac{V}{R_3} + \frac{V - V_n}{R_4}$$

$$= V \left[\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} \right] - \left(\frac{V_k}{R_1} + \frac{V_n}{R_4} \right)$$

if $-V_n \leq V < V_k$

$$I_1, I_2 \\ \times \quad \times$$

$$I = I_3 + I_4 = \frac{V}{R_3} + \frac{V - V_n}{R_4}$$

$$= V \left[\frac{1}{R_3} + \frac{1}{R_4} \right] - \frac{V_n}{R_4}$$

if $V < -V_n$


$$I_1 \times$$

$$I = -I_2 + I_3 + I_4$$


$$= \frac{V + V_n}{R_2} + \frac{V}{R_3} + \frac{V - V_n}{R_4}$$

$$= V \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] +$$
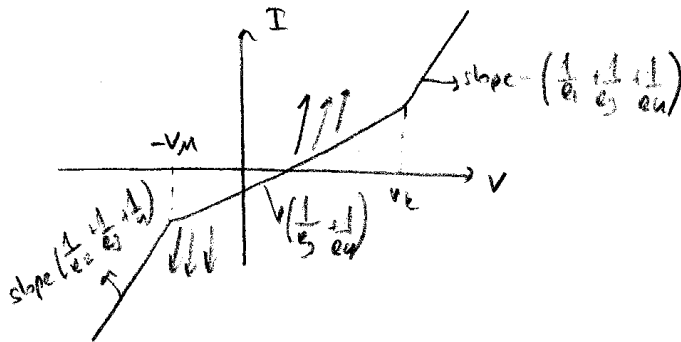
$$\left[\frac{V_n}{R_2} - \frac{V_n}{R_4} \right]$$



Ex.

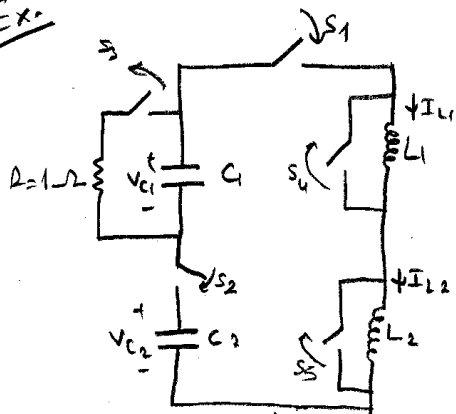

$$C_1 = C_2 = 1F$$

$$R = 1\Omega$$

$$L_1 = 1H$$

$$L_2 = 2H$$

$$V_{C1}(0) = 2V$$

$$V_{C2}(0) = 1V$$

$$I_{L1}(0) = 2A$$

$$I_{L2}(0) = 5A$$

S_1, S_2 closed when $t < \ln 2$

S_3, S_4, S_5 opened when $t = \ln 2$

Find $V_{C1}(t)$ for $t > 0$
also find $V_{C1}(t) + V_{C2}(t)$ when $t > \ln 2$

Soln.

$$0 < t < \ln 2$$

$C_1 \rightarrow$ operating

$C_2 \rightarrow$ remains in its initial condition

$L_1 \rightarrow$ " " " "

$L_2 \rightarrow$ " " " "

$$V_{C2}(\ln 2^-) = V_{C2}(0)$$

$$I_{L1}(\ln 2^-) = I_{L1}(0)$$

$$I_{L2}(\ln 2^-) = I_{L2}(0)$$

$$0 < t < \ln 2$$



$$I_{C1} = -I_R$$

$$C_1 \frac{dV_{C1}}{dt} + I_R = 0$$

$$C_1 \frac{dV_{C1}}{dt} + \frac{V_{C1}}{R} = 0$$

$$\frac{dV_{C1}}{dt} + \frac{1}{C_1 R} V_{C1} = 0 \quad V_{C1}(0) = 2$$

$$V_{C1}(t) = K e^{-\frac{t}{4}}$$

$$V_{C1}(t) = K e^{-t}$$

$$V_{C1}(0) = 2 = K$$

$$V_{C1}(t) = 2 e^{-t}$$

$$V_{C1}(\ln 2) = 2 e^{-\ln 2} = 1V$$

==>

$$t = \ln 2$$

$C_1, C_2 \rightarrow$ series

$L_1, L_2 \rightarrow$ series

$$V_C(\ln 2^+) = V_{C1}(\ln 2^-) + V_{C2}(\ln 2^-) = 1 + 1 = 2V$$


$$\phi(\ln 2^+) = \phi(\ln 2^-)$$

$$L_1 I_{L1}(\ln 2^+) + L_2 I_{L2}(\ln 2^-) = (L_1 + L_2) I_L(\ln 2^+)$$

$$1 \times 2 + 2 \times 5 = 3 \times I_L(\ln 2^+)$$

$$I_L(\ln 2^+) = 4A$$

$$t > \ln 2$$

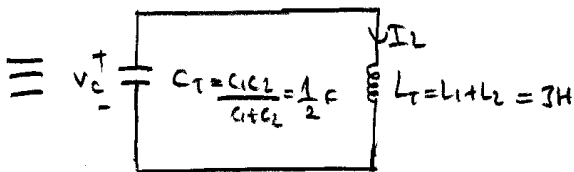

$$V_C = V_L$$

$$V_C = L_T \frac{dI_L}{dt}$$

$$\frac{dI_L}{dt} = \frac{1}{3} V_C$$

$$C \frac{dV_C}{dt} = I_C = -I_L$$

$$\frac{1}{2} \frac{dV_C}{dt} = -I_L$$

$$\frac{dV_C}{dt} = -2I_L$$

$$\frac{d^2 I_L}{dt^2} = \frac{1}{3} \frac{dV_C}{dt}$$

$$\frac{d^2 V_C}{dt^2} + \frac{2}{3} V_C = 0$$

$$\frac{d^2 I_L}{dt^2} + \frac{2}{3} I_L = 0$$

$$s^2 + \frac{2}{3} = 0 \text{ char. eq}$$

$$s = \pm j \sqrt{\frac{2}{3}} \text{ nat-freq}$$

$$V_C(t) = A_1 \cos\left(\sqrt{\frac{2}{3}}(t - \ln 2)\right) + A_2 \sin\left(\sqrt{\frac{2}{3}}(t - \ln 2)\right)$$

$$V_C(\ln 2^+) = 2V$$

$$\frac{dV_C}{dt}(\ln 2^+) = -2I_L(\ln 2^+)$$

$$= -2 \times 4 = -8$$

\Rightarrow

\Rightarrow


$$V_C(\ln 2^t) = 2 = A_1$$

$$\frac{dV_C}{dt} = -\sqrt{\frac{2}{3}} A_1 \sin\left(\sqrt{\frac{2}{3}}(t - \ln 2)\right) + \sqrt{\frac{2}{3}} A_2 \cos\left(\sqrt{\frac{2}{3}}(t - \ln 2)\right)$$


$$\frac{dV_C}{dt}(\ln 2^t) = 0 + \sqrt{\frac{2}{3}} A_2 = -8$$

$$A_2 = \frac{-8\sqrt{3}}{\sqrt{2}} = -4\sqrt{6}$$
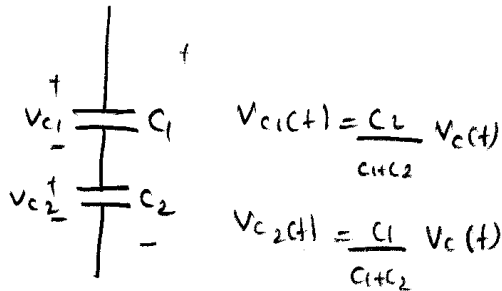
$$V_C(t) = 2 \cos\left(\sqrt{\frac{2}{3}}(t - \ln 2)\right) - 4\sqrt{6} \sin\left(\sqrt{\frac{2}{3}}(t - \ln 2)\right)$$



Ex. **

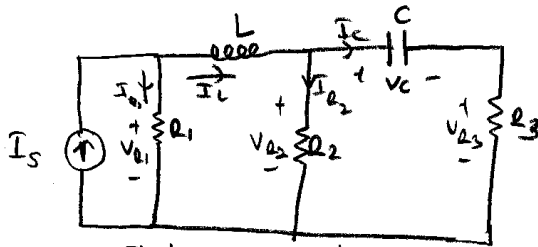

Soln. Find second order diff eqn. for V_C and I_L .

$$I_S = I_{R1} + I_L$$

$$V_{R1} = V_C + V_L + V_{R3}$$

$$I_S = \frac{V_{R1}}{R_1} + I_L$$

$$I_S = \frac{V_C + V_L + V_{R3}}{R_1} + I_L$$

$$I_S = \frac{V_C}{R_1} + \frac{L}{R_1} \frac{dI_L}{dt} + \frac{V_{R3}}{R_1} + I_L$$

$$I_S = \frac{V_C}{R_1} + \frac{L}{R_1} \frac{dI_L}{dt} + \frac{R_3}{R_1} C \frac{dV_C}{dt} + I_L$$

$$I_L = I_{R2} + I_C$$

$$I_L = \frac{V_{R2}}{R_2} + C \frac{dV_C}{dt}$$

$$I_L = \frac{V_C + V_{R3}}{R_2} + C \frac{dV_C}{dt}$$

$$I_L = \frac{V_C}{R_2} + \frac{R_3}{R_2} I_C + C \frac{dV_C}{dt}$$

$$I_L = \frac{V_C}{R_2} + \frac{R_3}{R_2} C \frac{dV_C}{dt} + C \frac{dV_C}{dt}$$

$$I_L = \frac{1}{R_2} V_C + \left[\frac{R_3}{R_2} C + C \right] \frac{dV_C}{dt}$$

⇒

$$I_L - \frac{V_C}{R_2} = \frac{(R_2 + R_3)C}{R_2} \frac{dV_C}{dt}$$

$$\frac{dV_C}{dt} = \frac{R_2}{(R_2 + R_3)C} I_L - \frac{1}{(R_2 + R_3)C} V_C$$

$$I_S = \frac{1}{R_1} V_C + \frac{L}{R_1} \frac{dI_L}{dt} + \frac{R_3 C}{R_1} \left[\frac{R_2}{(R_2 + R_3)C} I_L - \frac{1}{(R_2 + R_3)C} V_C \right] + I_L$$

$$I_S = \left[\frac{1}{R_1} - \frac{R_3}{R_1(R_2 + R_3)} \right] V_C + \left[\frac{R_2 R_3}{R_1(R_2 + R_3)} + 1 \right] I_L + \frac{L}{R_1} \frac{dI_L}{dt}$$

$$\frac{dI_L}{dt} = \frac{R_1}{L} I_S - \frac{1}{L} \left[1 - \frac{R_3}{(R_2 + R_3)} \right] V_C - \frac{1}{L} \left[\frac{R_2 R_3}{R_2 + R_3} + R_1 \right] I_L$$

$$\frac{1}{C} \frac{R_2}{R_2 + R_3} = A \quad \frac{1}{(R_2 + R_3)C} = B \quad \frac{dV_C}{dt} = AI_L - BV_C \quad *$$

$$\frac{R_1}{L} = K \quad \frac{1}{L} \left[1 - \frac{R_3}{R_2 + R_3} \right] = M \quad \frac{1}{L} \left[\frac{R_2 R_3}{R_2 + R_3} + R_1 \right] = N \quad \frac{dI_L}{dt} = K - MV_C - NI_L$$

**

$\frac{d}{dt}$ ** put * inside ;

$$V_C = \frac{K}{M} I_S - \frac{N}{M} I_L - \frac{1}{M} \frac{dI_L}{dt}$$

$$\frac{d^2 I_L}{dt^2} = K \frac{dI_S}{dt} - M \frac{dV_C}{dt} - N \frac{dI_L}{dt}$$

$$\frac{d^2 I_L}{dt^2} + N \frac{dI_L}{dt} = K \frac{dI_S}{dt} - M (AI_L - BV_C)$$

$$\frac{d^2 I_L}{dt^2} + N \frac{dI_L}{dt} + NA I_L = K \frac{dI_S}{dt} + MBV_C$$

$$\frac{d^2 I_L}{dt^2} + N \frac{dI_L}{dt} + NA I_L = K \frac{dI_S}{dt} + MB \left[\frac{K}{M} I_S - \frac{N}{M} I_L - \frac{1}{M} \frac{dI_L}{dt} \right]$$

$$\frac{d^2 I_L}{dt^2} (N + B) + \frac{dI_L}{dt} (MA + NB) + (MA + NB) I_L = K \frac{dI_S}{dt} + BK I_S$$

\Rightarrow

$\frac{d}{dt}$ * put * * inside

$$\frac{d^2 V_c}{dt^2} = A \frac{dI_L}{dt} - B \frac{dV_c}{dt}$$

$$\frac{d^2 V_c}{dt^2} + B \frac{dV_c}{dt} = A \left[K I_s - M V_c - N I_L \right]$$

$$I_L = \frac{1}{A} \frac{dV_c}{dt} + \frac{B}{A} V_c$$

$$\frac{d^2 V_c}{dt^2} + B \frac{dV_c}{dt} + A M V_c = A K I_s - A N I_L$$

$$\frac{d^2 V_c}{dt^2} + B \frac{dV_c}{dt} + A M V_c = A K I_s - \left[N \frac{dV_c}{dt} + N B V_c \right]$$

$$\boxed{\frac{d^2 V_c}{dt^2} + (B+N) \frac{dV_c}{dt} + (A M + B N) V_c = A K I_s}$$