


AC Circuits:

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} u_1(t) \\ u_2(t) \end{bmatrix}$$

state space representation

\downarrow derivatives of state variables
 \downarrow state variables
 \swarrow input vector (source vector)

Ex:

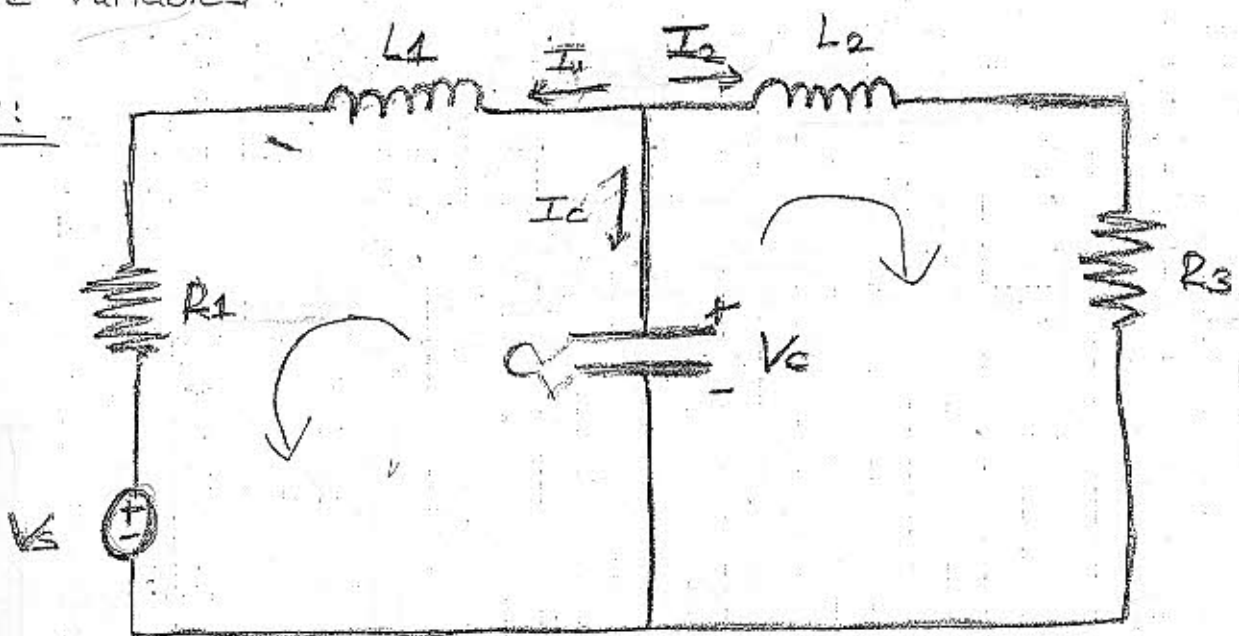

V_C, I_1, I_2 ← states

$$I_1 + I_2 + I_C = 0$$

$$I_1 + I_2 + C \frac{dV_C}{dt} = 0$$

$$-I_1 - I_2 = I_C$$

$$I_1 + I_2 + C \frac{dV_C}{dt} = 0$$

$$V_{L_1} + V_{R_1} + V_C = V_s$$

$$V_{L_2} + V_{R_3} = V_C$$

$$L_1 \frac{dI_1}{dt} + V_{R_1} + V_C = V_s$$

$$L_2 \frac{dI_2}{dt} + V_{R_3} = V_C$$

$$\frac{dI_2}{dt} = \frac{V_C - V_{R_3}}{L_2}$$

$$\Rightarrow \frac{dV_C}{dt} = -\frac{I_1}{C} - \frac{I_2}{C}$$

$$V_{L1} + V_{R1} + V_S = V_C$$

$$L_1 \frac{dI_1}{dt} + R_1 I_1 + V_S = V_C$$


$$\Rightarrow \boxed{\frac{dI_1}{dt} = \frac{-V_S}{L_1} - \frac{R_1}{L_1} I_1 + \frac{V_C}{L_1}}$$

$$V_C = V_{L2} + V_{R3}$$

$$V_C = L_2 \frac{dI_2}{dt} + I_2 R_3$$

$$\Rightarrow \boxed{\frac{dI_2}{dt} = \frac{V_C}{L_2} - \frac{R_3}{L_2} I_2}$$
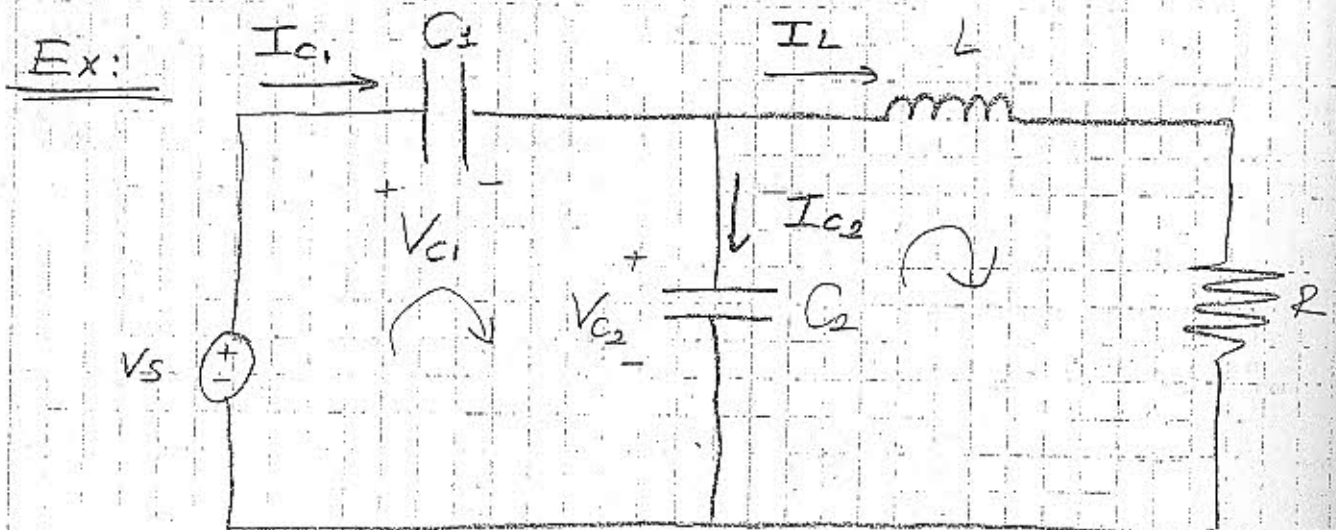
$$\begin{bmatrix} V_C \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/C & -1/C \\ 1/L_1 & -R_1/L_1 & 0 \\ 1/L_2 & 0 & -R_3/L_2 \end{bmatrix} \begin{bmatrix} V_C \\ I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} 0 \\ -1/L_1 \\ 0 \end{bmatrix} V_S$$



$$I_{C1} = I_{C2} + I_L$$

$$C_1 \frac{dV_{C1}}{dt} = C_2 \frac{dV_{C2}}{dt} + I_L$$

$$V_S = V_{C1} + V_{C2}$$

$$I_{C1} = C_1 \frac{dV_{C1}}{dt} \implies I_{C1} = C_1 \frac{d}{dt} [V_S - V_{C2}]$$

$$C_2 \frac{dV_{C2}}{dt} + I_L = C_1 \frac{d}{dt} [V_S - V_{C2}]$$

$$(C_1 + C_2) \frac{dV_{C2}}{dt} = C_1 \frac{dV_S}{dt} - I_L$$

$$\frac{dV_{C2}}{dt} = \frac{C_1}{C_1 + C_2} \frac{dV_S}{dt} - \frac{1}{C_1 + C_2} I_L$$

$$V_{C2} = V_L + V_R$$

$$V_{C2} = L \frac{dI_L}{dt} + R \cdot I_L \implies$$

$$\frac{dI_L}{dt} = \frac{V_{C2}}{L} - \frac{R}{L} I_L$$

$$\begin{bmatrix} \dot{V}_{C2} \\ \dot{I}_L \end{bmatrix} = \begin{bmatrix} 0 \\ 1/L \end{bmatrix} - \begin{bmatrix} -1/(C_1 + C_2) \\ -R/L \end{bmatrix} \begin{bmatrix} V_{C2} \\ I_L \end{bmatrix} + \begin{bmatrix} C_1/(C_1 + C_2) \\ 0 \end{bmatrix} \frac{dV_S}{dt}$$

$$I_{C1} - I_{C2} = I_L$$

$$-V_S + V_{C1} + V_{C2} = 0$$

$$V_L + V_R = V_{C2}$$

* Either V_{C1} or V_{C2} can be written in terms of the other variable without any state equation using $-V_S + V_{C1} + V_{C2} = 0$

Analysis of Nth order circuits:

$$\frac{d^n x}{dt^n} + a_1 \frac{d^{n-1} x}{dt^{n-1}} + \dots + a_n x = b_0 \frac{d^m u(t)}{dt^m} + b_1 \frac{d^{m-1} u(t)}{dt^{m-1}} + \dots + b_m u(t)$$

requires N initial conditions

$$x(0); \frac{dx}{dt}(0); \dots; \frac{d^{n-1} x}{dt^{n-1}}(0)$$

$$x(t) = \underbrace{x}_{\text{zero-state}}(t) + \underbrace{x}_{\text{zero-input}}(t)$$

due to input only (u(t))
and initial conditions
are zero (x(0) = 0;

$$\frac{dx}{dt}(0) = 0; \dots; \frac{d^{n-1} x}{dt^{n-1}}(0) = 0)$$

due to initial conditions
(initial conditions are
non-zero) but u(t) = 0

x(t) → state
u(t) → input

Let's find zero-input solution

assume u(t) = 0 ; instead of "d/dt" terms
put "s"

$$s^n + a_1 s^{n-1} + a_2 s^{n-2} + \dots + a_{n-1} s + a_n = 0$$

↪ characteristic equation

* Zeros (roots) of the characteristic equation are the natural frequencies of the circuit.

* If all the natural frequencies of the circuit are distinct (different from each other)

$$X_{\text{homogeneous}} = X_{\text{zero-input}} = \sum_{i=1}^n K_i e^{s_i t}$$

$n \rightarrow$ order of char. eqn.

(not always true)

\rightarrow parameters unknown due to initial condition

\rightarrow parameters are evaluated

$$s_i \neq s_k \quad \text{for all } \begin{matrix} 1 < i < n \\ 1 < k < n \end{matrix}$$

268
300

$s_i =$ natural frequency

$K_i =$ constant to be determined by initial conditions

* If there are some natural frequencies which are equal to each other. (for some i and k $s_i = s_k$)

\rightarrow meaning some natural frequency has a multiplicity.

(Ex: $s_1 = -2$, $s_2 = -2$, $s_4 = -2$
 $s_1 = s_2 = s_4$ multiplicity of $s = -2$ is 3)

$$X_h(t) = \sum_{i=1}^N \sum_{m=0}^{d_i-1} K_{im} t^m e^{s_i t}$$

$N = \#$ of distinct roots

↓
number

$s_k =$ natural frequencies with multiplicities d_k

Ex: $(s-1)(s-1)(s-2)(s+j)(s-j)(s+j)(s-j) = 0$

7 roots

4 distinct roots

multiplicity of $s_1 = 1$ 2

" " $s_2 = 2$ 1

" " $s_3 = -j$ 2

" " $s_4 = j$ 2

$$= K_{10} t e^t + K_{11} e^t + K_{20} e^{2t} + K_{30} t e^{-jt} + K_{31} e^{-jt} + K_{40} t e^{jt} + K_{41} e^{jt}$$

Complete Response:

$X(t) = X_h(t) + X_p(t)$ (generally $X_p(t)$ (particular solution) is similar to input $u(t)$)

Let $u(t) = V_0 \cos(\omega t + \theta)$

input ↓ amplitude ↓ angular frequency ↓ phase

what is $X_p(t)$?
↳ 2 situations

↳ ① $s_k \neq j\omega$ for $k=1, \dots, N$
 ↳ angular frequency of input
 ↳ any natural frequency

$$X_p(t) = A_m \cos(\omega t + \theta + \phi)$$

A_m → amplitude will change
 ω → angular frequency is same
 ϕ → extra phase difference

↳ ② $s_k = j\omega$ for some k (no real part for s_k exist)
 s_k is purely imaginary
 $s_k = 0 + j\omega$

$$X_p(t) = t^{d_k} A_m \cos(\omega t + \theta + \phi)$$

d_k is the multiplicity of s_k .

Characteristic of complete solution (giving same input)
 $(u(t) = V_0 \cos(\omega t + \theta))$

① K_{im} values are determined according to initial conditions such that $X_h(t) = 0$ in that case

$$X(t) = \underbrace{X_h(t)}_0 + X_p(t)$$

$X(t) = X_p(t)$ (since $X_h(t) = 0$ there will be no transient solution.)


② $\text{Re}\{s_k\} < 0 \quad k=1, \dots, N$

as $t \rightarrow \infty$, $|s^{kt}| \rightarrow 0$; homogeneous solution will go to 0 as $t \rightarrow \infty$ and only particular solution will remain. (Steady-state) (SS) $\hookrightarrow X_p(t)$

Special case ($u(t) = V_0 \cos(\omega t + \theta)$)

as $t \rightarrow \infty$, $x(t) = X_p(t) \rightarrow$ sinusoidal steady state solution is obtained (SSS)

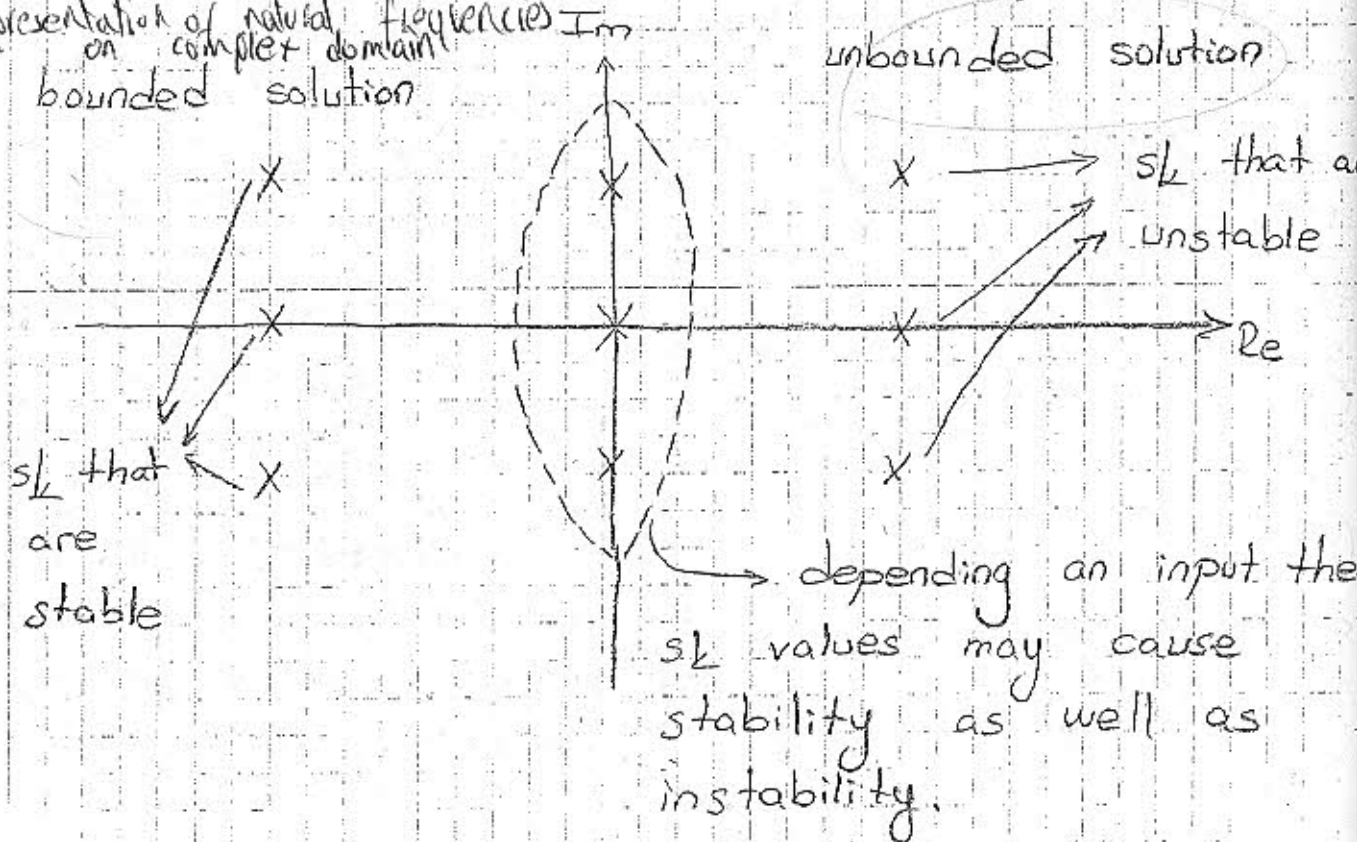Representation of natural frequencies on complex domain



$$\textcircled{3} \operatorname{Re}\{s_k\} \leq 0 \quad k=1, \dots, N \quad \left. \vphantom{\operatorname{Re}\{s_k\}} \right\} \text{same roots (zeros)}$$

have zero real parts} and $u(t) = V_0 \cos(\omega t + \theta)$
 \uparrow
 same input

$$\hookrightarrow a) s_k \neq j\omega$$

let $x_{ho}(t)$ be a linear combination of sinusoidals due to roots with zero real part.

$$x(t) = x_h(t) + x_p(t)$$

$$x_h(t) = \underbrace{x_{ho}(t)} + \underbrace{x_{hnon-0}(t)}$$

some sinusoidals
 + some DC terms

decaying terms

$$x(t) = x_h(t) + x_p(t)$$

$$\hookrightarrow A_m \cos(\omega t + \theta + \phi)$$

as $t \rightarrow \infty$;

$$x(t) = x_{ho}(t) + \underbrace{A_m \cos(\omega t + \theta + \phi)}_{x_p(t)}$$

$$x_p(t)$$

SSS

(sinusoidal steady state)

SS \rightarrow steady state part

↳ b) $s_k = j\omega \rightarrow$ unbounded situation

$$X_p(t) = t^{dk} A_m \cos(\omega t + \theta + \phi)$$

④ $\operatorname{Re}\{s_i\} > 0$ for some s_i (not important to look at the input)

$x(t)$ is unstable

⑤ $\operatorname{Re}\{s_i\} = 0$ and $s_i = j\omega_0$ but s_i has a

different from input

angular frequency ω ($\omega_0 \neq \omega$)

multiplicity, $x(t) \rightarrow$ unbounded

unbounded solution \rightarrow no steady state

Case 2:

$$\Delta = \frac{d}{dt}$$

$$\Delta' = \frac{d}{dt}$$

$$\Delta^2 = \frac{d^2}{dt^2}$$

$$(\Delta^3 + 4\Delta^2 + 6\Delta + 4) X(t) = u(t)$$

$$\text{char-equation} = s^3 + 4s^2 + 6s + 4 = 0$$

$$(s+1+j)(s+1-j)(s+2) = 0$$

$$s_1 = -1 - j$$

$$s_2 = -1 + j$$

$$s_3 = -2$$

all multiplicities are 1

$$\operatorname{Re}\{s_1\} < 0 \quad \operatorname{Re}\{s_2\} < 0 \quad \operatorname{Re}\{s_3\} < 0$$

2nd case

$$X_h(t) = \underbrace{A_1 e^{-2t}}_{\text{due to } s_3 = -2} + \underbrace{A_2 e^{-t} \cos(t) + A_3 e^{-t} \sin(t)}_{\text{due to } s_1 = s_2^*}$$

$$s_1 = -1 + j \quad s_2 = -1 - j$$

assume $w(t) = 4 \cos(2t + 30^\circ)$

$$X_p(t) = K \cos(2t + \phi) = K_1 \cos(2t) + K_2 \sin(2t)$$

↓
put this function in diff-eqn. and find K_1 and K_2

$$X_p(t) = \frac{1}{\sqrt{10}} \cos\left(2t + 30 - 180^\circ + \tan^{-1}\left(\frac{1}{3}\right)\right)$$

$$X(t) = X_h(t) + X_p(t)$$

$$\lim_{t \rightarrow \infty} X(t) = X_p(t)$$

bounded SSS

Case - 3a

Ex: $(D^3 + D^2 + D + 1) X(t) = u(t) = 4 \cos(2t + 30^\circ)$

$$\omega = 2$$

$$s_k \neq j\omega$$

$$s^3 + s^2 + s + 1 = 0 = (s+1)(s+j)(s-j) = 0$$

$$s_1 = -1 \quad \operatorname{Re}\{s_1\} < 0$$

$$s_2 = -j \quad \operatorname{Re}\{s_2\} = 0$$

$$s_3 = j \quad \operatorname{Re}\{s_3\} = 0$$

Case 3a is provided

$$X_h(t) = K_1 e^{-t} + K_2 \cos t + K_3 \overset{+j}{\sin t}$$

$$X_p(t) = \frac{4}{\sqrt{45}} \cos\left(2t + 30^\circ + 180^\circ - \underbrace{\tan^{-1}(2)}_{?}\right)$$

$$X(t) = X_h(t) + X_p(t)$$

as $t \rightarrow \infty$ $X(t) = \underbrace{K_2 \cos(t) + K_3 \sin(t)}_{SS} + \underbrace{X_p(t)}_{SSS}$

SS

Case 3b:

$$(D^3 + D^2 + 4D + 4) X(t) = u(t) = 4 \cos(2t + 30^\circ)$$

$$s^3 + s^2 + 4s + 4 = 0$$

$$(s+2j)(s-2j)(s+1) = 0$$

$$s_1 = 2j \quad s_2 = -2j \quad s_3 = -1$$

$$\operatorname{Re}\{s_1\} = \operatorname{Re}\{s_2\} = 0 \quad \operatorname{Re}\{s_3\} < 0 \quad \boxed{\omega = 2}$$

$$\boxed{s_1 = 2j = j\omega} \rightarrow \text{case 3b}$$

$$X_h(t) = K_1 e^{-t} + K_2 \cos(2t) + K_3 \sin(2t)$$

$$X_p(t) = M t \cos(2t + \phi)$$

$$X_p(t) = t [M_1 \cos 2t + M_2 \sin 2t]$$

$$X_p(t) = \frac{1}{\sqrt{5}} \cos\left(2t + 30 - 180 + \tan^{-1}\left(\frac{1}{2}\right)\right)$$

$$X(t) = X_h(t) + X_p(t)$$

$$\text{as } t \rightarrow \infty \quad X(t) = K_2 \cos(2t) + K_3 \sin(2t) + X_p(t)$$

$$X(t) \rightarrow \pm \infty$$

unbounded

no steady-state solution exist

4th case:

$$\underline{\text{Ex:}} \quad (s-1)(s+1)(s+j)(s-j) = 0$$

$$u(t) = 4 \cos(2t + 30^\circ)$$

$$s_1 = 1$$

$$s_3 = -j$$

$$k_1 e^t + k_2 e^{-t} + k_3 \cos(t) + k_4 \sin(t)$$

$$s_2 = -1$$

$$s_4 = j$$

$$X_h(t) = K_1 e^t + K_2 e^{-t} + K_3 \cos t + K_4 \sin t$$

$$X_p(t) = M \left[\cos(2t + \phi) \right]$$

as $t \rightarrow \infty$; $X(t) \rightarrow \infty$

Case 5:

$$(\mathcal{D}^5 + \mathcal{D}^4 + 2\mathcal{D}^3 + 2\mathcal{D}^2 + \mathcal{D} + 1) X(t) = u(t) = 4 \cos(2t + 30^\circ)$$

$$(s+1) (s+j)^2 (s-j)^2 = 0$$

$$s_1 = -1 \quad s_2 = -j \quad s_3 = j$$

multp = 2 multp = 2

$$X_h(t) = K_1 e^{-t} + K_2 \cos(t) + K_3 \sin(t) + K_4 t \cos t + K_5 t \sin t$$

due to multiplicity
of s_2 and s_3

$$s_k \neq j\omega = 2j \quad k = 1, 2, 3$$

$$X_p(t) = M \cos(2t + \phi)$$

$$\therefore = \frac{4}{\sqrt{2197}} \cos\left(2t + 30^\circ - \tan^{-1}\left(\frac{46}{9}\right)\right)$$