


AC Circuits:

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} u_1(t) \\ u_2(t) \end{bmatrix}$$

state space representation

↓ derivatives of state variables  
 ↓ state variables  
 ↘ input vector (source vector)

Ex:

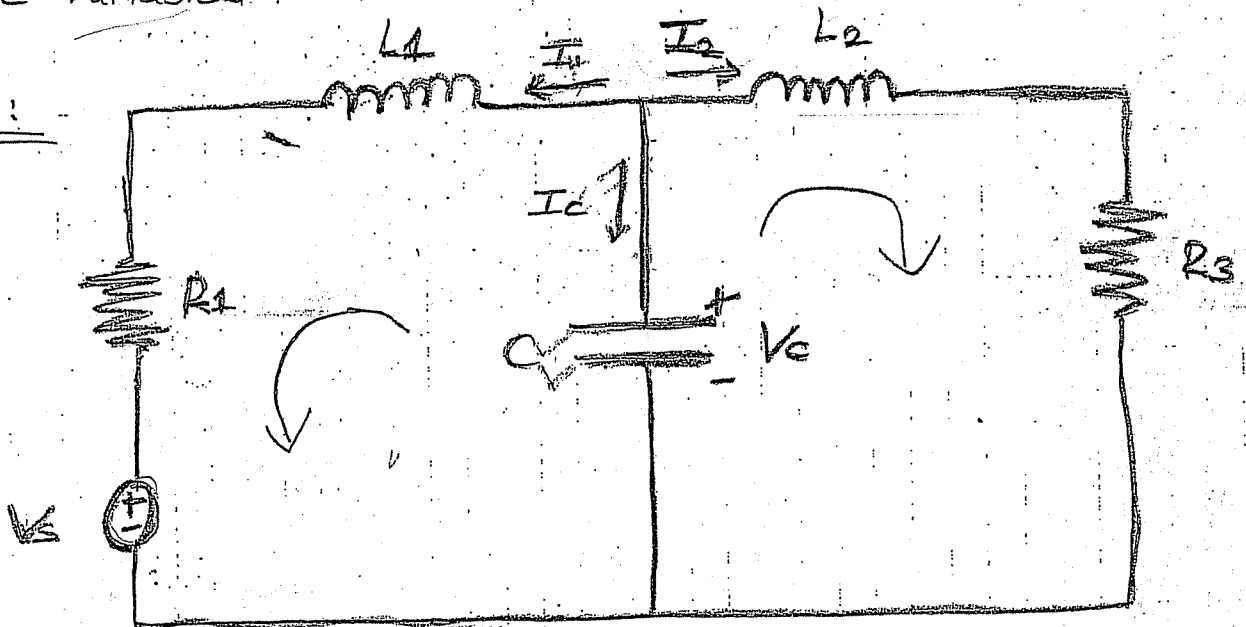

$V_C, I_1, I_2$  ← states

$$I_1 + I_2 + I_C = 0$$

$$I_1 + I_2 + C \frac{dV_C}{dt} = 0$$

$$\Rightarrow \frac{dV_C}{dt} = -\frac{I_1}{C} - \frac{I_2}{C}$$

$$-I_1 - I_2 = I_C$$

$$I_1 + I_2 + C \frac{dV_C}{dt} = 0$$

$$V_{L1} + V_{R1} + V_C = V_C$$

$$V_{L2} + V_{R3} = V_C$$

$$L_1 \frac{dI_1}{dt} + V_{R1} + V_C = V_C$$

$$L_2 \frac{dI_2}{dt} + V_{R3} = V_C$$

$$\frac{dI_2}{dt} = \frac{V_C - V_{R3}}{L_2}$$

$$V_{L1} + V_{R1} + V_S = V_C$$

$$L_1 \frac{dI_1}{dt} + R_1 I_1 + V_S = V_C$$

$$\Rightarrow \boxed{\frac{dI_1}{dt} = \frac{-V_S}{L_1} - \frac{R_1}{L_1} I_1 + \frac{V_C}{L_1}}$$


$$V_C = V_{L2} + V_{R3}$$

$$V_C = L_2 \frac{dI_2}{dt} + I_2 R_3$$

$$\Rightarrow \boxed{\frac{dI_2}{dt} = \frac{V_C}{L_2} - \frac{R_3}{L_2} I_2}$$

$$\begin{bmatrix} V_C \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/C & -1/C \\ 1/L_1 & -R_1/L_1 & 0 \\ 1/L_2 & 0 & -R_3/L_2 \end{bmatrix} \begin{bmatrix} V_C \\ I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} 0 \\ -1/L_1 \\ 0 \end{bmatrix} V_S$$

Ex:!

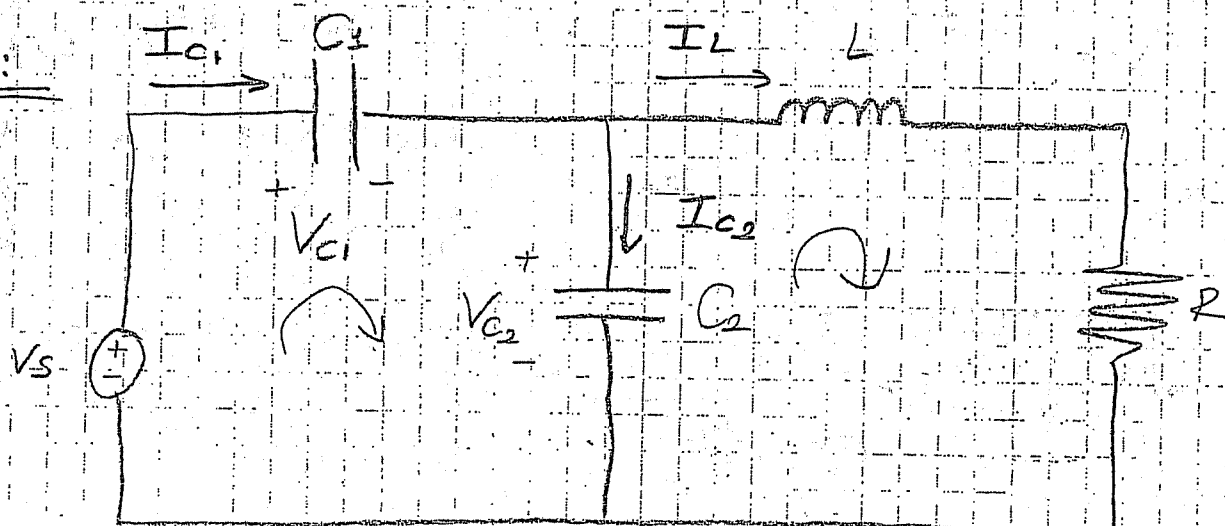

$$I_L = I_C + I_{C2}$$

$$I_{C1} = I_{C2} + I_L$$

$$C_1 \frac{dV_{C1}}{dt} = C_2 \frac{dV_{C2}}{dt} + I_L$$

$$V_S = V_{C1} + V_{C2}$$

$$I_{C1} = C_1 \frac{dV_{C1}}{dt} \implies I_{C1} = C_1 \frac{d}{dt} [V_S - V_{C2}]$$

$$C_2 \frac{dV_{C2}}{dt} + I_L = C_1 \frac{d}{dt} [V_S - V_{C2}]$$

$$(C_1 + C_2) \frac{dV_{C2}}{dt} = C_1 \frac{dV_S}{dt} - I_L$$

$$\frac{dV_{C2}}{dt} = \frac{C_1}{C_1 + C_2} \frac{dV_S}{dt} - \frac{1}{C_1 + C_2} I_L$$

$$V_{C2} = V_L + V_R$$

$$V_{C2} = L \frac{dI_L}{dt} + R \cdot I_L \implies$$

$$\frac{dI_L}{dt} = \frac{V_{C2}}{L} - \frac{R}{L} I_L$$

$$\begin{bmatrix} \dot{V}_{C2} \\ \dot{I}_L \end{bmatrix} = \begin{bmatrix} 0 & -1/(C_1 + C_2) \\ 1/L & -R/L \end{bmatrix} \begin{bmatrix} V_{C2} \\ I_L \end{bmatrix} + \begin{bmatrix} C_1/(C_1 + C_2) \frac{dV_S}{dt} \\ 0 \end{bmatrix}$$

$$I_{C1} - I_{C2} = I_L$$

$$-V_S + V_{C1} + V_{C2} = 0$$

$$V_L + V_R = V_{C2}$$

\* Either  $V_{C1}$  or  $V_{C2}$  can be written in terms of the other variable without any state equation

$$\text{using } -V_S + V_{C1} + V_{C2} = 0$$

## Analysis of $N^{\text{th}}$ order circuits:

$$\frac{d^n x}{dt^n} + a_1 \frac{d^{n-1} x}{dt^{n-1}} + \dots + a_n x = b_0 \frac{d^m u(t)}{dt^m} + b_1 \frac{d^{m-1} u(t)}{dt^{m-1}} + \dots + b_m u(t)$$

requires  $N$  initial conditions

$$x(0); \frac{dx}{dt}(0); \dots, \frac{d^{n-1} x}{dt^{n-1}}(0)$$

$$x(t) = \underbrace{X}_{\text{zero-state}}(t) + \underbrace{X}_{\text{zero-input}}(t)$$

due to input only ( $u(t)$ )  
and initial conditions  
are zero ( $x(0) = 0$ ;

due to initial conditions  
(initial conditions are  
non-zero) but  $u(t) = 0$

$$\frac{dx}{dt}(0) = 0; \dots; \frac{d^{n-1} x}{dt^{n-1}}(0) = 0$$

$x(t)$  → state

$u(t)$  → input

Let's find zero-input solution

assume  $u(t) = 0$ , instead of " $\frac{d}{dt}$ " terms  
put "s"

$$s^n + a_1 s^{n-1} + a_2 s^{n-2} + \dots + a_{n-1} s + a_n = 0$$

→ characteristic equation

\* Zeros (roots) of the characteristic equation are the natural frequencies of the circuit.

\* If all the natural frequencies of the circuit are distinct (different from each other)

$$X_{\text{homogeneous}} = X_{\text{zero-input}} = \sum_{i=1}^n K_i e^{s_i t}$$

$n \rightarrow$  order of char. eqn.

(not always true)

$\rightarrow$  parameters unknown due to initial condition

$\rightarrow$  parameters are evaluated

$$s_i \neq s_k \quad \text{for all } \boxed{1 < i < n} \\ \boxed{1 < k < n}$$

$s_i =$  natural frequency

$K_i =$  constant to be determined by initial conditions

\* If there are some natural frequencies which are equal to each other. (for some  $i$  and  $k$   $s_i = s_k$ )

$\hookrightarrow$  meaning some natural frequency has a multiplicity.

(Ex:  $s_1 = -2$ ,  $s_2 = -2$ ,  $s_4 = -2$ )

$s_1 = s_2 = s_4$  multiplicity of  $s = -2$  is 3)

$$X_h(t) = \sum_{i=1}^N \sum_{m=0}^{d_i-1} K_{im} t^m e^{s_i t}$$

$N = \#$  of distinct roots

↓  
number

$s_k =$  natural frequencies with multiplicities  $d_k$

Ex:  $(s-1)(s-1)(s-2)(s+j)(s-j)(s+j)(s-j) = 0$

$s_1=1$        $s_2=2$        $s_3=-j$        $s_4=j$

7 roots

4 distinct roots

multiplicity of  $s_1 = 1$       2

"      "       $s_2 = 2$       1

"      "       $s_3 = -j$       2

"      "       $s_4 = j$       2

$$= K_{10} t e^t + K_{11} e^t + K_{20} e^{2t} + K_{30} t e^{-jt} + K_{31} e^{-jt} + K_{40} t e^{jt} + K_{41} e^{jt}$$

Complete Response:

$\{ X(t) = X_h(t) + X_p(t) \}$  (generally  $X_p(t)$  (particular solution) is similar to input  $u(t)$ )

Let  $u(t) = V_0 \cos(\omega t + \theta)$

↑ input      ↓ amplitude      ↘ angular frequency      → phase

what is  $X_p(t)$ ?

↳ 2 situations

↳ ①  $s_k \neq j\omega$  for  $k=1, \dots, N$

angular frequency of input  
any natural frequency

$$X_p(t) = A_m \cos(\omega t + \theta + \phi)$$

amplitude will change      angular frequency is same      extra phase difference

↳ ②  $s_k = j\omega$  for some  $k$  (no real part for  $s_k$  exist)

$s_k$  is purely imaginary

$$s_k = 0 + j\omega$$

$$X_p(t) = t^{d_k} A_m \cos(\omega t + \theta + \phi)$$

$d_k$  is the multiplicity of  $s_k$

Characteristic of complete solution (giving some input  $u(t) = V_0 \cos(\omega t + \theta)$ )

①  $K_{im}$  values are determined according to initial conditions such that  $X_h(t) = 0$  in that case

$$X(t) = \underbrace{X_h(t)}_0 + X_p(t)$$

$X(t) = X_p(t)$  / since  $X_h(t) = 0$  there will be no transient solution.


②  $\text{Re}\{s_k\} < 0 \quad k=1, \dots, N$

as  $t \rightarrow \infty$ ,  $|s^{kt}| \rightarrow 0$ ; homogeneous solution will go to 0 as  $t \rightarrow \infty$  and only particular solution will remain. (Steady-state) (SS)  $\hookrightarrow X_p(t)$

Special case ( $u(t) = V_0 \cos(\omega t + \theta)$ )

as  $t \rightarrow \infty$ ,  $X(t) = X_p(t) \rightarrow$  sinusoidal steady state solution is obtained (SSS)

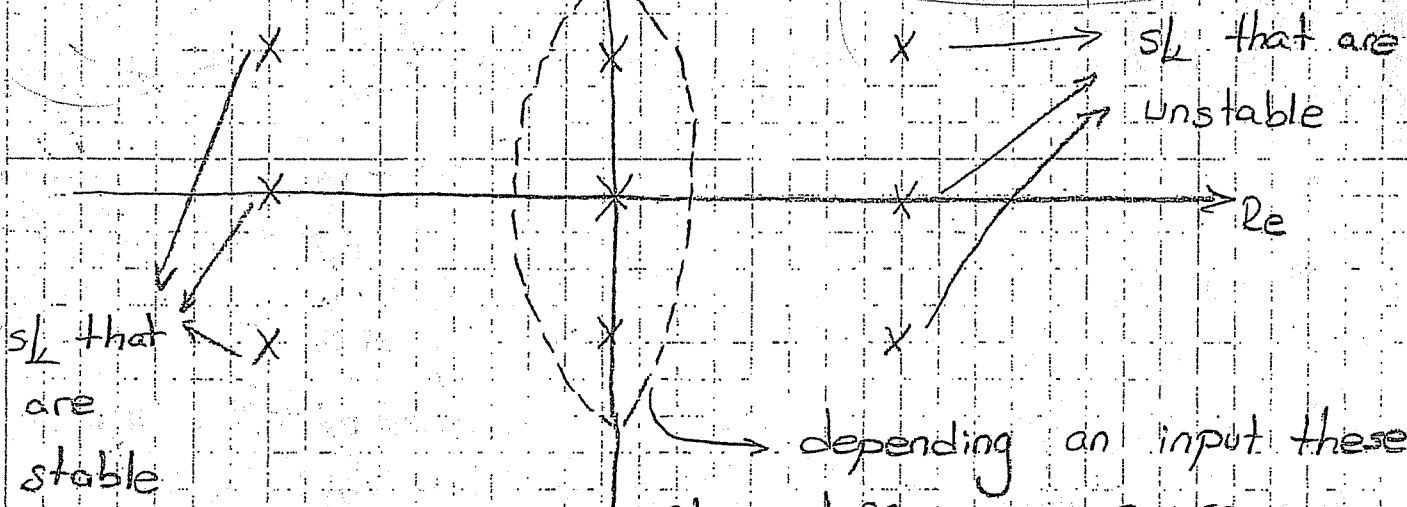Representation of natural frequencies on complex domain



depending on input these  $s_k$  values may cause stability as well as instability.



③  $\text{Re}\{s_k\} \leq 0 \quad k=1, \dots, N$  } same roots (zeros)

have zero real parts } and  $u(t) = V_0 \cos(\omega t + \theta)$   
 ↑  
 same input

↳ a)  $s_k \neq j\omega$

let  $x_{ho}(t)$  be a linear combination of sinusoidals due to roots with zero real part.

$$x(t) = x_h(t) + x_p(t)$$

$$x_h(t) = \underbrace{x_{ho}(t)}_{\text{some sinusoidals}} + \underbrace{x_{h, \text{non-0}}(t)}_{\text{decaying terms}}$$

+ some DC terms

$$x(t) = x_h(t) + x_p(t)$$

$$\hookrightarrow A_m \cos(\omega t + \theta + \phi)$$

as  $t \rightarrow \infty$ ,

$$x(t) = x_{ho}(t) + \underbrace{A_m \cos(\omega t + \theta + \phi)}_{x_p(t)}$$

$$x_p(t)$$

↓  
SSS

(sinusoidal steady state)

SS → steady state part

↳ b)  $s_k = j\omega \rightarrow$  unbounded situation

$$x_p(t) = t^{dk} A_m \cos(\omega t + \theta + \phi)$$

④  $\operatorname{Re}\{s_i\} > 0$  for some  $s_i$  (not important to look at the input)

$x(t)$  is unstable

⑤  $\operatorname{Re}\{s_i\} = 0$  and  $s_i = j\omega_0$  but  $s_i$  has a

different from input

angular frequency  $\omega$  ( $\omega_0 \neq \omega$ )

multiplicity,  $x(t) \rightarrow$  unbounded

unbounded solution  $\rightarrow$  no steady state

Case 2:

$$\Delta = \frac{d}{dt}$$

$$\Delta' = \frac{d}{dt}$$

$$\Delta^2 = \frac{d^2}{dt^2}$$

$$(\Delta^3 + 4\Delta^2 + 6\Delta + 4) X(t) = u(t)$$

$$\text{char-equation} = s^3 + 4s^2 + 6s + 4 = 0$$

$$(s+1+j)(s+1-j)(s+2) = 0$$

$$s_1 = -1 - j$$

$$s_2 = -1 + j$$

$$s_3 = -2$$

all multiplicities are 1

$$\operatorname{Re}\{s_1\} < 0 \quad \operatorname{Re}\{s_2\} < 0 \quad \operatorname{Re}\{s_3\} < 0$$

2<sup>nd</sup> case

$$X_h(t) = \underbrace{A_1 e^{-2t}}_{\text{due to } s_3 = -2} + \underbrace{A_2 e^{-t} \cos(t) + A_3 e^{-t} \sin(t)}_{\text{due to } s_1 = s_2^*}$$

$$s_1 = -1 + j \quad s_2 = -1 - j$$

assume  $u(t) = 4 \cos(2t + 30^\circ)$

$$X_p(t) = K \cos(2t + \phi) = \underbrace{K_1 \cos(2t)}_{\downarrow} + \underbrace{K_2 \sin(2t)}_{\downarrow}$$

put this function in diff. eqn. and find  $K_1$  and  $K_2$

$$X_p(t) = \frac{1}{\sqrt{10}} \cos\left(2t + 30 - 180^\circ + \tan^{-1}\left(\frac{1}{3}\right)\right)$$

$$X(t) = X_h(t) + X_p(t)$$

$$\lim_{t \rightarrow \infty} X(t) = \underbrace{X_p(t)}_{\text{bounded SSS}}$$

Case 3a

Ex:  $(D^3 + D^2 + D + 1) X(t) = u(t) = 4 \cos(2t + 30^\circ)$

$$\omega = 2$$

$$sk \neq j\omega$$

$$s^3 + s^2 + s + 1 = 0 = (s+1)(s+j)(s-j) = 0$$

$$s_1 = -1$$

$$\operatorname{Re}\{s_1\} < 0$$

$$s_2 = -j$$

$$\operatorname{Re}\{s_2\} = 0$$

Case 3a is provided

$$s_3 = j$$

$$\operatorname{Re}\{s_3\} = 0$$

$$X_h(t) = K_1 e^{-t} + K_2 \cos t + K_3 \overset{+j}{\sin t}$$

$$X_p(t) = \frac{4}{\sqrt{45}} \cos(2t + 30^\circ + 180^\circ - \tan^{-1}(2))$$

$$X(t) = X_h(t) + X_p(t)$$

as  $t \rightarrow \infty$   $X(t) = K_2 \cos(t) + K_3 \sin(t) + X_p(t)$

SSS

SS

Case 3b:

$$(D^3 + D^2 + 4D + 4) X(t) = u(t) = 4 \cos(2t + 30^\circ)$$

$$s^3 + s^2 + 4s + 4 = 0$$

$$(s+2j)(s-2j)(s+1) = 0$$

$$s_1 = 2j \quad s_2 = -2j \quad s_3 = -1$$

$$\operatorname{Re}\{s_1\} = \operatorname{Re}\{s_2\} = 0 \quad \operatorname{Re}\{s_3\} < 0 \quad \boxed{\omega = 2}$$

$$\boxed{s_1 = 2j = j\omega} \rightarrow \text{case 3b}$$

$$X_h(t) = K_1 e^{-t} + K_2 \cos(2t) + K_3 \sin(2t)$$

$$X_p(t) = M t \cos(2t + \theta)$$

$$X_p(t) = t [M_1 \cos 2t + M_2 \sin 2t]$$

$$X_p(t) = \frac{1}{\sqrt{5}} \cos(2t + 30 - 180 + \tan^{-1}(\frac{1}{2}))$$

$$X(t) = X_h(t) + X_p(t)$$

$$\text{as } t \rightarrow \infty \quad X(t) = K_2 \cos(2t) + K_3 \sin(2t) + X_p(t)$$

$$X(t) \rightarrow \pm \infty$$

unbounded

no steady-state solution exist

4<sup>th</sup> case:

$$\underline{\text{Ex:}} \quad (s-1)(s+1)(s+j)(s-j) = 0$$

$$u(t) = 4 \cos(2t + 30^\circ)$$

$$s_1 = 1 \quad s_3 = -j \quad K_1 e^t + K_2 e^{-t} + K_3 \cos(t) + K_4 \sin(t)$$

$$s_2 = -1 \quad s_4 = j$$

$$X_h(t) = K_1 e^t + K_2 e^{-t} + K_3 \cos t + K_4 \sin t$$

$$X_p(t) = M \left[ \cos(2t + \phi) \right]$$

as  $t \rightarrow \infty$ ,  $X(t) \rightarrow \infty$

Case 5:

$$(\mathcal{D}^5 + \mathcal{D}^4 + 2\mathcal{D}^3 + 2\mathcal{D}^2 + \mathcal{D} + 1) X(t) = u(t) = 4 \cos(2t + 30^\circ)$$

$$(s+1)(s+j)^2(s-j)^2 = 0$$

$$s_1 = -1 \quad s_2 = -j \quad s_3 = j$$

multp = 2      multp = 2


$$X_h(t) = K_1 e^{-t} + K_2 \cos(t) + K_3 \sin(t) + \underbrace{K_4 t \cos t + K_5 t \sin t}_{\substack{\downarrow \downarrow \\ \text{due to multiplicity} \\ s_2 \text{ and } s_3}}$$

$$s_k \neq j\omega = 2j \quad k = 1, 2, 3$$

$$X_p(t) = M \cos(2t + \phi)$$

$$\therefore = \frac{4}{\sqrt{2197}} \cos\left(2t + 30^\circ - \tan^{-1}\left(\frac{46}{9}\right)\right)$$

Ex:

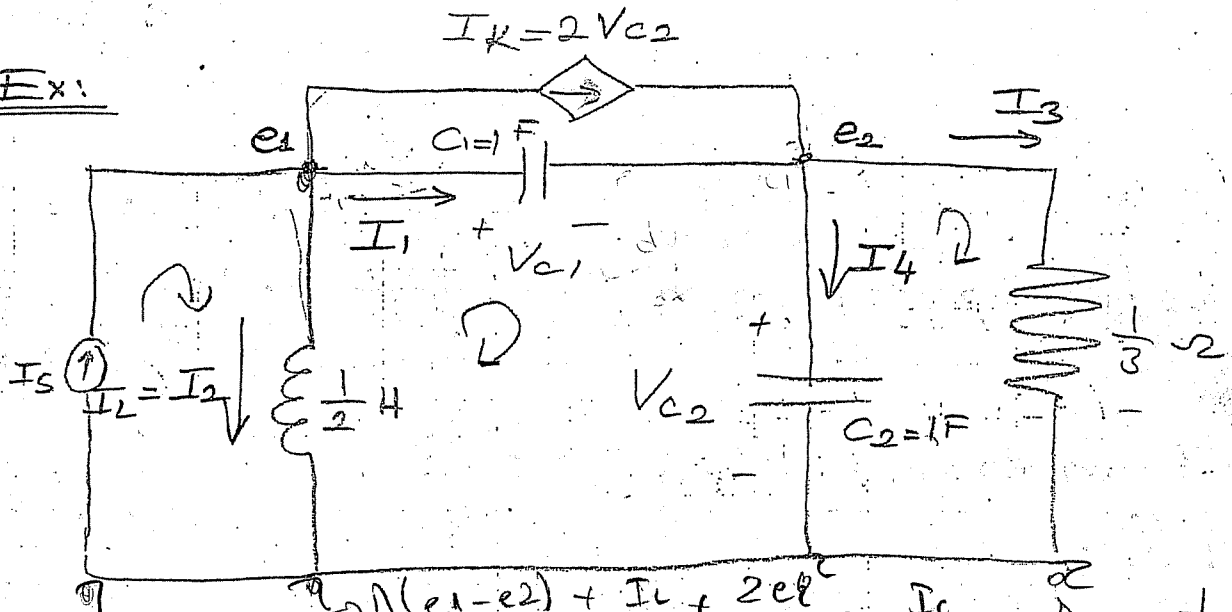

$$I_s = I_1 + I_2 + 2V_{c2}$$

$$I_s = \Delta(e_1 - e_2) + I_L + 2e_2$$

$$I_1 + I_k = I_4 + I_3$$

$$1 \cdot \Delta(e_1 - e_2) + 2e_2 = 1 \cdot \Delta \cdot e_2 + \frac{e_2}{1/3}$$

$$e_1 = \frac{1}{2} \Delta I_L$$

$$\Delta e_1 - \Delta e_2 + I_L = I_s$$

$$e_1(\Delta) + e_2(-\Delta + 2) + I_L(1) = I_s$$

$$\Delta e_1 + (-2\Delta - 1)e_2 = 0$$

$$\frac{1}{2} \Delta e_1 - I_L = 0$$

$$\begin{bmatrix} \Delta & -\Delta + 2 & 1 \\ \Delta & -2\Delta - 1 & 0 \\ 1 & 0 & \frac{1}{2}\Delta \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ I_L \end{bmatrix} = \begin{bmatrix} I_s \\ 0 \\ 0 \end{bmatrix}$$

P(Δ)

$$V_L = L \frac{dI_L}{dt}$$

$$e_1 = \frac{L}{2} \frac{dI_L}{dt}$$

Let's find  $\det(P(D))$

$$D \left[ (-2D-1) \frac{1}{2} D - 0 \right] - (-D+2) \left[ \frac{1}{2} D \cdot D - 0 \right] -$$

$$+ 1 \left[ -(-2D-1)(-1) \right]$$

$$= D^3 - \frac{D^2}{2} + \frac{D^3}{2} - D^2 - 2D - 1$$

$$= \frac{-D^3}{2} - \frac{3D^2}{2} - 2D - 1 = \det(P(D))$$

\* Natural frequencies of LTI network (circuit) are the roots of the polynomial  $\det(P(D)) = 0$  where  $P(D)$  is the matrix with differential equation terms that describe the network.

instead of  $D$  put  $s$  in the polynomial

$$-\frac{s^3}{2} - \frac{3}{2}s^2 - 2s - 1 = 0$$

$$-(s+1)(s^2+2s+2) = 0$$

$$s_1 = -1 \quad s_2, s_3 = -1 \mp j$$

$$\operatorname{Re}\{s_1\} < 0$$

$$\operatorname{Re}\{s_2\} < 0$$

Assume  $I_s = 0$  (no input)  
Natural response for all states



$$\begin{bmatrix} e_1 \\ e_2 \\ I_L \end{bmatrix} = \begin{bmatrix} c_1 e^{-t} + c_2 e^{(-1+j)t} + c_3 e^{(-1-j)t} \\ c_4 e^{-t} + c_5 e^{(-1+j)t} + c_6 e^{(-1-j)t} \\ c_7 e^{-t} + c_8 e^{(-1+j)t} + c_9 e^{(-1-j)t} \end{bmatrix}$$

3 initial conditions are necessary

$$e_1(0) = K_1 = c_1 + c_2 + c_3$$

$$e_2(0) = K_2 = c_4 + c_5 + c_6$$

$$I_L(0) = K_3 = c_7 + c_8 + c_9$$

$$\textcircled{3} \frac{1}{2} \Delta I_L = e_1 \quad \frac{1}{2} \frac{d}{dt} I_L = e_1$$

$$\frac{1}{2} \frac{d}{dt} I_L(0) = e_1(0)$$

$$\frac{d}{dt} I_L(0) = 2 e_1(0)$$

$$\begin{bmatrix} e_1 \\ e_2 \\ I_L \end{bmatrix} = \begin{bmatrix} c_1 e^{-t} + e^{-t} (a_1 \cos(t) + a_2 \sin(t)) \\ c_4 e^{-t} + e^{-t} (a_3 \cos(t) + a_4 \sin(t)) \\ c_7 e^{-t} + e^{-t} (a_5 \cos(t) + a_6 \sin(t)) \end{bmatrix} \leftarrow$$

## Solution of State equation with no input

$$\textcircled{1} \quad \dot{x} = Ax + \cancel{Bx} \quad u = 0$$

$$x(0) = x_0 \quad \uparrow \quad \text{no input}$$

\* First find the natural frequencies ( $s_i$  values)

① Find the roots of  $\det(sI - A) = 0$

② Find the eigenvalues of  $A$

$$AX_i = s_i X_i$$

$s_i$  = eigenvalue

$X_i$  = eigenvector

Solution of ① is

$$x_{\text{solution}}(t) = \underbrace{e^{At}}_{\text{Matrix}} \underbrace{x_0}_{\text{Vector}} \quad (\text{Natural response})$$

$$e^{At} = I + \frac{At}{1!} + \frac{(At)^2}{2!} + \frac{(At)^3}{3!} + \dots$$

$$e^{At} = \mathcal{L}^{-1} (sI - A)^{-1}$$

$$\mathcal{L} \left\{ \dot{x} = Ax \right\}$$

$$sIX(s) - IX(0) = AX(s)$$

$$sI X(s) - AX(s) = x(0)$$

$$(sI - A) X(s) = x(0)$$

$$X(s) = (sI - A)^{-1} x(0) \xrightarrow{\mathcal{L}^{-1}} x(t) = \mathcal{L}^{-1} \left[ (sI - A)^{-1} \right] x(0) \\ = e^{At} x(0)$$

$$e^{At} =$$

if  $A$  has distinct eigenvalues  $s_1, \dots, s_n$

$$e^{At} = \begin{bmatrix} c_{11} e^{s_1 t} & c_{12} e^{s_2 t} & \dots & c_{1n} e^{s_n t} \\ c_{21} e^{s_1 t} & c_{22} e^{s_2 t} & \dots & c_{2n} e^{s_n t} \\ \vdots & \vdots & \ddots & \vdots \end{bmatrix}$$


assume  $s_1$  has multiplicity  $m_1$  and other have multiplicity 1.

$$e^{At} = \begin{bmatrix} c_{11} e^{s_1 t} & c_{12} e^{s_1 t} & \dots & c_{1m_1} t^{m_1-1} e^{s_1 t} & c_{1m_1+1} e^{s_2 t} & \dots \\ c_{21} e^{s_1 t} & c_{22} e^{s_1 t} & \dots & c_{2m_1} t^{m_1-1} e^{s_1 t} & c_{2m_1+1} e^{s_2 t} & \dots \\ \vdots & \vdots & \ddots & \vdots & \vdots & \ddots \end{bmatrix}$$

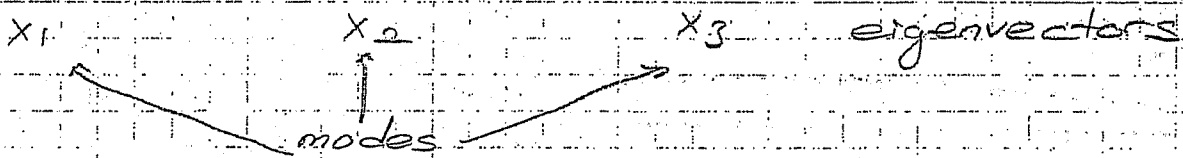
## Modes of operation:

If the initial state vector "namely  $x_0$ " is chosen equal (or proportional) to an eigenvalue or as linear combinations of some eigenvectors then  $x(t)$  will include only the corresponding natural-frequencies. In that case corresponding mode(s) are excited at the output.

$$s_1 = -1 \quad s_2 = -2 \quad s_3 = -3$$


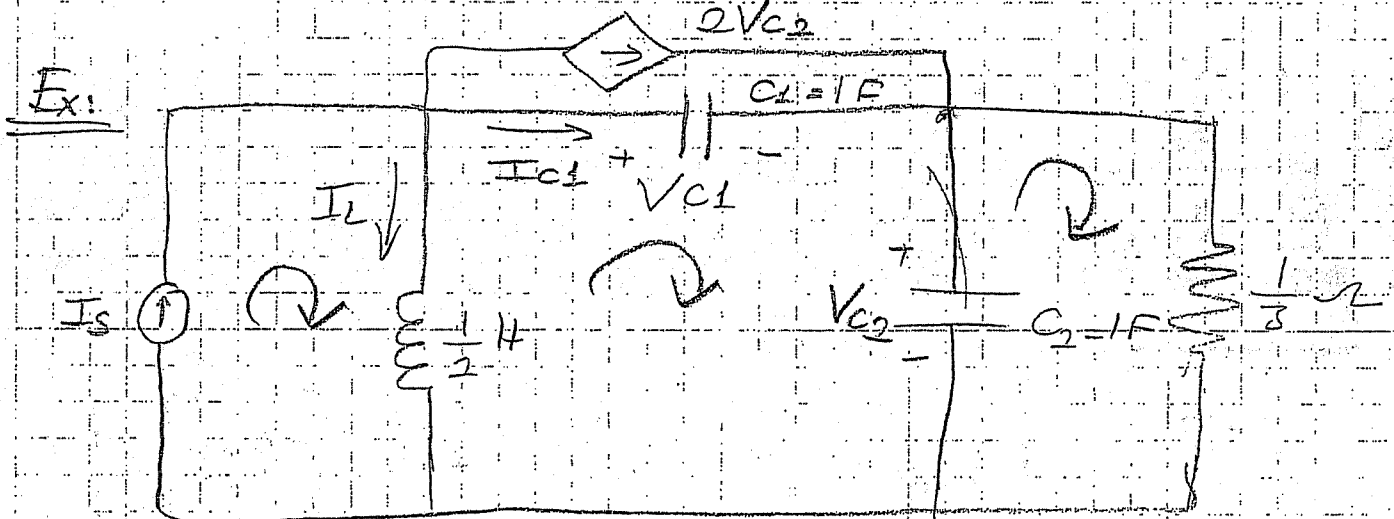
$$x_0 = k_1 x_1 \quad \rightarrow \quad x(t) = k_2 x_0 e^{s_1 t}$$



$$I_{c1} + 2V_{c2} = I_{c2} + I_R \quad \checkmark$$

$$C_1 \frac{dV_{c1}}{dt} + 2V_{c2} = \frac{V_{c2}}{\frac{1}{3}} + C_2 \frac{dV_{c2}}{dt}$$

$$I_s = I_L + 2V_{c2} + I_{c1} \quad \checkmark$$

$$I_s = I_L + 2V_{c2} + C_1 \frac{dV_{c1}}{dt} \quad \checkmark$$

$$C_1 \frac{dV_{c1}}{dt} = I_s - I_L - 2V_{c2} \quad \checkmark$$

$$I_s - I_L - \cancel{2V_{c2}} + \cancel{2V_{c2}} = -\frac{V_{c2}}{3} + C_2 \frac{dV_{c2}}{dt} \quad \checkmark$$

$$\frac{dV_{c1}}{dt} = I_s - I_L - 2V_{c2} \quad \checkmark$$

$$\frac{dV_{c2}}{dt} = I_s - I_L - 3V_{c2} \quad \checkmark$$

$$L \frac{dI_L}{dt} = V_L = V_{c1} + V_{c2}$$

$$\frac{1}{2} \frac{dI_L}{dt} = V_{c1} + V_{c2}$$

$$\begin{bmatrix} \dot{V}_{c1} \\ \dot{V}_{c2} \\ \dot{I}_L \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} V_{c1} \\ V_{c2} \\ I_L \end{bmatrix} = \begin{bmatrix} 0 & -2 & -1 \\ 0 & -3 & -1 \\ 2 & 2 & 0 \end{bmatrix} \begin{bmatrix} V_{c1} \\ V_{c2} \\ I_L \end{bmatrix} + \begin{bmatrix} 1 \\ 1 \\ 0 \end{bmatrix} I_s$$

Let's find natural frequencies

$$\det(sI - A) = \begin{bmatrix} s & 2 & 1 \\ 0 & s+3 & 1 \\ -2 & -2 & s \end{bmatrix}$$

$$= s \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} - \begin{bmatrix} 0 & -2 & -1 \\ 0 & -3 & -1 \\ 2 & 2 & 0 \end{bmatrix}$$

$$\det(sI - A) = (s+1)(s^2 + 2s + 2) = 0$$

$$s_1 = -1 \quad s_2 = -1 + j \quad s_3 = -1 - j$$

natural frequencies

Find the initial conditions which excites the complex modes only

Find complex eigenvalues conjugate

$$A x_i = s_i x_i$$

$$(s_i I - A) x_i = \vec{0} \rightarrow \text{zero vector}$$

$$s_i I x_i = A x_i$$

$$s = s_2$$

$$(sI - A) = \begin{bmatrix} -1+j & 2 & 1 \\ 0 & 2+j & 1 \\ -2 & -2 & -1+j \end{bmatrix}$$

$$\begin{bmatrix} -1+j & 2 & 1 \\ 0 & 2+j & 1 \\ -2 & -2 & -1+j \end{bmatrix} \begin{bmatrix} K_1 \\ K_2 \\ K_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$(-1+j)K_1 + 2K_2 + K_3 = 0$$

$$0 + (2+j)K_2 + K_3 = 0$$

$$-2K_1 - 2K_2 + (-1+j)K_3 = 0$$

assume  $K_3 = 1$

$$K_2 = \frac{-1}{2+j} \quad \text{and} \quad (-1+j)K_1 + 2\left(\frac{-1}{2+j}\right) + 1 = 0$$

$$K_1 = -1.19 + j0.075 \quad K_2 = \frac{-1}{2+j} = \frac{-2+j}{5}$$

$$x_2 = \begin{bmatrix} K_1 \\ K_2 \\ K_3 \end{bmatrix} = \begin{bmatrix} -1.19 + 0.075j \\ \frac{-2+j}{5} \\ 1 \end{bmatrix}$$

↓  
second mode related with  $s_2 = -1+j$

$$x_3 = x_2^* = \begin{bmatrix} -1.19 - j0.075 \\ \frac{-2}{5} - j \\ 1 \end{bmatrix}$$

third mode corresponding to  $s_3 = -1 - j$

choose  $x(0) = K_1 x_2 + K_2 x_3$

initial condition

$$x(0) = x_2 + x_3 = \begin{bmatrix} -1.19 \\ -2/5 \\ 1 \end{bmatrix}$$

in this case only effects of  $s_2$  and  $s_3$  will be observed at output.

//  $K_1$  ve  $K_2$  için seçtiğimiz değerler bizim verdiğimiz değerlerdir ve istediğimiz aynı rakamı verebiliriz.

### Complete Response:

$$x' = Ax + Bu$$

$$x(t) = x_{zi}(t) + x_{zs}(t)$$

zero-input

zero-state



For zero-input response:

$$\dot{x}_{zi}(t) = A x_{zi}(t)$$

$$x_{zi}(t) = x_0$$

For zero-state solution:

$$\dot{x}_{zs} = A x_{zs}(t) + B u(t)$$

$$x_{zs}(t_0) = 0$$

OR

$$x(t) = x_h(t) + x_p(t)$$

↖ homogeneous
↗ particular

let input  $u(t) = P e^{s_0 t}$  ( $s_0$  is not natural frequency of the system)

then  $x_p(t) = K e^{s_0 t}$

↳ vector

put particular solution in diff. equation

$$\dot{x}(t) = Ax + Bu$$

$$s_0 K e^{s_0 t} = A K e^{s_0 t} + B P e^{s_0 t}$$

$$s_0 K e^{s_0 t} = (A K + B P) e^{s_0 t}$$

$$(s_0 I K - A K) e^{s_0 t} = B P e^{s_0 t}$$

~~$$(s_0 I - A) K e^{s_0 t} = B P e^{s_0 t}$$~~

$$K = (s_0 I - A)^{-1} B P$$

## Sinusoidal Steady-State (SSS)

\* Given a circuit, SSS condition exist

(a)  $\operatorname{Re}\{s_k\} < 0$        $s_k \rightarrow$  natural frequencies

(b) if  $\operatorname{Re}\{s_k\} \leq 0$        $s_k \neq j\omega$

where input =  $A \cos(\omega t + \theta)$

\* After checking if SSS exist or not solve the circuit in phasor domain

\* In SSS the transient response is neglected

\* To find SSS we use phasors

### Phasor:

It is a complex number ( $\neq$ ) representing the amplitude and phase. It can be in polar or rectangular form.

#### Polar:

$$A e^{j\theta} \rightarrow \text{phase}$$

↓  
amplitude


#### Rectangular:

$$A \cos \theta + j A \sin \theta$$

Ex:  $V(t) = V_A \cos(\omega t + \theta)$

$$= V_A \operatorname{Re} \left\{ e^{j(\omega t + \theta)} \right\}$$

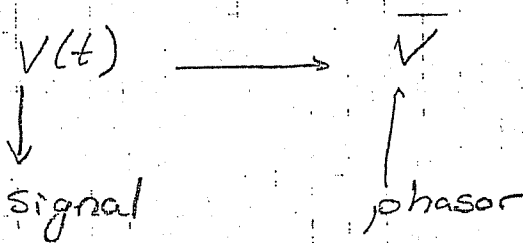
$$= \operatorname{Re} \left\{ V_A e^{j(\omega t + \theta)} \right\} = \operatorname{Re} \left\{ \underbrace{V_A e^{j\theta}}_{\text{phasor}} e^{j\omega t} \right\}$$



$$V(t) = V_A \cos(\omega t + \theta) \longrightarrow \bar{V} = V_A e^{j\theta} = V_A (\cos \theta + j \sin \theta)$$

\* From  $V(t)$  to  $\bar{V}$  we neglect the information of frequency.

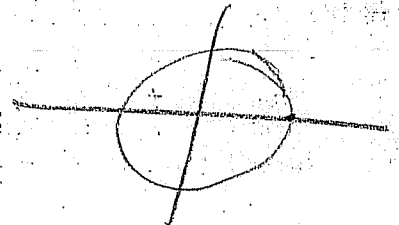\* But from  $\bar{V}$  to  $V(t)$  we should know the frequency information.



Ex:  $V(t) = 2 \sin(5t + 30^\circ)$

$$= 2 \sin(5t + 30^\circ) = 2 \cos(5t + 30^\circ - 90^\circ)$$

$$= 2 \cos(5t - 60^\circ)$$

$$\bar{V} = 2 e^{-j60^\circ} = 2 (\cos(-60^\circ) + j \sin(-60^\circ))$$

$$\bar{V} = 2 \left( \frac{1}{2} - \frac{\sqrt{3}}{2}j \right) = \underline{1 - \sqrt{3}j}$$

## Properties of phasors:

① Additive

$$v(t) = v_1(t) + v_2(t) \longrightarrow \bar{V} = \bar{V}_1 + \bar{V}_2$$

② Derivative


$$v(t) = \operatorname{Re} \{ \bar{V} e^{j\omega t} \}$$

$$\begin{aligned} \frac{dv(t)}{dt} &= \frac{d}{dt} \operatorname{Re} \{ \bar{V} e^{j\omega t} \} = \operatorname{Re} \left\{ \bar{V} \frac{d}{dt} e^{j\omega t} \right\} \\ &= \operatorname{Re} \{ \bar{V} j\omega e^{j\omega t} \} \end{aligned}$$

$$\left. \begin{array}{l} v(t) \longrightarrow \bar{V} \\ \frac{d}{dt} v(t) \longrightarrow \bar{V} j\omega \end{array} \right\}$$

\* We use phasors to find SSS solutions for circuits having bounded outputs.

Ex:

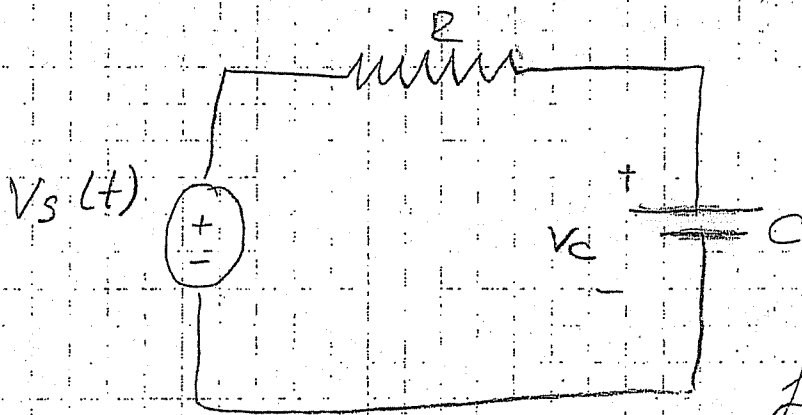

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{1}{RC} v_s$$

$$v_s(t) = V_A \cos(\omega t)$$

find  $V_{c,SSS}$  when

$$t \gg 0$$

$$V_s(t) = V_A \cos(\omega t) \\ = V_A e^{j\omega t}$$

$$V_p(t) = \operatorname{Re} \left\{ \bar{V}_p e^{j\omega t} \right\}$$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_s \rightarrow \frac{\operatorname{Re} \left\{ V_A e^{j\omega t} \right\}}{RC} \\ \rightarrow \operatorname{Re} \left\{ V_A \cos(\omega t) \right\}$$


$$\operatorname{Re} \left\{ \bar{V}_p j\omega e^{j\omega t} \right\} + \frac{1}{RC} \operatorname{Re} \left\{ \bar{V}_p e^{j\omega t} \right\} = \frac{1}{RC} \operatorname{Re} \left\{ V_A e^{j\omega t} \right\}$$

$$\operatorname{Re} \left\{ \bar{V}_p j\omega e^{j\omega t} + \frac{1}{RC} \bar{V}_p e^{j\omega t} \right\} = \operatorname{Re} \left\{ \frac{1}{RC} V_A e^{j\omega t} \right\}$$

$$\left( j\omega + \frac{1}{RC} \right) \bar{V}_p = \frac{1}{RC} V_A$$

$$\bar{V}_p = \frac{V_A}{j\omega RC + 1} = \frac{V_A (1 - j\omega RC)}{1 + (\omega RC)^2} = \frac{V_A (1 - j\omega RC)}{\sqrt{1 + (\omega RC)^2} \sqrt{1 + (\omega RC)^2}}$$
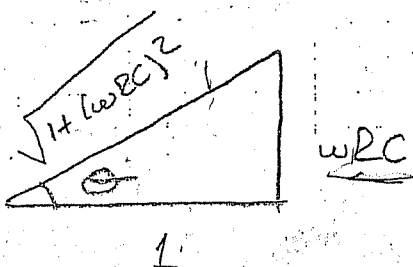
$$\bar{V}_p = \frac{V_A}{\sqrt{1 + (\omega RC)^2}} \left[ \frac{-j\omega RC}{\sqrt{1 + (\omega RC)^2}} + \frac{1}{\sqrt{1 + (\omega RC)^2}} \right]$$



$$\theta = \tan^{-1} \left( \frac{-\omega RC}{1} \right)$$

$$\underline{V_p} = \frac{V_A}{\underbrace{\sqrt{1 + (\omega RC)^2}}_{\text{amplitude}}} e^{j\theta} \rightarrow \text{phase}$$

$$V_p(t) = \text{Re} \left\{ \underline{V_p} e^{j\omega t} \right\} = \text{Re} \left\{ \frac{V_A}{\sqrt{1 + (\omega RC)^2}} e^{j(\omega t + \theta)} \right\}$$

$$V(t) = \frac{V_A}{\sqrt{1 + (\omega RC)^2}} \cos(\omega t + \theta)$$


$$V_p(t) = \frac{V_A}{\sqrt{1 + (\omega RC)^2}} \cos(\omega t + \tan^{-1}(-\omega RC))$$

↳ This solution is the particular solution  
it is also equal to  $V_{\text{steady}}(t)$

Circuit Analysis in Phasor Domain:


RVL, KCL → can be used

Devices

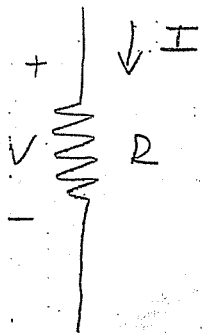


$$V = R \cdot I$$

$$\boxed{\bar{V} = R \cdot \bar{I}}$$

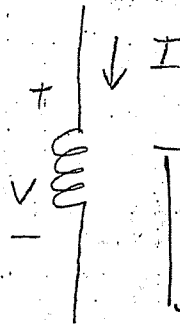

$$L \frac{dI}{dt} = V_L$$
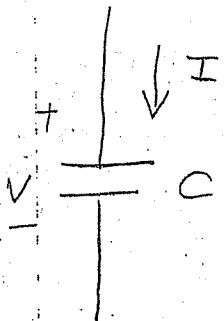
$$\boxed{L(j\omega) \bar{I} = \bar{V}_L}$$



$$C \frac{dV}{dt} = I$$

$$\boxed{C(j\omega) \bar{V} = \bar{I}}$$

phasor domain

Impedance and Admittance:

Impedance " $Z(j\omega)$ " at any angular frequency " $\omega$ " is the ratio of phasor of  $\bar{V}$  to phasor of  $\bar{I}$  in a two terminal element.

$$Z(j\omega) = \frac{\bar{V}}{\bar{I}} = \underbrace{\left| \frac{\bar{V}}{\bar{I}} \right|}_{\text{amplitude}} e^{j \underbrace{\angle \left( \frac{\bar{V}}{\bar{I}} \right)}_{\text{phase}}}$$

$$Z(j\omega) = \frac{\bar{V}}{\bar{I}}$$

impedance

amplitude


Admittance =  $\frac{1}{Z(j\omega)} = Y(j\omega)$  siemens

$$Z = R(j\omega) + jX(j\omega)$$

$R$  = resistance  $\rightarrow$  teptki

$X$  = reactance

$$|Z| = \sqrt{R^2 + X^2}$$

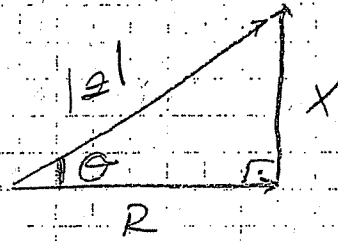


$$\angle Z(j\omega) = \theta$$

Admittance  $Y(j\omega) = \frac{1}{Z(j\omega)} = G + jB$

$G$  = conductance  $\rightarrow$  leticentk


$B$  = susceptance  $\rightarrow$  sanal qarr.

$$|Y| = \sqrt{G^2 + B^2}$$

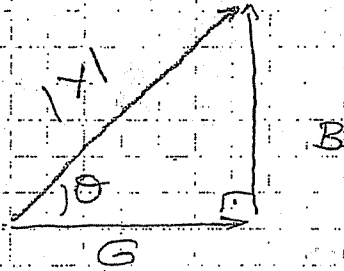

$$\angle Y(j\omega) = \theta$$


Impedance / Admittance of  $R, L, C$

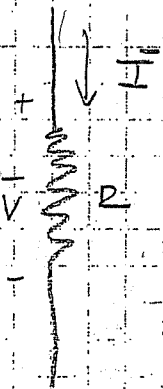

$$Z(j\omega) = R$$
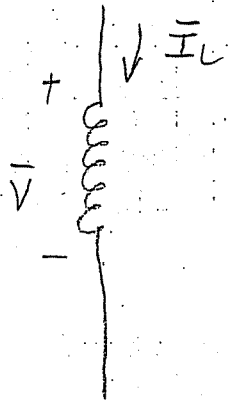
$$Y(j\omega) = \frac{1}{Z(j\omega)} = \frac{1}{R} = G$$





$$\bar{V} = j\omega L \bar{I}$$


$$V_L = L \frac{dI_L}{dt}$$

$$Z(j\omega) = j\omega L$$

$$\bar{V}_L = j\omega L \bar{I}_L$$

$$Y(j\omega) = \frac{1}{j\omega L}$$
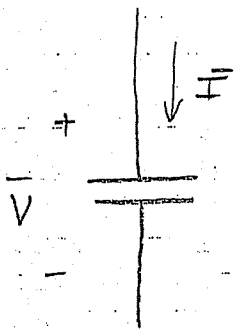
$$\bar{I}_L = \frac{\bar{V}_L}{j\omega L}$$




$$\bar{V} = \frac{\bar{I}}{j\omega C}$$

$$Y(j\omega) = j\omega C$$

$$Z(j\omega) = \frac{1}{j\omega C}$$

$$C \frac{dV}{dt} = I \xrightarrow{\text{phasor}} j\omega C \bar{V} = \bar{I}$$

Source

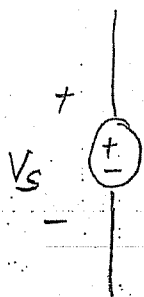



$$V_s(t) = V_m \cos(\omega t + \phi_s)$$

phasor

$$\bar{V}_s = V_m e^{j\phi_s}$$

$I_1(t)$

$I_2(t)$

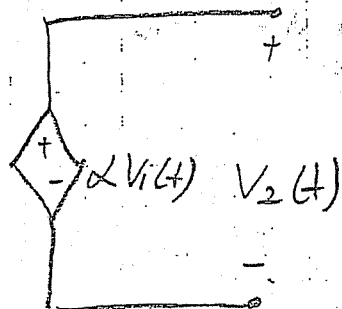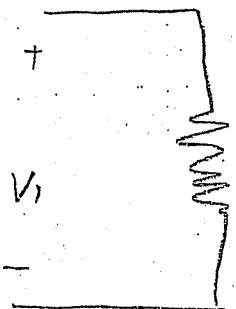


$$V_2(t) = \alpha V_1(t)$$

$$\bar{V}_2 = \alpha \bar{V}_1$$

Phasor domain circuit analysis: \* (only sinusoidal steady-state values are obtained, no transient part is evaluated)

- ① Turn all circuit parameters, variables, coefficients to phasor domain.
- ② Use KVL, KCL, mesh, node analysis methods.
- ③ After obtaining the result (signal), turn back into time domain.

Ex:

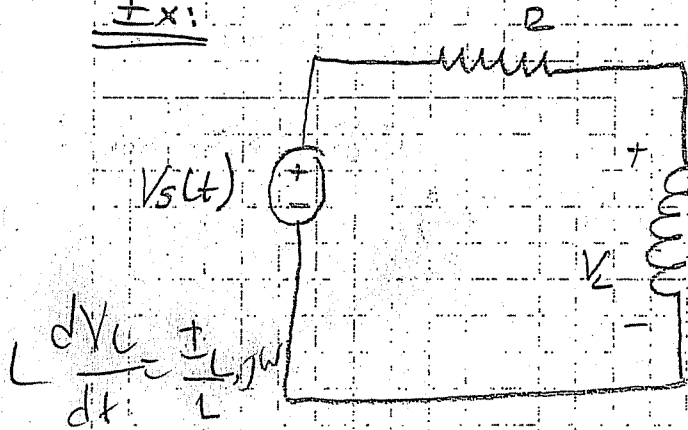

$V_s(t) = V_m \cos(\omega t + \phi_v)$

Does SSS exist?  
Yes.

$$s + \frac{R}{L} = 0$$


$$s = -\frac{R}{L} \neq j\omega$$

Find SSS response for  $I_L(t)$ ?

$$-V_s + V_R + V_L = 0$$

$$V_R + V_L = V_s$$

Transform into phasor domain

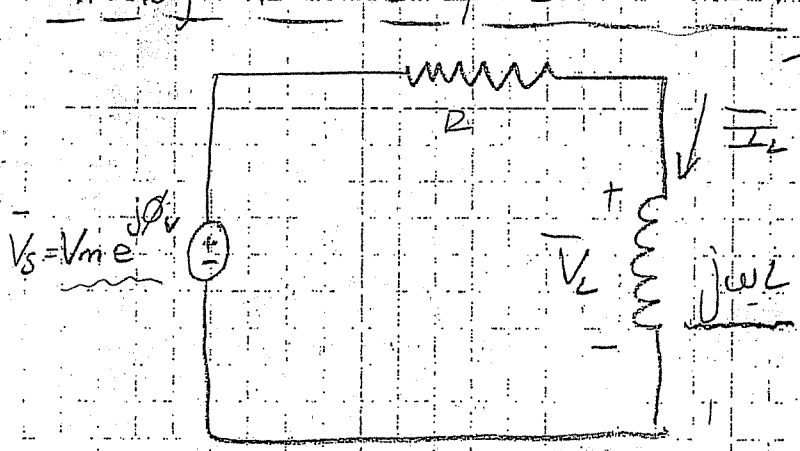


$$I_L = \frac{V_L}{j\omega L}$$

$$I_L = \frac{V_s}{R + j\omega L}$$

$$I_L = \frac{V_m e^{j\phi_v}}{R + j\omega L}$$
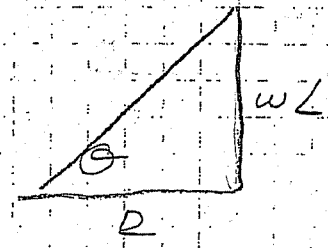
$$I_L = \frac{V_m e^{j\phi_v}}{\sqrt{R^2 + (\omega L)^2}} e^{j \tan^{-1}(\frac{\omega L}{R})}$$




$$\underline{I}_L = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} e^{j(\phi_v - \tan^{-1}(\frac{\omega L}{R}))}$$

back to time domain


$$I_L(t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \phi_v - \tan^{-1}(\frac{\omega L}{R}))$$

Ex:

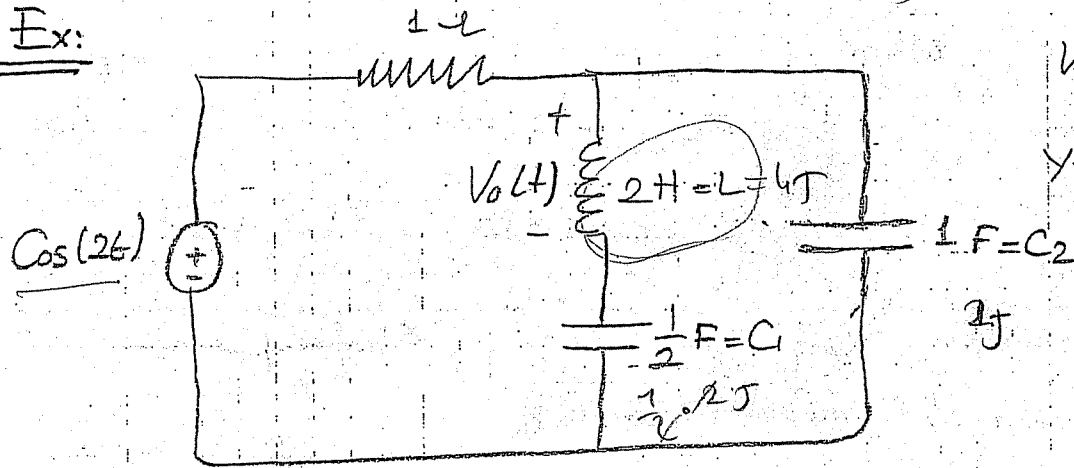


$V_o(t) \rightarrow$  SSS

YES SSS exist

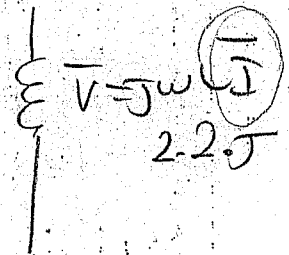

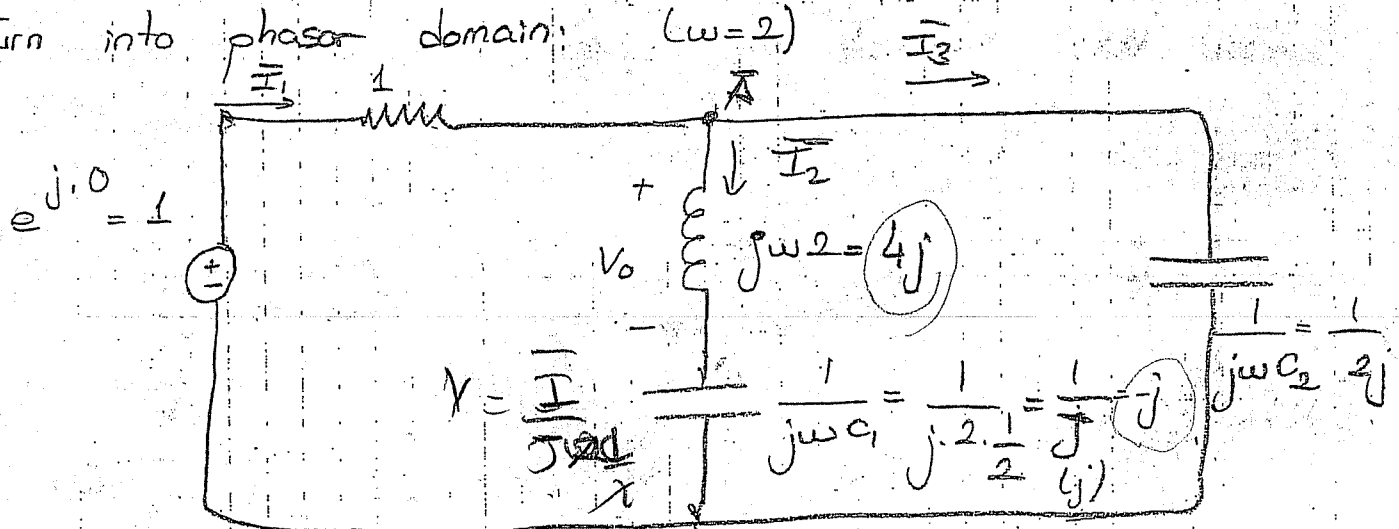Turn into phasor domain: ( $\omega = 2$ )



$$\underline{I}_1 = \underline{I}_2 + \underline{I}_3$$

$$1 - \underline{A} = \frac{\underline{A}}{3j} + 2j\underline{A}$$

$$\frac{1 - \underline{A}}{1} = \frac{\underline{A}}{4j + (-j)} + \frac{\underline{A}}{2j}$$

$$3j - 3j\underline{A} = \underline{A} - 6\underline{A}$$

$$\underline{A} = \frac{3j}{3j - 5} = \frac{-9 + 15j}{-34}$$

$$\frac{9 - 15j}{34}$$

$$1 - \underline{A} = \frac{j\underline{A}}{-j} + 2j\underline{A} + \frac{1}{j} - \frac{j}{0}$$

$$\vec{I} = \frac{A}{(j\omega R)}$$

36.

$$\vec{V}_0 = \frac{4}{2 + j\omega L + 5}$$

26/02/07

$$\vec{V}_0 = \frac{4j}{4j + (-j)} \Rightarrow \vec{V}_0 = \frac{4}{3} \angle \frac{90^\circ}{3} = \frac{4}{3} \angle 30^\circ$$

$$\vec{V}_0 = \frac{4}{3} \left( \frac{-9 - 15j}{34} \right)$$

$$\vec{V}_0 = 0.68 e^{j59.4^\circ} \rightarrow \text{phase}$$

$\downarrow$   
 magnitude


$$\left( \frac{-9}{34} - \frac{15j}{34} \right)$$

A ↔ Y Transformation:

Superposition:

- \* Superposition is always applicable in time domain.
- \* ① If the sources have same input frequency, superposition can be applied in phasor domain.
- ② If the sources have different input frequency, superposition can not be applied in phasor domain. Instead, time domain results of phasors should be added.


Ex:

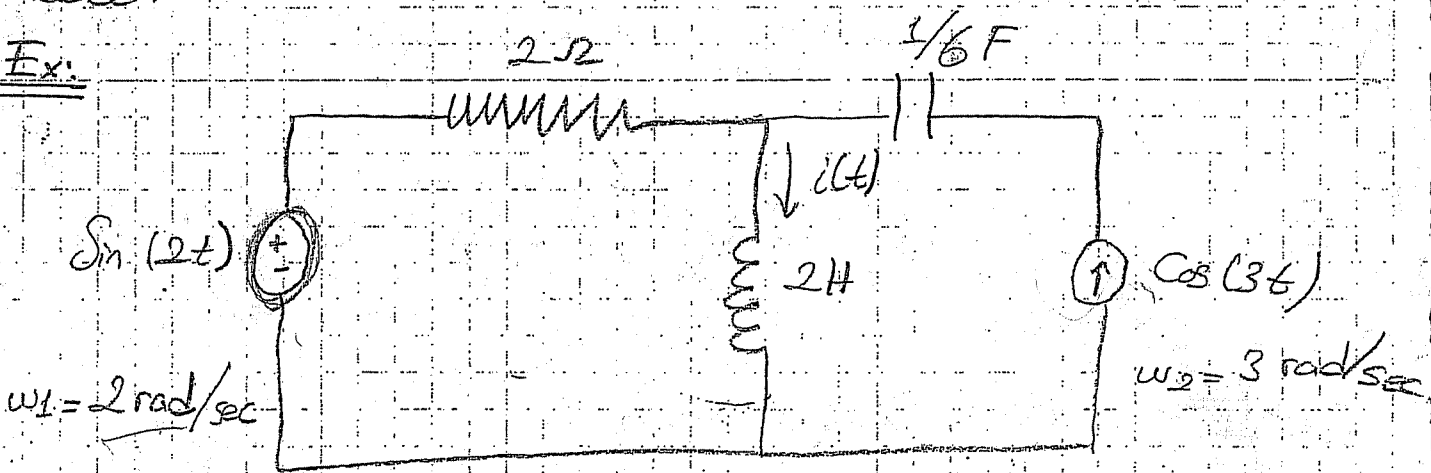


Find  $i(t)$  in SSS

Apply superposition

① Kill  $\cos(3t)$

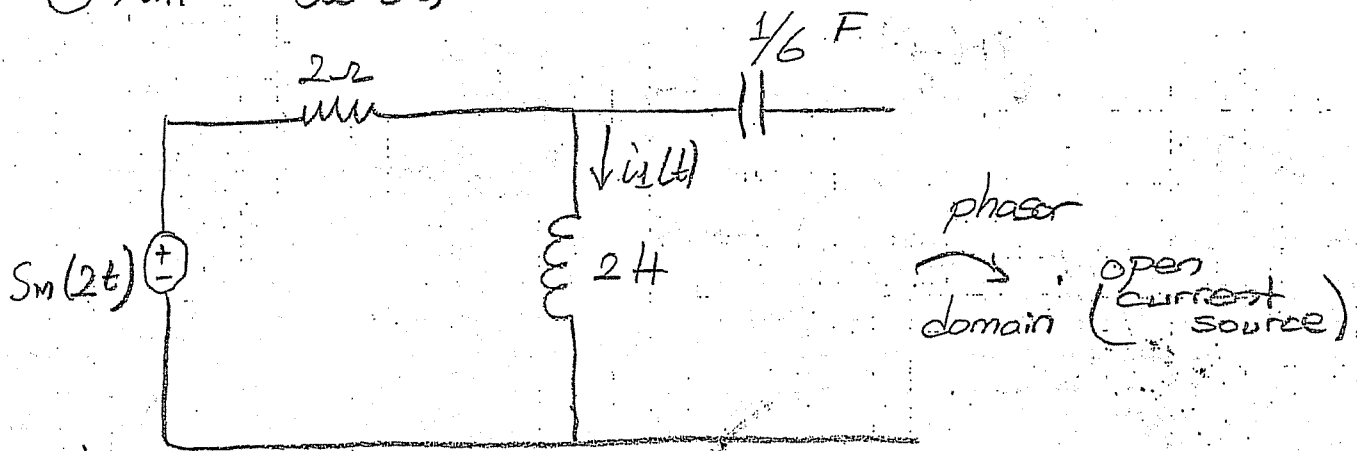

$$S_m(2t) = \cos(2t - 90^\circ)$$

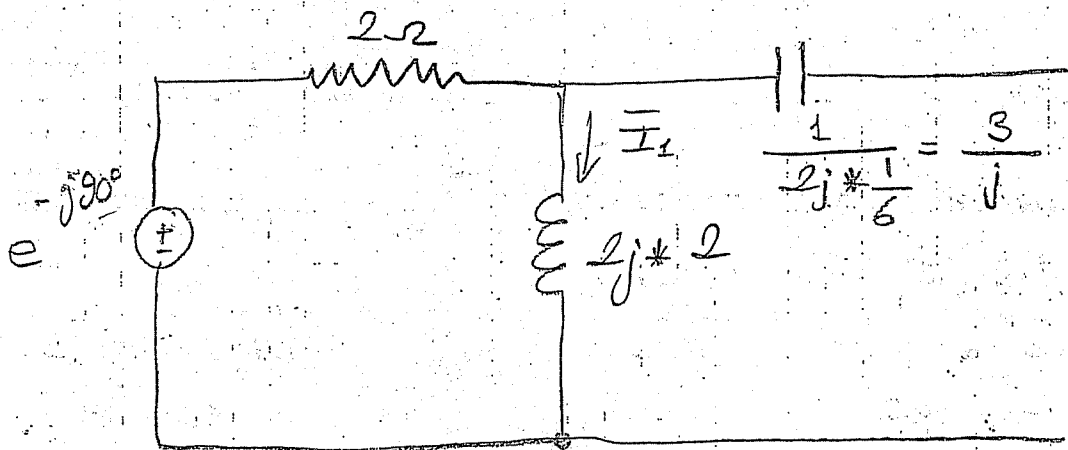



$$\bar{I}_1 = \frac{e^{-j90^\circ}}{2+4j} = \frac{-j}{2+4j} = \frac{-4-2j}{20} = -\left(\frac{1}{5} + \frac{1}{10}j\right)$$

$$\bar{I}_1 = -\left(\frac{1}{5} + \frac{1}{10}j\right) \Rightarrow I_1(t) = \sqrt{\left(\frac{1}{5}\right)^2 + \left(\frac{1}{10}\right)^2} \cdot \cos\left(2t + \tan^{-1} \frac{1/10}{1/5}\right)$$

$$I_1(t) = -0.374 \cos\left(2t + \tan^{-1} \frac{1}{2}\right)$$

$$I_1(t) = -0.374 \cos(2t + 26.56^\circ)$$

② Kill  $\sin(2t)$

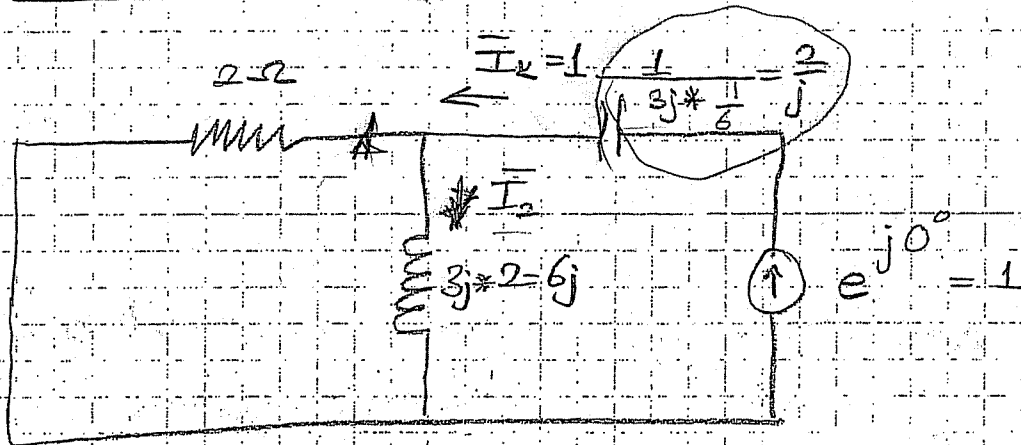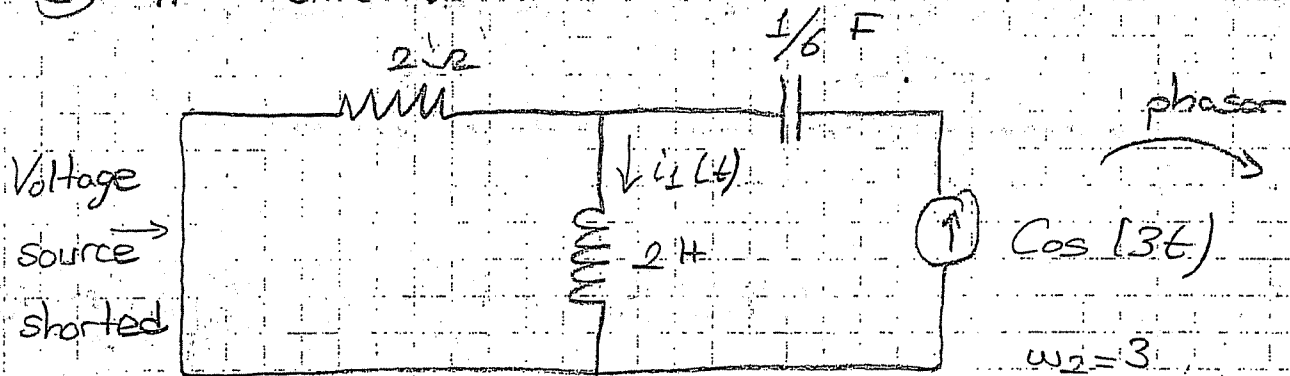

$$\vec{I}_2 = \frac{2 * \vec{I}_N}{2 + 6j} = \frac{2 * 1}{2 + 6j} = \frac{2}{2 + 6j} = \frac{2(2 - 6j)}{40}$$

$$= \frac{1}{10} - \frac{3}{10}j$$


$$\vec{I}_2(t) = \sqrt{\left(\frac{1}{10}\right)^2 + \left(-\frac{3}{10}\right)^2} \cos\left(3t + \tan^{-1} \frac{-3/10}{1/10}\right)$$

$$I_2(t) = 0.44 \cos(3t + \tan^{-1}(-3))$$

$$I_2(t) = 0.44 \cos(3t - 71.56^\circ)$$

$$I(t) = I_1(t) + I_2(t)$$

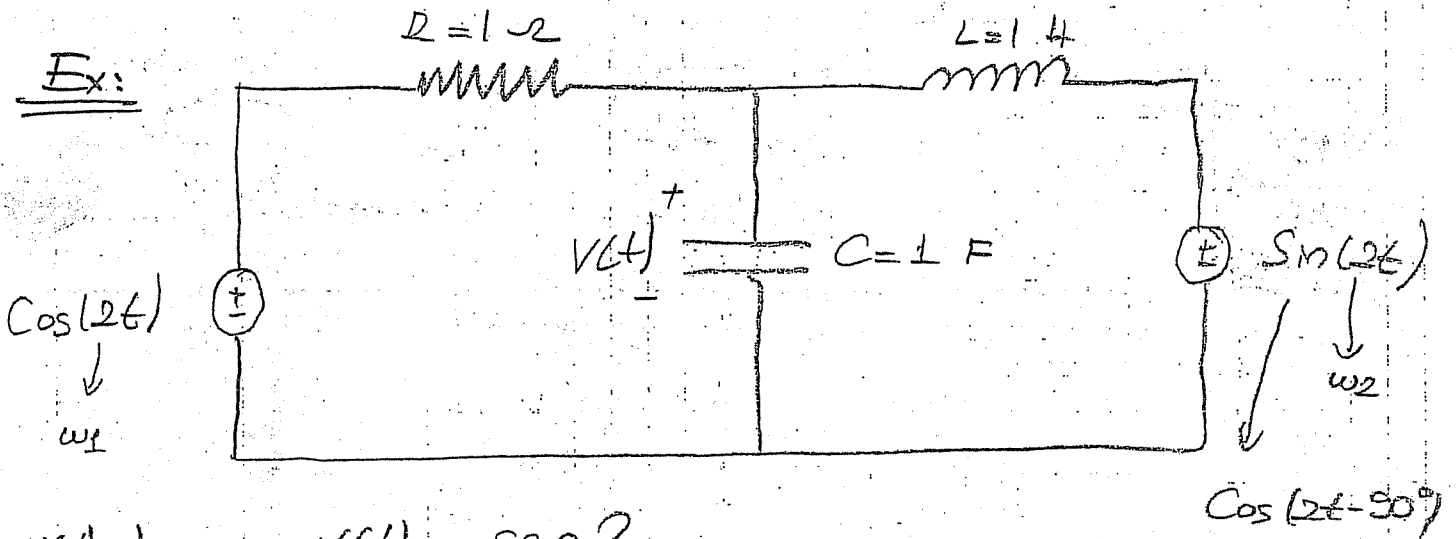
$$I(t) = -0.374 \cos(2t + 26.56^\circ) + 0.44 \cos(2t - 71.56^\circ)$$



What is  $V(t)$  SSS?

$$\omega_1 = \omega_2 = 2 \text{ rad/sec}$$

apply superposition in phasor domain

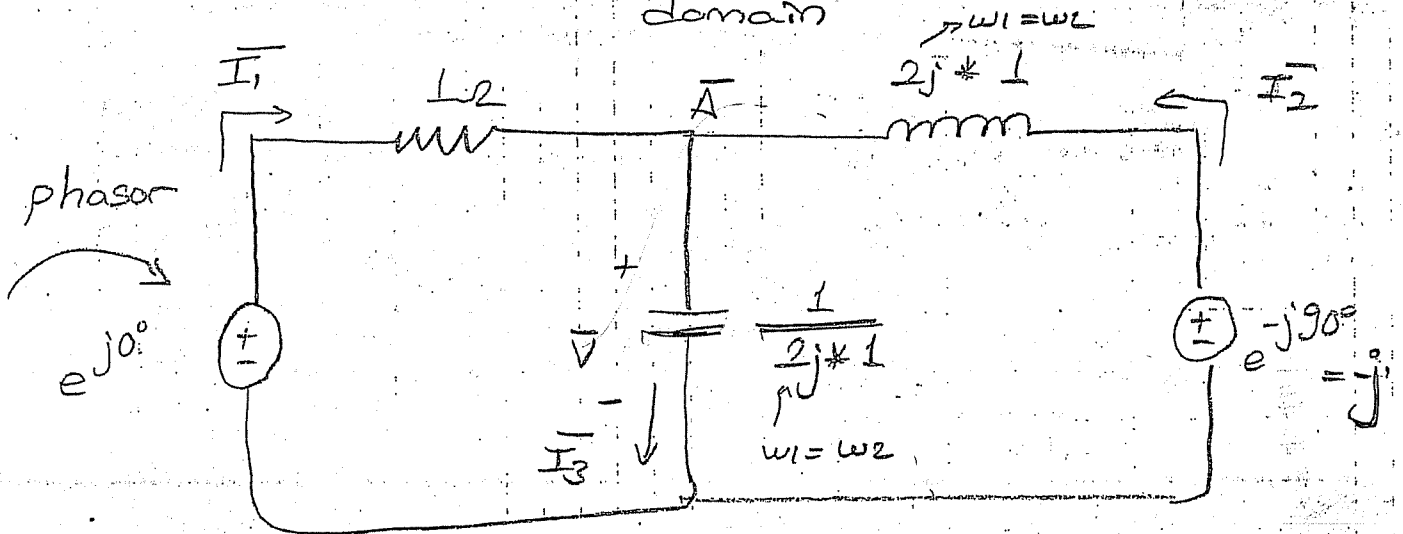

$$\bar{V} = \bar{A}$$

$$\bar{I}_1 + \bar{I}_2 = \bar{I}_3$$

$$\frac{1 - \bar{A}}{1} + \frac{-j - \bar{A}}{2j} = \frac{\bar{A}}{2j}$$

$$2j - 2j\bar{A} + j - \bar{A} = -4\bar{A}$$


$$j = 2j\bar{A} - 3\bar{A}$$

$$j = (2j - 3)\bar{A}$$


$$\bar{A} = \frac{-j}{2j - 3} = \frac{2 - 3j}{-13}$$

$$A = V(t) = \sqrt{\left(\frac{2}{13}\right)^2 + \left(\frac{-3}{13}\right)^2} \cos\left(2t + \arctan\left(\frac{-3/13}{2/13}\right)\right)$$


Phasor Diagram:

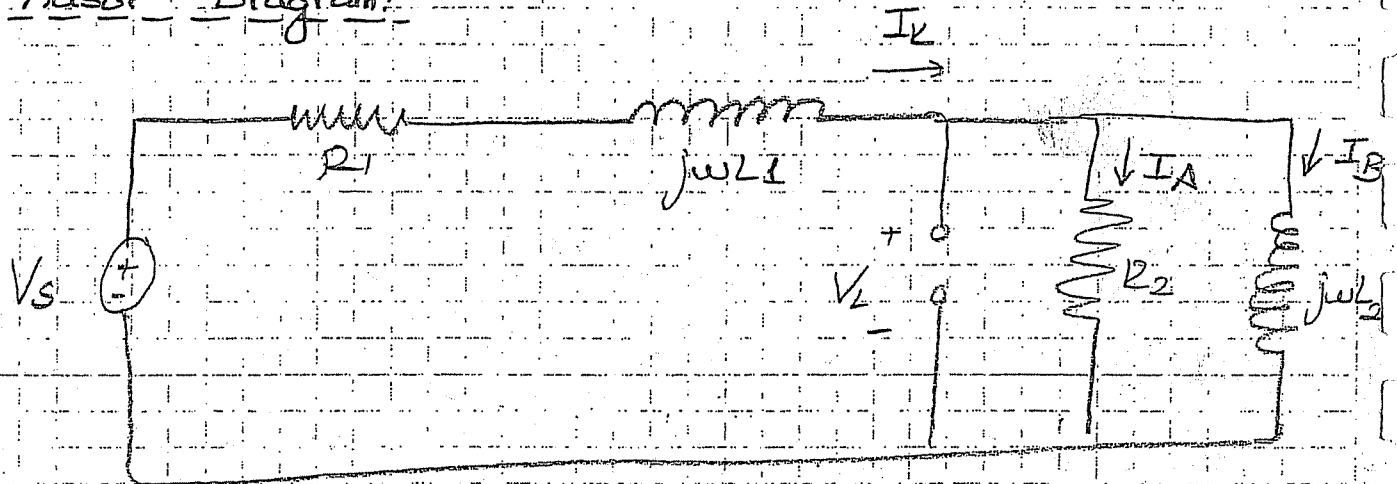

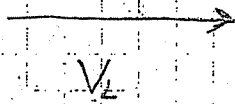① Choose one of the phasors as reference ( $V_L$ )



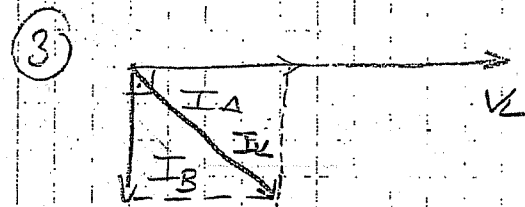②  $I_A$  is with the same direction with  $V_L$




$I_B$  lags  $V_L$  by  $90^\circ$  since it is the current over the inductor

$$|I_B| = \frac{|V_L|}{\omega L_2}$$



$$(4) I_k = I_A + I_B$$
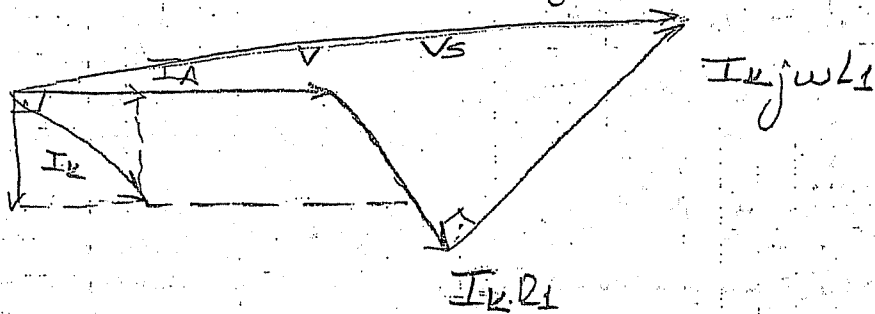
$$(5) V_s = V_L + I_k (R_1 + j\omega L_1)$$



## Sinusoidal Steady-State Power

Instantaneous Power: (Power at any instant)

$$P(t) = V(t) I(t) \text{ (Watts)}$$

Average Power: (It is associated with periodic signals)

It is the average of instantaneous power at one period

real power

$$P = P_{avg} = \frac{1}{T} \int_k^{k+T} P(t) dt \text{ (Watts)}$$

Complex Power: It is the complex sum of average power and reactive power.

↳ power due to energy storage

↳ complex power (VA)  
(volt-ampere)

↳ reactive power (VAR)  
(Volt-ampere-reactive)

↳ average power (W)  
(Watts)

$$S = P + jQ$$

$$|S| = \sqrt{P^2 + Q^2}$$



↙ apparent power (VA)

↘ angle of voltage

$$\theta = \theta_v - \theta_i$$

↘ angle of current

↓ power factor angle

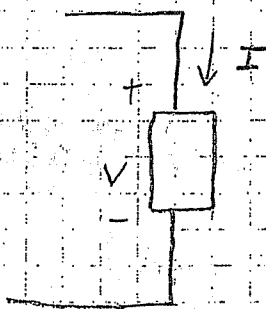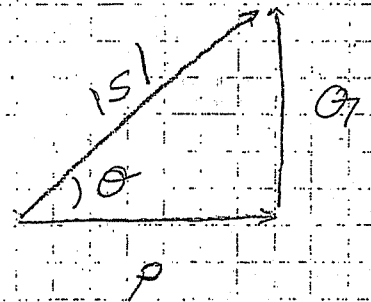

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$I(t) = I_m \cos(\omega t + \theta_i)$$

$$\text{power factor} = pf = \cos \theta = \frac{P}{|S|}$$

$$\text{reactive factor} = rf = \sin \theta = \frac{Q}{|S|}$$

R.M.S. values

$$V(t) = a \sin(\omega t)$$

$$V_{rms} = \frac{a}{\sqrt{2}}$$


$$V(t) = a \text{Tri}(\omega t)$$

$$V_{rms} = \frac{a}{\sqrt{3}}$$

$$V(t) = a \text{Sqr}(\omega t)$$

$$V_{rms} = a$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

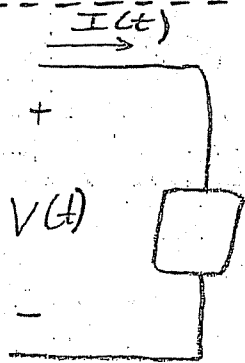Instantaneous Power:

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$I(t) = I_m \cos(\omega t + \theta_i)$$

assume  $I(t)$  is  
reference signal

$$V(t) = V_m \cos(\omega t + \theta_v - \theta_i)$$

$$I(t) = I_m \cos(\omega t)$$

(shift signals)  
(- $\theta_i$  units)

$$P(t) = V(t) \cdot I(t) = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t)$$

$$\cos(A) \cdot \cos(B) = \frac{1}{2} \cos(A+B) + \frac{1}{2} \cos(A-B)$$

$$\Rightarrow P(t) = V_m I_m \left[ \frac{1}{2} \cos(2\omega t + \theta_v - \theta_i) + \frac{1}{2} \cos(\theta_v - \theta_i) \right]$$

$$P(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$

$$\cos(a+b) = \cos a \cdot \cos b - \sin a \cdot \sin b$$

$$\Rightarrow P(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \left[ \cos(2\omega t) \cos(\theta_v - \theta_i) - \sin(2\omega t) \sin(\theta_v - \theta_i) \right]$$

$$P(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_P + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \underbrace{\frac{V_m I_m}{2} \sin(\theta_v - \theta_i)}_Q \sin(2\omega t)$$

$$P(t) = P + P \cos(2\omega t) - Q \sin(2\omega t)$$

$$P_{\text{avg}} = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{T} \int_0^T [P + P \cos(2\omega t) - Q \sin(2\omega t)] dt$$

$$P_{\text{avg}} = \frac{1}{T} \left[ P t \Big|_0^T + P \left( \frac{-\sin 2\omega t}{2\omega} \right) \Big|_0^T - Q \left( \frac{\cos 2\omega t}{2\omega} \right) \Big|_0^T \right]$$

$$P_{\text{avg}} = \frac{1}{T} \left[ P T + P \frac{1}{2\omega} \left[ \underbrace{-\sin(2\omega T) + \sin(0)}_0 \right] - Q \frac{1}{2\omega} \left[ \underbrace{\cos(2\omega T) - \cos(0)}_0 \right] \right]$$

$$P_{\text{avg}} = P$$

Energy:

$$W(t) = \int_0^t P(t') dt' \quad P(t) = \frac{dW(t)}{dt}$$

$$t = t_1 = \frac{2\pi}{2\omega} \quad (\text{period of power})$$

$$W(T_1) = \int_0^{T_1} (P + P \cos(2\omega t') - Q_r \sin(2\omega t')) dt'$$

$$W(T_1) = \int_0^{T_1} P dt' + \int_0^{T_1} P \cos(2\omega t') dt' + \int_0^{T_1} Q_r \sin(2\omega t') dt'$$

$$W(T_1) = PT_1$$

\*  $Q_r$  is the reactive power due to inductor or capacitor. Inductor or capacitor do not deliver a net amount of energy to the circuit.

Observations:

$$\textcircled{1} P_{\text{avg}} = P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

\textcircled{2} The frequency of  $P(t)$  (instantaneous power) is twice the frequency of voltage or current.

Ex:  $\theta_v = \theta_i$   $I_R = I_m \cos(\omega t)$   
 (purely resistive circuit)  $V_R = R \cdot I_m \cos(\omega t)$


$$P_R(t) = V_R \cdot I_R = R I_m^2 \cos(\omega t) \cos(\omega t)$$

↑  
instantaneous power

$$P_R(t) = R I_m^2 \left[ \frac{1}{2} \cos(2\omega t) + \frac{1}{2} \cos(\omega t - \omega t) \right]$$

$$P_R(t) = \frac{R I_m^2}{2} \left[ 1 + \cos(2\omega t) \right]$$

angular frequency of power

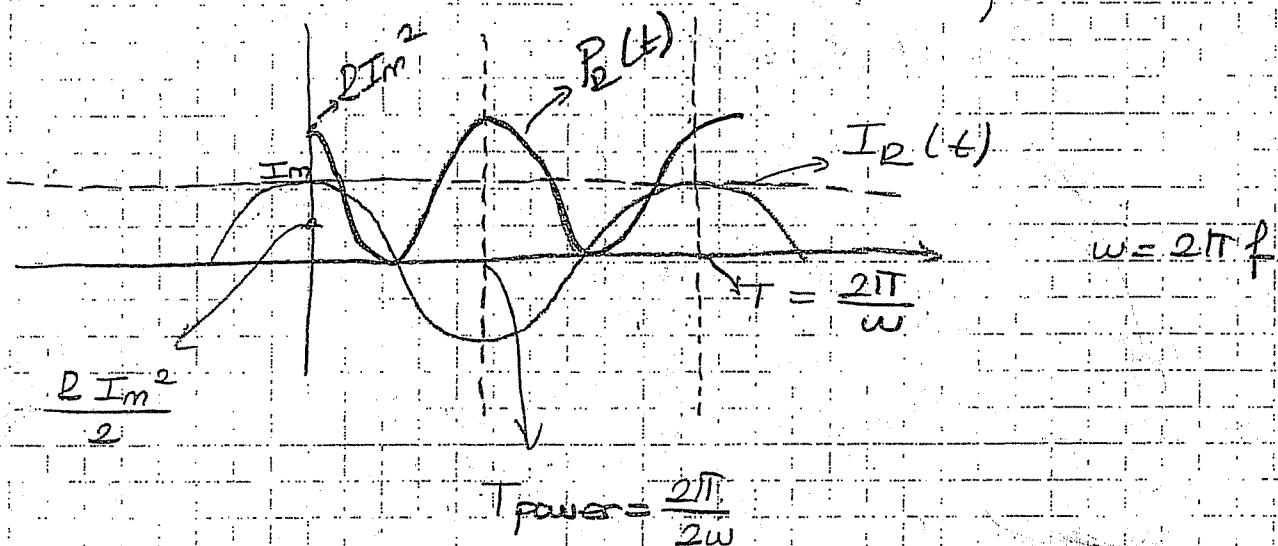

③ For purely resistive element

$$\theta_V = \theta_I \quad P(t) = P + P \cos(2\omega t)$$

$$P(t) \geq 0$$

④ For purely capacitor element C:

$$\theta_I - \theta_V = 90^\circ$$

$$V(t) = V_m \cos(\omega t) \quad T = \frac{1}{f} = \frac{2\pi}{\omega}$$

$$C \frac{dV(t)}{dt} = I(t) = \underbrace{C V_m \omega}_{I_m} (-\sin(\omega t))$$

$$\begin{aligned} P(t) &= V_m \cos(\omega t) \left[ C V_m \omega (-\sin(\omega t)) \right] \\ &= V_m^2 C \omega \left[ \cos(\omega t) \sin(\omega t) \right] \cdot \frac{2}{2} \\ &= -\frac{V_m^2 C \omega}{2} \sin(2\omega t) \end{aligned}$$

$$P(t) = -\frac{I_m V_m}{2} \sin(2\omega t) \quad \rightarrow \quad T_k = \frac{T}{2} = \frac{\pi}{\omega}$$

↳ instantaneous power

$$P_{avg} = \frac{1}{T} \int_0^T P(t) dt = 0$$

$$Q_1 = -\frac{\omega C V_m^2}{2} \text{ (VAR)}$$

$$W_{CA} = \frac{1}{2} C (V_{rms})^2 = \frac{1}{2} C \left(\frac{V_m}{\sqrt{2}}\right)^2$$

↓  
Average capacitor energy

$$Q_2 = -2\omega W_{CA}$$

⑤ For purely inductive element L:

$$\theta_v - \theta_i = 90^\circ$$

$$I(t) = I_m \sin(\omega t)$$

$$V(t) = L \frac{dI(t)}{dt} = \overbrace{L I_m \omega}^{V_m} \cos(\omega t)$$

$$P(t) = L\omega I_m^2 \sin(\omega t) \cos(\omega t) \cdot \frac{2}{2}$$

$$P(t) = \frac{V_m I_m}{2} \sin(2\omega t) = \frac{L\omega I_m^2}{2} \sin(2\omega t)$$

$$P_{avg} = \frac{1}{T} \int_0^T P(t) dt = 0$$

$$Q_r = \frac{\omega L I_m^2}{2} \text{ (VAR)}$$

$$W_{LA} = \frac{1}{2} L (I_{rms})^2 = \frac{1}{2} L \left( \frac{I_m}{\sqrt{2}} \right)^2$$

↓  
average inductor energy

$$Q_r = 2\omega W_{LA}$$

The power associated with pure inductive or capacitive circuit is referred as reactive power  $Q_r$ .

$$Q_r = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$I(t) = I_m \cos(\omega t + \theta_i)$$

$$V(t) = V_m \cos(\omega t + \theta_v)$$

for inductive elements  $0 < \theta_v - \theta_i < 90^\circ$   $Q_r > 0$

for capacitive elements  $-90^\circ < \theta_v - \theta_i < 0$   $Q_r < 0$

$$\text{Power factor} = pf = \cos(\theta_v - \theta_i)$$

$$\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v)$$

if  $\theta_v - \theta_i > 0$  (inductive) lagging power factor.

current lags voltage for inductive circuits

power factor =  $\cos(\theta_v - \theta_i)$  if  $\theta_v - \theta_i < 0$  (capacitive)  
leading power factor.



current leads voltage for capacitive circuits.

Ex:  $V(t) = 100 \cos(\omega t + 15^\circ)$  Volts

$I(t) = 4 \sin(\omega t - 15^\circ)$  Amps  $\begin{matrix} 4 \cos(\omega t - 15 - 90) \\ (\omega t - 105) \end{matrix}$

$P = ?$ ,  $Q = ?$

$\theta_v = 15^\circ$

$P = P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$   $\theta_i = -105^\circ$

$I(t) = 4 \cos(\omega t - 15^\circ - 90^\circ) = 4 \cos(\omega t - 105^\circ)$

$P = \frac{100 \cdot 4}{2} \cos(15 - (-105))$

$P = 200 \cos(120^\circ) = 200 * \left(\frac{-1}{2}\right) = -100$  Watts (source)

$P (-)$   $\rightarrow$  delivering power (source)  
 $P (+)$   $\rightarrow$  using power (resistive element)

$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{100 \cdot 4}{2} \sin(120^\circ) = \frac{200\sqrt{3}}{2}$

$Q = 173.21$  VAR (inductive since  $Q$  is positive)

Complex Power:

$S = P + jQ$  (VA)

$\downarrow$  complex  $\downarrow$  reactive

average

$S = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$


$$S = \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)}$$

$$S = \frac{1}{2} \underbrace{V_m e^{j\theta_v}}_{\text{phasor of voltage}} \underbrace{I_m e^{-j\theta_i}}_{\text{conjugate of phasor of current}}$$

$$S = \frac{1}{2} V I^*$$

$V \rightarrow$  voltage phasor  
 $I \rightarrow$  current phasor
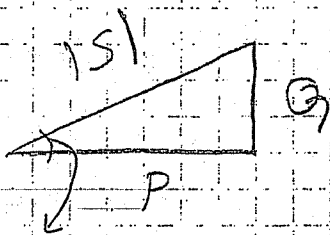
$$S = V_{rms} I_{rms}^* \quad \left( V_{rms} = \frac{V}{\sqrt{2}} \quad I_{rms} = \frac{I}{\sqrt{2}} \right)$$




$$|S| = \sqrt{Q^2 + P^2}$$

$$|S| = |V_{rms}| |I_{rms}^*|$$

$$\theta = \theta_v - \theta_i$$

$$|I_{rms}| = |I_{rms}^*|$$
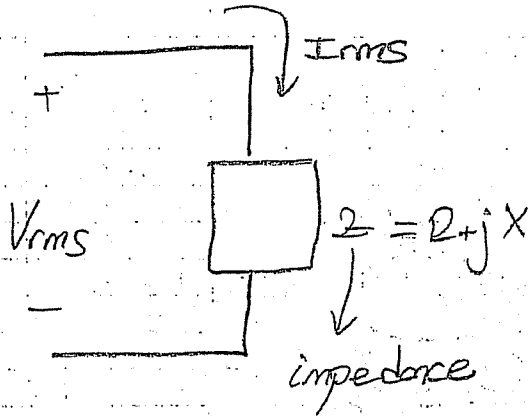
$$\tan \theta = \frac{Q}{P} \quad pf = \cos \theta = \cos(\theta_v - \theta_i)$$



$$S = V_{rms} \cdot I_{rms}^*$$

$$I_{rms} = \frac{V_{rms}}{Z}$$

$$S = V_{rms} \cdot \left(\frac{V_{rms}}{Z}\right)^* = V_{rms} \frac{V_{rms}^*}{Z^*}$$

$$S = \frac{|V_{rms}|^2}{Z^*}$$

$$S = \frac{|V_{rms}|^2}{Z^*} \cdot \frac{Z}{Z} = \frac{Z}{|Z|^2} |V_{rms}|^2 = Z |I_{rms}|^2$$

$$S = \frac{|V_{rms}|^2 Z}{|Z|^2} = |V_{rms}|^2 \frac{R}{R^2 + X^2} + j |V_{rms}|^2 \frac{X}{R^2 + X^2}$$

$$\text{power factor} = \cos(\underbrace{\theta_v - \theta_i}_{\theta})$$

$\theta = 0 \Rightarrow$  circuit is purely resistive


$\theta = \pm 90 \Rightarrow$  circuit is purely (reactive)

( +90 purely inductive  
-90 purely capacitive )


$P(t) \rightarrow$  instantaneous power

$$\cos \theta = 1 \quad \theta = 0 \text{ resistive}$$

$P(t)$

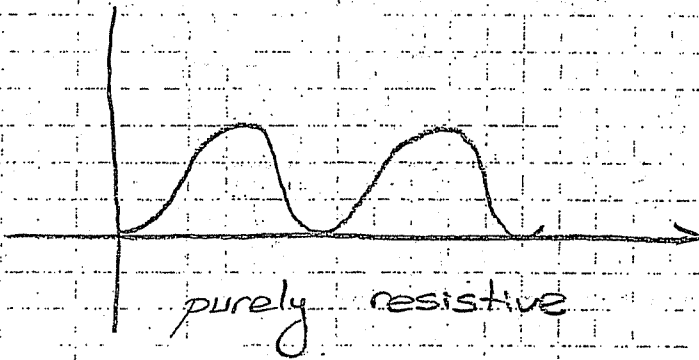

$P(t)$

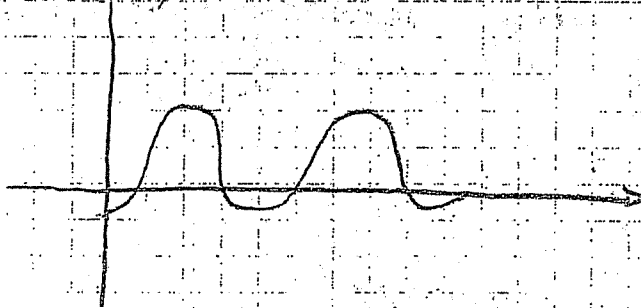


$$\cos \theta = 0.8$$

$$0 < \cos(\theta) < 1$$

resistance + reactance

$P(t)$

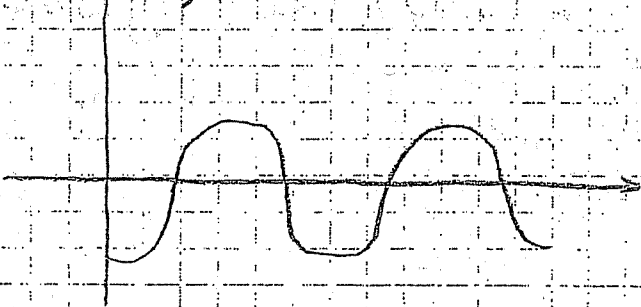


$$\cos \theta = 0$$

$$\theta = \pm 90$$

reactive  
(capacity)  
inductive

\* Reactive power is a measure of energy between the source and the circuit without being used by the circuit.

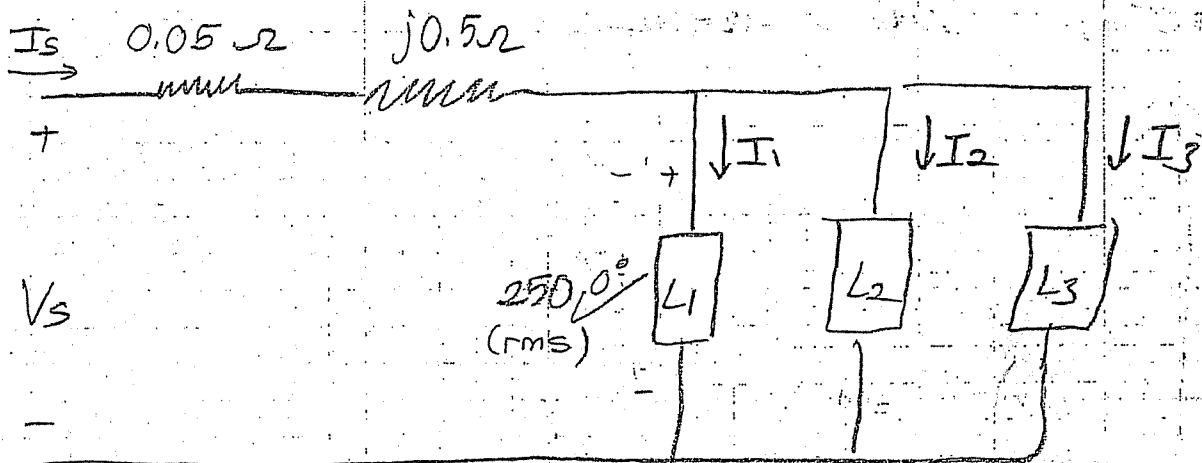Ex:

Load 1: uses 8 kW with lagging of 0.8  
 Load 2: absorbs 20 kVA with leading of 0.6  
 Load 3:  $Z = 2.5 + j5.0 \Omega$

$f = 60 \text{ Hz}$  (for  $V_s$ )  $V_s = ?$

$$V_s = I_s [0.05 + j0.5] + 250 \angle 0^\circ$$

$$V_s = I_s [0.05 + j0.5] + 250 [\cos 0^\circ + j \sin 0^\circ]$$

Load 1: (lagging = inductive)

$$\text{pf} = 0.8 = \theta_1 \quad P_1 = 8 \text{ kW}$$

$$|S_1| = \frac{P_1}{\text{pf}} = 10000 \text{ VA}$$

$$Q_1 = |S_1| \sin \theta = 6000 \text{ VAR}$$

$$S_1 = P_1 + jQ_1 = 8000 + j6000$$

$$V_1 \cdot I_1^* = S_1$$

$$250 \cdot I_1^* = 8000 + j6000 \Rightarrow I_1^* = 32 + j24 \text{ (rms)}$$


$$I_1 = 32 - j24 \text{ (rms)}$$

Load 2: (leading  $\Rightarrow$  capacitive)

$$|S_2| = 20000 \text{ VA}$$

$$G_2 < 0$$

$$P_2 = |S_2| \cdot \text{pf}$$

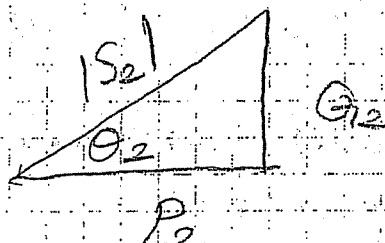

$$P_2 = 20000 \cdot 0.6 = 12000 \text{ Watts}$$

$$G_2 = -\sqrt{S_2^2 - P_2^2} = -16000 \text{ VAR}$$

↑  
since capacitive

$$S_2 = P_2 + jG_2$$

$$= 12000 - j16000 \text{ VA}$$

$$\sqrt{2} I_2^* = S_2$$

$$250 \angle 0^\circ I_2^* = 12000 - j16000$$

$$I_2^* = 48 - 64j$$

$$I_2 = 48 + 64j \text{ (rms)}$$

Load 3:  $Z = 2.5 + j5.0 \Omega$

$$I_3 = \frac{V_3}{Z} = \frac{250 \angle 0^\circ}{2.5 + j5.0 \Omega} = \frac{250 (\cos 0^\circ + j \sin 0^\circ)}{2.5 + j5.0}$$

$$I_3 = \frac{100}{1 + 2j} = \frac{100 - 200j}{5} = 20 - 40j$$

$$I_s = I_1 + I_2 + I_3$$

$$I_s = (32 - 24j) + (48 + 64j) + (20 - 40j)$$

$$I_s = 100 + 0j$$

$$V_s = 250 \angle 0^\circ + I_s (0.05 + j0.5)$$

$$V_s = 250 (\cos 0^\circ + j \sin 0^\circ) + 100 (0.05 + j0.5)$$

$$V_s = 250 + 5 + 50j$$

$$V_s = 255 + 50j \text{ (rms)} \rightarrow \text{phasor}$$


$$|V_s| = \sqrt{255^2 + 50^2} = 259.86$$

$$\angle V_s = \arctan \left( \frac{50}{255} \right) = 11.09^\circ$$

$$V_s(t) = 259.86 \cos(2\pi f t + 11.09^\circ)$$

$$V_s(t) = 259.86 \cos(120\pi t + 11.09^\circ) \text{ (rms)}$$
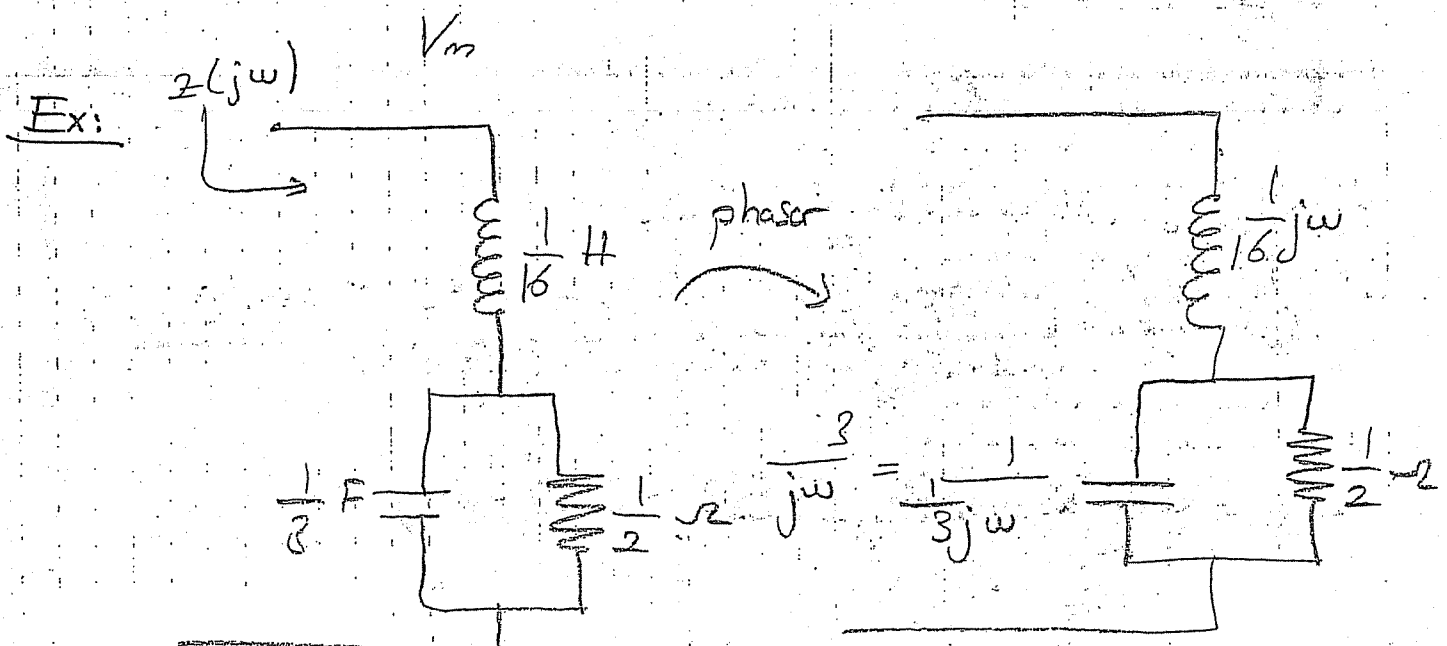
$$V_s(t) = \sqrt{2} (259.86) \cos(120\pi t + 11.09^\circ)$$



$$Z(j\omega) = \frac{j\omega}{16} + \frac{\frac{3}{j\omega} + \frac{1}{2}}{\frac{3}{j\omega} + \frac{1}{2}} = \frac{j\omega}{16} + \frac{3}{(6+j\omega)(16)}$$

$$Z(j\omega) = \frac{6j\omega - \omega^2 + 48}{16(6+j\omega)(6-j\omega)} = \frac{36j\omega + \cancel{6\omega^2} - \cancel{6\omega^2} + j\omega^3 + 288 - 48j}{16(36 + \omega^2)}$$

$$Z(j\omega) = \frac{j\omega^3 - 12j\omega + 288}{16(36 + \omega^2)} = \frac{288 + j\omega(\omega^2 - 12)}{16(36 + \omega^2)}$$

$$\omega = 0 \quad \text{or} \quad \omega = \sqrt{12} \text{ rad/sec.}$$

$$\omega = 0 \Rightarrow Z(j\omega) = \frac{288}{16 \times 36} \rightarrow \text{real number}$$

$Z(j\omega) \rightarrow$  purely resistive

$$\omega = \sqrt{12} \Rightarrow Z(j\omega) = \frac{288}{16(36+12)} = \frac{288}{16 \times 48} = \frac{6}{16} \rightarrow \text{purely resistive}$$


$$0 < \omega < \sqrt{12} \quad Z(j\omega) = A - Bj \quad B > 0$$

$\rightarrow$  capacitive

$$\sqrt{12} < \omega \quad Z(j\omega) = A + jC \quad C > 0$$



## Superposition in Power Calculations:

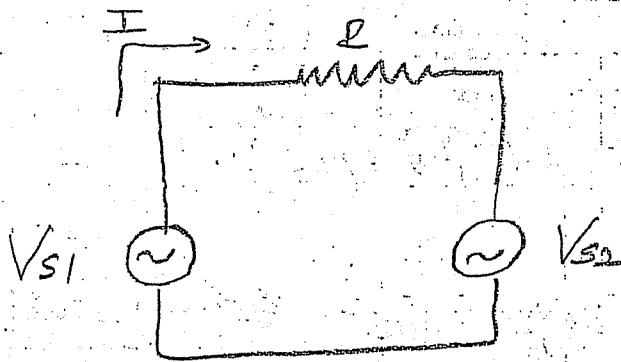

$$I_1 \rightarrow V_{s1} = V_{m1} \cos(\omega_1 t + \phi_1)$$

$$I_2 \rightarrow V_{s2} = V_{m2} \cos(\omega_2 t + \phi_2)$$

$$I(t) = I_1(t) - I_2(t)$$

## Instantaneous Power over Resistor R:

$$P(t) = R \cdot I^2(t)$$

$$P(t) = R (I_1(t) - I_2(t))^2 \neq 0$$

$$= R \cdot I_1^2(t) + R I_2^2(t) - 2 R I_1(t) I_2(t)$$

$$= P_1(t) + P_2(t)$$

$$P(t) \neq P_1(t) + P_2(t)$$

\* Superposition does not apply for instantaneous power

$$P(t) \neq P_1(t) + P_2(t)$$

\* Now consider average power

$$P_{avg} = P = \frac{1}{T} \int_0^T P(t) dt$$

$$P = \frac{1}{T} \int_0^T [R I_1^2(t) + R I_2^2(t) - 2 R I_1(t) I_2(t)] dt$$

$$P = \frac{1}{T} \int_0^T [P_1(t) + P_2(t) - 2 R I_1(t) I_2(t)] dt$$

$$P = P_{1 \text{ avg}} + P_{2 \text{ avg}} - \frac{2R}{T} \int_0^T I_1(t) I_2(t) dt$$

$$\int_0^T I_1(t) I_2(t) dt = I_{m1} I_{m2} \int_0^T \cos(\omega_1 t + \phi_1) \cos(\omega_2 t + \phi_2) dt$$


$$= \begin{cases} \frac{1}{2} I_{m1} I_{m2} T \cos(\phi_1 - \phi_2); & \omega_1 = \omega_2 \\ 0 & \omega_1 \neq \omega_2 \end{cases}$$

\* If  $\omega_1 = \omega_2$ , superposition does not apply for average power  $P \neq P_{1 \text{ avg}} + P_{2 \text{ avg}}$

\* If  $\omega_1 \neq \omega_2$ , superposition does apply for average power

$$P = P_{1 \text{ avg}} + P_{2 \text{ avg}}$$


Ex:

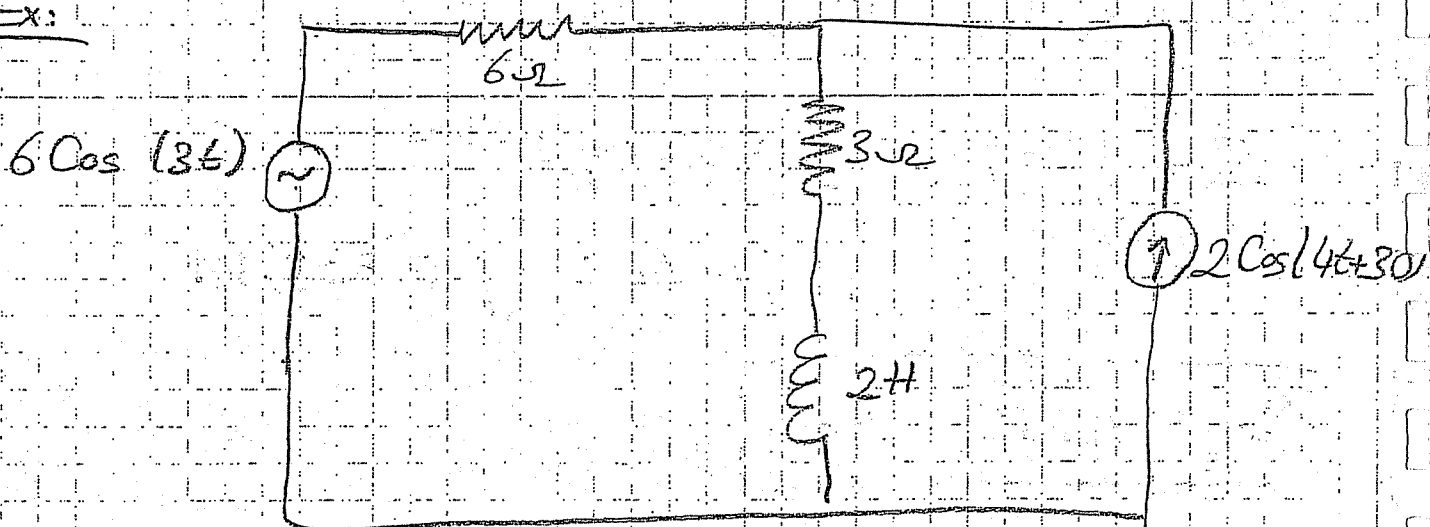

Find average power over  $3 \Omega$  resistor in SSS

To find average power we can use superposition for individual average power due to two different sources having two different frequencies.

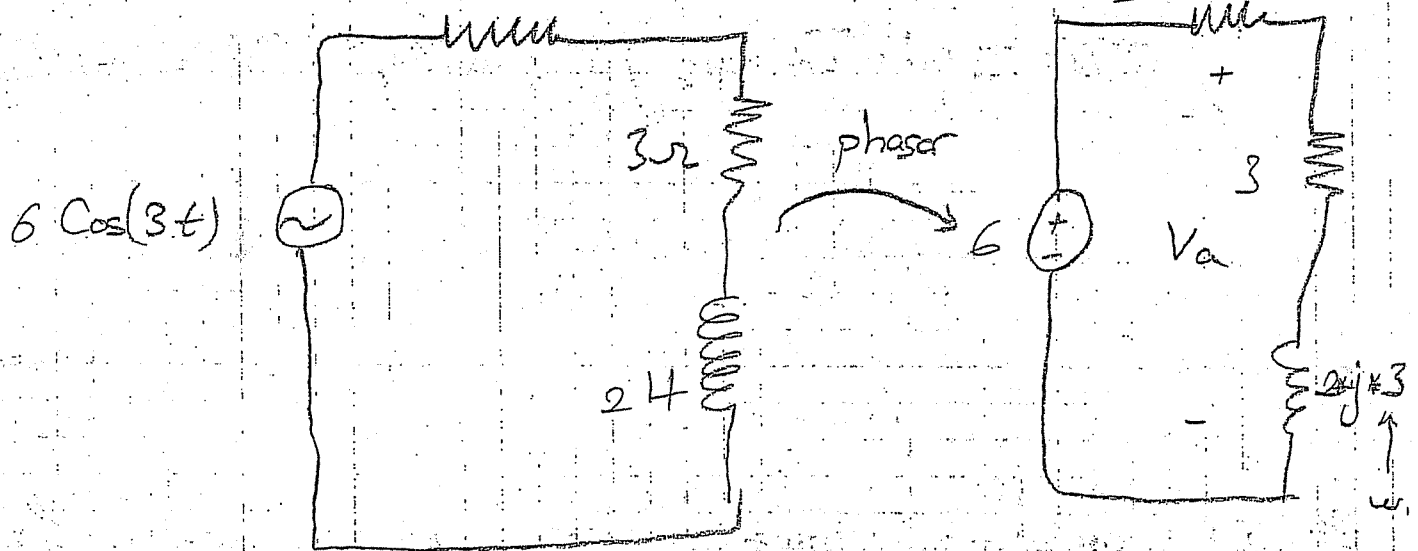Kill current ( $\omega_1 = 3$ )  
 $6\Omega$



$$I_a = \frac{6}{6 + 3 + 6j} = 0.555 e^{-j33.69^\circ}$$

$$V_a = I_a (3 + 6j)$$


$$V_a = 3.72 e^{j29.7^\circ} \text{ Volts}$$

$$S_a = \frac{1}{2} V_a I_a^* = 1.033 e^{j63.43^\circ}$$


$$= (0.462 + j0.923) \text{ VA}$$

$$P_{avg} = 0.462 \text{ Watts}$$

Kill voltage source

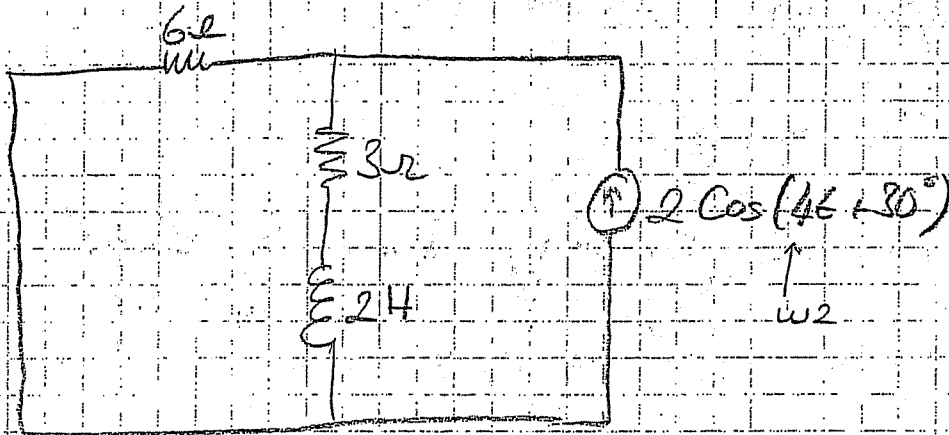

phasor

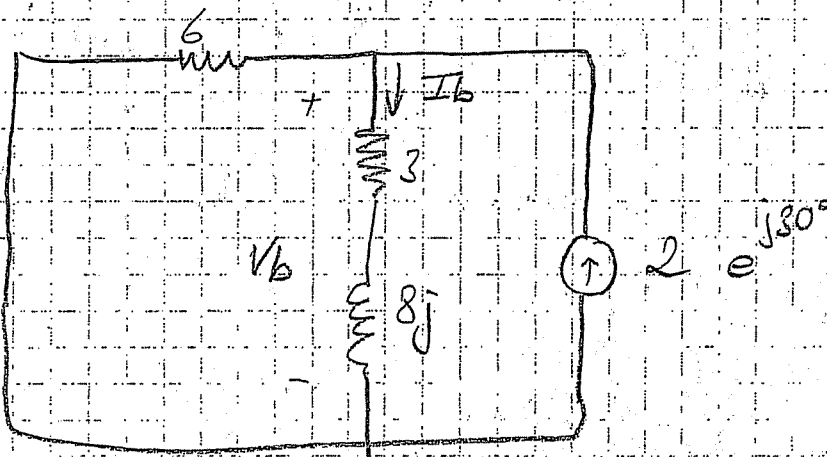

$$I_b = \frac{6}{6 + 8j + 3} 2 e^{j30^\circ} = 0.997 e^{-j11.6^\circ}$$

$$V_b = (3 + 8j) I_b = 8.518 e^{j57.81^\circ}$$

$$S_b = \frac{1}{2} V_b I_b^* = 4.246 e^{j69.44^\circ}$$

$$S_b = 1.491 + j3.976 \text{ VA}$$

$$P_{\text{avg}} = 1.491 \text{ Watts}$$

$$P_{avg} = P = P_{1avg} + P_{2avg} = 1.953 \text{ Watts}$$


(since source frequencies are different)

### Laplace Transform:


- \* time domain  $\rightarrow$  frequency domain transformation
- \* diff equation  $\rightarrow$  linear equation
- \* valid for LTI circuits
- \* initial conditions are all considered (different from phasor domain)
- \* IT gives the full-response for the circuit
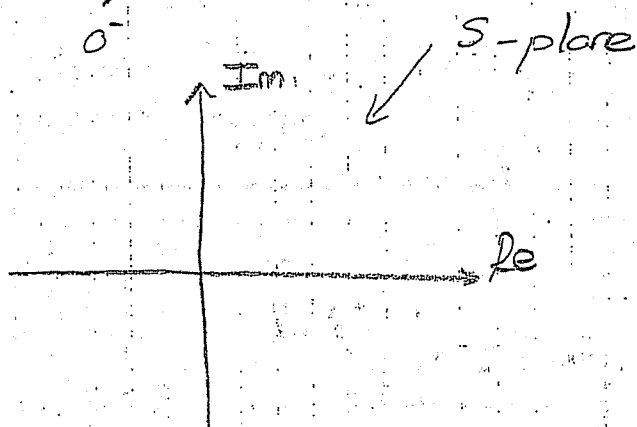
### Definition:

$$F(s) = \int_0^{\infty} f(t) e^{-st} dt$$



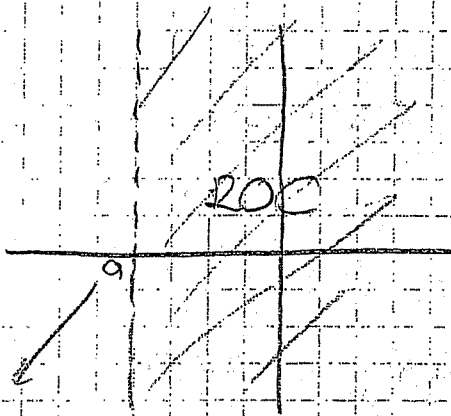ROC  $\rightarrow$  (Region of convergence): The region in s-plane such that the Laplace transform of the function  $f(t)$  converges



$$\text{ROC: } \text{Re}\{s\} > a$$

will be determined  
by  $f(t)$

Ex:  $f(t) = u(t)$  find  $F(s)$


$$f(t) \xrightarrow{\mathcal{L}} F(s)$$

$$F(s) = \int_{0^-}^{\infty} \underbrace{u(t)}_1 e^{-st} ds = \int_{0^-}^{\infty} e^{-st} dt = -\frac{1}{s} e^{-st} \Big|_{0^-}^{\infty}$$

$$= -\frac{1}{s} [e^{-\infty s} - e^{-0s}] = -\frac{1}{s} [0 - 1]$$

$$= \frac{1}{s}$$

ROC:  $\text{Re}\{s\} > 0$

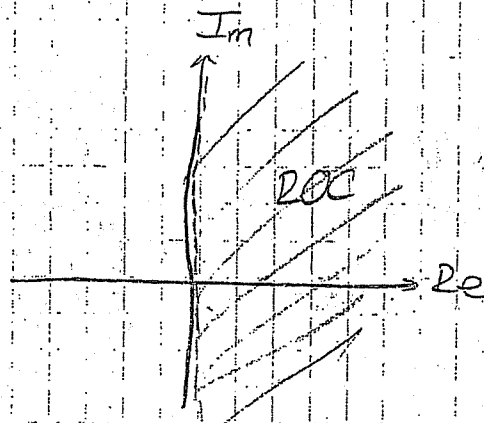


Ex:  $f(t) = e^{-at} u(t)$

$$F(s) = \frac{1}{s+a}$$

$$\text{ROC: } \text{Re}\{s+a\} > 0$$

$$\text{Re}\{s\} + a > 0$$

$$\text{Re}\{s\} > -a$$

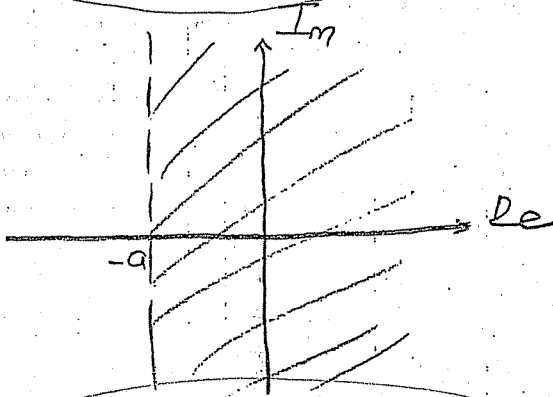

Ex:  $f(t) = \delta(t)$

$$f(t) \delta(t) = f(0) \delta(t)$$

$$F(s) = \int_{0^-}^{\infty} \delta(t) e^{-st} dt = \int_{0^-}^{\infty} \delta(t) \underbrace{e^{-s \cdot 0}}_1 dt = \int_{0^-}^{\infty} \delta(t) dt = 1$$

$$\delta(t) \xrightarrow{\mathcal{L}} 1$$

ROC: whole s-plane

Inverse Laplace Transform:

$$\mathcal{L}^{-1}[F(s)] = f(t)$$

$$f(t) = \frac{1}{2\pi j} \int_{\alpha-j\infty}^{\alpha+j\infty} F(s) e^{st} ds$$

uniqueness property:


$$f(t) \xrightarrow{\mathcal{L}} F(s) \iff \mathcal{L}^{-1}[F(s)] = f(t)$$

linearity:

$$\mathcal{L}[A f_1(t) + B f_2(t)] = A F_1(s) + B F_2(s)$$

Ex:

$$f(t) = A \sin(\omega t) u(t)$$

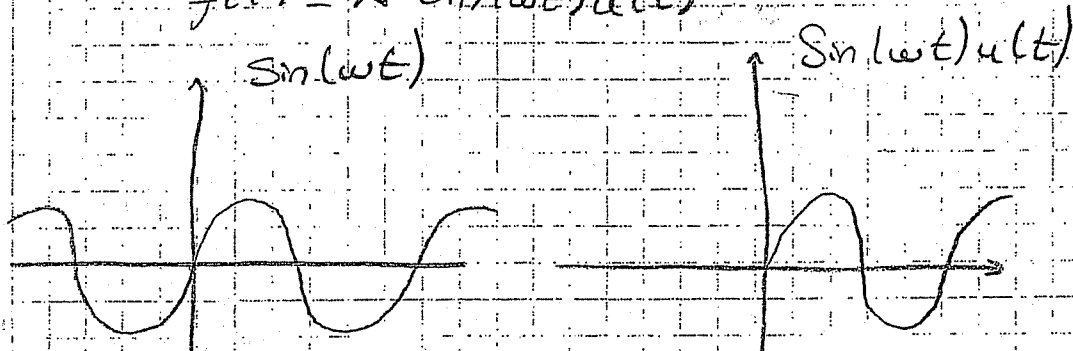

$$\sin(\omega t) = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

$$\cos(\omega t) = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

$$f(t) = A \sin(\omega t) u(t) = \frac{e^{j\omega t} - e^{-j\omega t}}{2j} u(t)$$

$$F(s) = \int_{0^-}^{\infty} \left[ \frac{e^{j\omega t} - e^{-j\omega t}}{2j} \right] u(t) e^{-st} dt$$

$$= \frac{1}{2j} \int_{0^-}^{\infty} \left[ e^{(j\omega - s)t} - e^{-(j\omega + s)t} \right] dt$$

$$= \frac{1}{2j} \left[ \frac{1}{s - j\omega} - \frac{1}{s + j\omega} \right] = \frac{1}{2j} \left[ \frac{1}{s - j\omega} - \frac{1}{s + j\omega} \right]$$



$$F(s) = \frac{1}{2j} \left[ \frac{s+j\omega - (s-j\omega)}{s^2 + \omega^2} \right] = \frac{1}{2j} \frac{2j\omega}{(s^2 + \omega^2)} = \frac{\omega}{s^2 + \omega^2}$$

$$\mathcal{L}\{ \sin(\omega t) \} \rightarrow \frac{\omega}{s^2 + \omega^2}$$

Integration:

$$k(t) = \int_{0^-}^t f(z) dz$$

$$\mathcal{L}\{k(t)\} = \mathcal{L}\left\{ \int_{0^-}^t f(z) dz \right\} = \int_{0^-}^{\infty} \left[ \int_{0^-}^t f(z) dz \right] e^{-st} dt$$

(use integration by parts)

$$y = \int_{0^-}^t f(z) dz \quad dx = e^{-st} dt$$

$$dy = f(t) dt \quad x = -\frac{1}{s} e^{-st}$$

$$\int_a^b y dx = yx \Big|_a^b - \int_a^b x dy = \left[ \int_{0^-}^t f(z) dz \right] \left( -\frac{1}{s} e^{-st} \right) \Big|_0^{\infty}$$

$$- \int_{0^-}^{\infty} f(t) \left( -\frac{1}{s} e^{-st} \right) dt$$

$$= \underbrace{\left( \int_{0^-}^{\infty} f(\alpha) d\alpha \right)}_M \underbrace{\left( -\frac{1}{s} e^{-s\infty} \right)}_0 - \underbrace{\left( \int_{0^-}^{\infty} f(\alpha) d\alpha \right)}_0 \underbrace{\left( -\frac{1}{s} e^{-0 \cdot s} \right)}_{-1/s}$$

$$\underbrace{\int_{0^-}^{\infty} f(t) e^{-st} dt}_{F(s)/s} = \frac{F(s)}{s}$$

$$\mathcal{L} \left\{ \int_{0^-}^t f(\alpha) d\alpha \right\} = \frac{F(s)}{s}$$

Ex:  $f(t) = t u(t) = r(t)$

$$r(t) = \int_{0^-}^t u(\alpha) d\alpha$$

$$\mathcal{L} \{ r(t) \} = \mathcal{L} \left\{ \int_{0^-}^t u(\alpha) d\alpha \right\} = \frac{1}{s} \mathcal{L} \{ u(t) \} = \frac{1}{s} * \frac{1}{s} = \frac{1}{s^2}$$

Differentiation:

$$\mathcal{L} \left\{ \frac{d}{dt} f(t) \right\} = sF(s) - f(0^-)$$

$$\mathcal{L} \left\{ \frac{d^2}{dt^2} f(t) \right\} = s^2 F(s) - sf(0^-) - f'(0^-) \quad \text{HW proof}$$

$$\mathcal{L} \left\{ \frac{d^n}{dt^n} f(t) \right\} = s^n F(s) - s^{n-1} f(0^-) - s^{n-2} f'(0^-) - s^{n-3} f''(0^-) - \dots - sf^{(n-2)}(0^-) - f^{(n-1)}(0^-)$$

$$\mathcal{L} \left\{ \sin(\omega t) \right\} = \frac{\omega}{s^2 + \omega^2}$$

$$\cos(\omega t) = \frac{1}{\omega} \frac{d}{dt} \sin(\omega t)$$

$$\mathcal{L} \left\{ \cos(\omega t) \right\} = \frac{1}{\omega} \mathcal{L} \left\{ \frac{d}{dt} \sin(\omega t) \right\}$$

$$= \frac{1}{\omega} \left[ s \mathcal{L} \left\{ \sin(\omega t) \right\} - \sin(\omega \cdot 0^-) \right]$$

$$= \frac{1}{\omega} \left[ s \frac{\omega}{s^2 + \omega^2} - 0 \right] = \frac{s}{s^2 + \omega^2}$$

$$\mathcal{L} \left\{ \cos(\omega t) \right\} = \frac{s}{s^2 + \omega^2}$$

Differentiation in s-domain:

$$-t x(t) \xrightarrow{\mathcal{L}} \frac{dX(s)}{ds}$$

Shift in time domain:

$$\mathcal{L}\{f(t-a)\} = e^{-sa} F(s)$$

Shift in frequency domain:

$$\mathcal{L}\{e^{-at} f(t)\} = F(s+a)$$

$$\mathcal{L}\{e^{-at} \sin(\omega t)\} = \frac{\omega}{(s+a)^2 + \omega^2}$$

Scaling Property:

$$\mathcal{L}\{f(at)\} = \frac{1}{a} F\left(\frac{s}{a}\right) \quad a > 0$$

Pole - Zero Diagram:

$$F(s) = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s - b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s - a_0}$$

$$F(s) = \frac{\overbrace{(b_m)}^{\text{scalar}} (s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_n)}$$

scalar

$p_1, p_2, \dots, p_n \rightarrow$  poles  $\rightarrow X$

$z_1, z_2, \dots, z_n \rightarrow$  zeros  $\rightarrow O$

Ex:  $f(t) = [e^{-2t} + \cos(2t) - \sin(2t)] u(t)$

find pole zero diagram

$F(s) = ?$


$$\mathcal{L}\{f(t)\} = F(s) = \frac{1}{s+2} + \frac{s}{s^2+4} - \frac{2}{s^2+4}$$

$$F(s) = \frac{s^2+4 + s^2+2s - 2s-4}{(s^2+4)(s+2)} = \frac{2s^2}{(s+2)(s+2j)(s-2j)}$$

$p_1 = -2 \quad p_2 = -2j \quad p_3 = 2j$

$z_1 = 0 \quad z_2 = 0$

Pole-zero diagram:

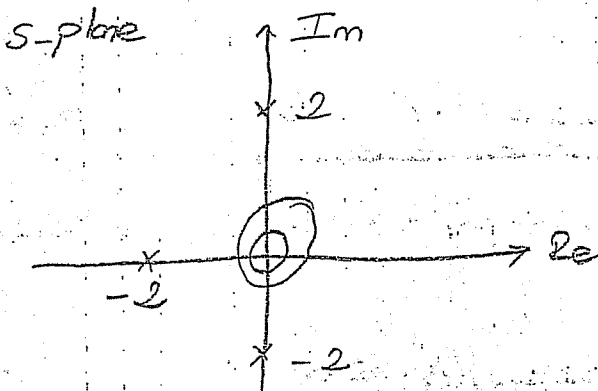

Note that: The poles (pi values) give the natural frequencies of the circuit when there is no input.

Relation between the zeros and poles in s-plane:


Ex1  $\alpha > 0$   $f(t) = e^{-\alpha t} \cos(\omega_0 t) u(t)$

$$F(s) = \frac{s + \alpha}{(s + \alpha)^2 + \omega_0^2} = \frac{N(s)}{D(s)}$$

poles  $\Rightarrow D(s) = 0$  (roots)

zeros  $\Rightarrow N(s) = 0$  (roots)


pole-zero diagram:  
s-plane

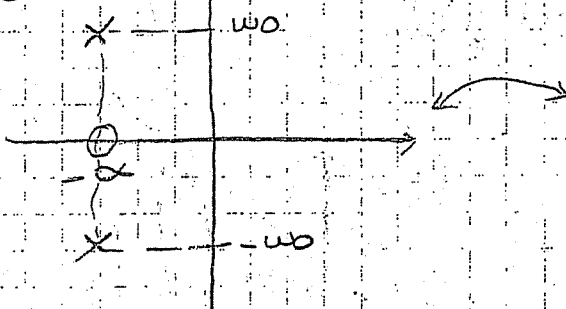


$$z_1 = -\alpha$$

$$p_1 = -\alpha + j\omega_0$$


$$p_2 = -\alpha - j\omega_0$$

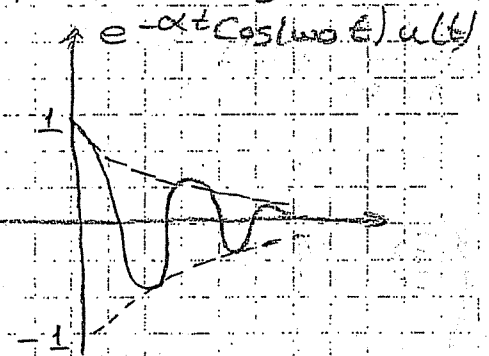

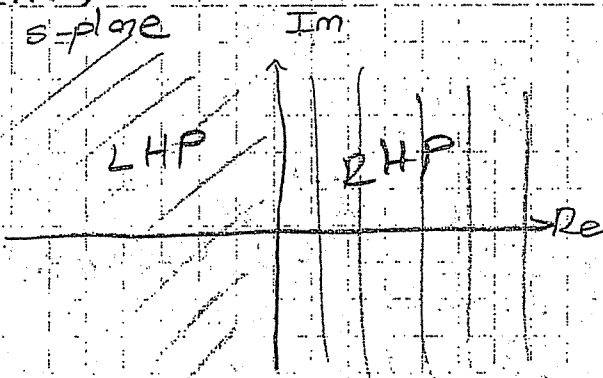
\* If the poles of a circuit are on the left half plane (LHP)



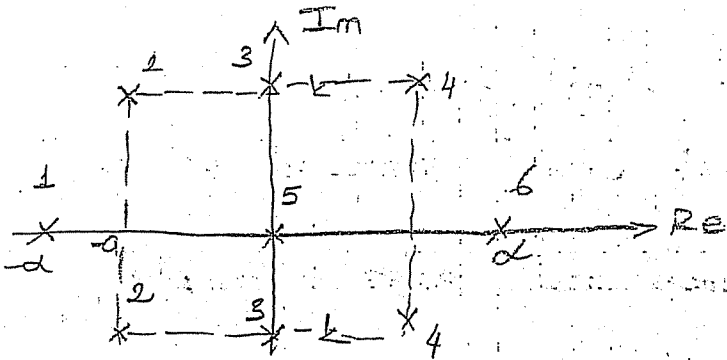the time waveform is bounded otherwise unbounded




①

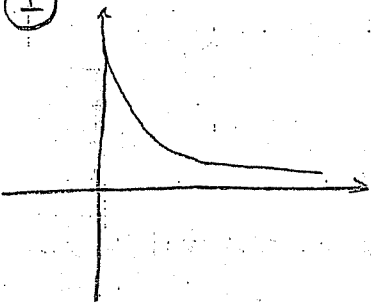


$$\frac{1}{s + \alpha} \xrightarrow{\mathcal{L}^{-1}} e^{-\alpha t}$$

②

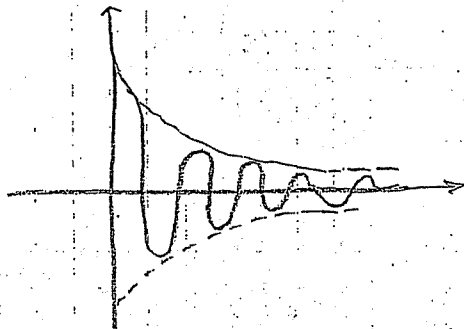


$$\frac{A_1^*}{(s + a + jk)} + \frac{A_1}{(s + a - jk)} \xrightarrow{\mathcal{L}^{-1}} e^{-at} [K_1 \cos(kt) + K_2 \sin(kt)]$$

③

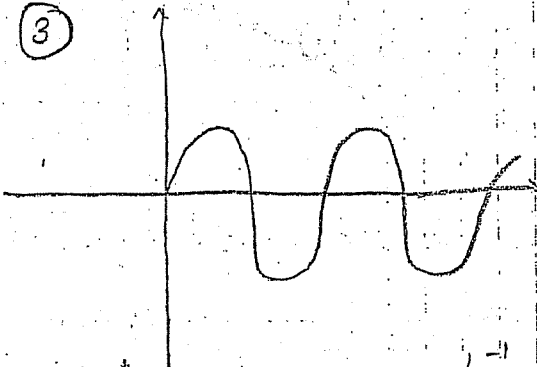


$$\frac{A_1^*}{s + jk} + \frac{A_1}{s - jk} \xrightarrow{\mathcal{L}^{-1}} K_1 \cos(kt) + K_2 \sin(kt)$$

④

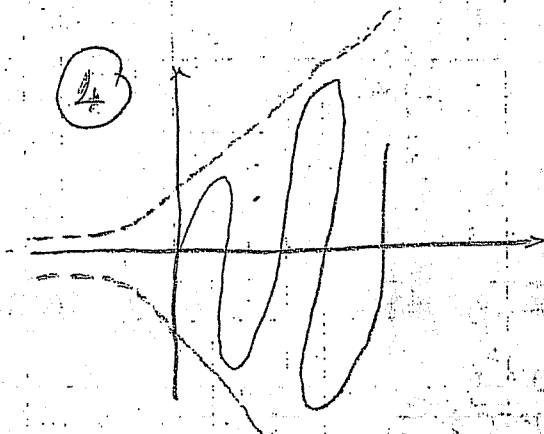


$$\frac{A_1}{-s + a + jk} + \frac{A_1^*}{s - a - jk} \xrightarrow{\mathcal{L}^{-1}} e^{at} [K_1 \cos(kt) + K_2 \sin(kt)]$$

⑤


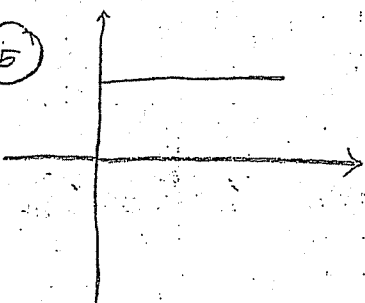


$$\frac{1}{s} \xrightarrow{\mathcal{L}^{-1}} u(t)$$


⑥

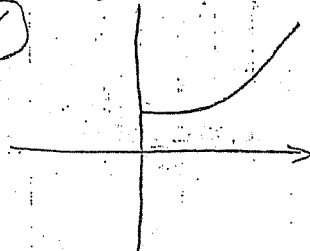

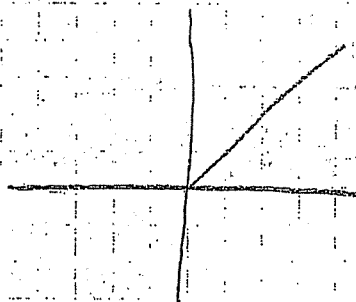
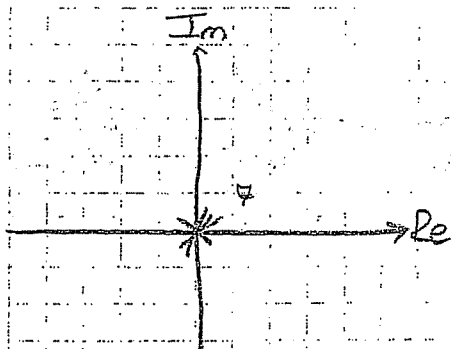
$$\frac{1}{s - \alpha} \xrightarrow{\mathcal{L}^{-1}} e^{\alpha t} u(t)$$


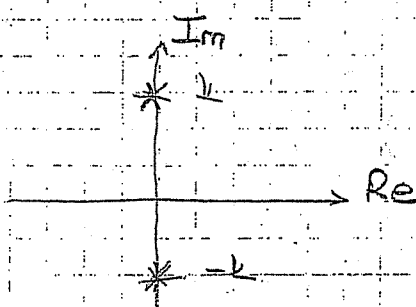
$$\frac{1}{s^2} \xrightarrow{\mathcal{L}^{-1}} r(t)$$


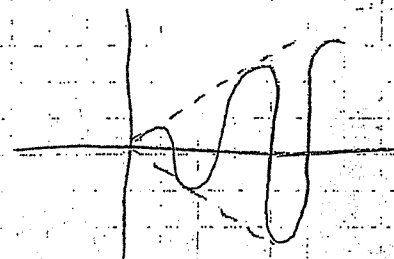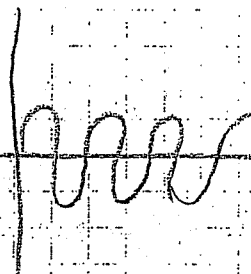
$$\frac{1}{(s^2+k^2)^2} \xrightarrow{\mathcal{L}^{-1}} [A_1 \cos(kt) + A_2 \sin(kt)] + t [A_3 \cos(kt) + A_4 \sin(kt)]$$



Find inverse Laplace transform:

$$\frac{A(s)}{B(s)} = \underbrace{P(s)}_{\text{improper expression}} + \underbrace{\frac{N(s)}{D(s)}}_{\text{proper rational function}}$$

$$\deg(N(s)) < \deg(D(s))$$



Ex1 (For proper part)

$$F(s) = \frac{K(s-z_1)}{(s-p_1)(s-p_2)(s-p_3)} = \frac{A_1}{s-p_1} + \frac{A_2}{s-p_2} + \frac{A_3}{s-p_3}$$

partial fraction expansion

Find  $A_1; A_2; A_3$

$A_1; A_2; A_3 \rightarrow$  residues

$$A_1 = (s-p_1) F(s) \Big|_{s=p_1} = \frac{K(s-z_1)}{(s-p_1)(s-p_3)} \Big|_{s=p_1}$$

Ex1  $F(s) = \frac{2(s+3)}{s(s+1)(s+2)} = \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+2}$

$(s+1)(s+2) \quad s(s+2) \quad s(s+1)$

$$\Rightarrow 2(s+3) = K_1(s+1)(s+2) + K_2 s(s+2) + K_3 s(s+1)$$

$$2s+6 = s^2 K_1 + 3s K_1 + 2K_1 + K_2 s^2 + 2s K_2 + K_3 s^2 + K_3 s$$

$$K_1 + K_2 + K_3 = 0 \Rightarrow -K_2 + K_3 = -3$$

$$3K_1 + 2K_2 + K_3 = 2 \Rightarrow 2K_2 + K_3 = -7$$

$$2K_1 = 6 \Rightarrow K_1 = 3$$

$$K_2 = -4 \quad K_3 = 1$$

$$F(s) = \frac{3}{s} + \frac{-4}{s+1} + \frac{1}{s+2}$$

$\mathcal{L}^{-1}$

$$f(t) = [3 - 4e^{-t} + e^{-2t}] u(t)$$

(Simple poles)  $\rightarrow$  all poles are real and distinct from each other

complex but simple poles

\* If  $F(s)$  is a rational expression with real coefficients then (if exist) the complex zeros and poles should appear in conjugate pairs

assume poles exist  $p_1 = -\alpha + j\beta$ ,  $p_2 = -\alpha - j\beta$

$$F(s) = \underbrace{\dots}_{\text{other poles}} + \frac{K}{s + \alpha - j\beta} + \frac{K^*}{s - \alpha - j\beta} + \underbrace{\dots}_{\text{other poles}}$$

$K \rightarrow$  complex number

$$K = |K| e^{j\theta} \quad K^* = |K| e^{-j\theta}$$

$$F(s) \xrightarrow{\mathcal{L}^{-1}} f(t) = \underbrace{\dots}_{\text{terms due to other terms}} + |K| e^{j\theta} e^{(-\alpha + j\beta)t} + |K| e^{-j\theta} e^{(-\alpha - j\beta)t}$$

terms due to other terms

$$f(t) = \dots + |K| e^{-\alpha t} \left[ \frac{e^{j(\theta + \beta t)} + e^{-j(\theta + \beta t)}}{2} \right] \dots$$

$$f(t) = \left[ \dots + 2|K| e^{-\alpha t} \cos(\beta t + \theta) + \dots \right] u(t)$$

$$\text{Ex: } F(s) = \frac{20(s+3)}{(s+1)(s^2+2s+5)} = \frac{20(s+3)}{(s+1)[(s+1)^2+2^2]}$$

$$\begin{array}{l} \text{poles } p_1 = -1 \quad p_2 = -1+2j \quad p_3 = -1-2j \\ \text{zeros } z_1 = -3 \end{array}$$

$$F(s) = \frac{K_1}{s+1} + \frac{K_2}{s+1-2j} + \frac{K_2^*}{s+1+2j}$$

$$K_2 = (s+1-2j) F(s) \Big|_{s=-1+2j}$$

$$\begin{aligned} K_2 &= \frac{20(s+3)}{(s+1)(s+1+2j)} \Big|_{s=-1+2j} = \frac{20(-1+2j+3)}{(-1+2j+1)(-1+2j+1+2j)} \\ &= \frac{20(2+2j)}{2j4j} = \frac{-40(1+j)}{8} \end{aligned}$$

$$K_2 = -5 - 5j$$

$$|K_2| = \sqrt{(-5)^2 + (-5)^2} = 5\sqrt{2}$$

$$K_2 = 5\sqrt{2} e^{j\frac{5\pi}{4}} \Rightarrow K_2^* = 5\sqrt{2} e^{-j\frac{5\pi}{4}}$$

$$\text{H.W. } K_1 = 10$$

$$f(t) = \left[ 10 e^{-t} + 2 \cdot 5\sqrt{2} e^{-t} \cos\left(2t + \frac{5\pi}{4}\right) \right] u(t)$$

Multiple pole

$$F(s) = \frac{N(s)}{(s-p_1)^n} = \frac{A_1}{(s-p_1)} + \frac{A_2}{(s-p_1)^2} + \dots + \frac{A_n}{(s-p_1)^n}$$

$$A_n = F(s) (s-p_1)^n \Big|_{s=p_1}$$

$$A_{n-1} = \frac{d}{ds} [F(s) (s-p_1)^n] \Big|_{s=p_1}$$

$$A_{n-2} = \frac{d^2}{ds^2} [F(s) (s-p_1)^n] \Big|_{s=p_1}$$

Ex: Improper rational expression  $\deg(N(s)) \geq \deg(D(s))$

$$F(s) = \frac{s^3 + 6s^2 + 12s + 8}{s^2 + 4s + 3} = \frac{N(s)}{D(s)} = s + 2 + \frac{s + 2}{s^2 + 4s + 3}$$

$$\frac{N(s)}{D(s)} = \left( \begin{array}{l} s^3 + 6s^2 + 12s + 8 \\ s^3 + 4s^2 + 3s \\ \hline 2s^2 + 9s + 8 \\ 2s^2 + 8s + 6 \\ \hline s + 2 \end{array} \right)$$

polynomial  
improper

proper  
rational  
expression

$$\mathcal{L}\{f(t)\} = 1$$

$$\begin{aligned}\mathcal{L}\left\{\frac{d}{dt}f(t)\right\} &= s\mathcal{L}\{f(t)\} - f(0) \\ &= s \cdot 1 - 0 = s\end{aligned}$$

$$F(s) = s + 2 + \frac{1/2}{s+1} + \frac{1/2}{s+3}$$

$\mathcal{L}^{-1}$

$$f(t) = \delta(t) + 2f(t) + \frac{1}{2}e^{-t}u(t) + \frac{1}{2}e^{-3t}u(t)$$

### Initial and Final Value Theorems:

Final value  $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$

Initial value theorem  $\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s)$

### Constraints

① Initial value theorem is valid when  $F(s)$  is a proper function.

$$F(s) = \frac{s^2 + s + 1}{s^2 + s - 1} = \frac{N(s)}{D(s)}$$

$$\deg(N(s)) = 2$$

$$\deg(D(s)) = 2$$

$$\begin{array}{r|l} s^2 + s + 1 & s^2 + s - 1 \\ \hline s^2 + s - 1 & 1 \end{array}$$

2


$$F(s) = \frac{N(s)}{D(s)} = 1 + \frac{2}{s^2 + s - 1} \rightarrow \text{improper}$$

real number  
(polynomial)


\* In order to obtain a proper function  $\deg(N(s)) < \deg(D(s))$

② Final value theorem is valid when the poles of  $s F(s)$  are all in left half plane

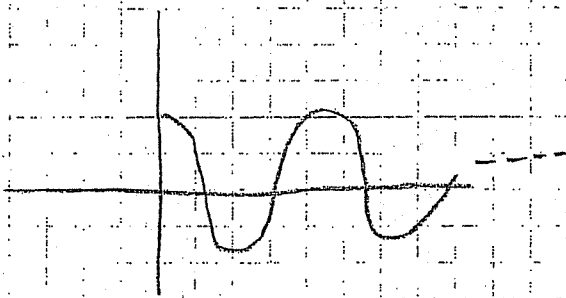Ex:  $\lim_{t \rightarrow \infty} \cos(\beta t) = \text{Unknown}$


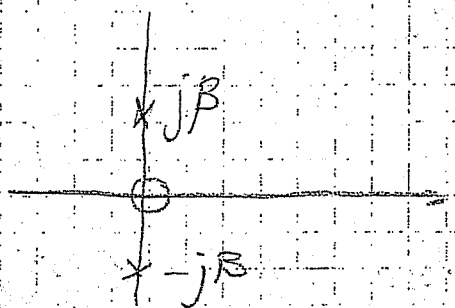
$$\cos(\beta t) \rightarrow \frac{s}{s^2 + \beta^2}$$



poles are at imaginary axis  
(these poles are not in left half plane)

(unknown)


$$\lim_{t \rightarrow \infty} \cos(\beta t) \stackrel{?}{=} \lim_{s \rightarrow 0} s \frac{s}{s^2 + \beta^2} = 0$$

contradiction

### Circuit Analysis in Laplace Domain:

- ① Find differential equation
- ② Transform the differential equation to Laplace domain.
- ③ Find the answer and again turn to time domain using  $\mathcal{L}^{-1}$

Ex:

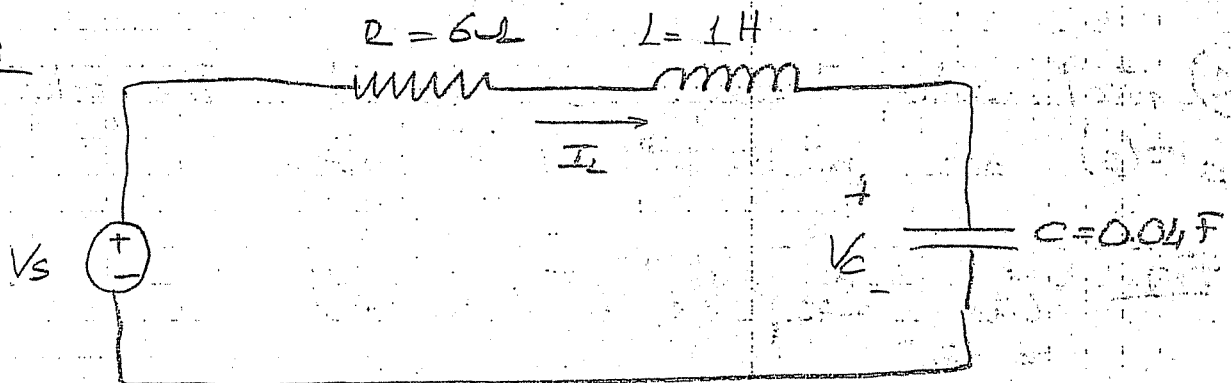

$$V_C(0^-) = 1V$$

$$I_L(0^-) = 5A$$

$$V_S(t) = 12 \sin(5t) \quad t \geq 0$$

KVL:  $V_S = V_R + V_L + V_C$

$$V_S = I_L \cdot R + L \frac{dI_L}{dt} + V_C$$

$$I_C = C \frac{dV_C}{dt}$$

$$\int_0^t \frac{1}{C} I_C(t') dt' = \int_{V_C(0^-)}^{V_C(t)} dV_C \quad \frac{1}{C} \int_0^t I_C(t') dt' = V_C(t) - V_C(0^-)$$

$$V_C(t) = V_C(0^-) + \frac{1}{C} \int_0^t I_L(t') dt'$$

$$V_S = I_L \cdot R + L \frac{dI_L}{dt} + V_C(0^-) + \frac{1}{C} \int_0^t I_L(t') dt'$$

(integro-differential equation.)

$$V_S(s) = R \cdot I_L(s) + L \left[ s I_L(s) - I_L(0^-) \right] + \frac{V_C(0^-)}{s}$$

Integrating  
Laplace  
must always

$$I_L(s) = \frac{s V_S(s) \frac{1}{L} + \frac{5 I_L(0^-) - \frac{1}{L} V_C(0^-)}{s^2 + \frac{R}{L} s + \frac{1}{LC}}}{s^2 + \frac{R}{L} s + \frac{1}{LC}}$$

$$I_L(s) = \frac{s V_S(s)}{(s+3)^2 + 4^2} + \frac{5s - 1}{(s+3)^2 + 4^2}$$

complete  
response

zero-state  
response

zero-input  
response

$$I_{cs}(s)$$


$$I_{ci}(s)$$



pole location

$$s_1 = -3 + 4j$$

$$s_2 = -3 - 4j$$

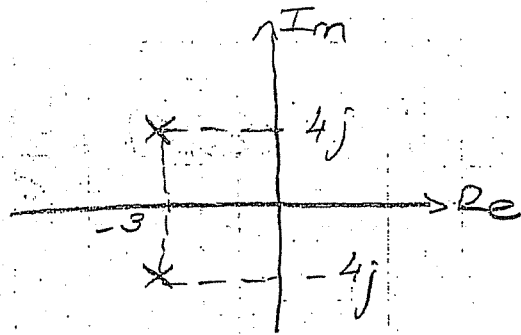let's find zero-state response  $I_{zs}(t)$ 

$$V_s(s) = 12 * \frac{5}{s^2 + 5^2} = \frac{60}{s^2 + 5^2}$$

$$I_{zs}(s) = \frac{s \cdot 60}{(s+3)^2 + 4^2} * \frac{1}{(s+3)^2 + 4^2} = \frac{K_1}{s+3-4j} + \frac{K_1^*}{s+3+4j} + \frac{K_2}{s-5j} + \frac{K_2^*}{s+5j}$$

$$I_{zs}(t) = 2.5 e^{-3t} \cos(4t + 90^\circ) + 2 \cos(5t - 90^\circ)$$

$$I_{zs}(t) = -2.5 e^{-3t} \sin(4t) + 2 \sin(5t) \quad 5 \geq 0$$

$$K_1 = \left. (s+3-4j) I_{zs}(s) \right|_{s=-3+4j}$$

$$K_2 = \left. (s-5j) I_{zs}(s) \right|_{s=5j}$$

$$\frac{K}{(s+\alpha-j\beta)} + \frac{K^*}{(s+\alpha+j\beta)}, \quad K = |K| e^{j\theta}$$

 $\mathcal{L}^{-1} \downarrow$ 

$$2|K| e^{-\alpha t} \cos(\beta t + \theta)$$

$$\underline{I}_{z0}(s) = \frac{5s-1}{(s+3)^2+4^2} = \frac{K_3}{s+3-4j} + \frac{K_3^*}{s+3+4j}$$

$$K_3 = \left. \frac{5s-1}{(s+3)^2+4^2} (s+3-4j) \right|_{s=-3+4j}$$

$$K_3 = \left. \frac{5s-1}{s+3+4j} \right|_{s=-3+4j} = \frac{5(-3+4j)-1}{8j}$$

$$\underline{K}_3 = \frac{-16+20j}{8j} = 2j + 2.5$$

$$|K_3| = \sqrt{(1+2)^2 + (1+2.5)^2} \approx 3.2$$

$$\angle K_3 = \theta = 38.7^\circ = \arctan\left(\frac{2}{2.5}\right)$$

$$K_3^* = 2.5 - 2j$$

$$I_{zc}(t) = 21k_3 | e^{-3t} \cos(4t + \theta)$$

$$I_L(t) = I_{Lzs}(t) + I_{Lzc}(t)$$

$$= \underbrace{-2.5 e^{-3t} \sin(4t)}_{\text{transient}} + \underbrace{2 \sin(5t)}_{\text{SSS}} + \underbrace{6.4 e^{-3t} \cos(4t)}_{\text{transient}}$$

↑  
sinusoidal  
steady  
state

zero-state response

zero-input  
response

Let  $V_s(t) = 12 \sin(5t)$

$$V_s(t) = \delta(t) \xrightarrow{\mathcal{L}} V_s(s) = 1$$

Find zero-state response due to this input

$$I_{Lzs}(s) = \frac{V_s * s}{(s+3)^2 + 4^2} = \frac{s}{(s+3)^2 + 4^2}$$

$$= \frac{K_1}{s+3-4j} + \frac{K_1^*}{s+3+4j}$$

$$(s+3+4j) \quad (s+3-4j)$$

$$s = K_1(s+3+4j) + K_1^*(s+3-4j)$$

$$s = (K_1 + K_1^*)s \quad 0 = K_1(3+4j) + K_1^*(3-4j)$$

$$K_1 = a + bj$$

$$s = (a + bj + a - bj) s \Rightarrow 2a = 1 \Rightarrow a = \frac{1}{2} = \frac{4}{8}$$

$$0 = (a + bj)(3 + 4j) + (a - bj)(3 - 4j)$$

$$0 = 3a - 4b + \cancel{3bj} + \cancel{4aj} + 3a - 4b - \cancel{4aj} - \cancel{3bj}$$

$$0 = 6a - 8b \Rightarrow b = \frac{3}{8}$$

$$K = \frac{4}{8} + \frac{3}{8}j$$

$$|K| = \frac{5}{8} \quad \angle K = \arctan \frac{3/8}{4/8} = \theta = 36.87^\circ$$

$$\frac{I_{L25}(t)}{25} = 2|K| e^{-3t} \cos(4t + \theta)$$

$$\frac{I_{L25}(t)}{25} = \frac{2 \times 5}{8} e^{-3t} \cos(4t + 36.87^\circ)$$

↑  
zero-state  
response

Zero-State Response (Network Function)  
for the previous question

$$I_{L25} = \frac{V_s(s) \cdot s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\frac{I_{L25}(s)}{V_s(s)} = \frac{s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

\* No initial condition (all initial conditions are zero)

\* The relation between input ( $V_s(s)$ ) and output ( $I_{L_{25}}(s)$ )

### Network function (Transfer function):

The relation between input and output when the initial conditions are all 0.

$$Y(s) = H(s) U(s)$$

↑                    ↑                    ↑  
 output            transfer          input  
                     function


$$H(s) = \frac{Y(s)}{U(s)}$$

$\mathcal{L}^{-1} \swarrow$

$h(t)$

impulse response

$$u(t) = \delta(t)$$

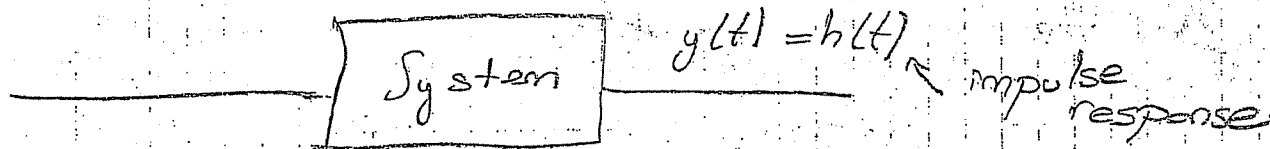

$$h(t) \xrightarrow{\mathcal{L}} H(s)$$

Observations:

① For LTI networks, zero-state (z.s.) response is obtained by convolution.

$$y(t) = \int_{0^-}^{\infty} h(t-\tau) u(\tau) d\tau \quad t \geq 0$$

↑  
output  
(zero-state)

②  $Y(s) = H(s)U(s)$

↑  
zero-state  
response

Convolution Theorem:


$$\int_{0^-}^{\infty} f_1(t-\tau) f_2(\tau) d\tau = \int_{0^-}^{\infty} f_2(\tau) f_1(t-\tau) d\tau = f_3(t)$$

$$\mathcal{L} \rightarrow F_3(s) = F_1(s)F_2(s)$$

For circuit analysis in Laplace Domain:

KVL, KCL; node-mesh analysis; source conversions, dependent, independent sources

RLC elements in s-domain:

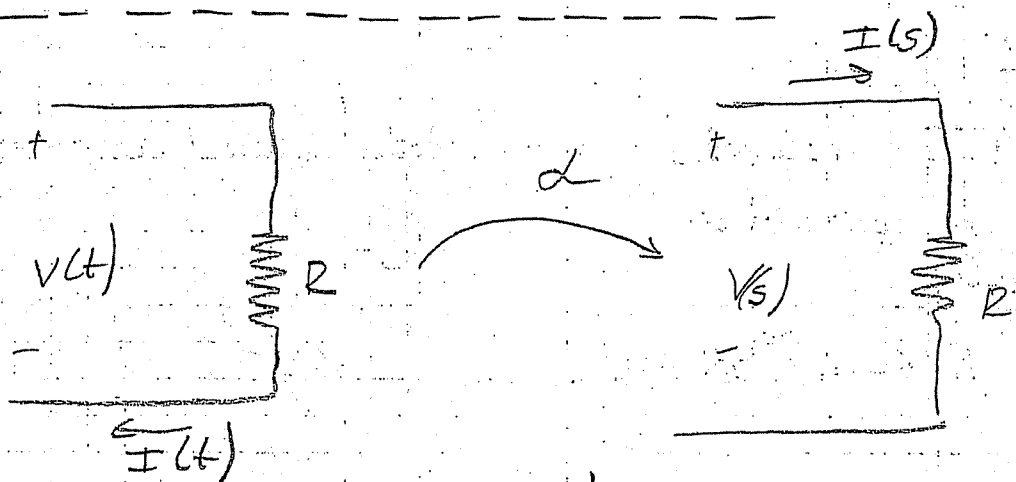


$$I(t) = C \frac{dV(t)}{dt}$$

$$I(s) = C [sV(s) - V(0^-)]$$

$$V(s) = \frac{I(s)}{sC} + \frac{V(0^-)}{s}$$

$$V(t) = R I(t)$$

$$V(s) = R I(s)$$

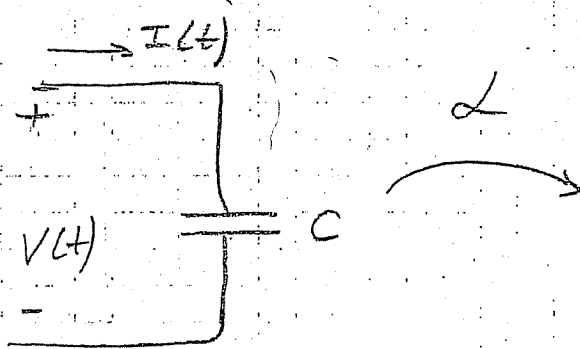




$$I(t) = C \frac{dV(t)}{dt}$$

$$I(s) = C [sV(s) - V(0^-)]$$

↑  
initial condition

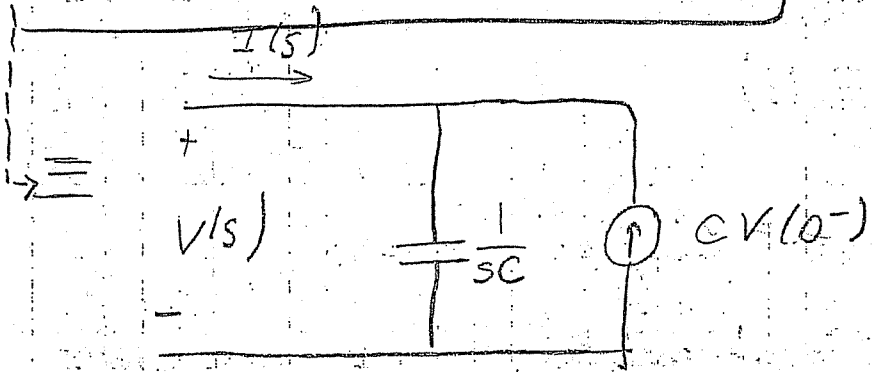
$$V(s) = I(s) \frac{1}{sC} + \frac{V(0^-)}{s}$$



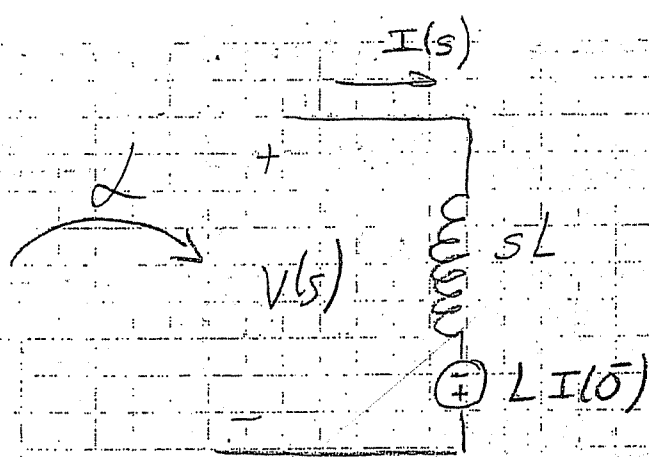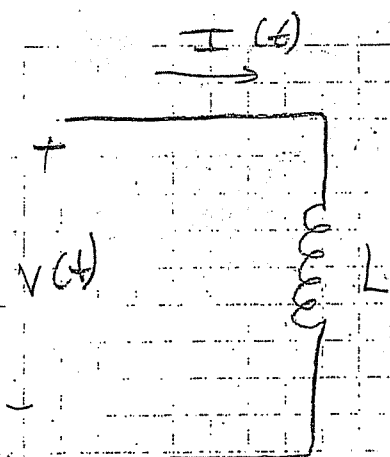


$$L \frac{dI}{dt} = V(t)$$

$$L [s I(s) - I(0^-)]$$

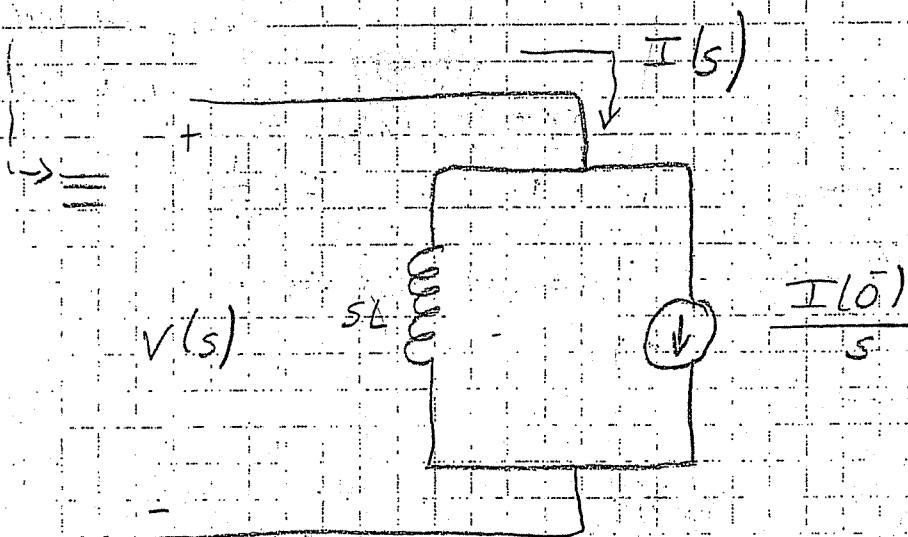

$$I(s) = \frac{V(s)}{sL} + \frac{I(0^-)}{s}$$

Impedance and Admittance:

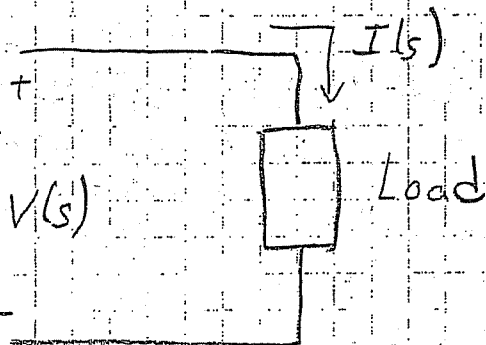

$$Z(s) = \frac{V(s)}{I(s)}$$

↑ impedance

zero initial condition  
(zero-state)



$R \longrightarrow Z(s) = R \longrightarrow Y(s) = \frac{1}{R}$

$L \longrightarrow Z(s) = sL \longrightarrow Y(s) = \frac{1}{sL}$

$C \longrightarrow Z(s) = \frac{1}{sC} \longrightarrow Y(s) = sC$


$Y(s) = \text{Admittance} = \frac{1}{Z(s)}$

$I_s = \frac{V(s)}{sL} + \frac{I(0)}{s}$

$V_s = \frac{I_s}{C \cdot s} + \frac{V(0)}{s}$

Voltage division, current division, series parallel connections

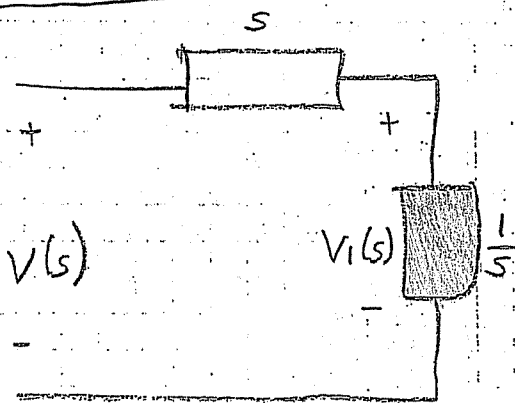(similar to time domain resistive circuits)



$V_1(s) = V(s) \frac{s}{s + \frac{1}{s}}$


$Z_{\text{Total}} = \frac{1}{s} + s$

$\frac{1/s}{s + 1/s}$

Ex:

$V_1(s) = A$

$B = V_2(s)$

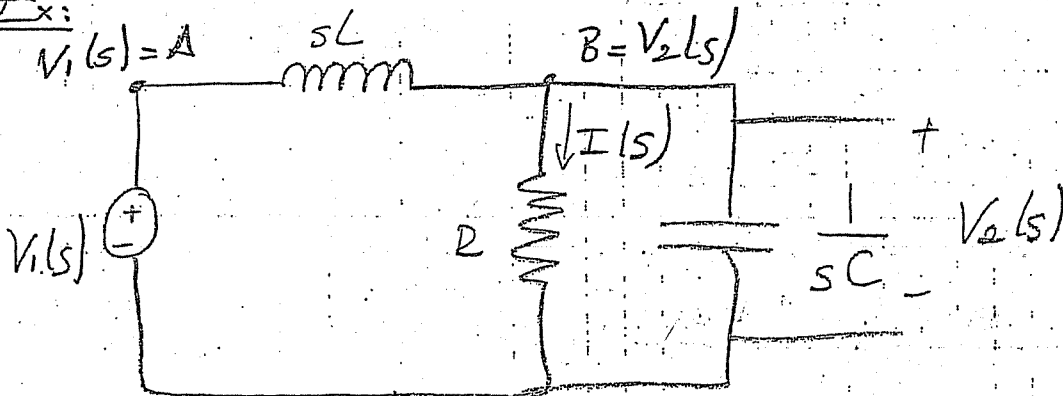

Find

$H(s) = \frac{V_2(s)}{V_1(s)}$

transfer function

$H_2(s) = \frac{I(s)}{V_1(s)}$

(another transfer function)


$$\frac{V_1(s) - V_2(s)}{sL} = \frac{V_2(s)}{R} + \frac{V_2(s)}{sC}$$

$$\frac{V_1(s)}{sL} = \frac{V_2(s)}{sL} + \frac{V_2(s)}{R} + sC V_2(s)$$

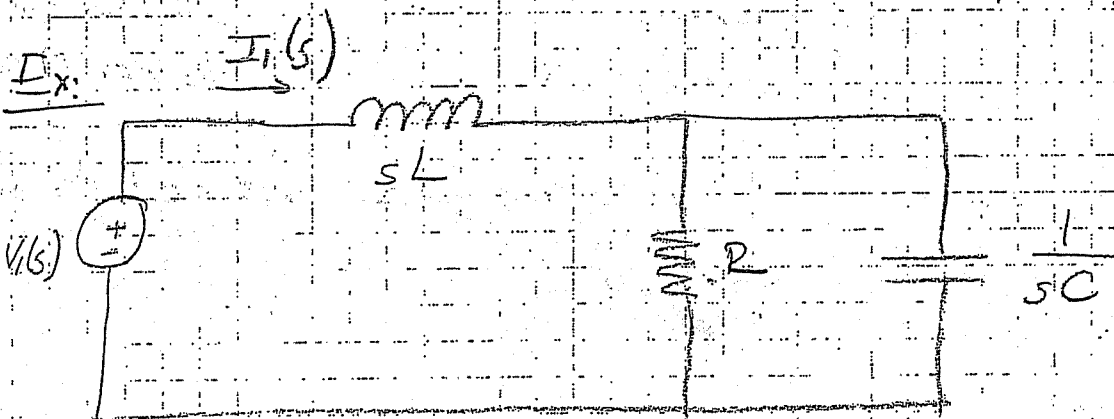(D)            (D)            (sL)            (R sL)

$$R V_1(s) = (R + sL + s^2 RLC) V_2(s)$$

$$\frac{V_2(s)}{V_1(s)} = H(s) = \frac{R}{R + sL + s^2 RLC} = \frac{1/RC}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$




$$Z_i = \frac{V_1(s)}{I_1(s)} = sL + \left( \frac{1}{sC} \parallel R \right)$$

↑  
input impedance

$$sL + \frac{\frac{1}{sC} \cdot R}{\frac{1}{sC} + R} = Z_i(s) = sL + \frac{R}{R + sRC}$$

Superposition:

Ex:

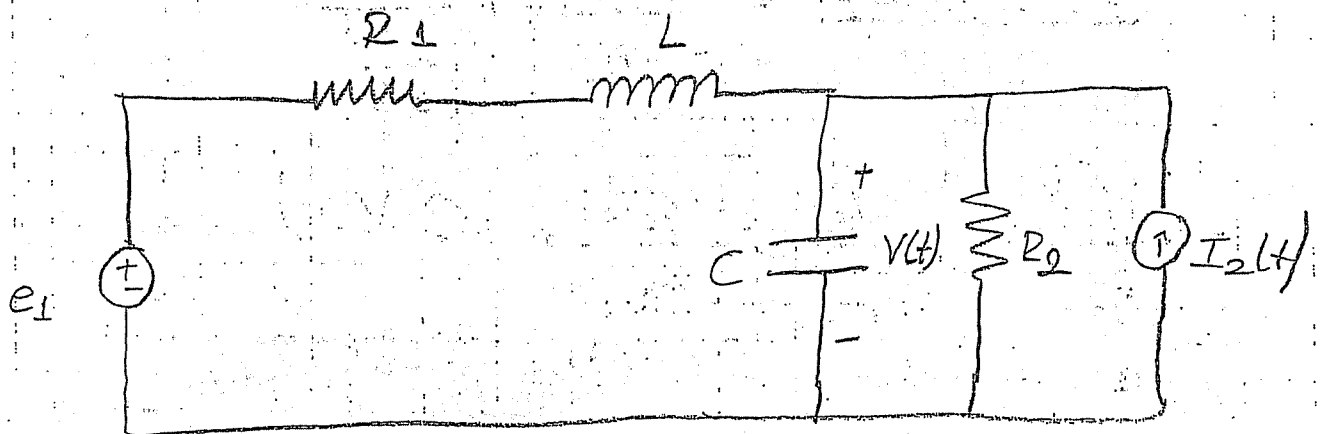

$$V(s) = H_1(s) E_1(s) + H_2(s) I_2(s)$$

$$H_1(s) = \frac{V(s)}{E_1(s)}$$

$$H_2(s) = \frac{V(s)}{I_2(s)}$$

$$I_2(s) = 0$$


↳ open circuit

$$E_1(s) = 0$$

↳ short circuit

in this question initial conditions are assumed to be equal to 0.

For  $H_1(s)$

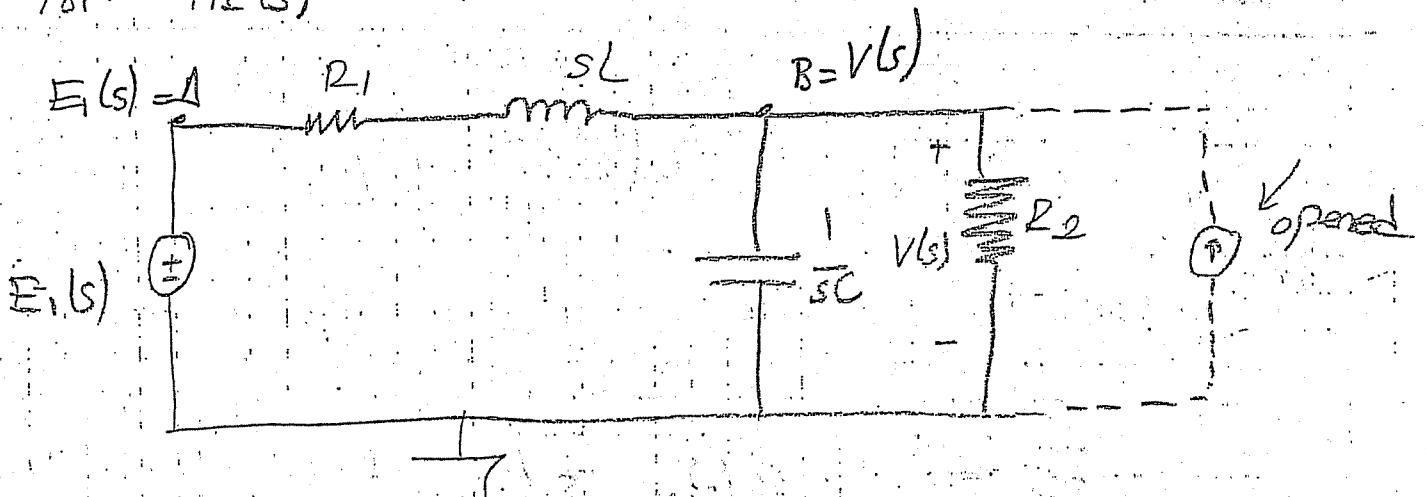

$$E_1(s) = V(s) = R_1 s C V(s) + V(s) + U_s$$

$$E_1(s) = (2 + R_1 s C) \frac{V(s)}{E_1(s)}$$


$$\frac{E_1(s) - V(s)}{R_1 + sL} = \frac{V(s)}{\frac{1}{sC}} + \frac{V(s)}{R_2} \quad \text{with } E_1(s)$$

$$H_1(s) = \frac{V(s)}{E_1(s)} = \frac{1}{1 + (R_1 + sL) \left( \frac{1}{R_2} + sC \right)}$$

$I_2(s) = 0$

$$L + \frac{R_1 + sL}{R_2} + \frac{R_1 s C L}{R_2}$$

For  $H_2$ :

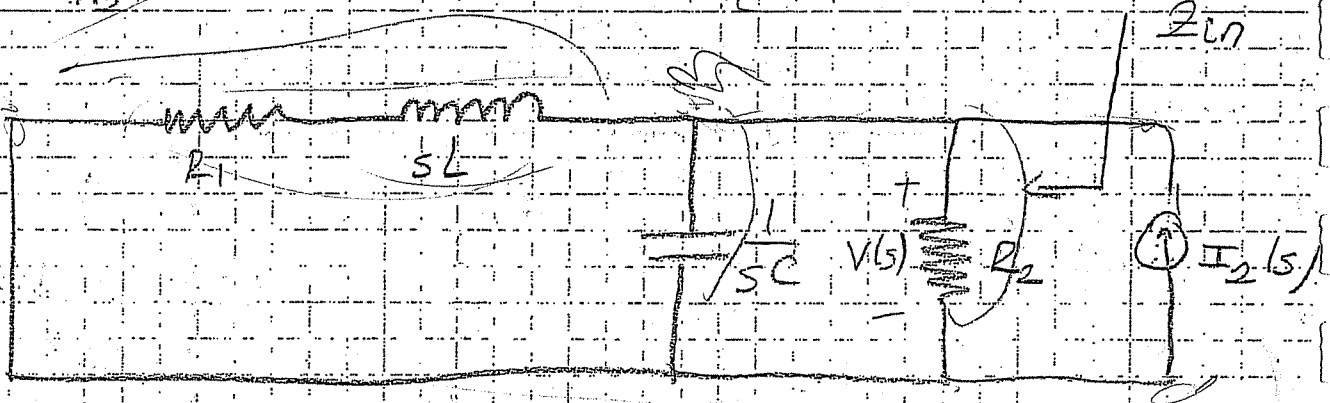

$$V(s) = I(s) Z_{in}(s)$$

$$Z_{in}(s) = \frac{V(s)}{I(s)} = H_2(s)$$

$$\frac{1}{Z_{in}(s)} = \frac{1}{R_1 + sL} + \frac{1}{\frac{1}{sC}} + \frac{1}{R_2}$$

$$\frac{1}{Z_{in}(s)} = \frac{1}{R_2} + \frac{1}{(R_1 + sL)R_2}$$

$$Z_{in}(s) = \frac{R_2 + sC(R_1 + sL)R_2 + R_1 + sL}{R_2(R_1 + sL)}$$

$$Z_{in}(s) = \frac{R_1 R_2 + sL R_2}{s^2 C L R_2 + s(C R_1 R_2 + L) + R_1 + R_2}$$


Phasor domain is used for a specific frequency whereas Laplace domain is used for all frequencies

For s-domain analysis: superposition theorem to find the response as the sum of


- (a) zero-input response (all inputs are turned off)
- (b) zero-state response (all initial conditions are assumed to be equal to 0)

$$Y(s) = Y_{zi}(s) + Y_{zs}(s)$$

Ex:

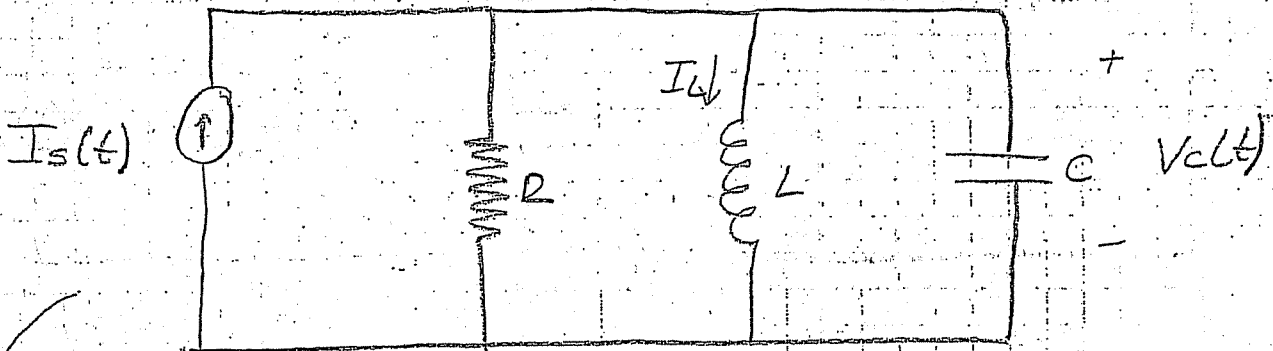

$V_C(0^-) = V_0$      $I_L(0^-) = I_0$

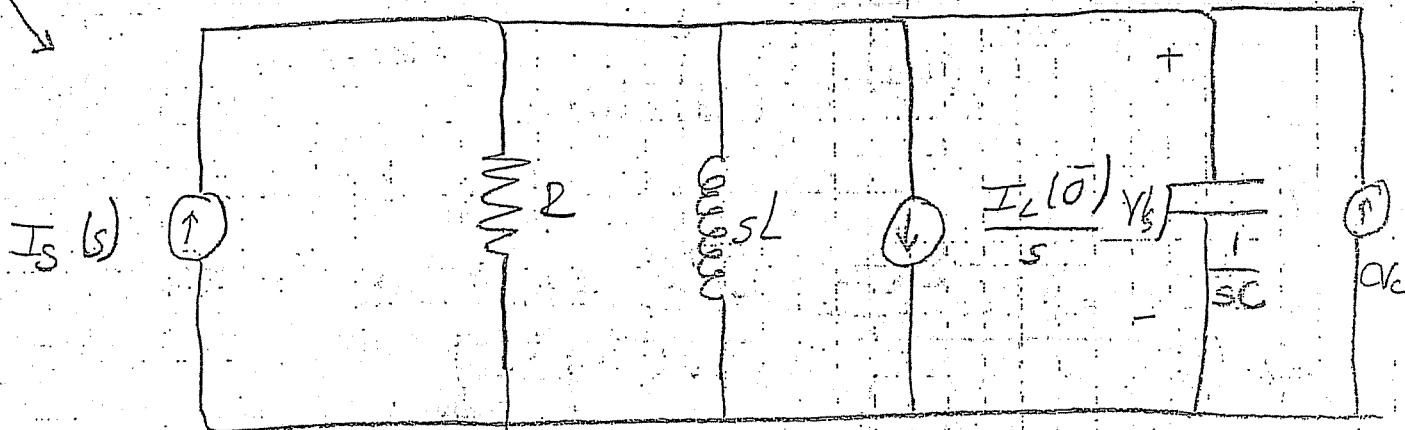

Model for inductor

model for capacitor


$V(s)$  can be written as the superposition of these 3 sources (2 of them obtained from initial conditions, 1 of them obtained from real source  $I_s(s)$ )

$\int_0$

$$V(s) = V_{ss}(s) + V_{ci}(s)$$


$\uparrow$  due to  $I_s(s)$ 
 $\uparrow$  due to  $I_L(0^-)$  and  $V_C(0^-)$

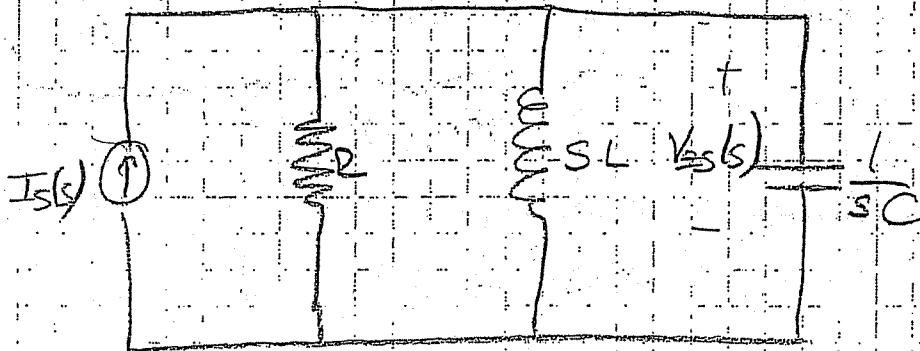For  $V_{ss}(s)$ : (turn off sources due to initial conditions)



$$V_{ss}(s) = \frac{sRL}{s^2LRC + sL + R} I_s(s)$$

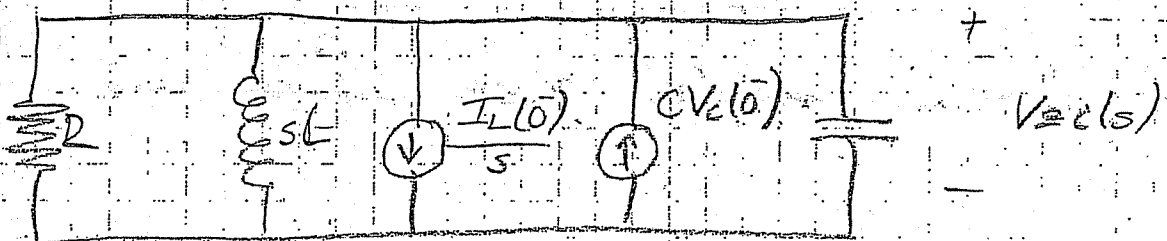For  $V_{ci}(s)$ : (turn of the real source)



$$V_{z1}(s) = \frac{-RLs}{s^2RLC + sL + R} \underbrace{\frac{I_L(0)}{s}}_{\text{source due to initial condition}}$$


$$V_{z2}(s) = \frac{RLs}{s^2RLC + sL + R} \underbrace{C V_C(0)}_{\text{due to second initial condition}}$$

$$V_{\text{total}}(s) = V_{zs}(s) + V_{z1}(s) + V_{z2}(s)$$

$$= \underbrace{\frac{RLs I(s)}{s^2 + RLC + sL + R}}_{\text{zero-state}} + \underbrace{\frac{RLs}{s^2RLC + sL + R} \left( C V_C(0) - \frac{I_L(0)}{s} \right)}_{\text{zero-input}}$$


Thevenin - norton valid in Laplace

Ex:

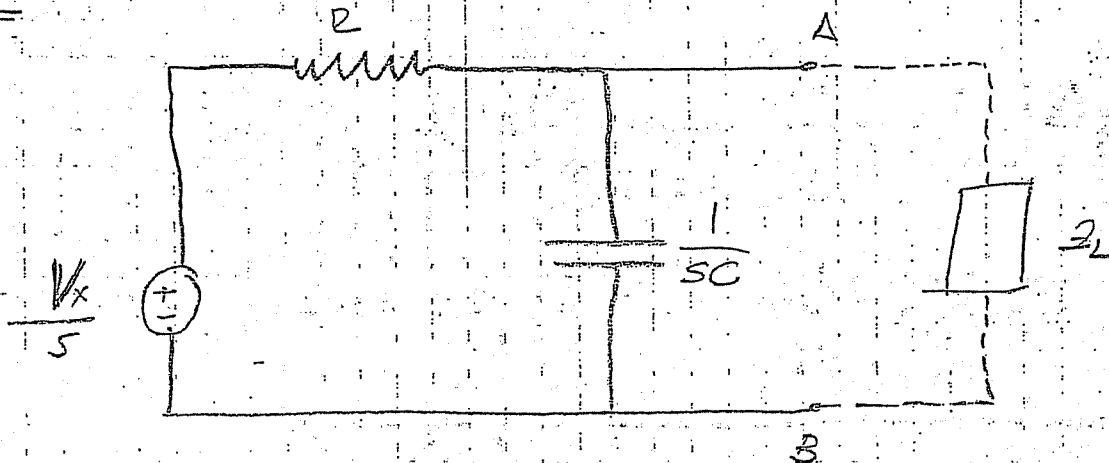

Find thevenin equivalent circuit between A-B

For  $Z_{TH}$

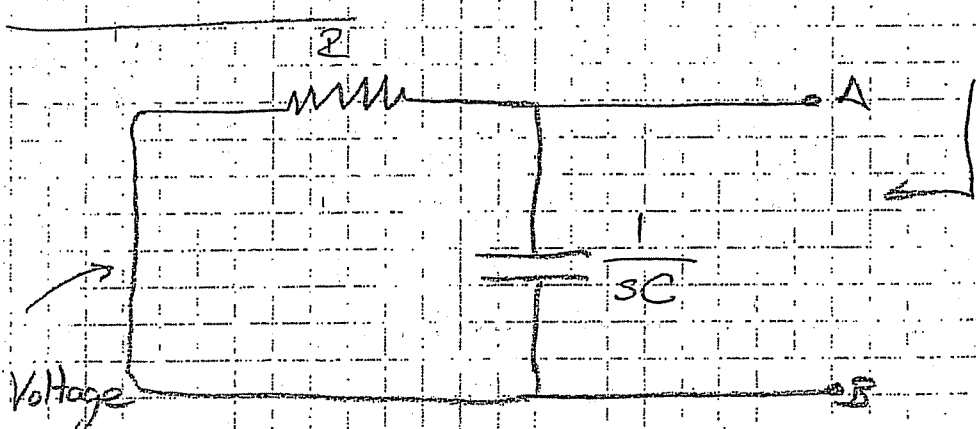


$$Z_{TH} = \frac{R \times \frac{1}{sC}}{R + \frac{1}{sC}}$$


$$Z_{TH} = \frac{R}{sRC + 1}$$

Voltage source is shorted

For  $V_{TH}$

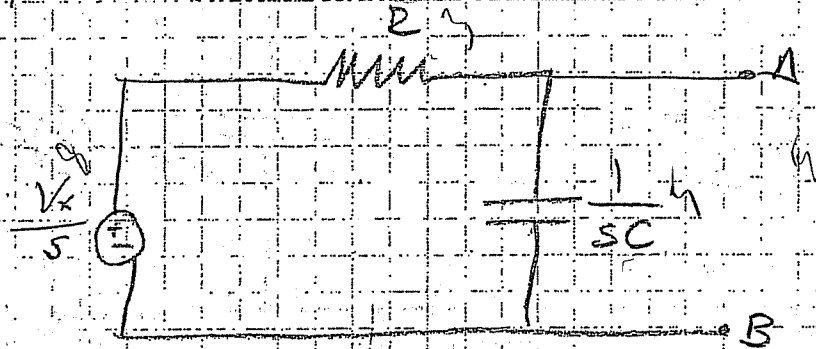

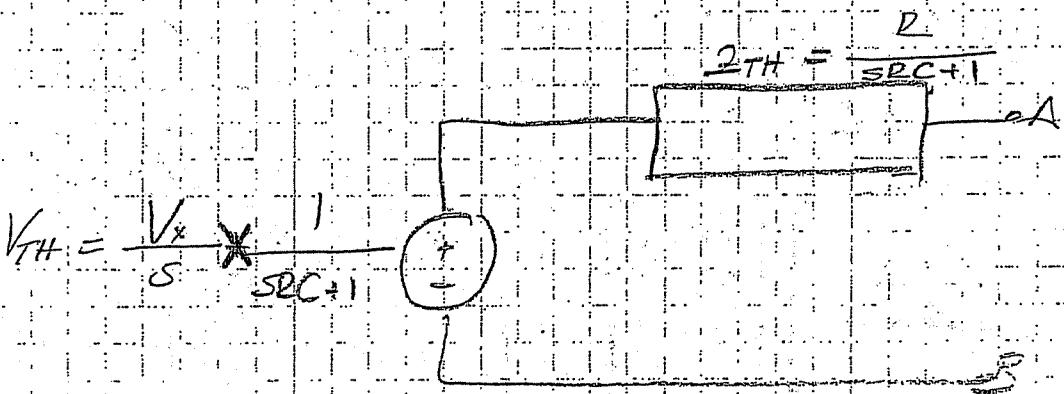
$$V_{AB} = V_{TH} = \frac{V_x}{s} \times \frac{1/sC}{R + 1/sC} \Rightarrow V_{TH} = \frac{V_x}{s} \times \frac{1}{sRC + 1}$$



Thevenin equivalent circuit.




Ex:

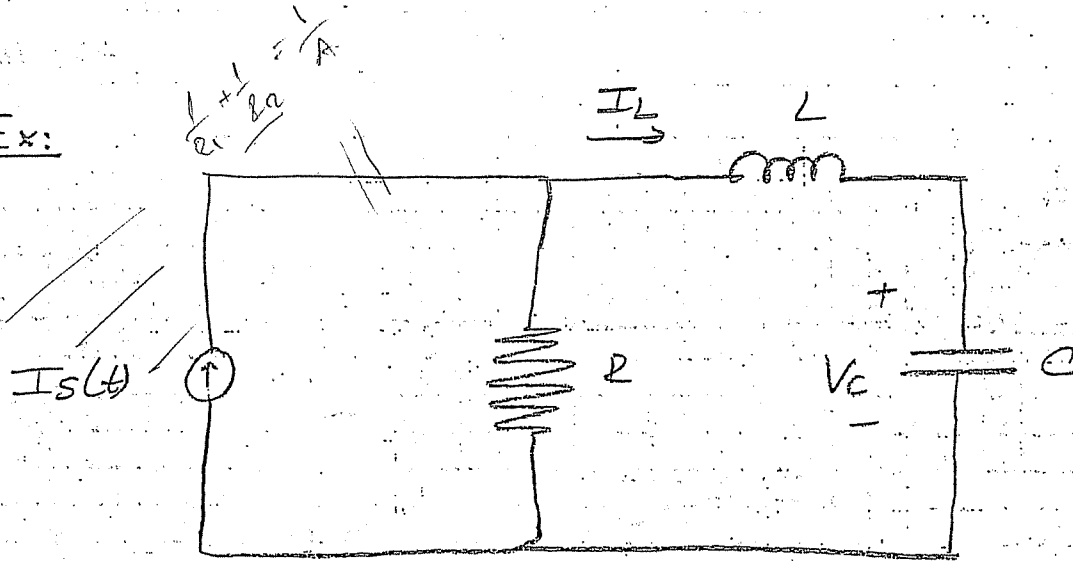

$$I_L(0^-) = I_0$$

$$V_C(0^-) = V_0$$

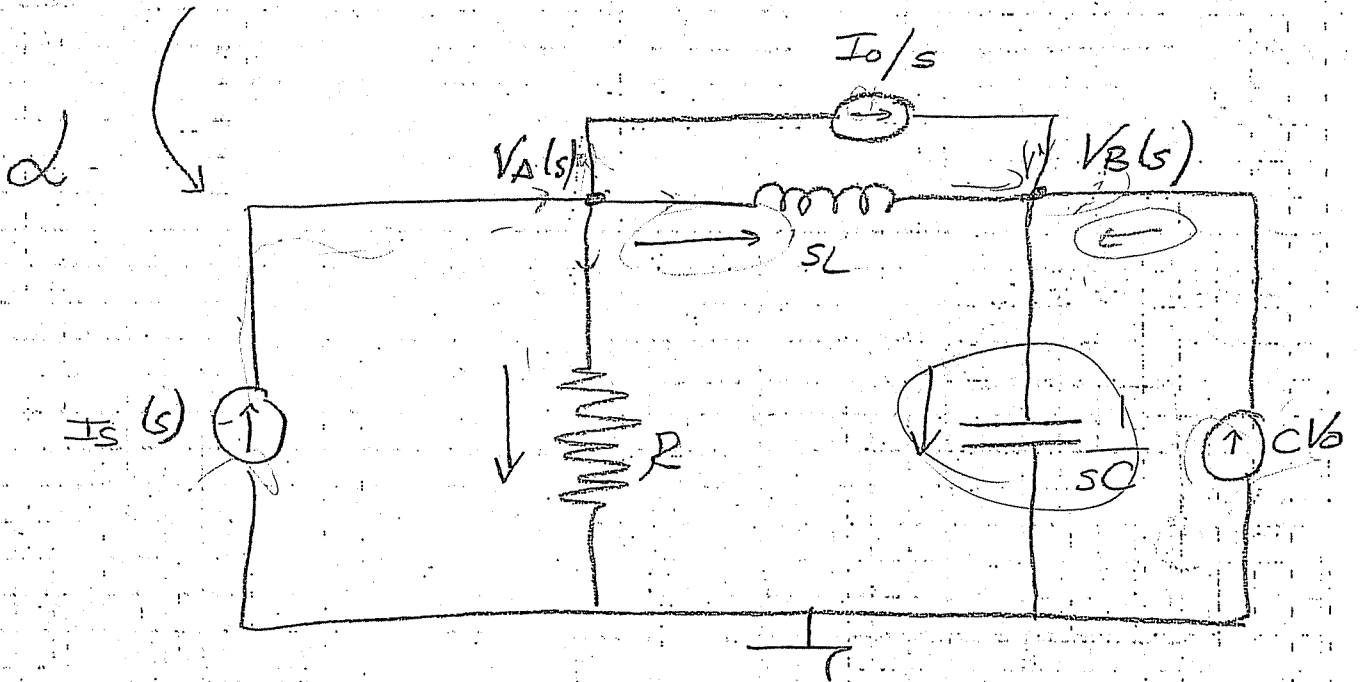

Node A:

$$I_s(s) = \frac{V_A(s)}{R} + \frac{V_A(s) - V_B(s)}{sL} + \frac{I_0}{s}$$

Node B:

$$\frac{V_A(s) - V_B(s)}{sL} + \frac{I_0}{s} + CV_0 = \frac{V_B(s)}{\frac{1}{sC}}$$

$$\begin{bmatrix} \frac{1}{R} + \frac{1}{sL} & -\frac{1}{sL} \\ -\frac{1}{sL} & sC + \frac{1}{sL} \end{bmatrix} \begin{bmatrix} V_A(s) \\ V_B(s) \end{bmatrix} = \begin{bmatrix} I_s(s) - \frac{I_0}{s} \\ \frac{I_0}{s} + CV_0 \end{bmatrix}$$

$$\begin{bmatrix} V_A(s) \\ V_B(s) \end{bmatrix} = K^{-1} M$$

Notes:

$$X = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

$$X^{-1} = \frac{1}{ad - bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

$$X^{-1} = \frac{\text{adj}(X)}{\det(X)}$$

$$X = \begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix}$$

$$(-1)^{1+1} \begin{vmatrix} e & f \\ h & i \end{vmatrix}$$

$$(-1)^{1+2} \begin{vmatrix} d & f \\ g & i \end{vmatrix}$$

$$(-1)^{1+3} \begin{vmatrix} d & e \\ g & h \end{vmatrix}$$

$$(-1)^{2+1} \begin{vmatrix} b & c \\ h & i \end{vmatrix}$$

$$(-1)^{2+2} \begin{vmatrix} a & c \\ g & i \end{vmatrix}$$

$$(-1)^{2+3} \begin{vmatrix} a & b \\ c & h \end{vmatrix}$$

$$(-1)^{3+1} \begin{vmatrix} b & c \\ e & f \end{vmatrix}$$

$$(-1)^{3+2} \begin{vmatrix} a & c \\ d & f \end{vmatrix}$$

$$(-1)^{3+3} \begin{vmatrix} a & b \\ d & e \end{vmatrix}$$

$X^{-1} =$

$\det(X)$

$$K^{-1} = \frac{\begin{bmatrix} sC + \frac{1}{sL} & \frac{1}{sL} \\ \frac{1}{sL} & \frac{1}{R} + \frac{1}{sL} \end{bmatrix}}{\left(\frac{1}{R} + \frac{1}{sL}\right)\left(sC + \frac{1}{sL}\right) - \left(\frac{1}{sL}\right)\left(\frac{1}{sL}\right)}$$

$$K^{-1} = \frac{\begin{bmatrix} sC + \frac{1}{sL} & \frac{1}{sL} \\ \frac{1}{sL} & \frac{1}{R} + \frac{1}{sL} \end{bmatrix}}{\left(\frac{1}{R} + \frac{1}{sL}\right)\left(sC + \frac{1}{sL}\right) - \left(\frac{1}{sL}\right)\left(\frac{1}{sL}\right)}$$

$$\frac{sC}{R} + \frac{1}{s^2 L^2} + \frac{1}{sLR} + \frac{C}{L} - \frac{1}{s^2 L^2}$$

$$V_A = \underbrace{\frac{(LCs^2 + 1) T_s(s)}{\frac{1}{R} LCs^2 + Cs + \frac{1}{R}}}_{\text{zero-state}} + \underbrace{\frac{-LCs I_0 + CV_0}{\frac{1}{R} LCs^2 + Cs + \frac{1}{R}}}_{\text{zero-input}}$$

For zero input response

\* If  $V_0 = 0$ ;  $I_0 = 0$  the  $V_{A_{zi}}(s) = 0 \xrightarrow{\mathcal{L}^{-1}} V_{A_{zi}}(t) = 0$

\* by choosing suitable initial conditions

$$V_{A_{zi}}(s) \frac{\cancel{(s+a)}}{(s+b)(s+a)} = \frac{\cancel{K}}{s+b} \xrightarrow{\mathcal{L}^{-1}} K e^{-bt} u(t)$$

\* Initial conditions can be chosen such that some natural frequencies are not observable at output.

In general:


→ Total response

$$V_x(s) = \frac{\Delta_x(s)}{\Delta(s)}$$

\* The roots of  $\Delta(s)$  are natural poles

\* The poles of  $\Delta_x(s)$  are the forced poles due to input and they create the forced response.

Ex: Switching operation

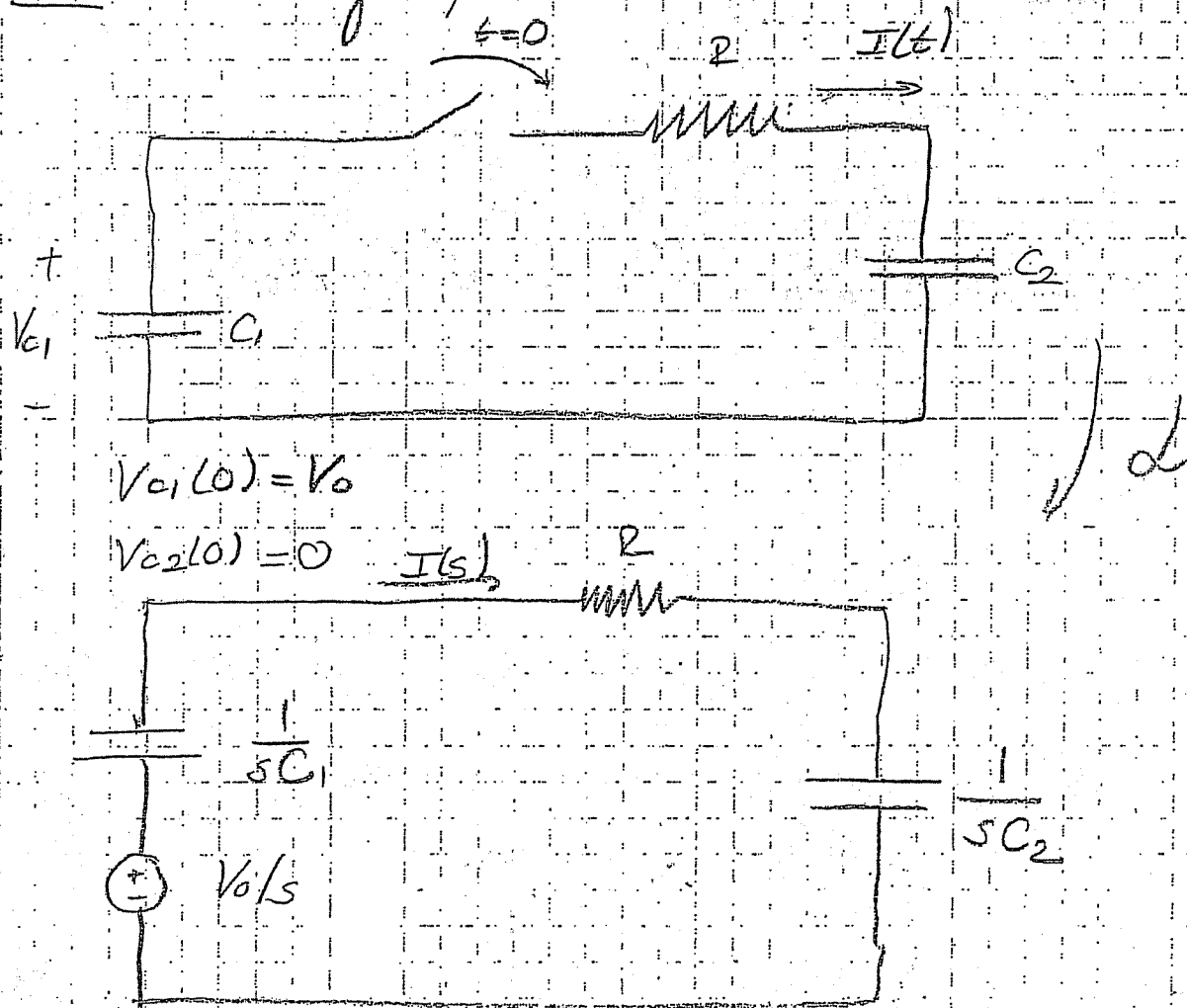

26 03 07

saglikbank  
www.saglikbank.com

Osman Kulog  
Z. Aded

215 44 43 (pbx) Fax: 0 312 215 44 46 e-mail: info@saglikbank.com

$$= \frac{V_0/R}{s + \frac{1}{RC_e}}$$

$$C_e = \frac{C_1 C_2}{C_1 + C_2}$$

$\mathcal{L}^{-1}$


$$I(t) = \frac{V_0}{R} e^{-\frac{t}{RC_e}} u(t)$$

If  $R \rightarrow 0$

$$I(s) = \frac{V_0/s}{s C_1 + \frac{1}{s C_2}} = \frac{V_0}{\frac{C_1 C_2}{C_1 + C_2}}$$

$\mathcal{L}^{-1}$
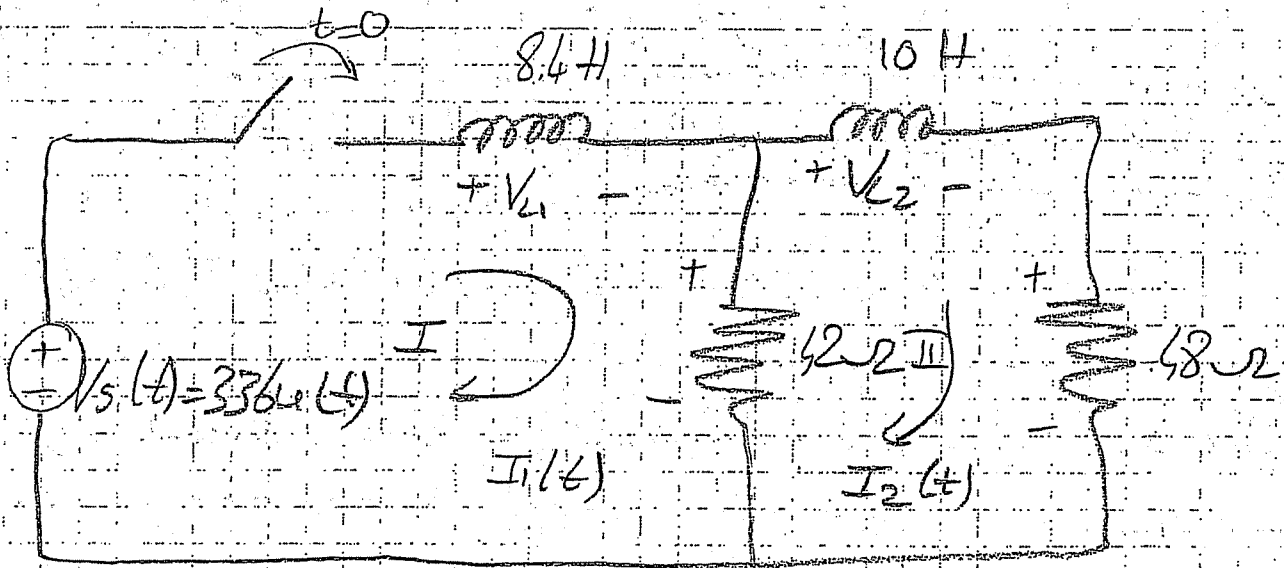
$$I(t) = \frac{V_0 \cdot C_1 + C_2}{C_1 \cdot C_2} f(t) = V_0 C_e f(t)$$



$$I_1(t) = ? \quad I_2(t) = ?$$

Mesh I

$$-v_s(t) + v_{L1} + v_{42\Omega} = 0$$

$$-v_s(t) + L_1 \frac{dI_1(t)}{dt} + 42(I_1(t) - I_2(t)) = 0$$

$$\downarrow \quad \downarrow \quad \uparrow$$

$$-v_s(s) + L_1 [sI_1(s) - I_1(0^-)] + 42[I_1(s) - I_2(s)] = 0$$

$8.4 \text{ H}$

Mesh II

$$v_{L2} + v_{48\Omega} - v_{42\Omega} = 0$$

$$L_2 \frac{dI_2}{dt} + 48I_2 + 42(I_2 - I_1) = 0$$

$$\downarrow \quad \uparrow$$

$$L_2 [sI_2(s) - I_2(0^-)] + 48I_2(s) + 42(I_2(s) - I_1(s)) = 0$$

$10 \text{ H}$

$$10s I_2(s) - 10 I_2(0^-) + 48 I_2(s) + 42 I_2(s) - 42 I_1(s) = 0$$

$$\boxed{(90 + 10s) I_2(s) - 42 I_1(s) = 10 I_2(0^-)}$$

$$-V_s(s) + 8.4s I_1(s) - 8.4 I_1(0^-) + 42 I_1(s) - 42 I_2(s) =$$

$$\boxed{(8.4s + 42) I_1(s) - 42 I_2(s) = V_s(s) + 8.4 I_1(0^-)}$$

$$\underbrace{\begin{bmatrix} 8.4s + 42 & -42 \\ -42 & 90 + 10s \end{bmatrix}}_A \underbrace{\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}}_X = \underbrace{\begin{bmatrix} V_s(s) + 8.4 I_1(0^-) \\ 10 I_2(0^-) \end{bmatrix}}_B$$

$$X = A^{-1} B$$

$$A^{-1} = \frac{\text{adj}(A)}{\det(A)} = \frac{\begin{bmatrix} 90 + 10s & 42 \\ 42 & 8.4s + 42 \end{bmatrix}}{(8.4s + 42)(90 + 10s) - (-42)(-42)}$$

$$A^{-1} = \frac{\begin{bmatrix} 90 + 10s & 42 \\ 42 & 8.4s + 42 \end{bmatrix}}{84s^2 + (420s - 756s) - 4320}$$

$$X = \frac{\begin{bmatrix} 90 + 10s & 42 \\ 42 & 8.4s + 42 \end{bmatrix}}{84s^2 + 1176s - 4320} \begin{bmatrix} V_s(s) + 8.4 I_1(0^-) \\ 10 I_2(0^-) \end{bmatrix}$$

of the ...

...

...

...

...

...

...

...

...

...

...

...

...

...

...

...



$$10s I_2(s) - 10 I_2(0^-) + 48 I_2(s) + 42 I_2(s) - 42 I_1(s) = 0$$

$$(90 + 10s) I_2(s) - 42 I_1(s) = 10 I_2(0^-)$$

$$-V_s(s) + 8.4s I_1(s) - 8.4 I_1(0^-) + 42 I_1(s) - 42 I_2(s) = 0$$

$$(8.4s + 42) I_1(s) - 42 I_2(s) = V_s(s) + 8.4 I_1(0^-)$$


$$\underbrace{\begin{bmatrix} 8.4s + 42 & -42 \\ -42 & 90 + 10s \end{bmatrix}}_A \underbrace{\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}}_X = \underbrace{\begin{bmatrix} V_s(s) + 8.4 I_1(0^-) \\ 10 I_2(0^-) \end{bmatrix}}_B$$

$$X = A^{-1} B$$

$$A^{-1} = \frac{\text{adj}(A)}{\det(A)} = \frac{\begin{bmatrix} 90 + 10s & 42 \\ 42 & 8.4s + 42 \end{bmatrix}}{(8.4s + 42)(90 + 10s) - (-42)(-42)}$$

$$A^{-1} = \frac{\begin{bmatrix} 90 + 10s & 42 \\ 42 & 8.4s + 42 \end{bmatrix}}{84s^2 + (420s - 756s) - 4320}$$
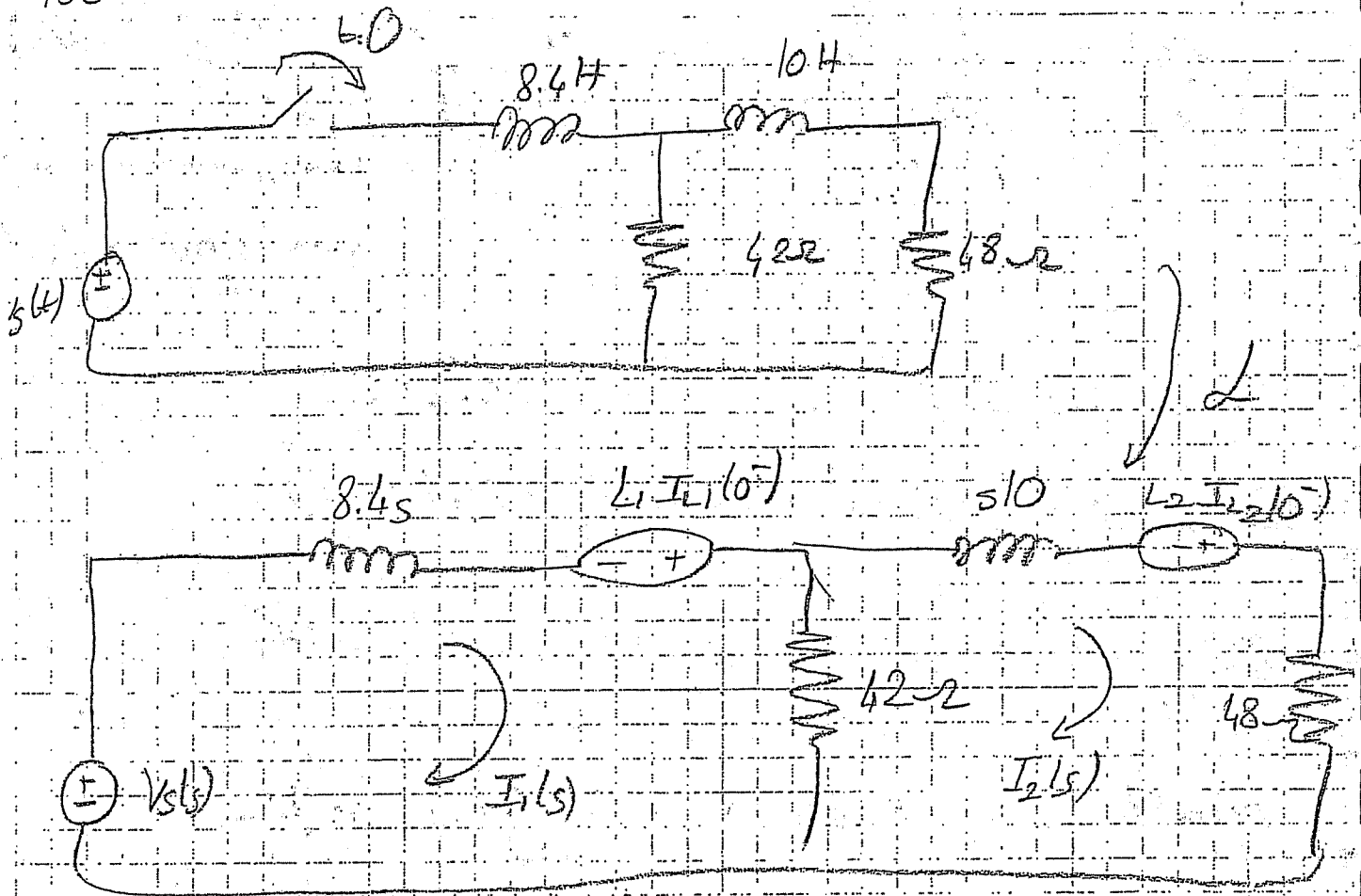
$$X = \frac{\begin{bmatrix} 90 + 10s & 42 \\ 42 & 8.4s + 42 \end{bmatrix}}{84s^2 + 1176s - 4320} \begin{bmatrix} V_s(s) + 8.4 I_1(0^-) \\ 10 I_2(0^-) \end{bmatrix}$$



$$I_{L1}(0^-) = I_1(0^-)$$

$$I_{L2}(0^-) = I_2(0^-)$$

$$-V_s(s) + (8.4s)I_1(s) - L_1 I_1(0^-) + 42(I_1(s) - I_2(s)) = 0$$

$$510 I_2(s) - L_2 I_2(0^-) + 42(I_2(s) - I_1(s)) + 48 I_2(s) = 0$$

$$I_1(s) = \frac{(510 + 90)V_s(s)}{84(s+2)(s+12)} + \frac{84(s+9)I_1(0^-) + 42I_2(0^-)}{84(s+2)(s+12)}$$

Find any initial condition such that only one mode (either  $s = -2$  or  $s = -12$ ) is excited at the output of zero input response.

$$I_1(0^-) = k I_2(0^-)$$

$$\frac{N(s)}{D(s)} = \frac{M(s+12)}{84(s+2)(s+2)} = \frac{M}{84(s+2)} \xrightarrow{\mathcal{L}^{-1}} \frac{M}{84} e^{-2t} u(t)$$

zero input output

$$84(s+9)I_1(\bar{0}) + 42I_2(\bar{0}) = M(s+12)$$

$$42 \left[ 2s + 18I_1(\bar{0}) + I_2(\bar{0}) \right] = M(s+12)$$

$$84 \left[ s + 9I_1(\bar{0}) + \frac{I_2(\bar{0})}{2} \right] = M(s+12)$$

$$M=84 \quad s + 9I_1(\bar{0}) + \frac{I_2(\bar{0})}{2} = s+12$$

$$9I_1(\bar{0}) + \frac{I_2(\bar{0})}{2} = 12$$

$$I_1(\bar{0}) = 0 \Rightarrow I_2(\bar{0}) = 24$$

$$I_1(\bar{0}) = 0 \quad I_2(\bar{0}) = 0 \quad \text{but } V_s(t) \neq 336 u(t)$$

$$V_s(t) = \sin(3t) \xrightarrow{\mathcal{L}} \frac{3}{s^2+9}$$

$$I_{2-s}(s) = \frac{(10s+90)V_s(s)}{84(s+2)(s+12)}$$

$$= \frac{10(s+9)}{(s+2)(s+12)(s^2+9) \cdot 84} = \frac{s+9}{(s+2)(s+12)(s^2+9) \cdot 14}$$

$$\mathcal{L}^{-1} = \frac{A}{s+2} + \frac{B}{s+12} + \frac{C}{s-3i} + \frac{C^*}{s+3i}$$


$$A e^{-2t} u(t) + B e^{-12t} u(t) + \frac{210}{1} \cos(3t + \theta) u(t)$$

transient part

SSS


$$\theta = \angle C$$

Ex:

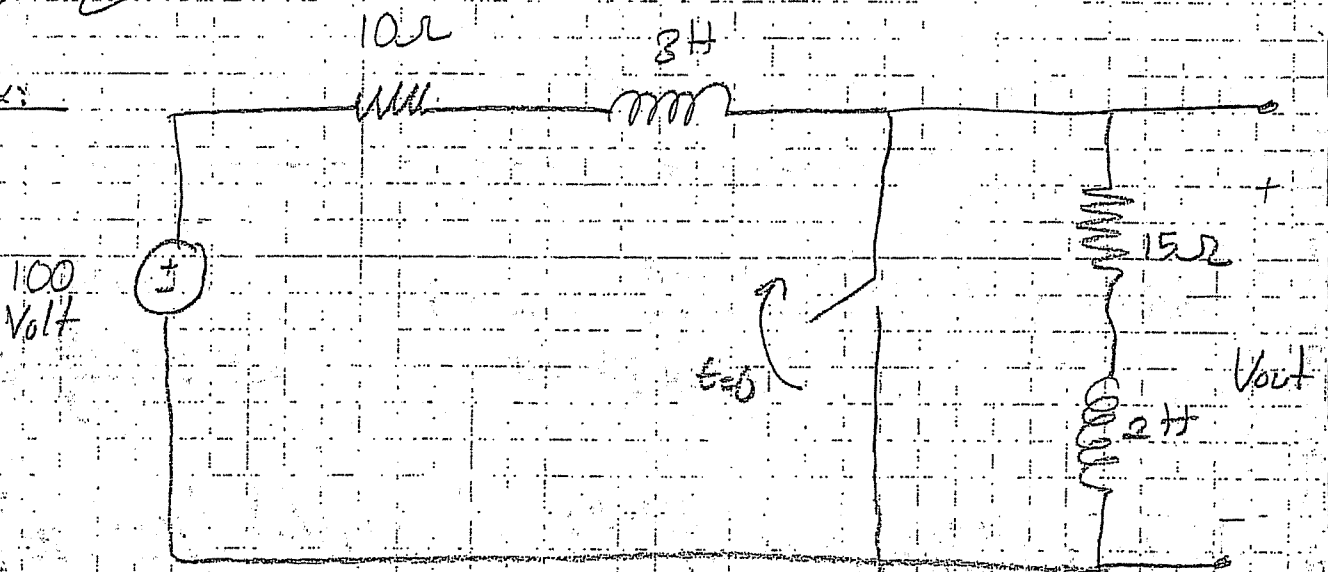

Find  $V_{out} \Rightarrow 0$


$t < 0$

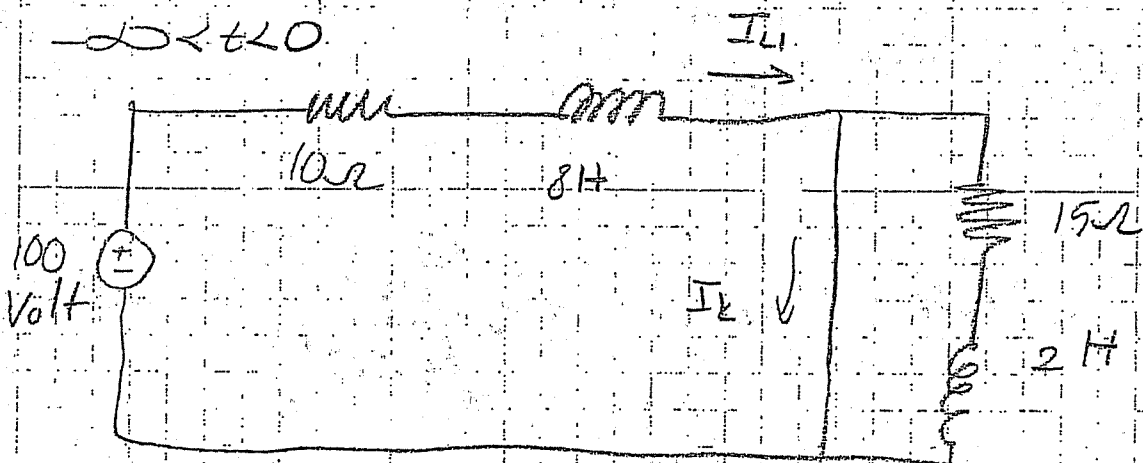

$$I_2(0^-) = 0$$

$$I_1(0^-) = I_2(0^-)$$

$$I_1(0^-) = \frac{100}{10} = 10A$$

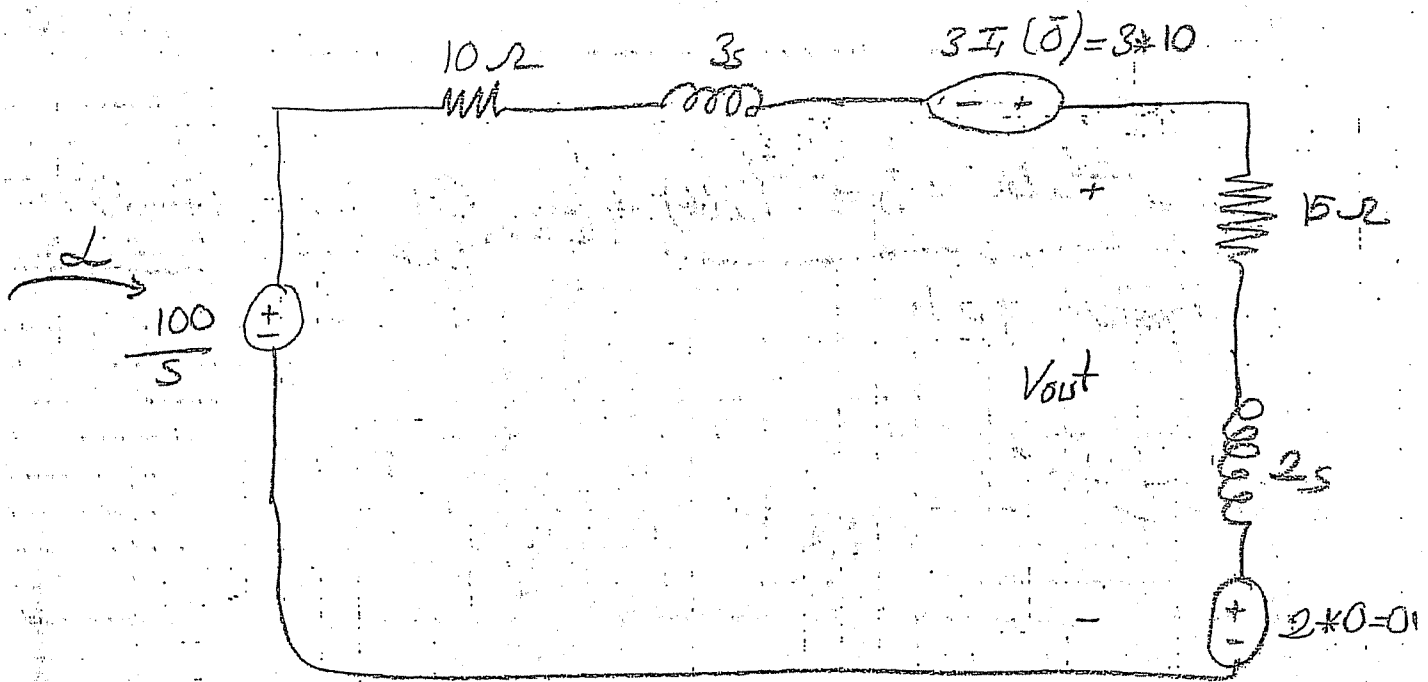

$$V_{out} = \left( \frac{100}{s} + 30 \right) \frac{15 + 2s}{15 + 2s + 10 + 3s} \Rightarrow \begin{array}{r|l} 2s + 15 & 5s + 25 \\ -2s + 10 & 2 \\ \hline & 5 \end{array} \frac{2}{5}$$

$$V_{out}(s) = \left( \frac{100}{s} + 30 \right) \frac{15 + 2s}{25 + 5s} \quad V_{out}(s) = \left( \frac{100}{s} + 30 \right) \left( \frac{2}{5} + \frac{5}{5s+25} \right)$$


$$V_{out}(s) = \frac{40}{s} + 12 - \frac{100}{s(s+5)}$$

$\mathcal{L}^{-1} \downarrow$

$$V_{out}(t) = 40u(t) + 12\delta(t) - \mathcal{L}^{-1} \left\{ \frac{100}{s(s+5)} \right\} = \frac{k_1}{s} + \frac{k_2}{s+5}$$

$$100 = k_1(s+5) + sk_2 \quad k_1 = 20 \quad \text{and} \quad k_2 = -20$$
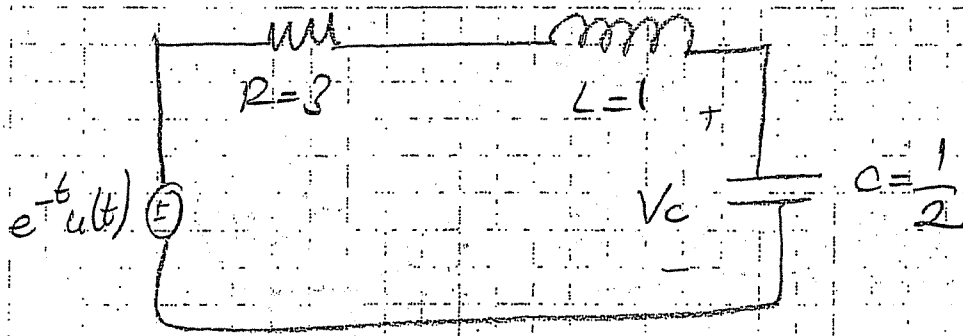
$$40u(t) + 12\delta(t) - \mathcal{L}^{-1} \left\{ \frac{20}{s} + \frac{-20}{s+5} \right\} = 60u(t) + 12\delta(t) - 20e^{-5t}$$



$$I_L(0^-) = 0$$


$$V_C(0^-) = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s^2 + 3s + 2 = 0$$

$$(s+1)(s+2) = 0$$

2

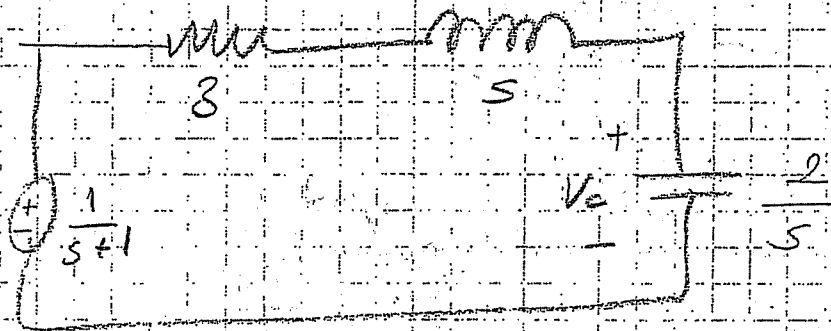

$$V_C(s) = \frac{\frac{2}{s}}{s^2 + 3s + 2} \cdot \frac{1}{s+1}$$

$$V_C(s) = \frac{2}{s^2 + 3s + 2} \cdot \frac{1}{s+1} = \frac{2}{(s+1)^2(s+2)} = \frac{A}{s+2} + \frac{B}{s+1} + \frac{C}{(s+1)^2}$$

$$2 = A(s+1)^2 + B(s+1)(s+2) + C(s+2)$$

$$2 = (A+B)s^2 + (2A+3B+C)s + A+2B+2C$$

$$A+B=0 \Rightarrow A=-B \quad A=2$$

$$2A+3B+C=0 \Rightarrow B+C=0 \quad B=-2$$



$$A+2B+2C=2 \quad C=2$$

$$V(s) = \frac{2}{s+2} + \frac{-2}{(s+1)} + \frac{2}{(s+1)^2}$$


$$V(t) = \underbrace{2e^{-2t}u(t) - 2e^{-t}u(t)}_{\text{homogeneous}} + \underbrace{2te^{-t}u(t)}_{\text{particular}}$$

Two Parts:
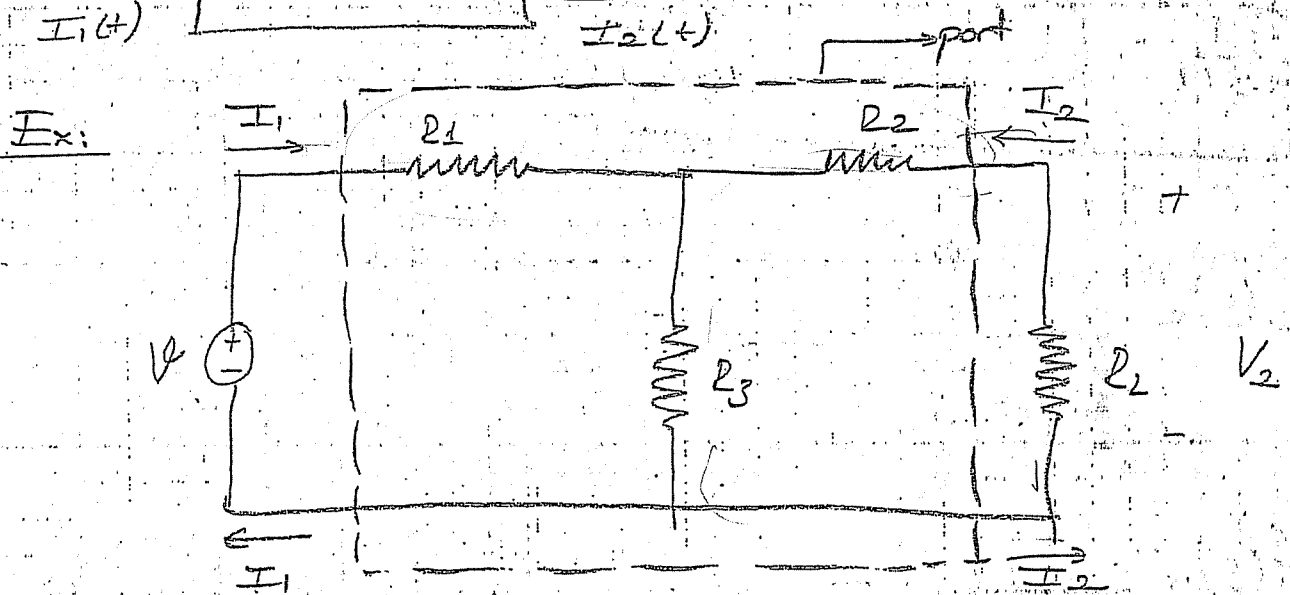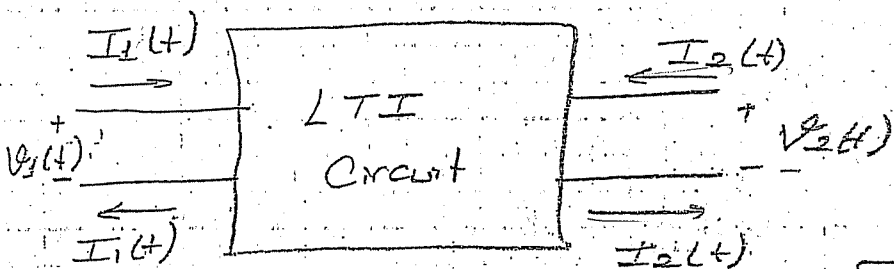
$$f(V_1(t), V_2(t), I_1(t), I_2(t), t) = 0$$



$$I_1 = I_1' \quad I_2 = I_2'$$

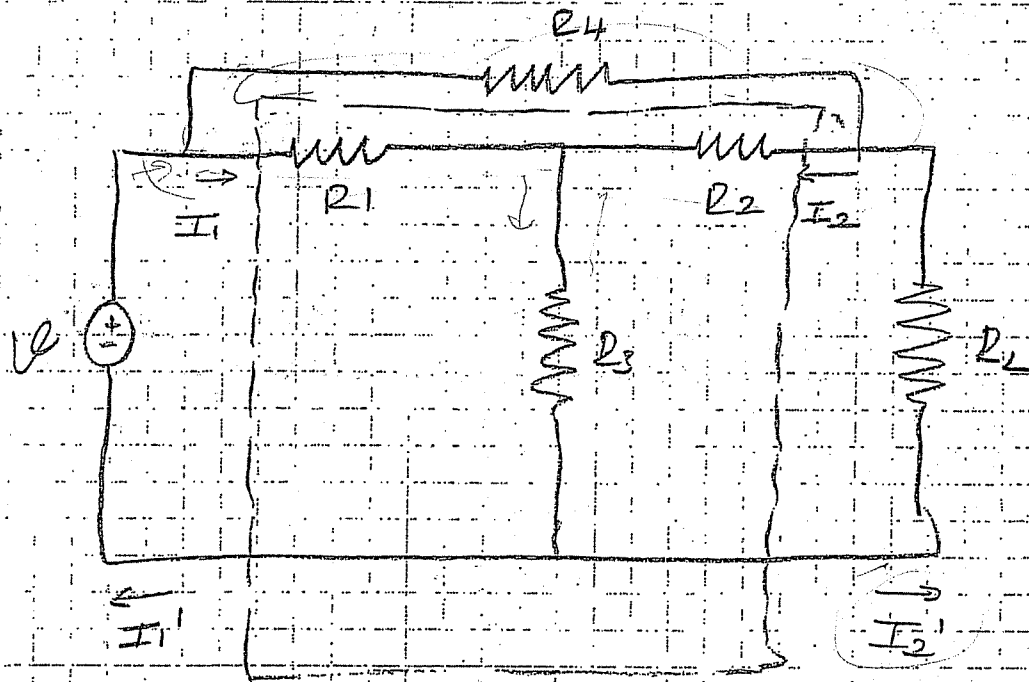

$$I_1 \neq I_1'$$

$$I_2 = I_2'$$

\* It is assumed that LTI parts has no independent sources. By using superposition, the effect of independent sources could be further analyzed.

Resistance Matrix (open-circuit matrix)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = r_{11} I_1 + r_{12} I_2$$

$$V_2 = r_{21} I_1 + r_{22} I_2$$

$$r_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$r_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$




$$r_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$r_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$I_2=0$$

$$I_1=0$$

Ex:

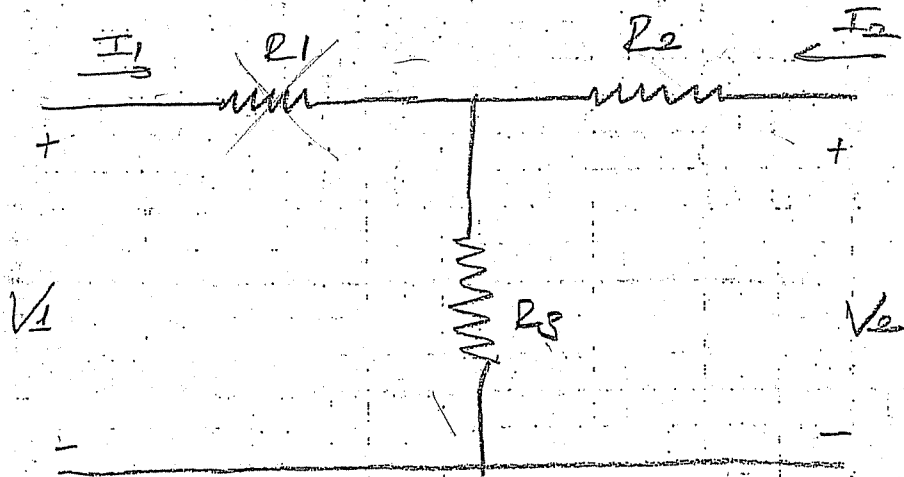


$$r_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = R_1 + R_3$$

$$V_1 = R_1 I_1 + R_3 (I_1 + I_2)$$

when  $I_2=0$

$$r_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = R_1 + R_3$$

$$r_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = R_3$$

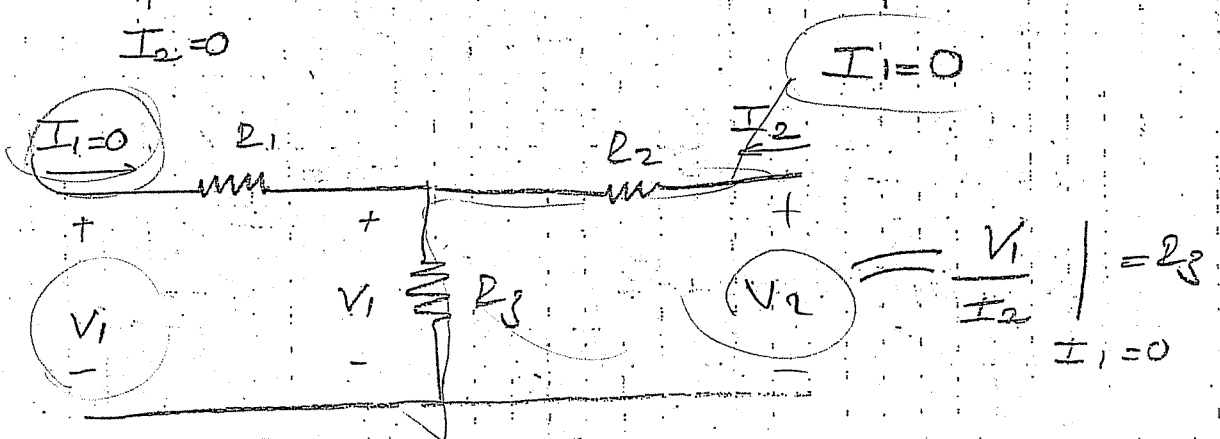

$$r_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$V_2 = R_2 I_2 + (I_1 + I_2) R_3$$

$$r_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = R_3$$

$$r_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$


$$r_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = R_2 + R_3$$

$$\underline{R} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \underline{R} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Transmission Matrix (ABCD matrix)
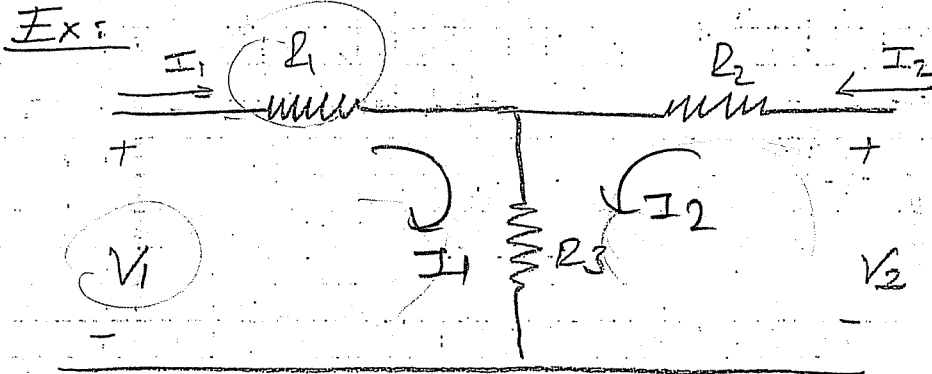
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$



$$A = \left. \frac{V_1}{V_2} \right|_{-I_2=0}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

$$V_1 = R_1 I_1 + (I_1 + I_2) R_3$$

$$V_2 = R_2 I_2 + (I_1 + I_2) R_3$$

$$I_2 = 0 \Rightarrow \left. \begin{array}{l} V_1 = (R_1 + R_3) I_1 \\ V_2 = R_3 I_1 \end{array} \right\} \Rightarrow \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{R_1 + R_3}{R_3}$$

$$V_2 = 0$$

$$(R_2 + R_3) I_2 = -I_1 R_3 \Rightarrow I_1 = \frac{(R_2 + R_3) I_2}{-R_3}$$

$$V_1 = R_1 \frac{(R_2 + R_3) I_2}{-R_3} + \left( \frac{(R_2 + R_3) I_2}{-R_3} + I_2 \right) R_3$$

$$V_1 = \left[ \frac{R_1 (R_2 + R_3)}{-R_3} - (R_1 + R_3) + R_3 \right] I_2$$

$$V_1 = \left[ \frac{-R_1 R_2 - R_1 R_3 - R_1 R_3 - R_3^2 + R_3^2}{R_3} \right] I_2$$

$$V_1 = \left[ \frac{+R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3} \right] I_2$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$V_1 = R_3 I_2 + (R_1 + R_3) I_1$$

$$V_2 = R_3 I_2 + (R_2 + R_3) I_1$$

$$I_2 = 0 \Rightarrow V_2 = R_3 I_1 \Rightarrow C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{R_3}$$

$$\Delta = \begin{vmatrix} I_1 \\ -I_2 \end{vmatrix} \Bigg|_{V_2=0}$$

$$V_2=0 \Rightarrow (R_2 + R_3) I_2 + R_3 I_1 = 0$$

$$\frac{I_1}{I_2} = - \frac{R_2 + R_3}{R_3}$$

$$\Delta = \begin{vmatrix} I_1 \\ -I_2 \end{vmatrix} \Bigg|_{V_2=0} = \frac{R_2 + R_3}{R_3}$$


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{R_1 + R_3}{R_3} & \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3} \\ \frac{1}{R_3} & \frac{R_2 + R_3}{R_3} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Conductance Matrix: (short circuit)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}}_{\bar{G}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\bar{G} = \bar{R}^{-1}$$

$$\boxed{G = \frac{1}{R}}$$

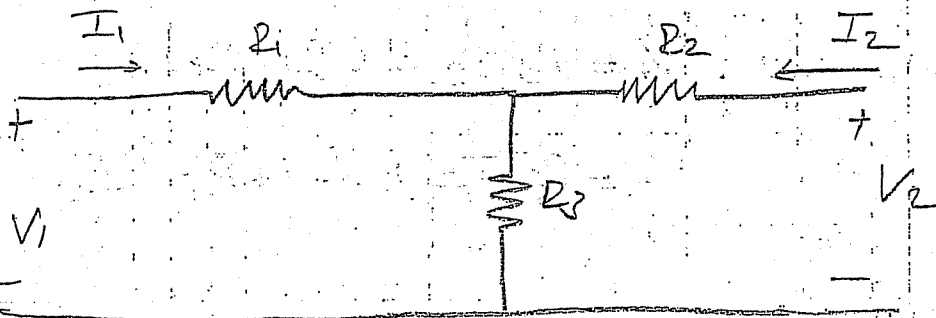

$$V_1 = (R_1 + R_3) I_1 + R_3 I_2$$

$$V_2 = R_3 I_1 + (R_2 + R_3) I_2$$


$$g_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$g_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$g_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$g_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

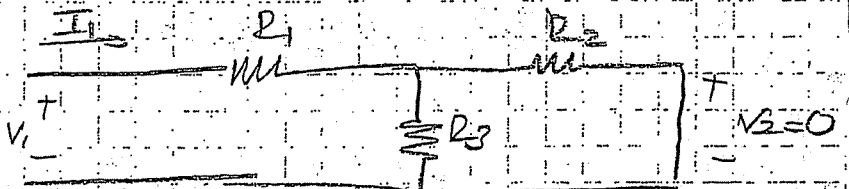


$$\left. \frac{V_1}{I_1} \right|_{V_2=0} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$\frac{V_1}{I_1} = R_1 + (R_2 \parallel R_3)$$

$$\left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3}$$


$$g_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{R_2 + R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

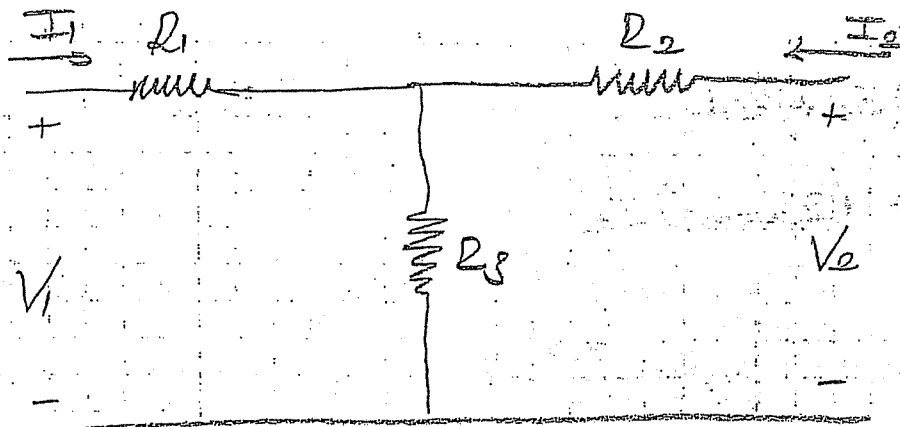

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$g_{11} = \frac{R_2 + R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$g_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

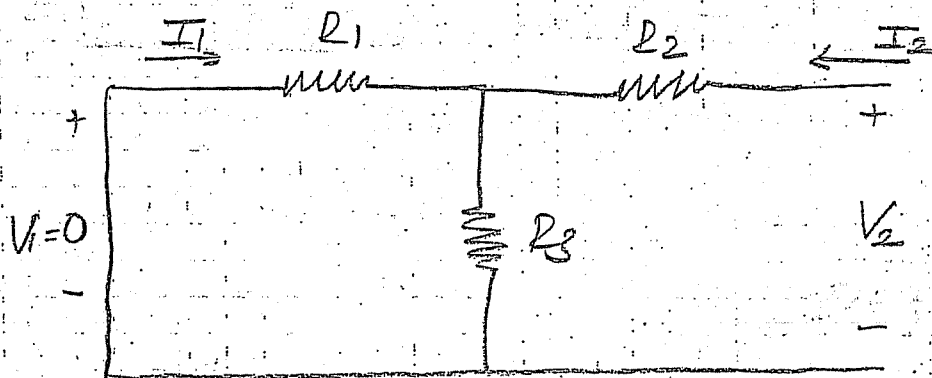

$$I_1 = I_2 + \frac{-R_3}{R_1 + R_3} \Rightarrow I_2 = I_1 \frac{R_1 + R_3}{-R_3}$$

$$\frac{V_2}{I_2} = (R_1 \parallel R_3) + R_2 = \frac{R_1 R_3}{R_1 + R_3} + R_2 = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 + R_3}$$

$$V_2 = \frac{R_1 R_3 + R_1 R_2 + R_2 R_3}{R_1 + R_3} I_2$$

$$V_2 = \frac{R_1 R_3 + R_1 R_2 + R_2 R_3}{R_3} I_1$$

$$g_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{-R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

HW:  $g_{21} \neq g_{12}$

$$g_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$V_1 = (R_1 + R_3) I_1 + R_3 I_2$$

$$V_2 = R_3 I_1 + (R_2 + R_3) I_2$$

$$0 = (R_1 + R_3) I_1 + R_3 I_2$$

$$-\frac{R_3 I_2}{R_1 + R_3} = I_1$$

$$V_2 = R_3 \left( \frac{-R_3}{R_1 + R_3} I_2 \right) + (R_2 + R_3) I_2$$

$$V_2 \left[ \frac{-R_3^2 + R_1 R_2 + R_1 R_3 + R_2 R_3 + R_3^2}{R_1 + R_3} \right] I_2$$



$$g_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{R_1 + R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$\bar{G} = \begin{bmatrix} \frac{R_2 + R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} & \frac{-R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \\ \frac{-R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} & \frac{R_1 + R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \end{bmatrix}$$

H.W: Show that  $\bar{R} = \bar{G}^{-1}$


Hybrid Matrix:

$$H_1 \longrightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$H_2 \longrightarrow \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} h'_{11} & h'_{12} \\ h'_{21} & h'_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$H' = H^{-1}$$

Ex:

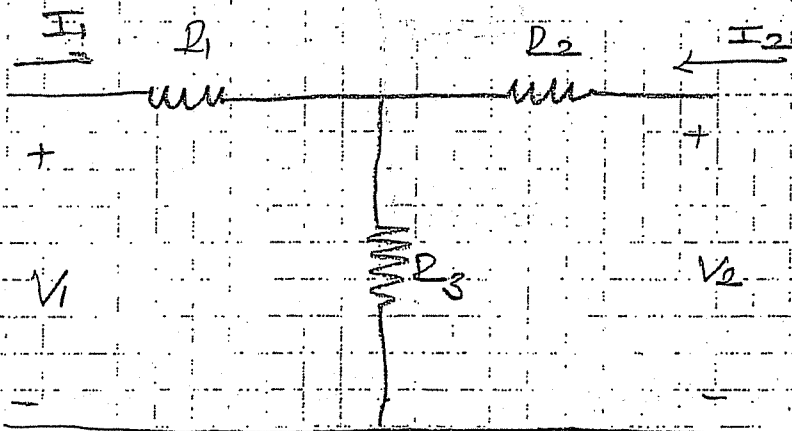

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$V_1 = (R_1 + R_3) I_1 + R_3 I_2 \leftarrow$$

$$V_2 = R_3 I_1 + (R_2 + R_3) I_2$$

$$0 = R_3 I_1 + (R_2 + R_3) I_2 \Rightarrow I_2 = \frac{-R_3 I_1}{R_2 + R_3}$$

$$V_1 = (R_1 + R_3) I_1 + R_3 \left( \frac{-R_3}{R_2 + R_3} I_1 \right)$$

$$\left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3} = h_{11}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{12} = \frac{R_3}{R_2 + R_3} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{-R_3}{R_2 + R_3}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_2 + R_3}$$

$$H = \begin{bmatrix} \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3} & \frac{R_3}{R_2 + R_3} \\ \frac{-R_3}{R_2 + R_3} & \frac{1}{R_2 + R_3} \end{bmatrix}$$

$$H^{-1} = H^{-1} =$$

$$X = \underbrace{\begin{bmatrix} a & b & | & 1 & 0 \\ c & d & | & 0 & 1 \end{bmatrix}}_A \xrightarrow[\text{row operations}]{\text{elementary}} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} A^{-1}$$

$$H = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \Rightarrow H^{-1} = \frac{\begin{bmatrix} d & -b \\ -c & a \end{bmatrix}}{ad - bc}$$

$$H^{-1} = \begin{bmatrix} \frac{1}{R_2 + R_3} & \frac{-R_3}{R_2 + R_3} \\ \frac{R_3}{R_2 + R_3} & \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3} \end{bmatrix}$$

Ex:

$$Z = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \rightarrow \text{ABCD matrix} \\ \text{in terms of } r_{11}, r_{12}, r_{21}, r_{22}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \begin{aligned} V_1 &= r_{11} I_1 + r_{12} I_2 \\ V_2 &= r_{21} I_1 + r_{22} I_2 \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \begin{aligned} A = \left. \frac{V_1}{V_2} \right|_{I_2=0} &= \frac{r_{11}}{r_{21}} \end{aligned}$$


$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \begin{aligned} V_2=0 &= r_{21} I_1 + r_{22} I_2 \\ I_1 &= -\frac{r_{22} I_2}{r_{21}} \end{aligned}$$

$$V_1 = r_{11} I_1 + r_{12} I_2 = -\frac{r_{11} r_{22} I_2}{r_{21}} + r_{12} I_2$$

$$V_1 = \left[ \frac{-r_{11} r_{22}}{r_{21}} + r_{12} \right] I_2 \quad \begin{aligned} B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} &= \frac{r_{11} r_{22}}{r_{21}} - r_{12} \end{aligned}$$


$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{r_{21}} \quad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = \frac{r_{22}}{r_{21}}$$

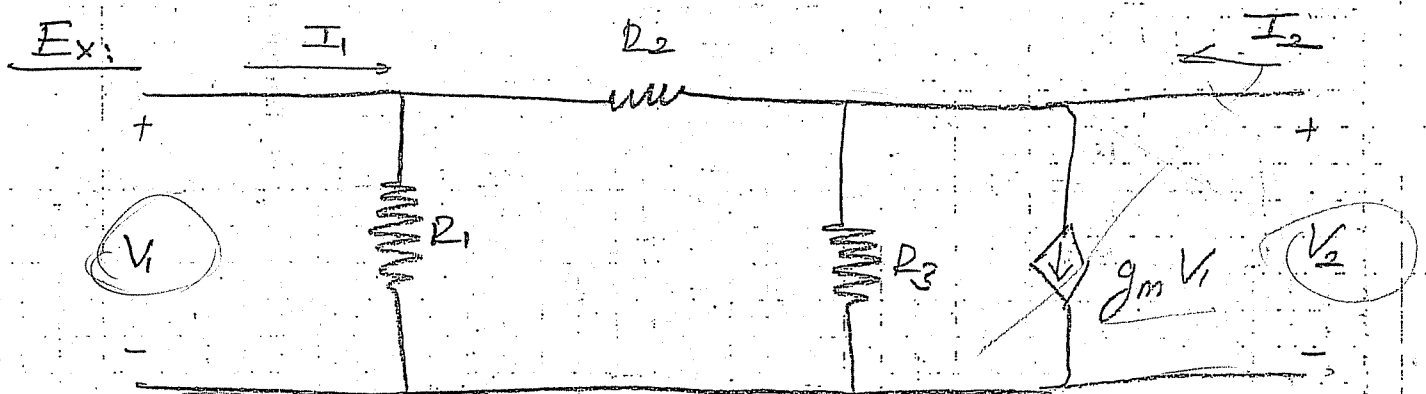H.W (ABCD)  $\rightarrow$   $H = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$   
 known



Z matrix

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad r_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

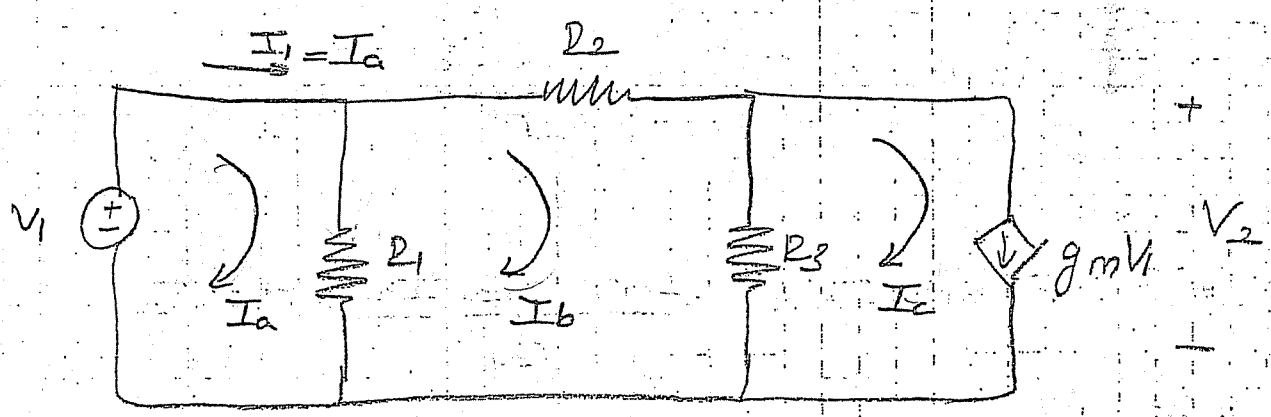

- ①  $-V_1 + R_1(I_a - I_b) = 0$
- ②  $R_1(I_b - I_a) + R_2(I_b) + R_3(I_b - I_c) = 0$
- ③  $I_c = g_m V_1$

$$\textcircled{1} \oplus \textcircled{2} \quad -V_1 + R_2 I_b + R_3 (I_b - I_c) = 0 \quad \text{put } \textcircled{3}$$


$$-V_1 + R_2 I_b + R_3 [I_b - g_m V_1] = 0$$

$$I_b = \frac{1 + g_m R_3}{R_2 + R_3} V_1 \quad \text{put } \textcircled{1}$$

$$-V_1 + R_1 I_a - R_1 \left( \frac{1 + g_m R_3}{R_2 + R_3} \right) V_1 = 0$$

$$R_1 I_a = V_1 \left[ 1 + \frac{R_1 + g_m R_1 R_3}{R_2 + R_3} \right]$$
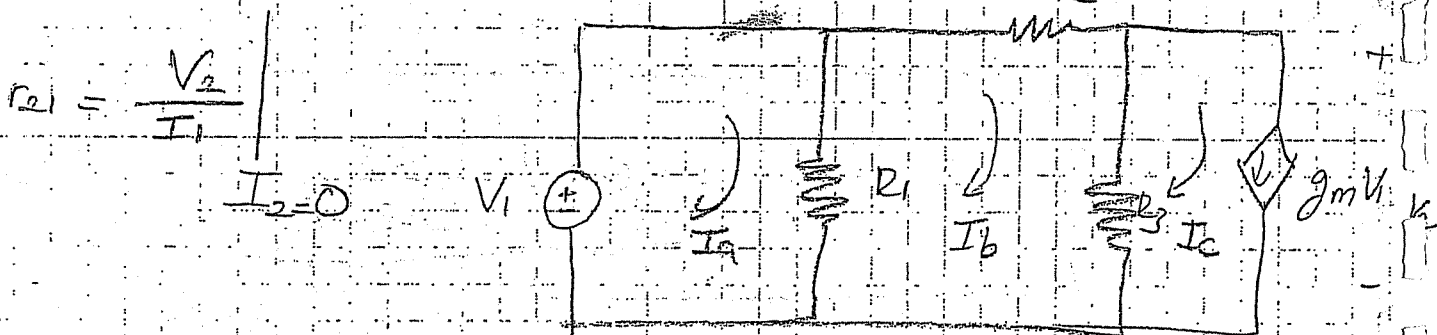
$$\frac{V_1}{I_a} = \frac{R_1 (R_2 + R_3)}{R_2 R_3 + R_1 + g_m R_1 R_3} = \frac{V_1}{I_a} \quad \left. \begin{array}{l} = r_{11} \\ I_2 = 0 \end{array} \right\}$$



$$V_2 = R_3 (I_b - I_c)$$

$$V_2 = R_3 \left( \frac{1 + g_m R_3}{R_2 + R_3} V_1 - g_m V_1 \right) = R_3 \left( \frac{1 - g_m R_2}{R_2 + R_3} \right) V_1$$


$$V_2 = \frac{R_3 [1 - g_m R_2]}{R_2 + R_3} V_1$$

$$\left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \frac{R_1 (R_2 + R_3)}{R_2 + R_3 + R_1 + g_m R_1 R_3} I_1$$

$$r_{21} = \frac{R_1 R_3 [1 - g_m R_2]}{R_2 + R_3 + R_1 + g_m R_1 R_3} = \frac{V_2}{I_1} \quad \left. \begin{array}{l} \\ \\ \end{array} \right|_{I_2=0}$$

$$r_{12} = \frac{V_1}{I_2} \quad \left. \begin{array}{l} \\ \\ \end{array} \right|_{I_1=0}$$

$$r_{22} = \frac{V_2}{I_2} \quad \left. \begin{array}{l} \\ \\ \end{array} \right|_{I_1=0}$$

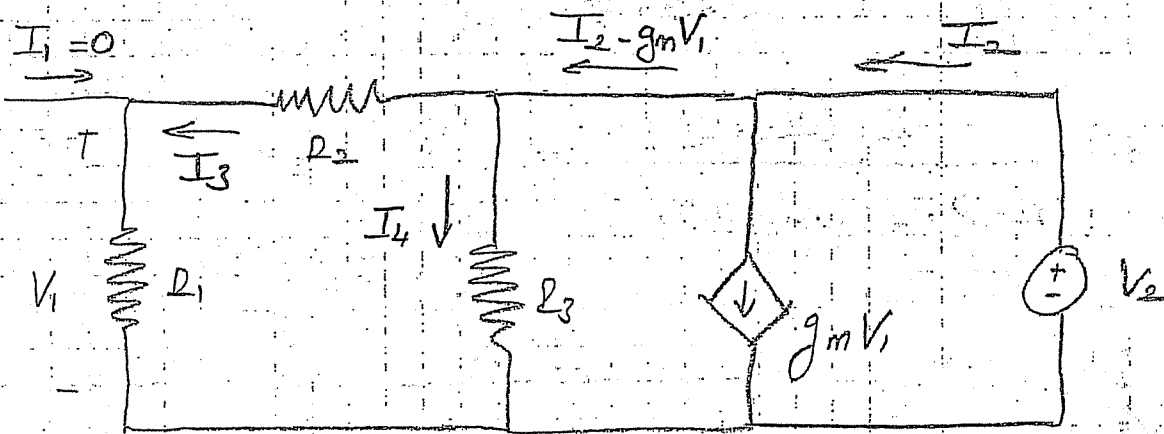

$$V_1 = R_1 I_3 \quad I_3 = \frac{(I_2 - g_m V_1) R_3}{R_1 + R_2 + R_3}$$

$$V_1 = \frac{R_1 R_3 (I_2 - g_m V_1)}{R_1 + R_2 + R_3} = \frac{R_1 R_3}{R_1 + R_2 + R_3} I_2 - \frac{g_m R_1 R_3}{R_1 + R_2 + R_3} V_1$$

$$\left( 1 + \frac{g_m R_1 R_3}{R_1 + R_2 + R_3} \right) V_1 = \frac{R_1 R_3}{R_1 + R_2 + R_3} I_2$$

$$\left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{R_1 + R_3}{R_1 + R_2 + R_3 + g_m R_1 R_3} = r_{12}$$


$$I_4 = (I_2 - g_m V_1) \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3}$$

$$V_2 = I_4 R_3 = \left( I_2 - g_m \frac{R_1 R_3}{R_1 + R_2 + R_3 + g_m R_1 R_3} I_2 \right) \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3}$$

$$\left. \frac{V_2}{I_2} \right|_{I_1=0} = \left[ 1 - g_m \frac{R_1 R_3}{R_1 + R_2 + R_3 + g_m R_1 R_3} \right] \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3}$$

$$r_{22} = \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3 + g_m R_1 R_3}$$

Terminated Two Ports.

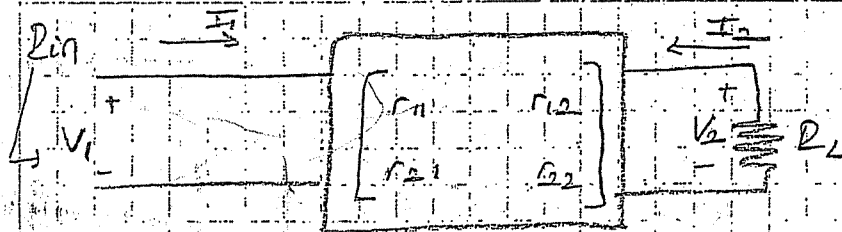

$$r_{in} = \frac{V_1}{I_1}$$

$$V_1 = r_{11} I_1 + r_{12} I_2$$

$$V_2 = r_{21} I_1 + r_{22} I_2$$

$$\frac{V_2}{I_2} = -R_L$$

$$\frac{V_2}{I_2} = r_{21} \frac{I_1}{I_2} + r_{22} = -R_L$$




$$\frac{-R_L + r_{22}}{r_{21}} = \frac{I_1}{I_2}$$

$$\frac{V_1}{I_1} = r_{11} + r_{12} \frac{I_2}{I_1}$$

$$\frac{V_1}{I_1} = r_{11} + r_{12} \frac{r_{21}}{-(R_L + r_{22})}$$

$$\frac{V_1}{I_1} = R_{in} = r_{11} - \frac{r_{12} r_{21}}{(R_L + r_{22})}$$

H.W.:

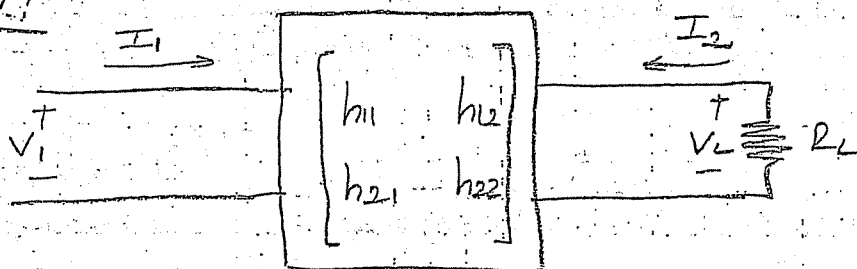


Find  $R_{in} = \frac{V_1}{I_1}$

in terms of hybrid parameters.

Interconnection of Two Ports:

Parallel Connection:

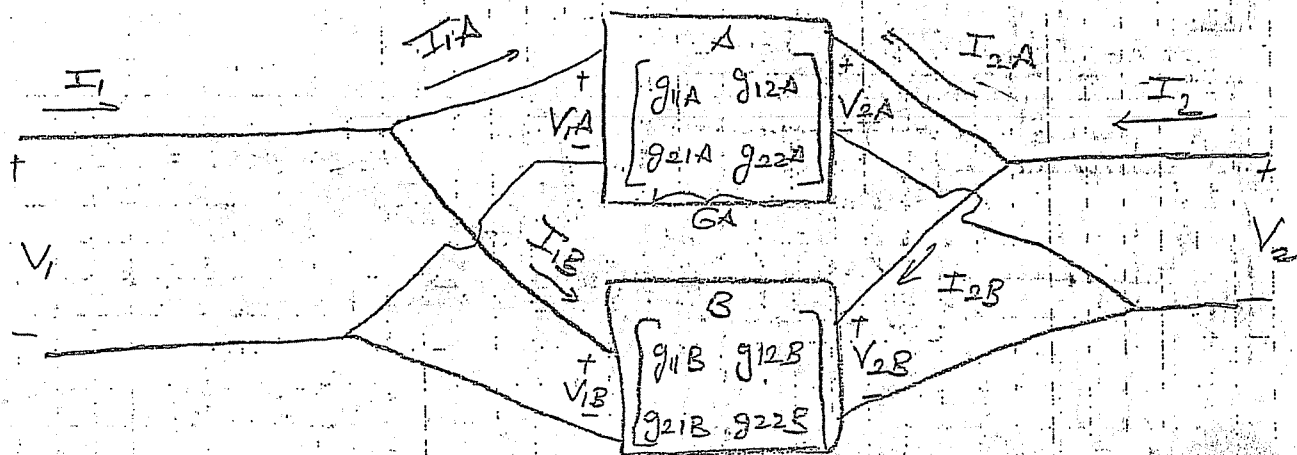

$$I_1 = I_{1A} + I_{1B}$$

$$V_{1A} = V_{1B} = V_1$$

$$I_2 = I_{2A} + I_{2B}$$


$$V_{2A} = V_{2B} = V_2$$

$$\begin{bmatrix} I_{1A} \\ I_{2A} \end{bmatrix} = G_A \begin{bmatrix} V_{1A} \\ V_{2A} \end{bmatrix} \quad \begin{bmatrix} I_{1B} \\ I_{2B} \end{bmatrix} = G_B \begin{bmatrix} V_{1B} \\ V_{2B} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{1A} + I_{1B} \\ I_{2A} + I_{2B} \end{bmatrix} = G_A \begin{bmatrix} V_{1A} \\ V_{2A} \end{bmatrix} + G_B \begin{bmatrix} V_{1B} \\ V_{2B} \end{bmatrix} = (G_A + G_B) \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$G = \begin{bmatrix} g_{11A} + g_{11B} & g_{12A} + g_{12B} \\ g_{21A} + g_{21B} & g_{22A} + g_{22B} \end{bmatrix}$$

Series connection:


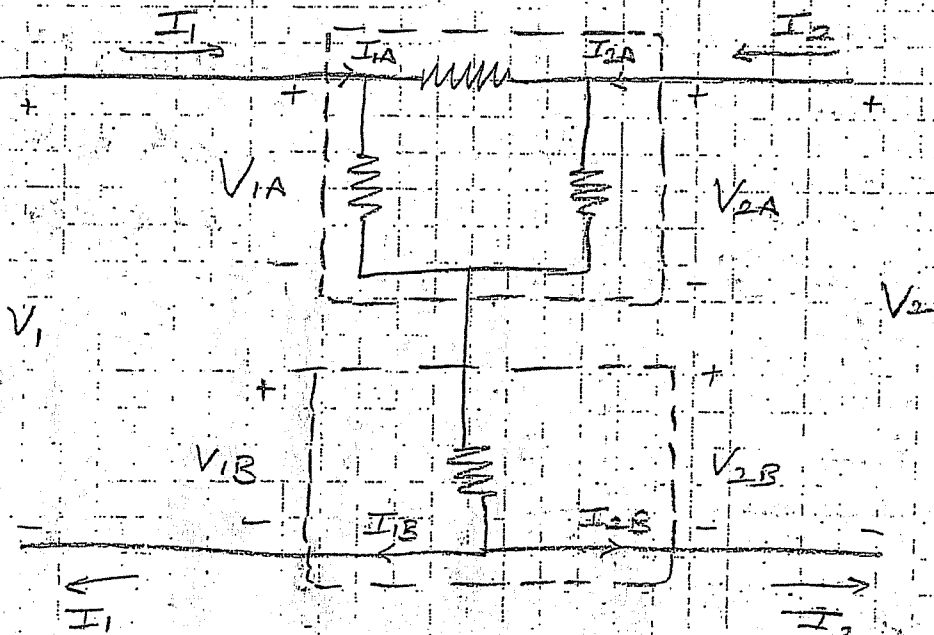


$$I_1 = I_{1A} = I_{1B}$$


$$V_1 = V_{1A} + V_{1B}$$

$$I_2 = I_{2A} = I_{2B}$$

$$V_2 = V_{2A} + V_{2B}$$

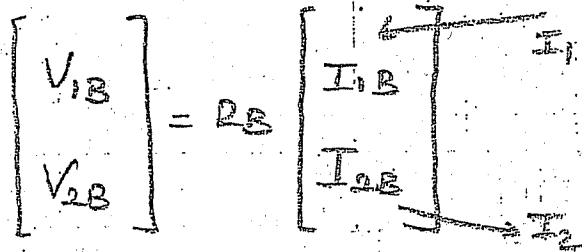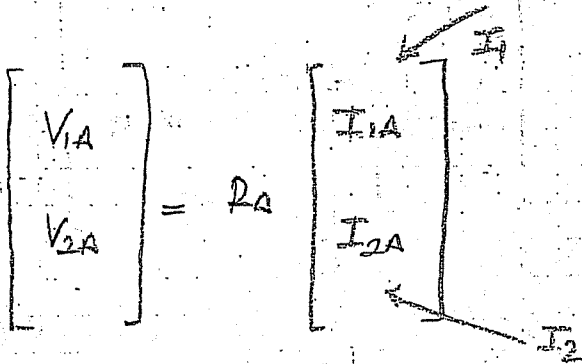
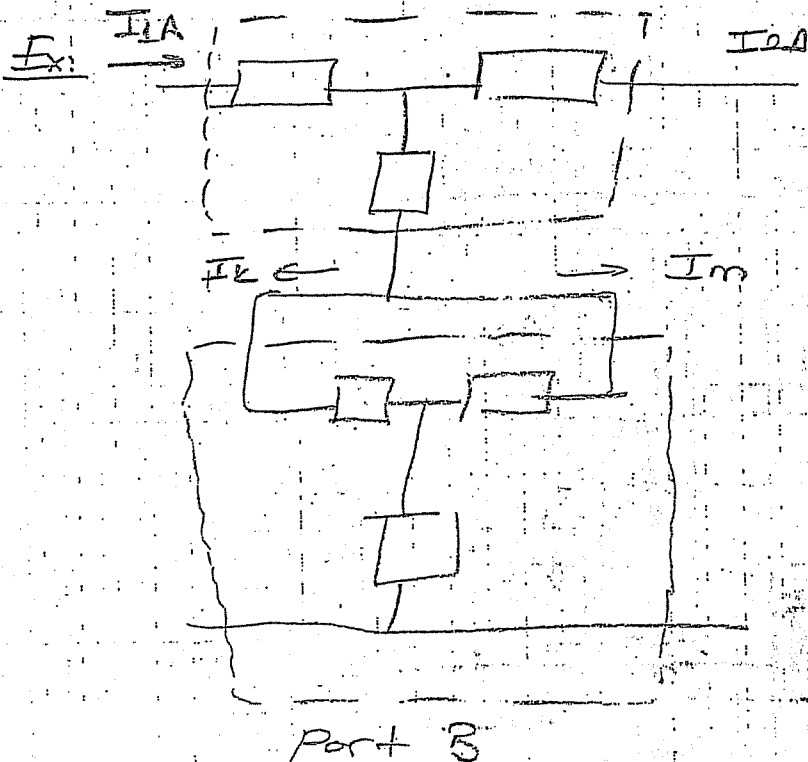
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = (R_A + R_B) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$




$$I_1 = I_{1A}$$

$$I_m = I_{2A}$$

not a series connection.

Series - Parallel Connection:

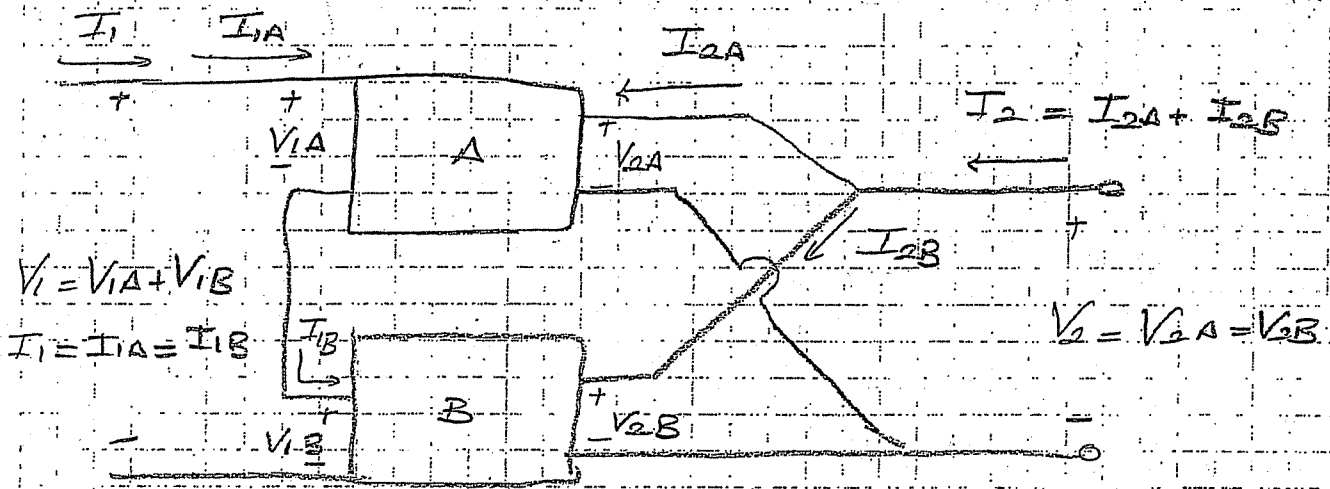

$$* \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\textcircled{2} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} h_{11}' & h_{12}' \\ h_{21}' & h_{22}' \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$


$$V_1 = V_{1A} + V_{1B}$$

$$I_2 = I_{2A} + I_{2B}$$



$$\begin{bmatrix} V_{1A} \\ I_{2A} \end{bmatrix} = \begin{bmatrix} h_{11A} & h_{12A} \\ h_{21A} & h_{22A} \end{bmatrix} \begin{bmatrix} I_{1A} \\ V_{2A} \end{bmatrix}$$

$$\begin{bmatrix} V_{1B} \\ I_{2B} \end{bmatrix} = \begin{bmatrix} h_{11B} & h_{12B} \\ h_{21B} & h_{22B} \end{bmatrix} \begin{bmatrix} I_{1B} \\ V_{2B} \end{bmatrix}$$
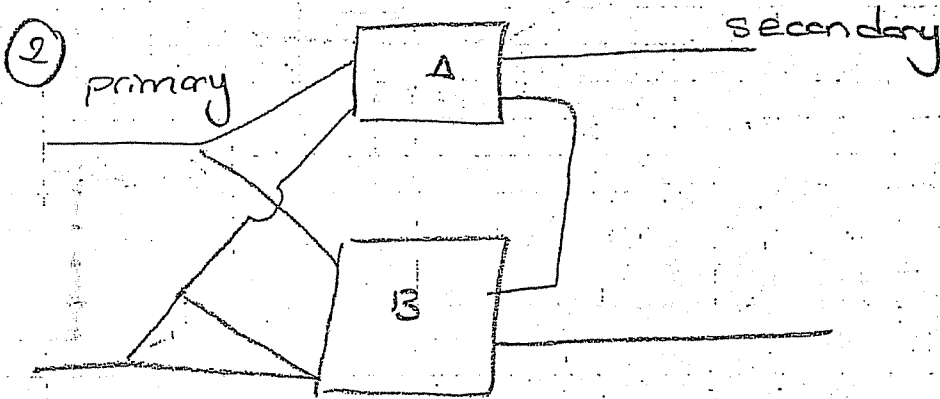
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11A} + h_{11B} & h_{12A} + h_{12B} \\ h_{21A} + h_{21B} & h_{22A} + h_{22B} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$



Cascade Connection:

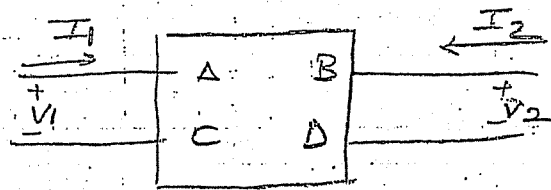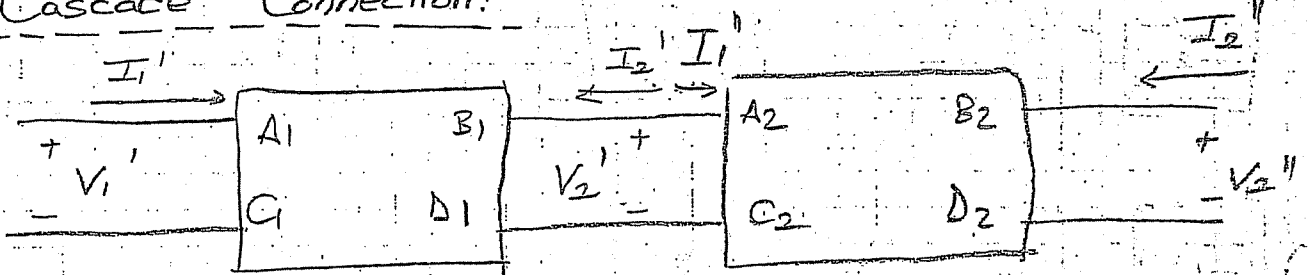

$$\begin{bmatrix} V_1' \\ I_1' \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} \quad \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2'' \\ -I_2'' \end{bmatrix}$$

$$V_2' = V_1''$$


$$I_2' = -I_1''$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


ABCD

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Ex:

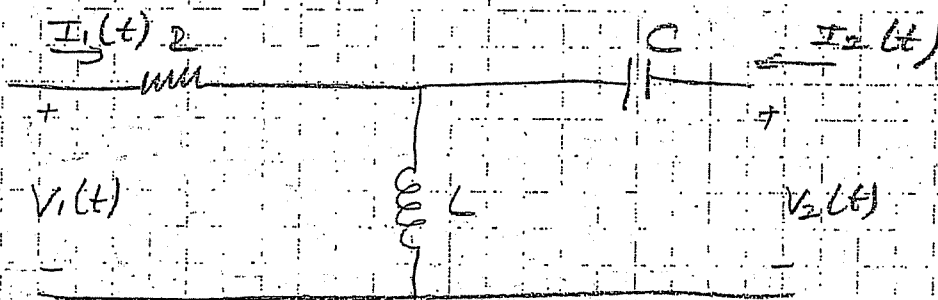

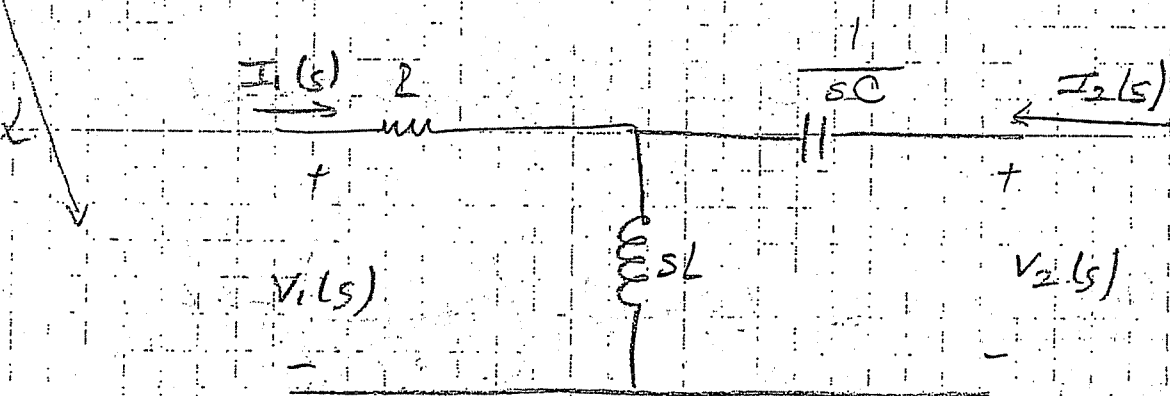Find port equation in Laplace domain ABCD



$$\begin{bmatrix} V_1(s) \\ I_1(s) \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2(s) \\ -I_2(s) \end{bmatrix}$$

$$V_1(s) = R I_1(s) + sL (I_1(s) + I_2(s)) = [R + sL] I_1(s) + sL I_2(s)$$

$$V_2(s) = \frac{1}{sC} I_2(s) + sL (I_1(s) + I_2(s)) = sL I_1(s) + \left( sL + \frac{1}{sC} \right) I_2(s)$$

$$A = \left. \frac{V_1(s)}{V_2(s)} \right|_{-I_2(s)=0} = \frac{R + sL}{sL}$$

$$B = \left. \frac{V_1(s)}{-I_2(s)} \right|_{V_2(s)=0}$$

$$V_2(s) = 0 \Rightarrow sL I_1(s) + \left( sL + \frac{1}{sC} \right) I_2(s) = 0$$

$$I_1(s) = \frac{- \left( sL + \frac{1}{sC} \right) I_2(s)}{sL} = - \left( 1 + \frac{1}{s^2 LC} \right) I_2(s)$$

$$V_1(s) = - (R + sL) \left( 1 + \frac{1}{s^2 LC} \right) I_2(s) + sL I_2(s)$$

$$B = \left. \frac{V_1(s)}{-I_2(s)} \right|_{V_2(s)=0} = (R + sL) \left( 1 + \frac{1}{s^2 LC} \right) - sL$$

$$C = \left. \frac{I_1(s)}{V_2(s)} \right|_{I_2(s)=0} = \frac{1}{sL}$$

$$D = \left. \frac{-I_1(s)}{-I_2(s)} \right|_{V_2(s)=0} = \frac{sL + \frac{1}{sC}}{sL} = 1 + \frac{1}{s^2LC}$$

Coupled Inductors and Transformers:




$$\frac{d\phi}{dt} = V$$


Primary

Secondary

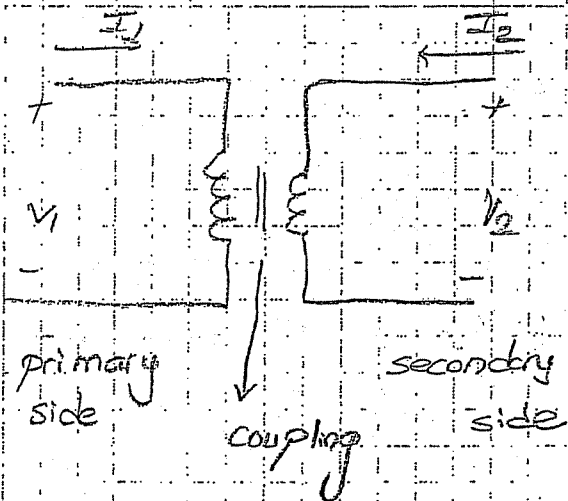
Mutual inductance: The coupling (relation) between the current in the first coil and produced voltage due to this current in the second coil.





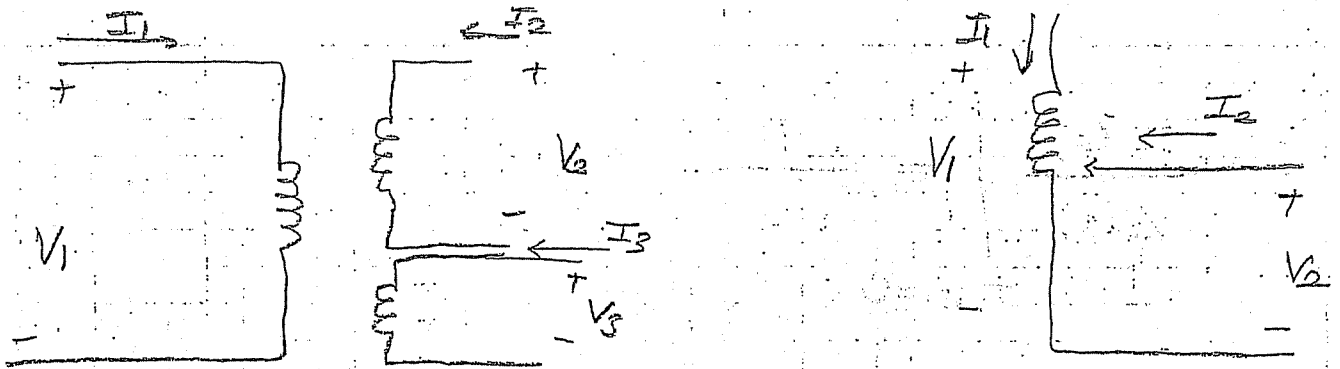

### LTI 2-branch coupled inductors

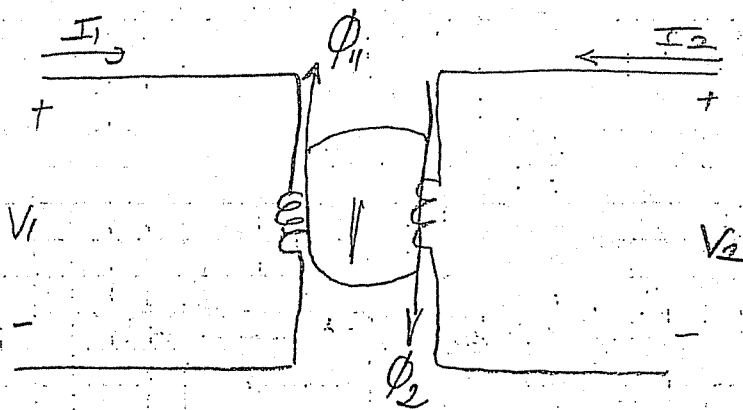

$$\Phi_1 = L_1 I_1 + M I_2$$

$$\Phi_2 = M I_1 + L_2 I_2$$

$$\begin{bmatrix} \Phi_1 \\ \Phi_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$L_1$  = self inductance of primary coil

$L_2$  = " " " secondary "

$M$  = mutual inductance

by Faraday's law  $V_k = \frac{d\Phi_k}{dt}$   $k = 1, 2, \dots, n$

$$V_1(t) = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$

$$V_2(t) = M \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$

$$\underline{V} = \underline{L} \frac{d\underline{I}}{dt}$$

$$\underline{L} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}$$

If  $\det[\underline{L}] \neq 0$ ;  $\underline{L}$  is non-singular

$\underline{A} = \underline{L}^{-1}$ , reciprocal inductance matrix

$$\underline{V} dt = \underline{L} d\underline{I}$$

$$\int_{t_0}^t \underline{V}(\varrho) d\varrho = \underline{L} \int_{\underline{I}_0}^{\underline{I}(t)} d\underline{I}$$

$$\int_{t_0}^t \underline{V}(\varrho) d\varrho = \underline{L} \left[ \underline{I}(t) - \underline{I}_0 \right]$$

$$\underline{L}^{-1} \int_{t_0}^t \underline{V}(\varrho) d\varrho = \left[ \underline{I}(t) - \underline{I}_0 \right]$$


$$\underline{I}(t) = \underline{I}_0 + \underline{A} \int_{t_0}^t \underline{V}(\varrho) d\varrho$$

$$L = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \rightarrow \Gamma = \begin{bmatrix} \Gamma_{11} & \Gamma_{12} \\ \Gamma_{12} & \Gamma_{22} \end{bmatrix}$$

$$i_1(t) = i_1(t_0) + \Gamma_{11} \int_{t_0}^t v_1(\alpha) d\alpha + \Gamma_{12} \int_{t_0}^t v_2(\alpha) d\alpha$$

$$i_2(t) = i_2(t_0) + \Gamma_{12} \int_{t_0}^t v_1(\alpha) d\alpha + \Gamma_{22} \int_{t_0}^t v_2(\alpha) d\alpha$$

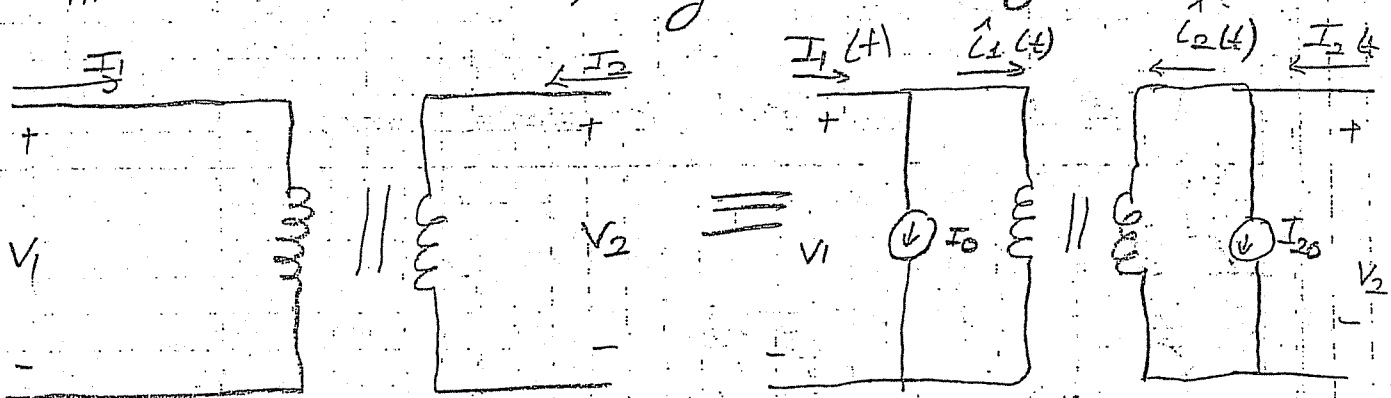
initial currents over primary and secondary coils.



$$i_1(t_0) = I_{10}$$


$$i_2(t_0) = I_{20}$$

$$i_1(t_0) = 0 \quad i_2(t_0) = 0$$

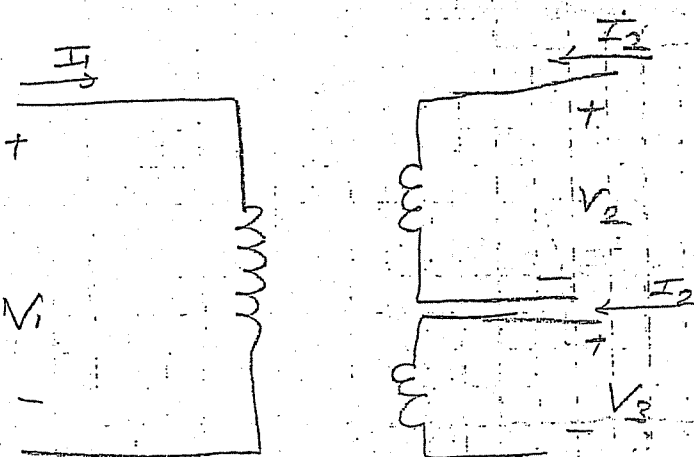

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} & M_{13} \\ M_{12} & L_2 & M_{23} \\ M_{13} & M_{23} & L_3 \end{bmatrix} \frac{d}{dt} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

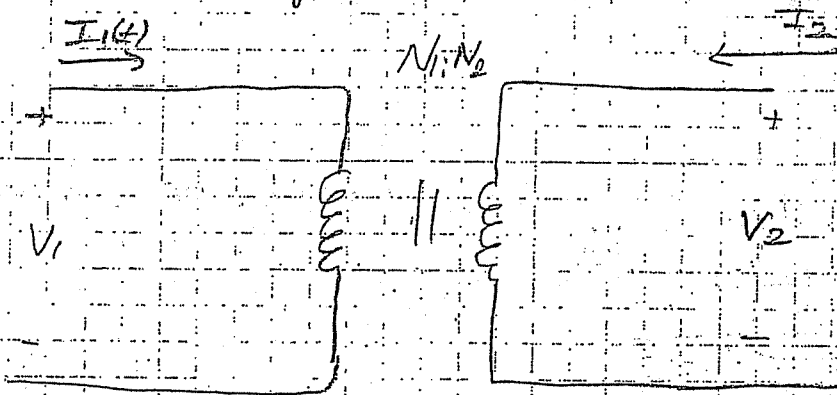Ideal Transformer: (LTI, passive, lossless circuit element)



is used for changing direction and magnitude of AC current and voltage.)

$N_1$  = Number of turns of windings in primary

$N_2$  = " " " " " " " secondary

$n = \frac{N_1}{N_2}$  ratio of turns

$$V_1(t) = n V_2(t)$$


$$I_2(t) = -n I_1(t)$$

$$\begin{aligned} \text{Instantaneous Power} = P(t) &= \overbrace{V_1(t) I_1(t)}^{P_1(t)} + \overbrace{V_2(t) I_2(t)}^{P_2(t)} \\ &= n V_2(t) \left( \frac{-I_2(t)}{n} \right) + V_2(t) I_2(t) \end{aligned}$$


$$P(t) = -V_2(t) I_2(t) + V_2(t) I_2(t) = 0$$

$\Rightarrow$  No power dissipation  $\Rightarrow$  no loss

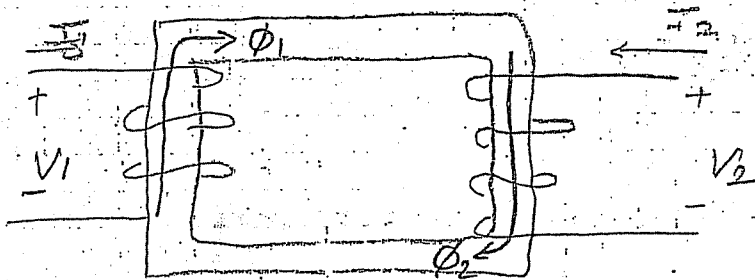For ideal transformers ( $L_1, L_2$ ) (self inductance values) of inductors are assumed to be equal to  $\infty$ .  
 (Observed from the equations  $V_1 = n V_2$   $I_2 = -n I_1$ )



$\Phi_1$  and  $\Phi_2$  are additive

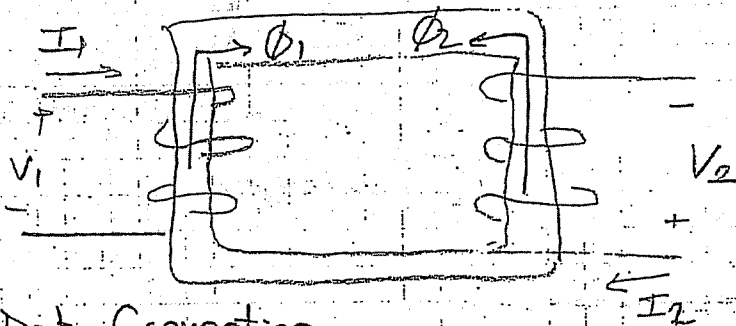


$\Phi_1$  and  $\Phi_2$  are subtractive

**Dot Convention**

if positive rate of change of current of the primary part produces (+)'ve effect on the secondary side induced voltage or vice versa, the mutual inductance values ( $M$ ) will be (+)'ve; otherwise mutual inductance values ( $M$ ) will be (-)'ve.





Actually the sign of  $M$  depends on

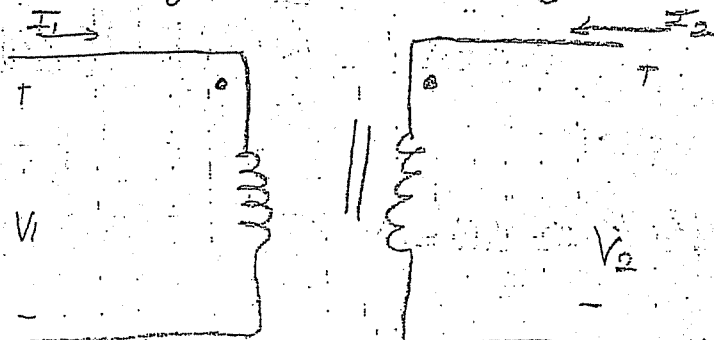- ① The spatial orientation of coil.
- ② The reference marks given to the coil voltages and currents.






$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$

$M > 0$  additive

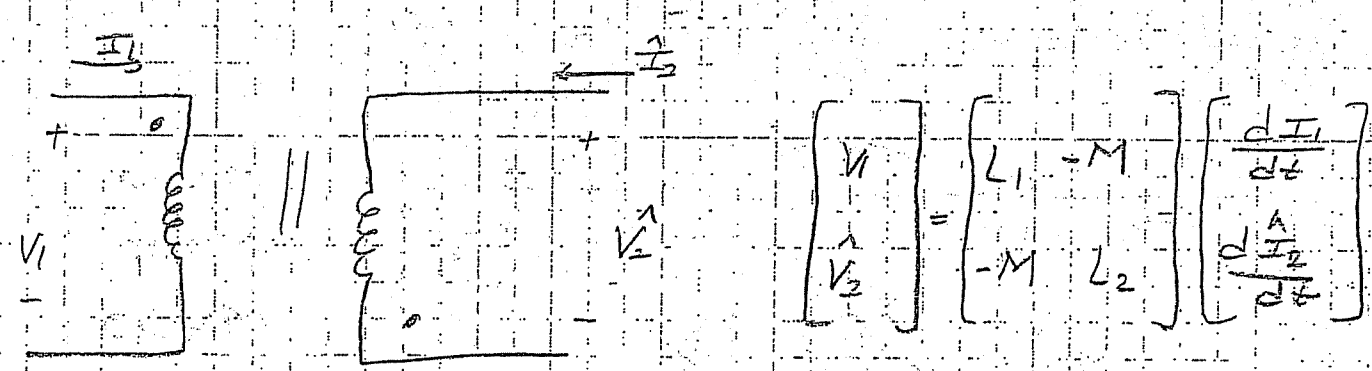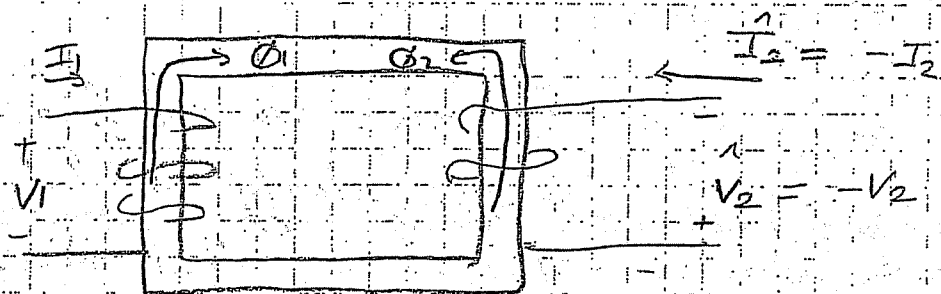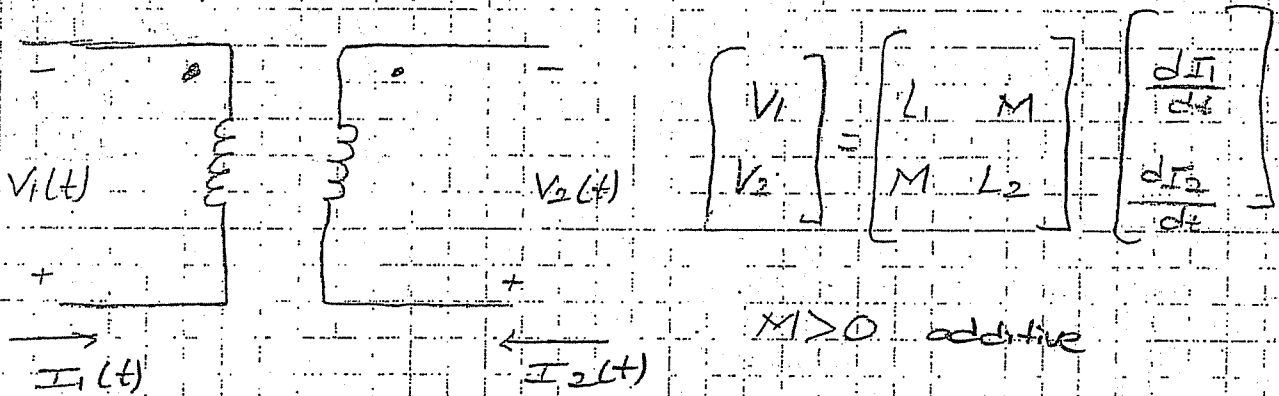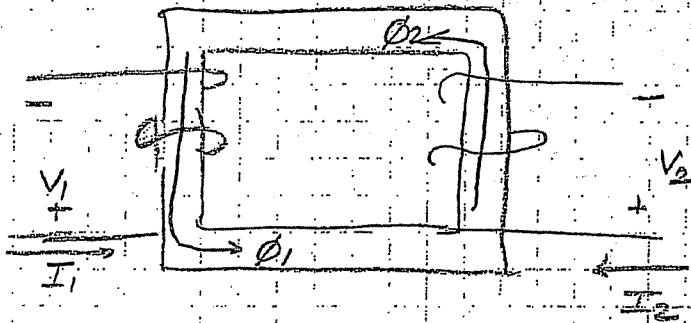

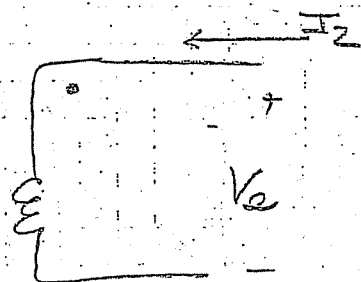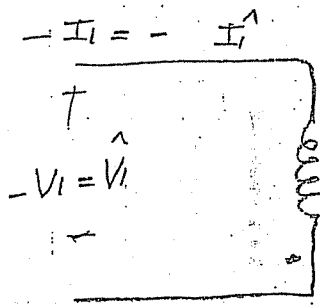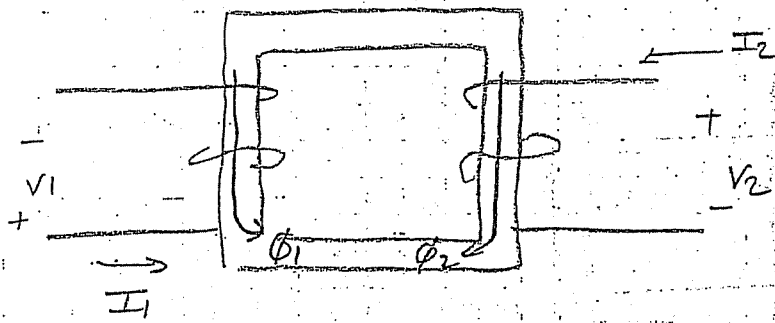
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 & -M \\ -M & L_2 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$

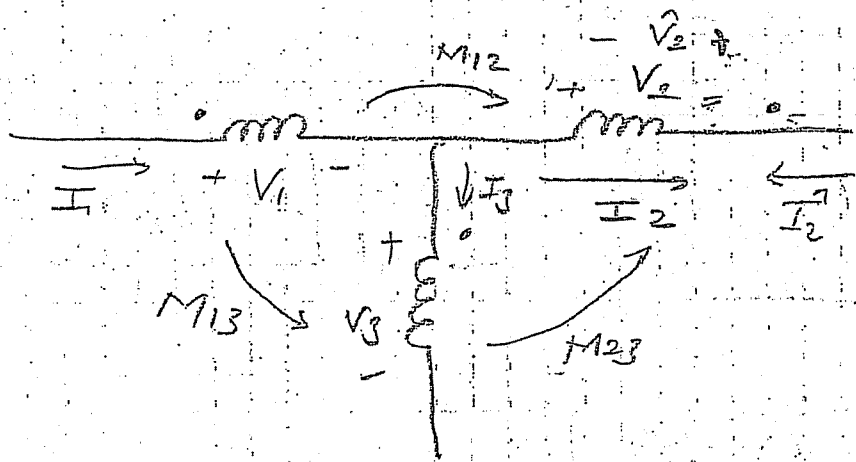\* In a circuit: If the current enters the coil from the "•" direction and if the voltage polarity is "•" direction is chosen as positive polarity then take mutual inductance value to be 't'




- $M_{12} > 0$
- $M_{13} > 0$
- $M_{23} > 0$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} L_1 & -M_{12} & M_{13} \\ -M_{12} & L_2 & M_{13} \\ M_{13} & -M_{23} & L_3 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \\ \frac{dI_3}{dt} \end{bmatrix}$$


$$\begin{bmatrix} V_1 \\ \hat{V}_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} & M_{13} \\ M_{12} & L_2 & M_{13} \\ M_{13} & M_{23} & L_3 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \\ \frac{dI_3}{dt} \end{bmatrix}$$

Ex:  $I_1(t)$

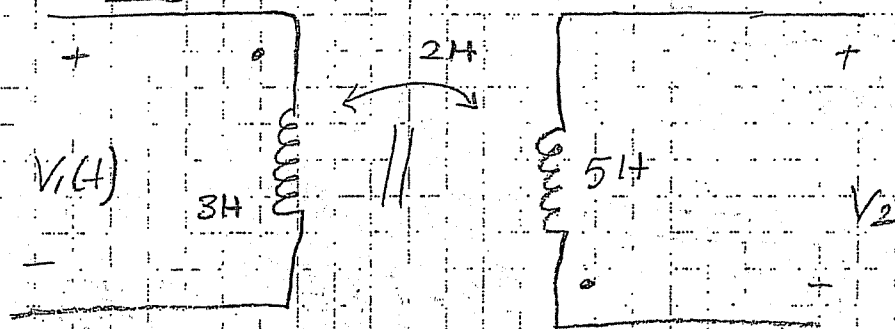
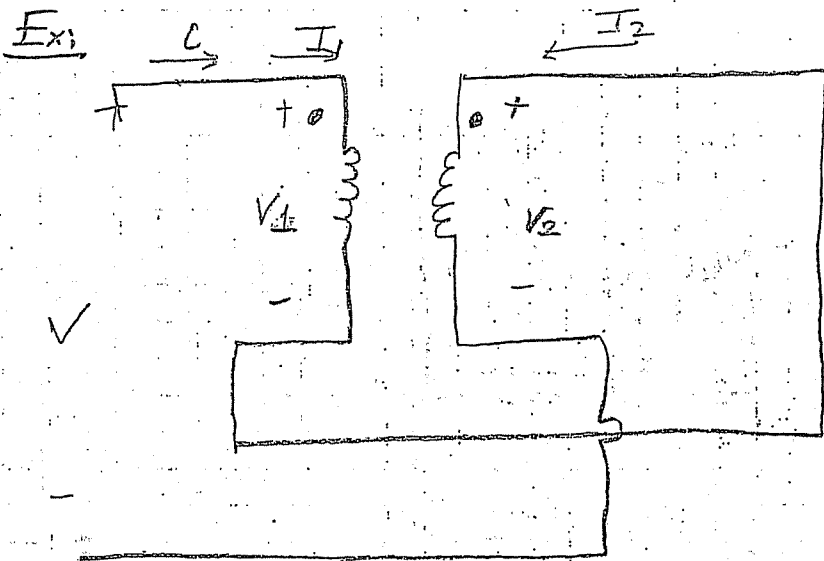
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 & -2 \\ -2 & 5 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$





$$V_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$


$$V_2 = M \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$

$$i = I_1(t) = -I_2(t)$$

$$V = V_1(t) + V_2(t) = (L_1 + M) \frac{dI_1}{dt} + (M + L_2) \frac{dI_2}{dt}$$

$$= (L_1 + M) \frac{di}{dt} + (M + L_2) \frac{di}{dt}$$
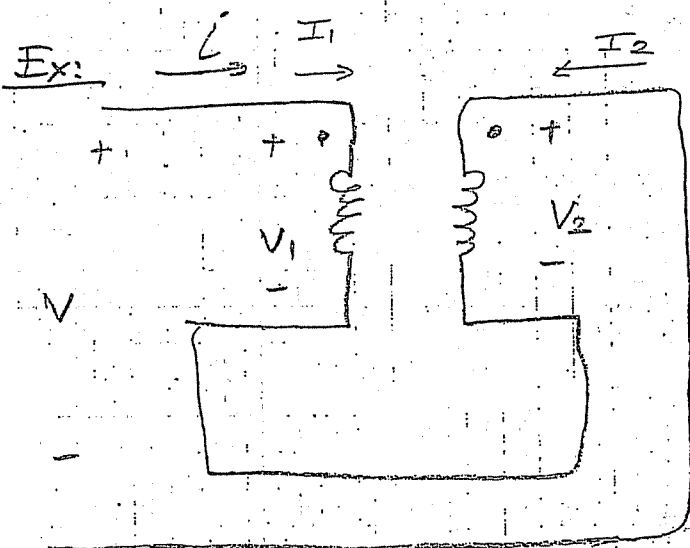
$$V(t) = \underbrace{[L_1 + L_2 + 2M]}_{L_{eq}} \frac{di}{dt}$$



$$V_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$


$$V_2 = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt}$$

$$i = I_1(t) = -I_2(t)$$

$$V = V_1(t) - V_2(t) = (L_1 - M) \frac{dI_1}{dt} + (M - L_2) \frac{dI_2}{dt}$$

$$= (L_1 - M) \frac{di}{dt} + (M - L_2) \frac{d[-i]}{dt}$$
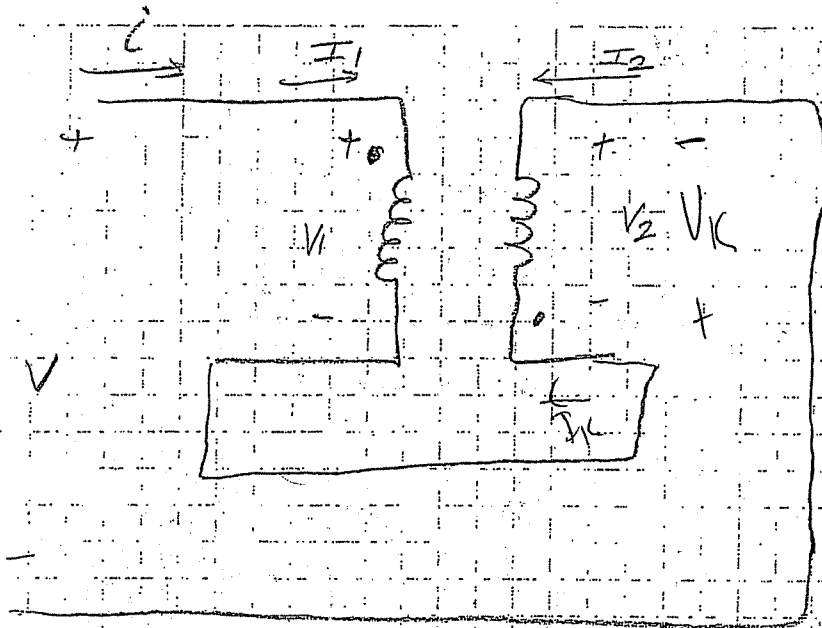
$$V = \underbrace{[L_1 + L_2 - 2M]}_{L_{eq}} \frac{di}{dt}$$



$$V_1 = L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt}$$


$$V_2 = -M \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$

$$I = I_1(t) = I_2(t)$$

$$V(t) = V_1(t) - V_2(t) = [L_1 + M] \frac{dI_1}{dt} - [L_2 + M] \frac{dI_2}{dt}$$

$$= (L_1 + M) \frac{dI}{dt} - [L_2 + M] \frac{d(-I)}{dt}$$
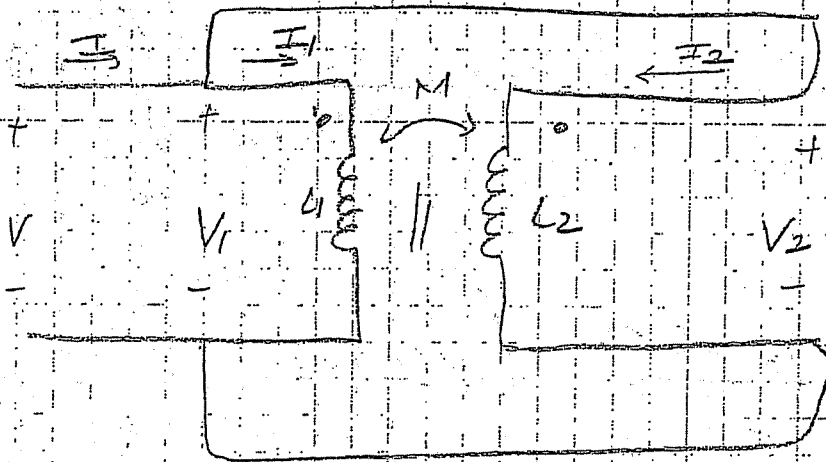
$$V = \underbrace{(L_1 + L_2 + 2M)}_{\text{Leq}} \frac{dI}{dt}$$



$$L_1 L_2 \neq M^2$$

$$V = V_1 = V_2$$

$$I = I_1 + I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$

$$V = M \frac{dI}{dt}$$

$$I = I_0 + \int_{t_0}^t \underline{V}(\underline{z}) d\underline{z}$$

$$L = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \rightarrow L^{-1} = \frac{\begin{bmatrix} L_2 & -M \\ -M & L_1 \end{bmatrix}}{L_1 L_2 - M^2}$$

$$\underline{I} = \begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} I_{10} \\ I_{20} \end{bmatrix} + \frac{\begin{bmatrix} L_2 & -M \\ -M & L_1 \end{bmatrix}}{L_1 L_2 - M^2} \int_{t_0}^t \begin{bmatrix} V_1(\underline{z}) \\ V_2(\underline{z}) \end{bmatrix} d\underline{z}$$

currents

initial conditions


$$I_1(t) = I_{10} + \frac{L_2}{L_1 L_2 - M^2} \int_{t_0}^t V_1(\underline{z}) d\underline{z} - \frac{M}{L_1 L_2 - M^2} \int_{t_0}^t V_2(\underline{z}) d\underline{z}$$

$$I_2(t) = I_{20} - \frac{M}{L_1 L_2 - M^2} \int_{t_0}^t V_1(\underline{z}) d\underline{z} + \frac{L_1}{L_1 L_2 - M^2} \int_{t_0}^t V_2(\underline{z}) d\underline{z}$$

$$\underline{I} = \underbrace{I_{10} + I_{20}}_{I_0} + \frac{L_1 + L_2 - 2M}{L_1 L_2 - M^2} \int_{t_0}^t V(\underline{z}) d\underline{z}$$

$$L_{eq}^{-1} = \frac{1}{L_{eq}}$$
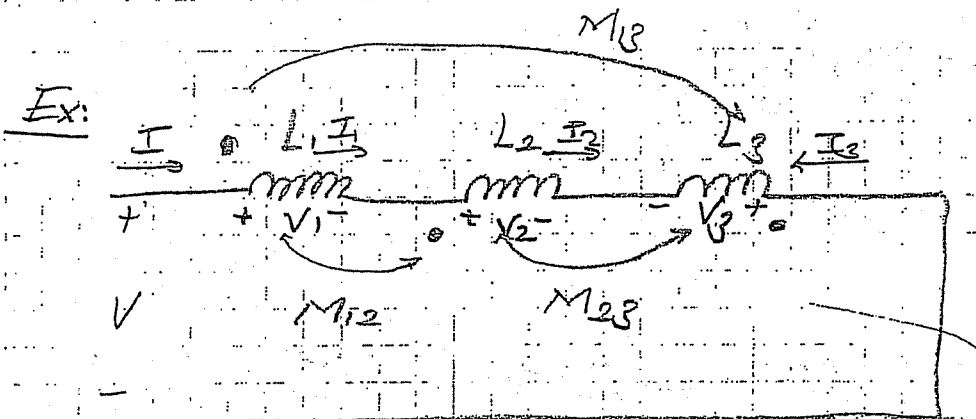
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$



$$\text{Leg } \frac{dI}{dt} = V$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} & M_{13} \\ M_{12} & L_2 & M_{23} \\ M_{13} & M_{23} & L_3 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \\ \frac{dI_3}{dt} \end{bmatrix}$$

$$V = V_1 + V_2 - V_3$$

$$= L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_2}{dt} + M_{13} \frac{dI_3}{dt}$$

$$+ M_{12} \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt} + M_{23} \frac{dI_3}{dt}$$

$$- M_{13} \frac{dI_1}{dt} - M_{23} \frac{dI_2}{dt} - L_3 \frac{dI_3}{dt}$$


$$V = \left( L_1 + M_{12} - M_{13} \right) \frac{dI_1}{dt} + \left( M_{12} + L_2 - M_{23} \right) \frac{dI_2}{dt}$$

$$+ \left( M_{13} + M_{23} - L_3 \right) \frac{dI_3}{dt}$$

$$I_1 = I \quad I_2 = I \quad I_3 = -I$$

$$V = (L_1 + M_{12} - M_{13}) \frac{dI}{dt} + (M_{12} + L_2 - M_{23}) \frac{dI}{dt} + (L_3 - M_{13} - M_{23}) \frac{dI}{dt}$$
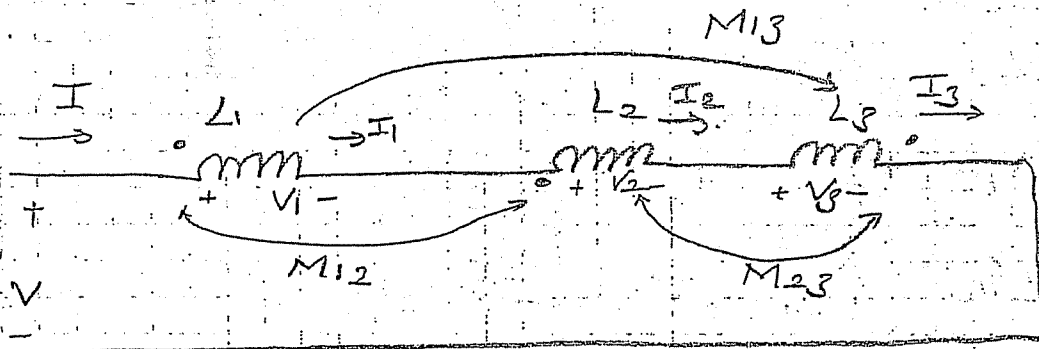
$$V = \underbrace{(L_1 + L_2 + L_3 + 2M_{12} - 2M_{13} - 2M_{23})}_{L_{eq}} \frac{dI}{dt}$$



$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} & -M_{13} \\ M_{12} & L_2 & -M_{23} \\ -M_{13} & -M_{23} & L_3 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \\ \frac{dI_3}{dt} \end{bmatrix}$$


$$V = V_1 + V_2 + V_3 \quad I = I_1 = I_2 = I_3$$

$$V = L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_2}{dt} - M_{13} \frac{dI_3}{dt} + M_{12} \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt} - M_{23} \frac{dI_3}{dt} - M_{13} \frac{dI_1}{dt} - M_{23} \frac{dI_2}{dt} + L_3 \frac{dI_3}{dt}$$

$$V = \left[ L_1 + L_2 + L_3 + 2M_{12} - 2M_{13} - 2M_{23} \right] \frac{dI}{dt}$$

Leg

Power and Energy

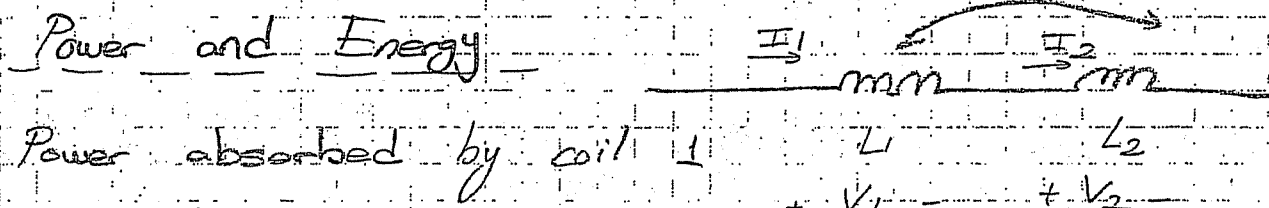

Power absorbed by coil 1

$$P_1(t) = V_1(t) I_1(t)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} \\ M_{12} & L_2 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$

$$P_1(t) = \left( L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_2}{dt} \right) I_1$$

Power absorbed by coil 2

$$P_2(t) = V_2(t) I_2(t) = \left( M_{12} \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt} \right) I_2$$

Total power =  $P_1 + P_2$

$$\begin{aligned} P_1(t) + P_2(t) &= P(t) = L_1 I_1 \frac{dI_1}{dt} + L_2 I_2 \frac{dI_2}{dt} + M_{12} \left( \frac{dI_2}{dt} I_1 + \frac{dI_1}{dt} I_2 \right) \\ &= \frac{d}{dt} \left[ \frac{1}{2} L_1 I_1^2(t) \right] + \frac{d}{dt} \left[ \frac{1}{2} L_2 I_2^2(t) \right] \\ &\quad + M_{12} \frac{d}{dt} \left[ I_1(t) I_2(t) \right] \end{aligned}$$

$$P(t) = \frac{d}{dt} \left[ \frac{1}{2} L_1 I_1^2(t) + \frac{1}{2} L_2 I_2^2(t) \pm M_{12} I_1(t) I_2(t) \right]$$

$W(t; t_0)$  is the stored energy in the coils between time instances starting from  $t_0$  up to  $t$ .

$$W(t; t_0) = \int_{t_0}^t P(t') dt' = \int_{t_0}^t \left[ \frac{d}{dt'} \left[ \frac{1}{2} L_1 I_1^2(t') + \frac{1}{2} L_2 I_2^2(t') \pm M_{12} I_1(t') I_2(t') \right] dt' \right]$$

$$W(t; t_0) = \frac{1}{2} L_1 I_1^2(t) + \frac{1}{2} L_2 I_2^2(t) \pm M_{12} I_1(t) I_2(t)$$

$$- \left[ \frac{1}{2} L_1 I_{10}^2 + \frac{1}{2} L_2 I_{20}^2 \pm M_{12} I_{10} I_{20} \right]$$

$$\left( I_1(t_0) = I_{10} \quad I_2(t_0) = I_{20} \right)$$

Now assume  $I_{10} = 0$   $I_{20} = 0$  (the inductors are initially uncharged)

$$W(t; t_0) = \frac{1}{2} L_1 I_1^2(t) + \frac{1}{2} L_2 I_2^2(t) \pm M_{12} I_1(t) I_2(t)$$

$$W(t; t_0) = \frac{1}{2} \begin{bmatrix} I_1(t) & I_2(t) \end{bmatrix} \begin{bmatrix} L_1 & M_{12} \\ M_{12} & L_2 \end{bmatrix} \begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix}$$

$$W(t; t_0) = \frac{1}{2} \underline{I}^T(t) \underline{L} \underline{I}(t)$$

\* The coupled inductor is passive element

$$\iff W(t) \geq 0$$

$\Rightarrow \underline{L}$  should be positive semi-definite

$$\begin{bmatrix} L_1 & M_{12} \\ M_{12} & L_2 \end{bmatrix} \quad \begin{array}{l} L_1 \geq 0 \\ L_2 \geq 0 \\ \det = L_1 L_2 - M_{12}^2 \geq 0 \end{array} \quad L_1 L_2 \geq M_{12}^2$$

Coupling coefficient  $k = \frac{M_{12}}{\sqrt{L_1 L_2}} \leq 1$

if  $M_{12} = 0 \Rightarrow k = 0$  (the coupling between the coils is zero)


if  $k = 1$  (perfect coupling)  $M_{12}^2 = L_1 L_2$   $\det = L_1 L_2 - M_{12}^2 = 0$

$\Rightarrow \underline{L}$  matrix =  $\begin{bmatrix} L_1 & M_{12} \\ M_{12} & L_2 \end{bmatrix}$  is singular


$$\det[\underline{L}] = 0$$



## Ideal Transformers:

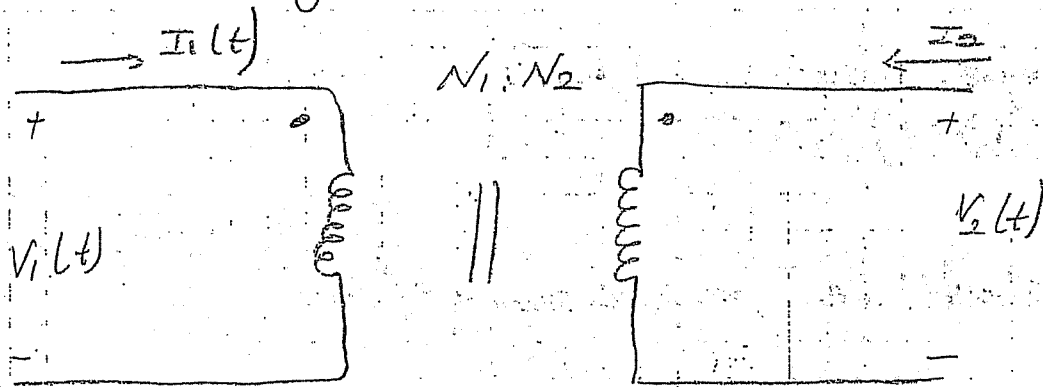

4 terminal, 2 branches

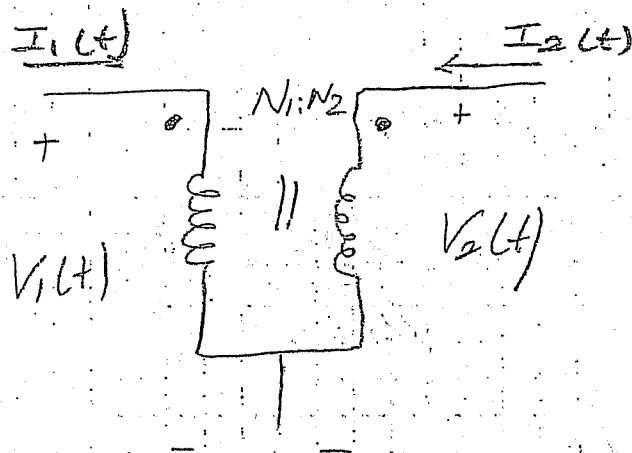

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = n = \text{turn ratio}$$

$N_1$ : # of primary turns

$N_2$ : # of secondary turns

$$I_1 N_1 + I_2 N_2 = 0$$

$$\frac{I_1}{I_2} = -\frac{N_2}{N_1}$$


Ideal transformers

① No losses (no core loss; no winding loss, leakage loss)


②  $\mu \rightarrow \infty$  (the magnetic element core is made of <sup>is made of</sup> should confine the total flux in the core only)

③  $k=1$  (perfect coupling between the coupled inductors)

Ex:  $\frac{I_1}{I_2}$

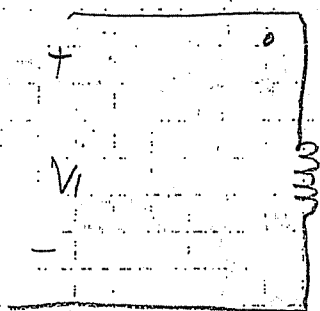


$n:1$

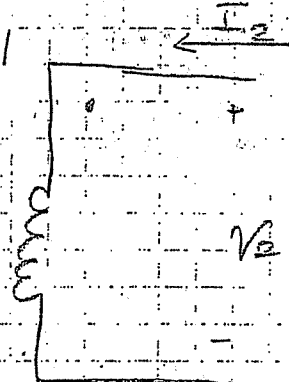


$L_1$   $L_2$

$$\frac{V_1}{V_2} = n \quad \frac{I_1}{I_2} = \frac{1}{n}$$

Ex:

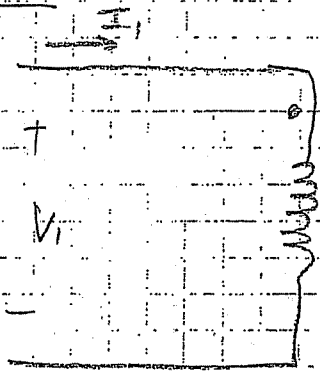


$n:1$

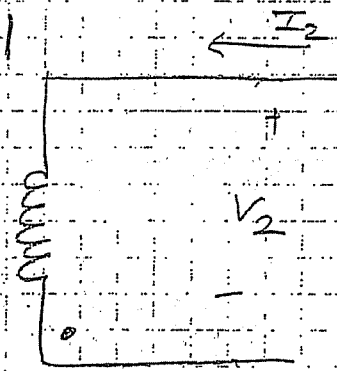


$$\frac{V_1}{V_2} = n$$

$$\frac{I_1}{I_2} = \frac{1}{n}$$

Ex:  $\frac{I_1}{I_2}$

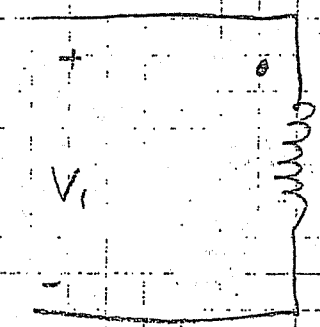

$n:1$

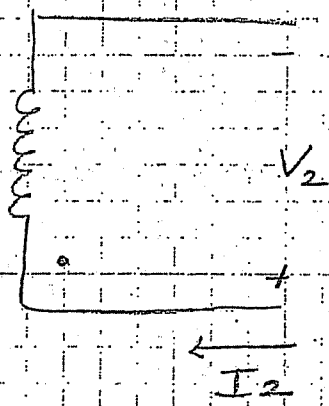

$$\frac{V_1}{V_2} = n$$

$$\frac{I_1}{I_2} = -\frac{1}{n}$$

$n > 1$      $|V_1| > |V_2|$     step down transformer  
 primary voltage high  
 " current low

$n < 1$      $|V_1| < |V_2|$     step up transformer  
 primary voltage low  
 " current high

\* Transformers are used by AC signals.


$$P_1(t) \text{ (primary power)} = V_1(t) I_1(t)$$

$$P_2(t) \text{ (secondary ")} = V_2(t) I_2(t) = \frac{V_1}{n} (-n I_1)$$

$$= -V_1 I_1$$

$$P(t) = P_1(t) + P_2(t) = 0 \quad \left( \begin{array}{l} \text{no power dissipation} \\ \text{" " storage} \end{array} \right)$$

Equivalent input resistance:

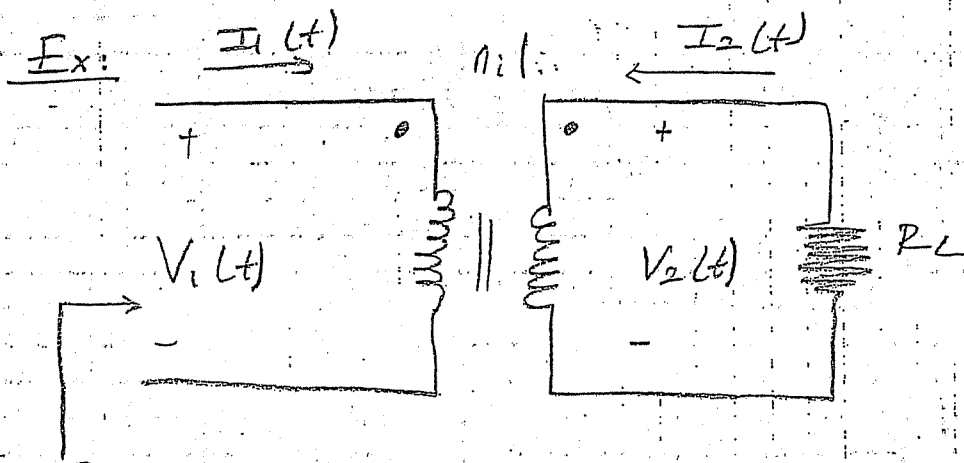

Req

$$V_1 = n V_2$$

$$I_1 = -\frac{1}{n} I_2 \Rightarrow I_2 = -n I_1$$


$$R_L I_2 = -V_2 \Rightarrow V_2 = -R_L I_2$$

$$V_1 = n V_2 = n [-R_L I_2]$$

$$V_1 = -n R_L I_2$$

$$V_1 = -n R_L (-n I_1) = n^2 R_L I_1$$

$$R_{eq} = \frac{V_1}{I_1} = n^2 R_L$$

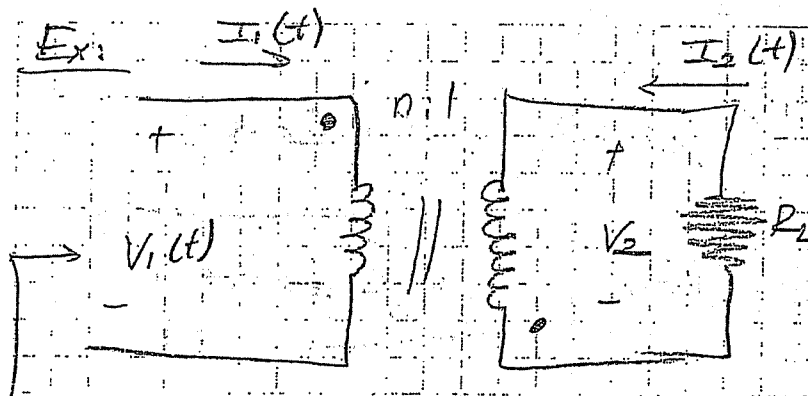

Req

$$V_1 = -n V_2$$


$$I_1 = \frac{1}{n} I_2$$

$$\frac{V_2}{R_L} = -I_2$$



$$V_1 = -n (-I_2 R_L) = -n (-\frac{1}{n} I_1 R_L) = I_1 R_L$$

$$R_{eq} = \frac{V}{I_1} = R_L$$

Ex:

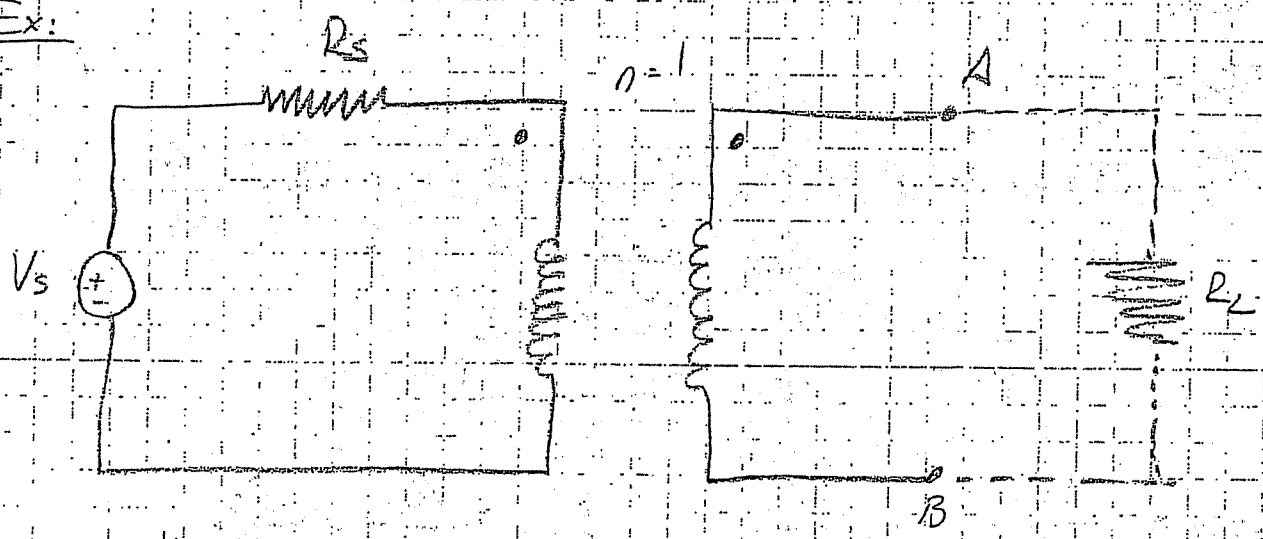

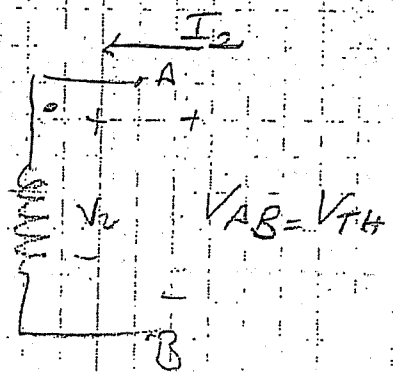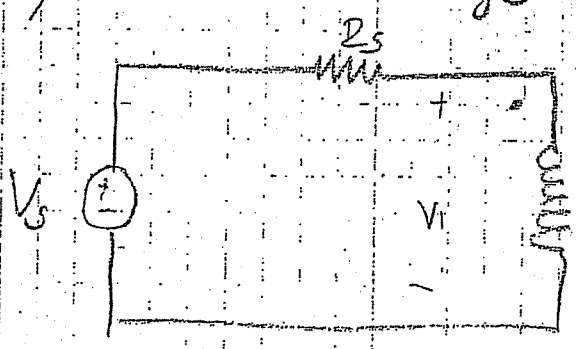Find thevenin equivalent circuit between A-B  
open circuit voltage



$$I_2 = 0$$

$$I_1 = -\frac{1}{n} I_2 = 0$$

$$V_1 = nV_2$$


$$V_s = V_1 + R_s I_1 = V_1 + R_s \cdot 0$$

$$V_s = V_1$$

$$\frac{V_1}{n} = V_2 = \frac{V_s}{n} = V_{AB} = V_{TH}$$

$$\boxed{\frac{V_s}{n} = V_{TH}}$$

short circuit current  $I_N$

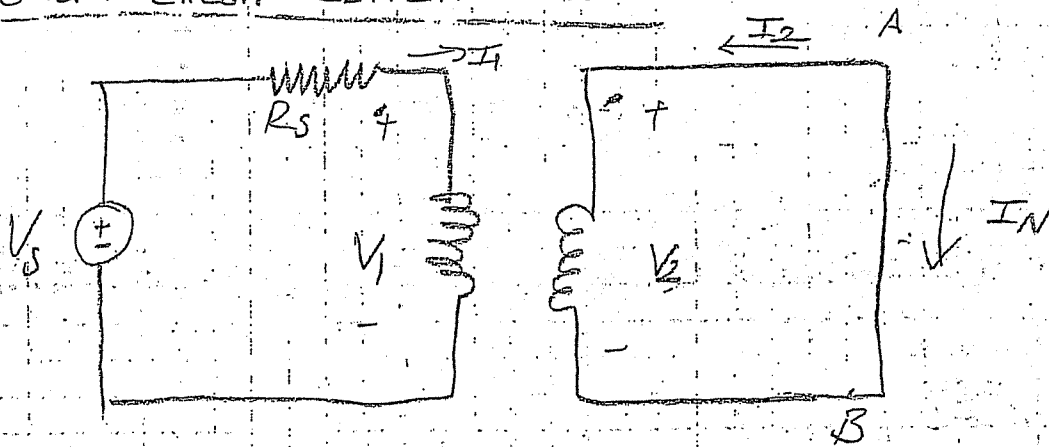


$$V_2 = 0 \quad V_1 = nV_2 = 0$$

$$I_2 = -n I_1$$


$$V_s = I_1 R_s + V_1 = I_1 R_s + 0 \Rightarrow I_1 = \frac{V_s}{R_s}$$

$$I_2 = -n \frac{V_s}{R_s} \quad \boxed{I_N = n \frac{V_s}{R_s}}$$


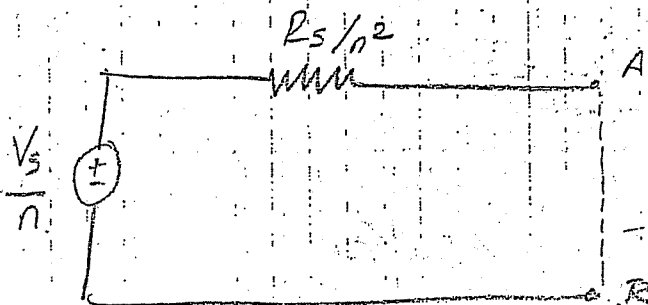
$$R_{TH} = \frac{V_{TH}}{I_N} = \frac{V_s/n}{n V_s/R_s} = \frac{V_s}{n} \cdot \frac{R_s}{n V_s} = \frac{R_s}{n^2}$$



Ex:

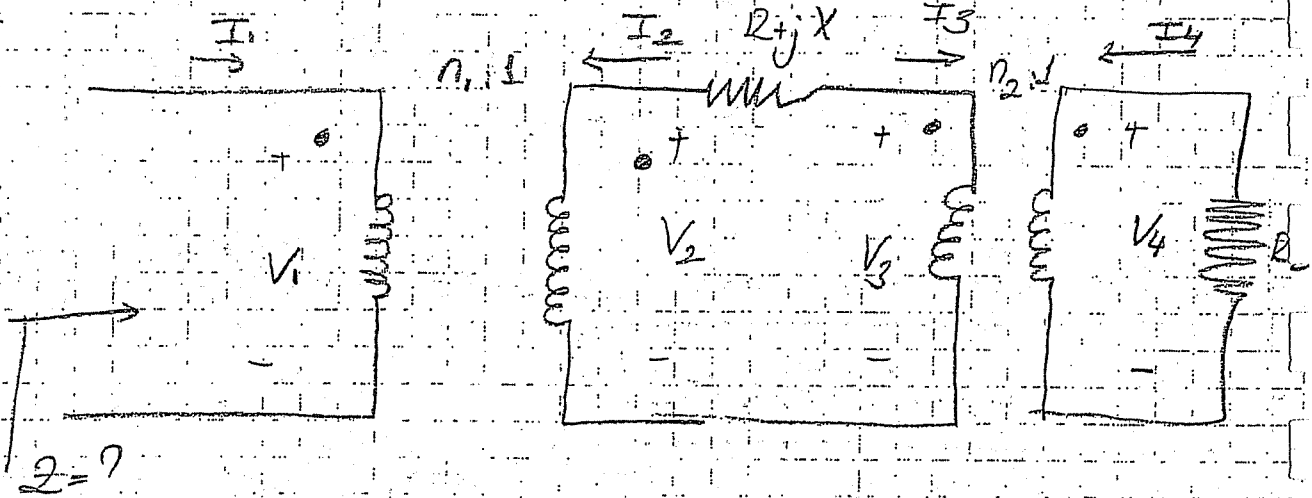

$$Z = (n_2^2 R_L + R + jX) n_1^2$$

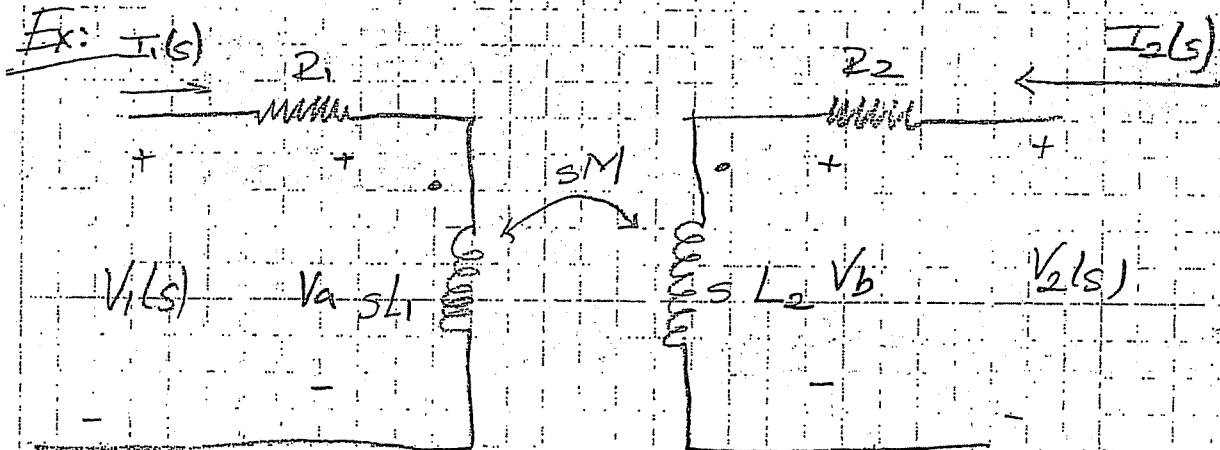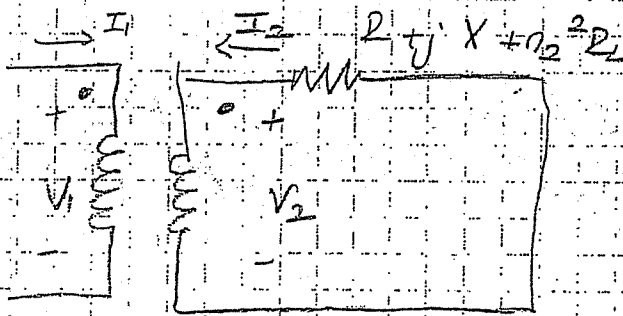

Find ABCD parameters in Laplace domain

$$\begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} sL_1 & sM \\ sM & sL_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = V_a + I_1 R_1 \Rightarrow V_1 = sL_1 I_1 + sM I_2 + I_1 R_1$$

$$V_1 = [R_1 + sL_1] I_1 + sM I_2$$

$$V_2 = V_b + R_2 I_2 \Rightarrow V_2 = sL_2 I_2 + sM I_1 + I_2 R_2$$

$$V_2 = [R_2 + sL_2] I_2 + sM I_1$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{(R_1 + sL_1) I_1}{sM I_1} = \frac{R_1 + sL_1}{sM}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad V_2=0 = (R_2 + sL_2) I_2 + sM I_1$$


$$I_1 = \frac{-(sL_2 + R_2) I_2}{sM}$$

$$V_1 = \frac{-[R_1 + sL_1] (sL_2 + R_2) I_2}{sM} + sM I_2$$

$$V_1 = \left[ \frac{-[R_1 + sL_1] [sL_2 + R_2]}{sM} + sM \right] I_2$$


$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = \left[ \frac{+[R_1 + sL_1] [sL_2 + R_2]}{sM} - sM \right] \quad \begin{matrix} C=? \\ D=? \end{matrix}$$

Cascade Connection and Loading:

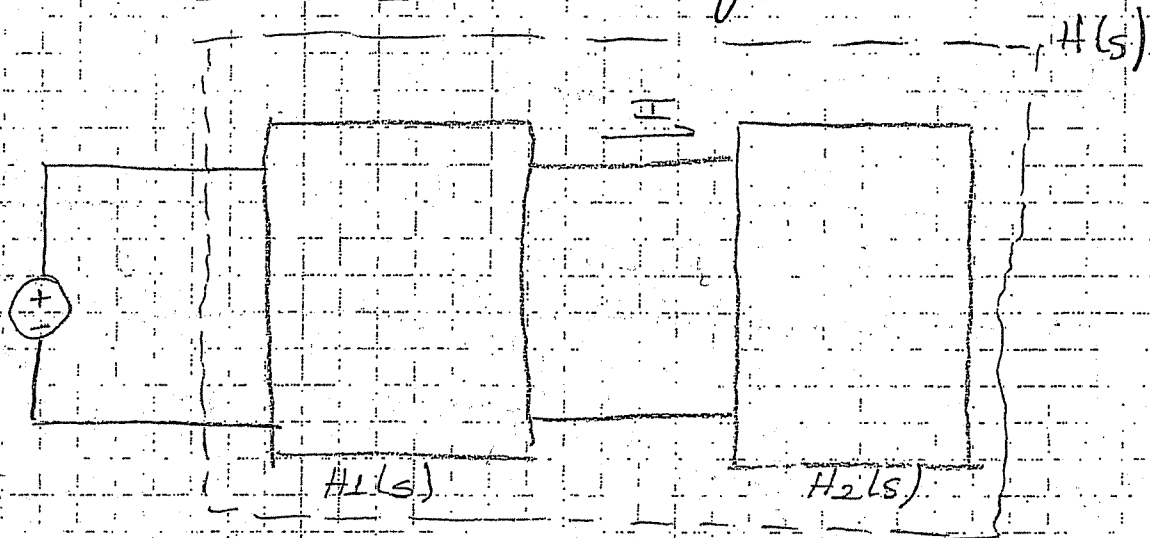

if  $I=0$  there is no loading and


$$H(s) = H_1(s) * H_2(s)$$

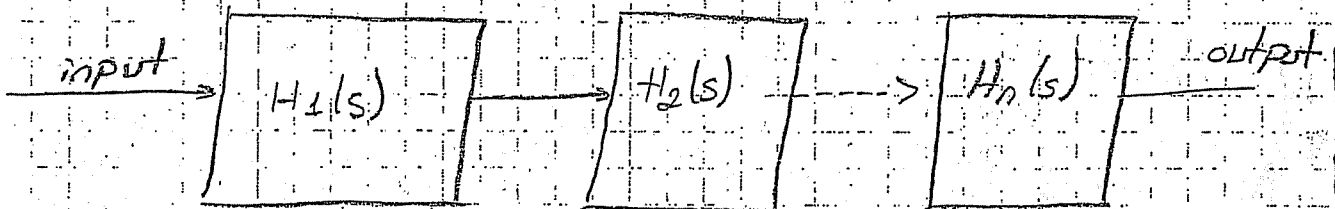

$$H_n(s) = H_1(s) H_2(s) \dots H_n(s)$$

(Assuming that no loading effect is observed between the stages)

When does loading occurs or not occurs?

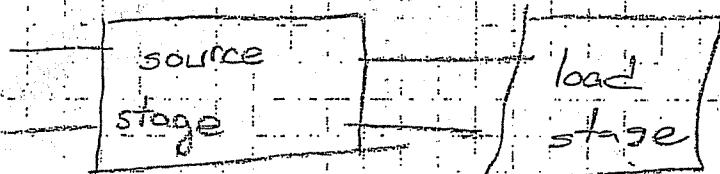




(a)  $Z_{TH} = 0$  for source stage


(input impedance = 0)

(b)  $Z_{in} = \infty$  for load stage

Ex:

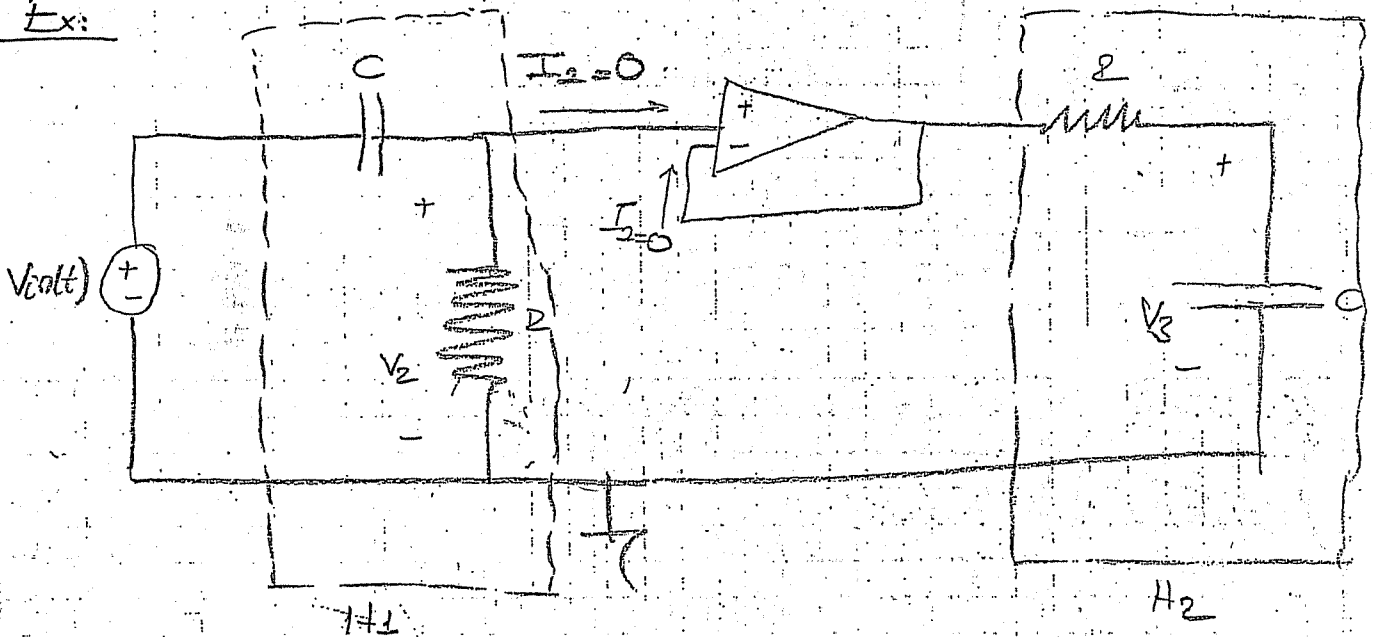

$$H_1 = \frac{V_2(s)}{V_{in}(s)}$$

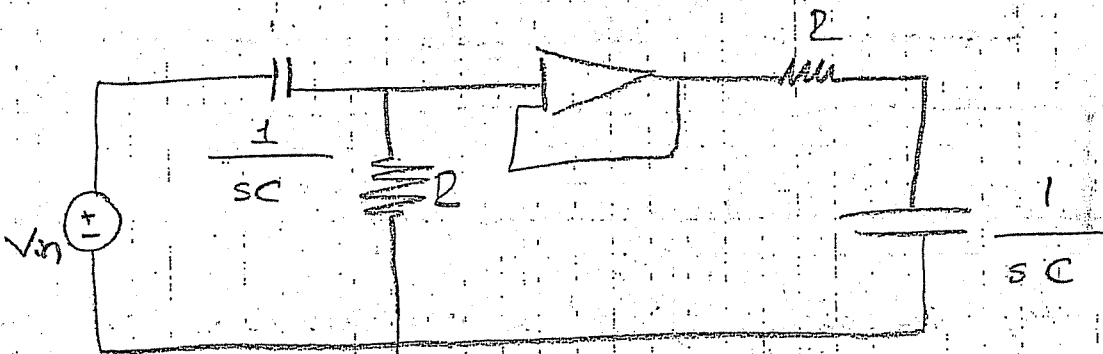

$$H_1 = \frac{R}{\frac{1}{sC} + R} = \frac{R s C}{1 + R s C}$$


(high pass)

$$H_2 = \frac{V_2(s)}{V_2(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{sRC + 1}$$

(low pass)

$$\frac{V_3}{V_{in}} = H_1(s) \cdot H_2(s) = \frac{R \cdot sC}{1 + sRC} \cdot \frac{1}{1 + sRC} = \frac{sRC}{s^2 RC^2 + 2sRC + 1}$$

(bandpass)  
(no loading)

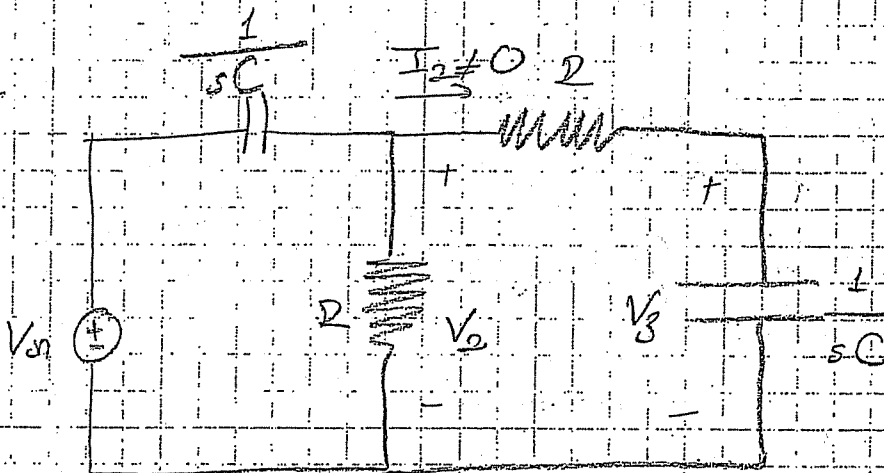

$$\frac{V_{in} - V_2}{\frac{1}{sC}} = \frac{V_2}{R} + \frac{V_2}{R + \frac{1}{sC}}$$

$$\frac{V_2 - V_3}{R} = \frac{V_3}{\frac{1}{sC}}$$


$$H(s) = \frac{V_3}{V_{in}} = \frac{RCs}{s^2 RC^2 + 3sRC + 1}$$

(loading effect is observed)


$H(s) \neq H_1(s) \cdot H_2(s)$

$H(s) \approx H_1(s) \cdot H_2(s)$

Ex:

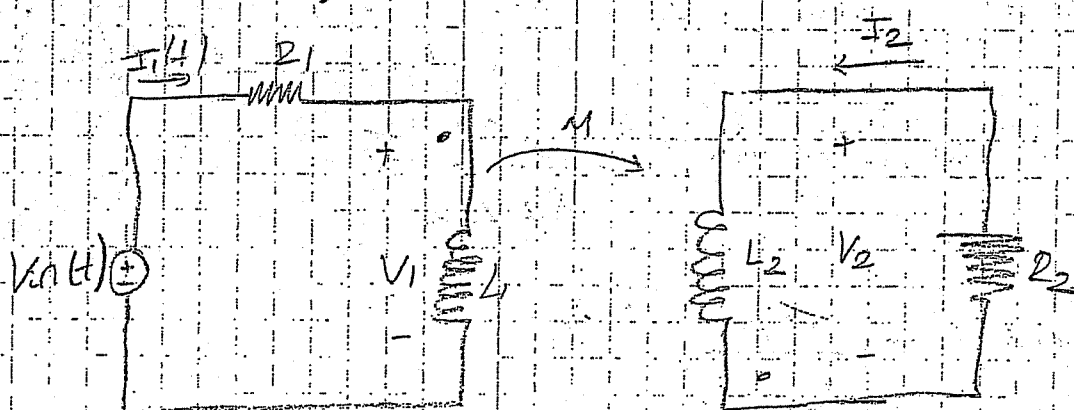
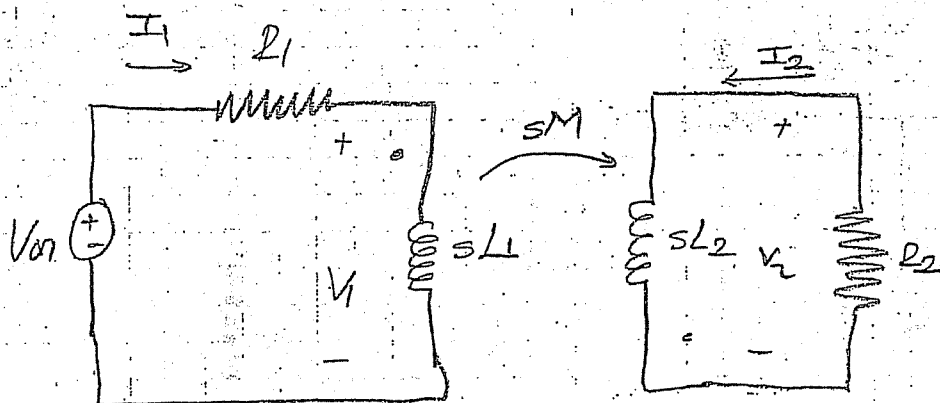
$$Z_{in}(s) = \frac{V_{in}(s)}{I_1(s)} = \text{Driving point impedance (input " " " )}$$



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} sL_1 & -sM \\ -sM & sL_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_{in} = R_1 I_1 + V_1 = R_1 I_1 + sL_1 I_1 - sM I_2$$

$$V_2 = -sM I_1 + sL_2 I_2$$

$$V_2 = R_2 (-I_2)$$

$$-R_2 I_2 = -sM I_1 + sL_2 I_2$$


$$sM I_1 = [R_2 + sL_2] I_2 \Rightarrow \boxed{I_2 = \frac{sM}{R_2 + sL_2} I_1}$$

$$V_{in} = [R_1 + sL_1] I_1 - sM \frac{sM}{R_2 + sL_2} I_1$$


$$V_{in} = \left[ R_1 + sL_1 - \frac{s^2 M^2}{R_2 + sL_2} \right] I_1$$

$$\frac{V_{in}}{I_1} = \frac{[R_1 + sL_1 - \frac{s^2 M^2}{R_2 + sL_2}]}{I_1} = R_1 + sL_1 - \frac{s^2 M^2}{R_2 + sL_2}$$


Poly-phase circuits:

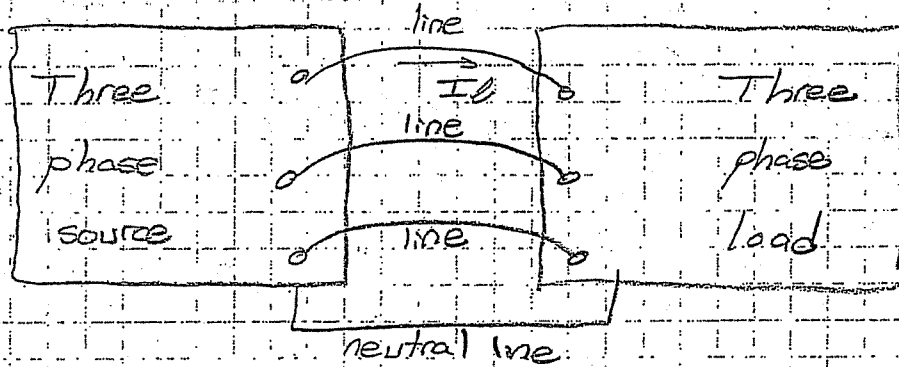

$I_L \rightarrow$  Line current

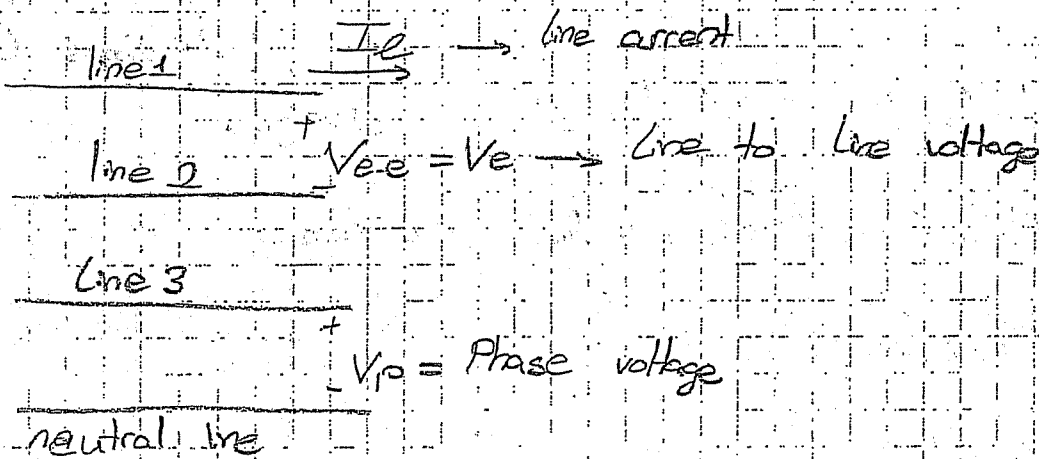

\* A balanced three phase voltage is the one which the phase currents or the voltages have equal magnitudes with phase difference of  $120^\circ$ . Source or load sides of the system can be configured to have  $\Delta$  or  $Y$  connection

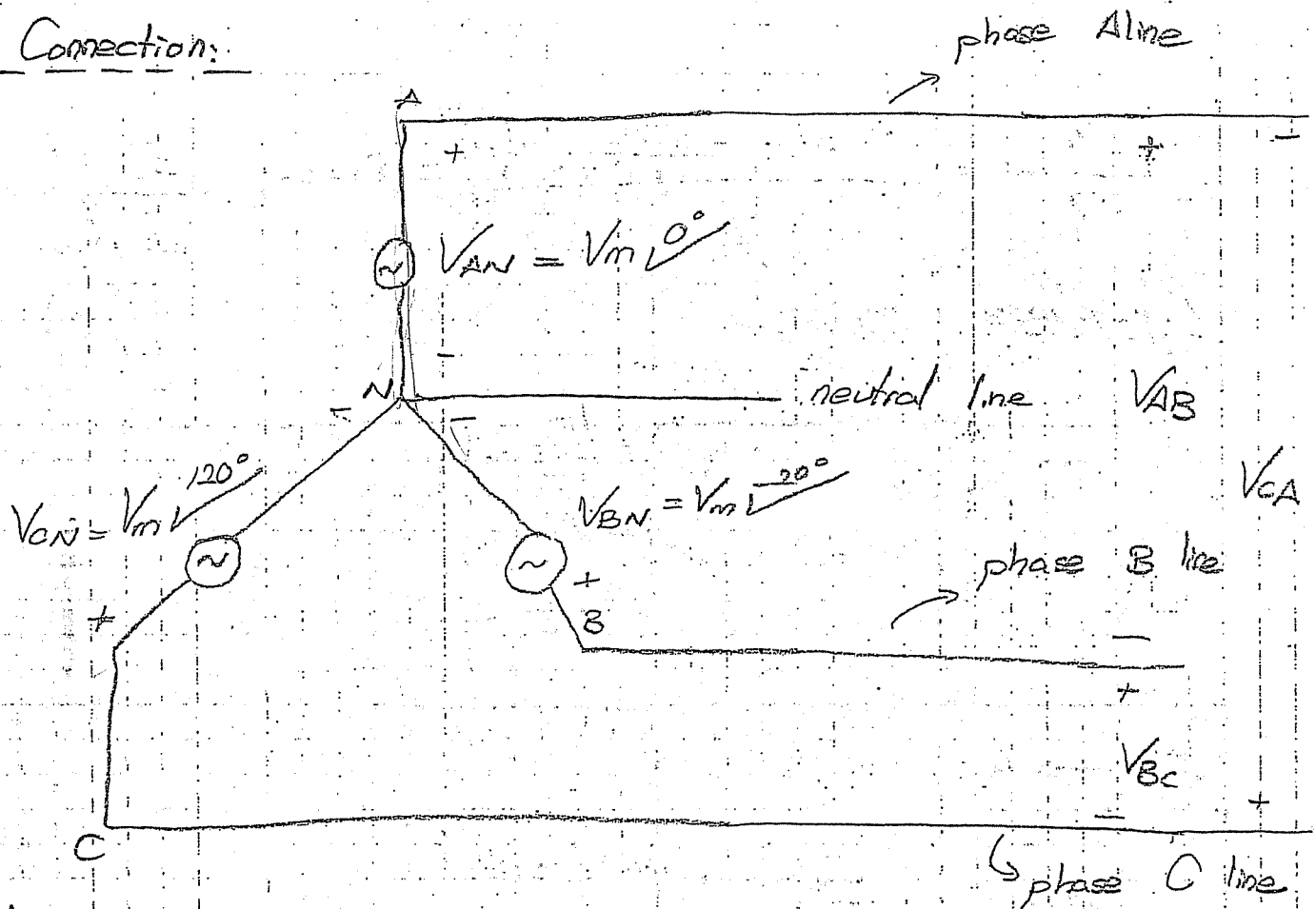Y Connection:

$$|V_{AN}| = |V_{BN}| = |V_{CN}| = \text{phase voltages}$$

$$|V_{AB}| = |V_{BC}| = |V_{CA}| = \text{line voltages}$$

$$V_{AN} = V_m \angle 0^\circ$$

$$V_{line} = \sqrt{3} V_{phase}$$


$$V_{BN} = V_m \angle -120^\circ$$

$$V_{CN} = V_m \angle 120^\circ$$

$$V_{AN} + V_{BN} + V_{CN} = 0 + j0 = 0$$

(for balance 3 phase system)

$$3 \text{ phase} = 3 \phi$$

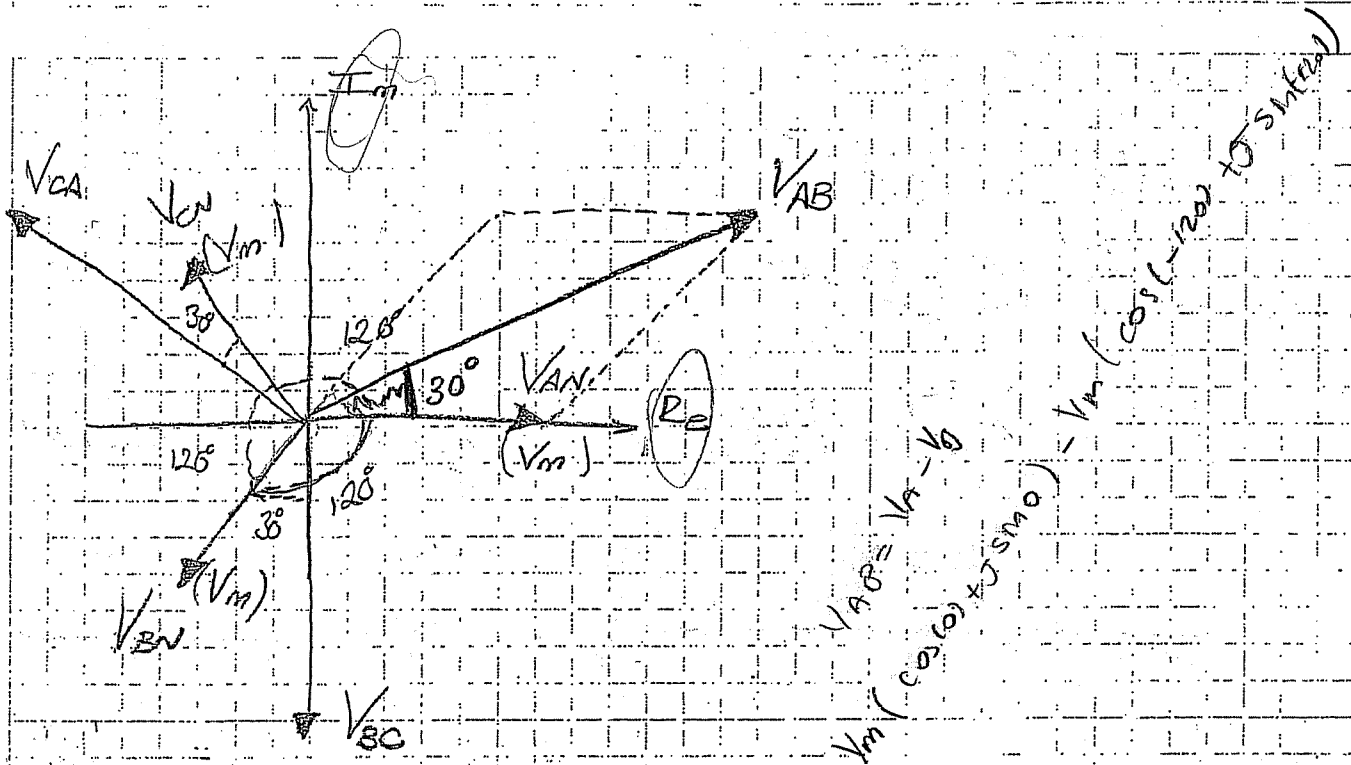

phase sequence

$V_{AN}, V_{BN}, V_{CN}$  line to neutral (phase) voltages

$V_{AB}, V_{BC}, V_{CA}$  line to line voltages

$$\begin{aligned}
 V_{AB} &= -V_A - V_B = V_m \angle 0^\circ - V_m \angle 120^\circ \\
 &= V_m (\cos 0 + j \sin 0) - V_m (\cos 120 + j \sin 120) \\
 &= V_m - V_m \left[ -\frac{1}{2} + j \frac{\sqrt{3}}{2} \right] \\
 &= V_m + \frac{V_m}{2} + \frac{V_m \sqrt{3}}{2} j \\
 &= \frac{3}{2} V_m + \frac{\sqrt{3}}{2} V_m j
 \end{aligned}$$

$$\text{angle } \theta = \frac{\frac{\sqrt{3}}{2}}{\frac{3}{2}} = \frac{1}{\sqrt{3}} \Rightarrow \theta = 30^\circ$$


$$\text{mag} = \sqrt{\left(\frac{3}{2} V_m\right)^2 + \left(\frac{\sqrt{3}}{2} V_m\right)^2} = \sqrt{3} V_m$$

$$V_{AB} = \sqrt{3} V_m \angle 30^\circ$$

$$V_{CA} = \sqrt{3} V_m \angle 150^\circ$$

$$V_{BC} = \sqrt{3} V_m \angle -90^\circ$$

$$|V_{AB}| = |V_{CA}| = |V_{BC}| = |V_{line}| = |V_{line-line}|$$

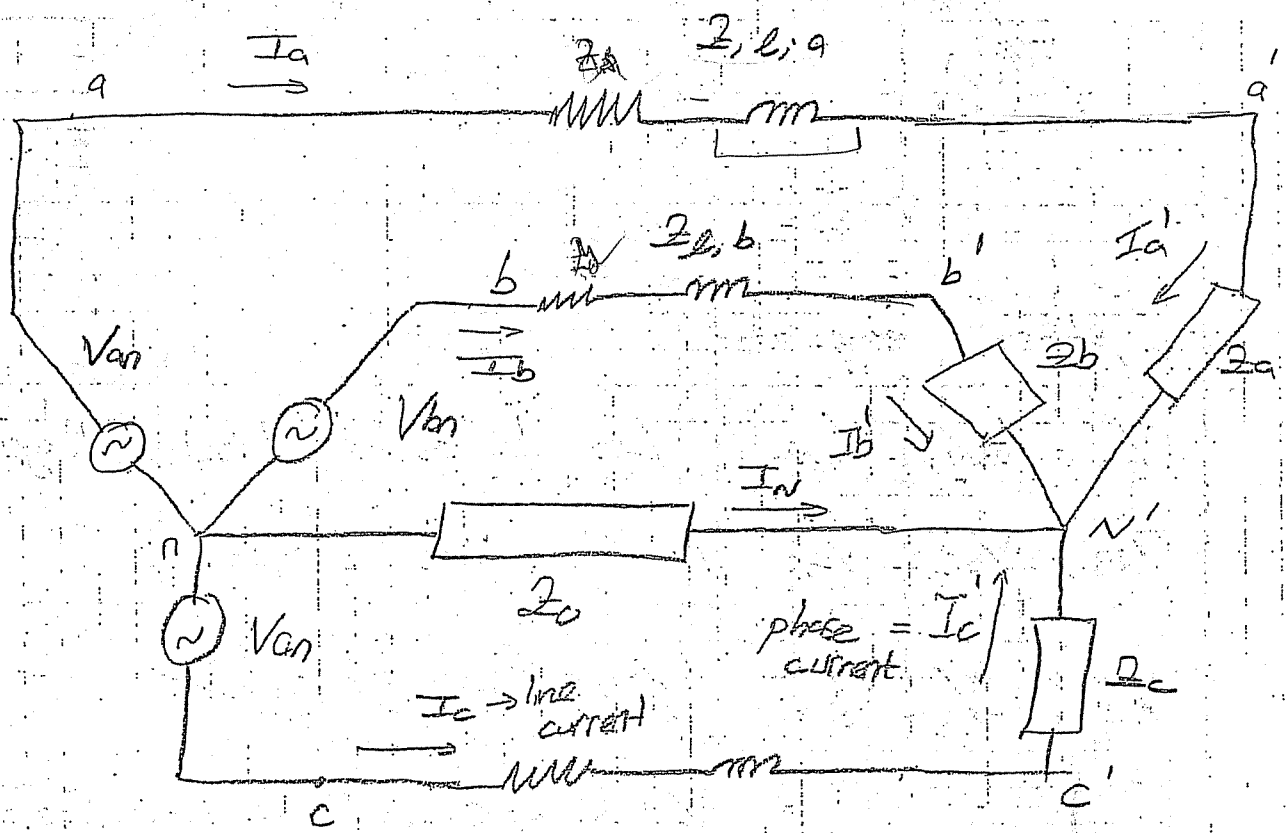

$Z_{la}$ ;  $Z_{lb}$ ;  $Z_{lc}$  → transmission line impedances

To have a balanced 3 $\phi$  system

①  $|V_{an}| = |V_{bn}| = |V_{cn}|$  and they should form a balanced 3 $\phi$  source configuration

② Transmission lines should be balanced

$$Z_{la} = Z_{lb} = Z_{lc}$$

③ load should be balanced

$$Z_a = Z_b = Z_c$$

\* If this system is balanced; all phase currents are equal in magnitude with  $120^\circ$  phase difference

$$|I_a| = |I_b| = |I_c| \rightarrow \text{line current}$$

$$|I_a'| = |I_b'| = |I_c'| \rightarrow \text{phase current}$$

$$|I_a| = |I_a'|$$

$$I_a + I_b + I_c = I_N$$

$$\frac{V_{an}}{Z_a + Z_a} + \frac{V_{bn}}{Z_b + Z_b} + \frac{V_{cn}}{Z_c + Z_c} = I_N$$

$$Z = Z_a + Z_a = Z_b + Z_b = Z_c + Z_c$$


$$\Rightarrow \frac{V_{an}}{Z} + \frac{V_{bn}}{Z} + \frac{V_{cn}}{Z} = I_N$$

$$\frac{1}{Z} \left[ \underbrace{V_{an} + V_{bn} + V_{cn}}_0 \right] = I_N = 0$$


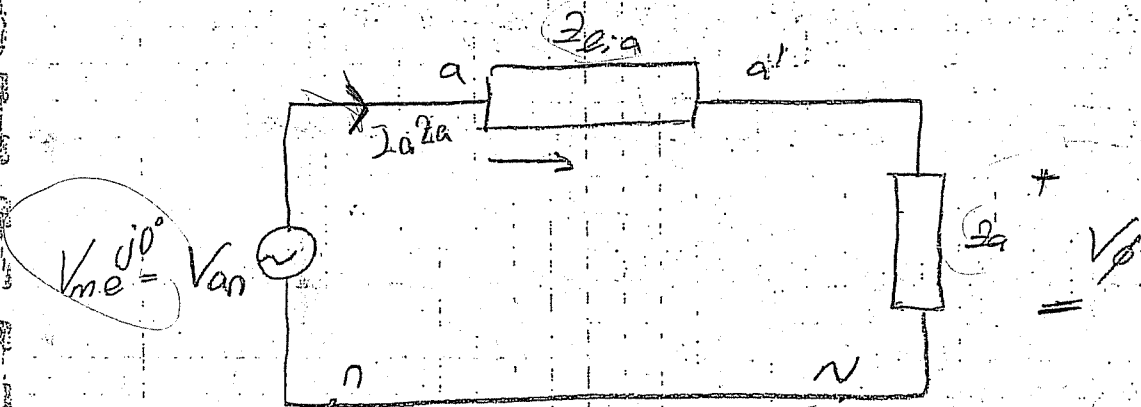
## Single Phase Approach

For a balanced Y-Y connected system; we need to consider only one phase circuit to find all the currents and voltages.



$$I_a = \frac{V_m e^{j0^\circ}}{Z_{l,a} + Z_a} \quad \text{Line current}$$

$$V_\phi = I_a Z_a = V_m e^{j0^\circ} \frac{Z_a}{Z_a + Z_{l,a}}$$

phase voltage

$$|V_{line-line}| = \sqrt{3} |V_\phi|$$

Let  $V_\phi = V_{an}$  as the reference

$$V_{a'n} = V_\phi \angle 0^\circ$$

$$V_{a'b'} = \sqrt{3} V_\phi \angle 30^\circ$$

$$V_{b'c'} = \sqrt{3} V_\phi \angle -90^\circ$$

$$V_{c'a'} = \sqrt{3} V_\phi \angle 150^\circ$$

line voltages  
at the load  
side

Power (assuming RMS values)

$$P_p = \operatorname{Re} \{ V_p I_a^* \} = \operatorname{Re} \{ Z_a I_a I_a^* \}$$

Average power for a single phase of the load

$$= |I_a|^2 \operatorname{Re} \{ Z_a \}$$

$$Q_p = \operatorname{Im} \{ V_p I_a^* \} = \operatorname{Im} \{ Z_a I_a I_a^* \}$$

Reactive power for a single phase at the load

$$= |I_a|^2 \operatorname{Im} \{ Z_a \}$$

$$|S_{pt}| = |V_p| |I_a|$$

$$S_p = P_p + j Q_p$$

↳ apparent power

overall average power at load is


$$P_{\text{total}} = 3 P_p \text{ (phase power)}$$

$$P_{\text{total}} = P_{3\phi} = 3 |I_a|^2 \operatorname{Re} \{ Z_a \}$$

$$Q_{\text{total}} = Q_{3\phi} = 3 |I_a|^2 \operatorname{Im} \{ Z_a \}$$


$$|S_{3\phi}| = |S_{\text{total}}| = 3 |I_a| |V_p|$$

Ex:

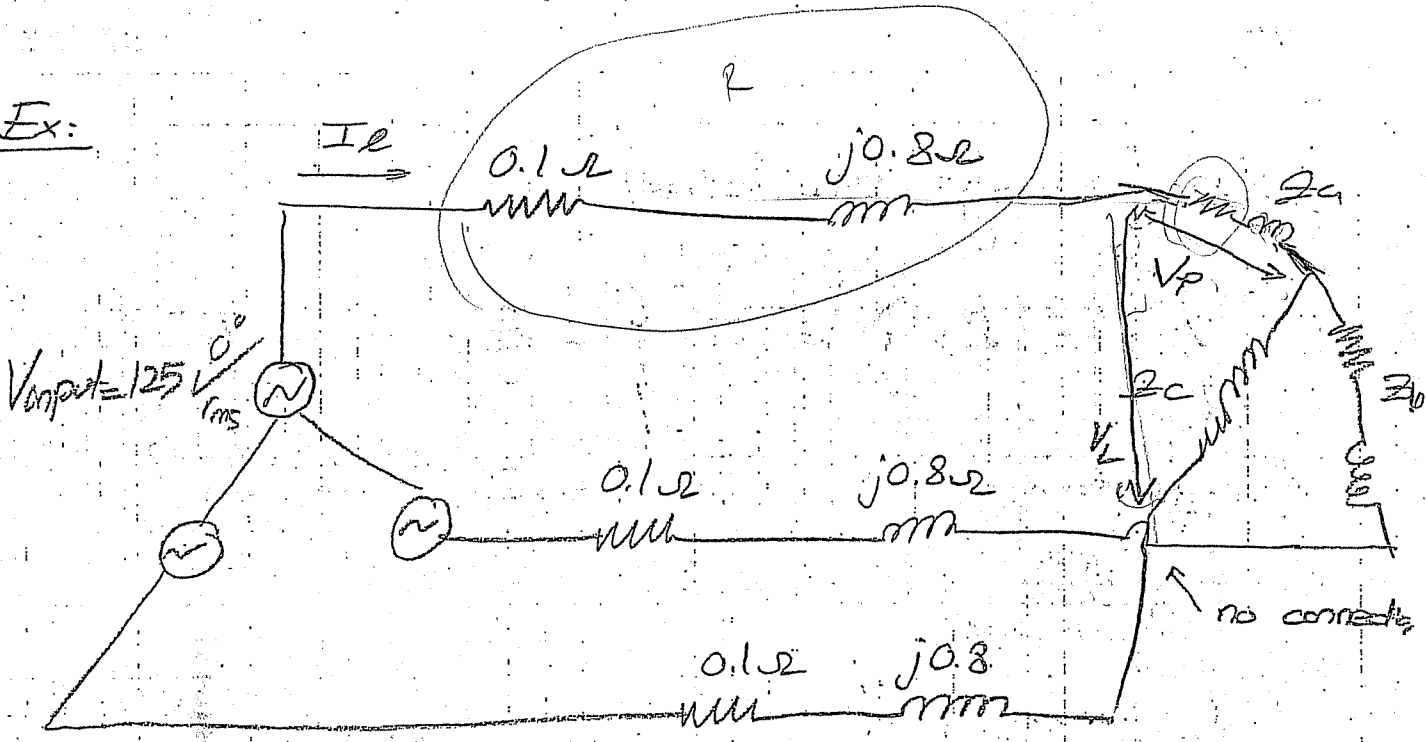

$$Z_a = Z_b = Z_c = [9.9 + j14.2] \Omega$$

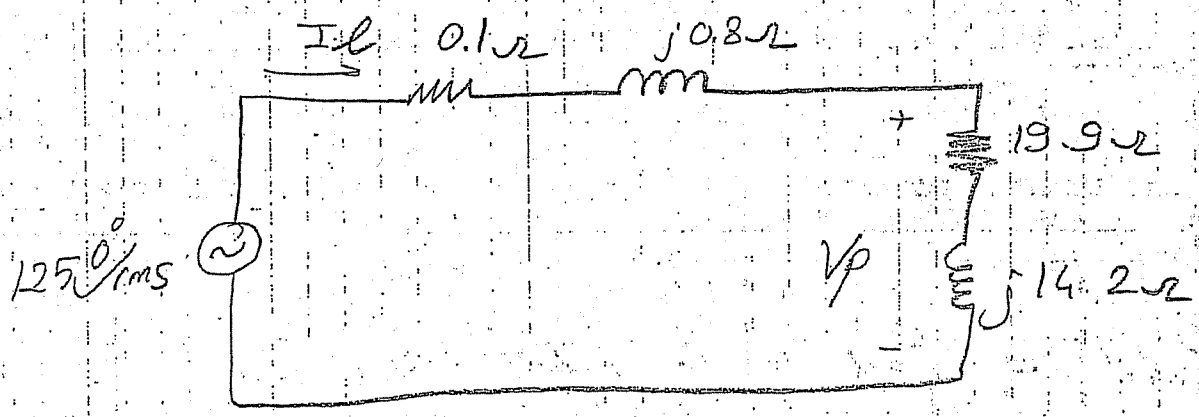- (a) Find  $I_L$ ,  $V_L$ ,  $V_o$  at load side
  - (b) Find the total 3 $\phi$  average and reactive absorbed at the load
- Use single phase approach.



$$I_L = \frac{125 \angle 0^\circ}{0.1 + j0.8 + 19.9 + j14.2} = \frac{125 (\cos 0 + j \sin 0)}{20 + 15j}$$

$$= \frac{125}{20 + 15j} = \frac{25}{4 + 3j} = \frac{100 - 75j}{16 + 9} = \frac{100 - 75j}{25} = 4 - 3j$$

$$I_L = 4 - 3j = 5 \angle -37^\circ \text{ Amper (rms)}$$

$$V_p = I_L (19.9 + j14.2)$$

$$V_p = 5 \angle -37^\circ [19.9 + j14.2] = 122.2 \angle -1.5^\circ \text{ Volt (rms)}$$

$$V_L = \sqrt{3} |V_p| = 211.7 \text{ Volt (rms)}$$

$$\begin{aligned} \text{(b) } P_{3\phi} &= 3 |I_L|^2 \operatorname{Re} \{ Z_a \} = 3 \{ 33.6 + 56.8j \} = 122.2 - 2.3j \\ \downarrow \\ \text{load} &= 3 / 5^2 (19.9) \text{ Watt} \end{aligned}$$

$$\begin{aligned} Q_{3\phi} &= 3 |I_L|^2 \operatorname{Im} \{ Z_a \} \\ \downarrow \\ \text{load} &= 3 / 5^2 (14.2) \text{ VAR} \end{aligned}$$

\* For a balanced three phase system, total instantaneous power is constant and it is = 3 \* average power per phase

$$\left. \begin{array}{l} V_a(t); I_a(t) \\ V_b(t); I_b(t) \\ V_c(t); I_c(t) \end{array} \right\} \text{ instantaneous values}$$

$$P(t) = P_1(t) + P_2(t) + P_3(t)$$

instantaneous power =  $V_1(t) I_1(t) + V_2(t) I_2(t) + V_3(t) I_3(t)$


$$P_T = 3 V_p I_p \cos \theta = 3 * P_p$$

↓  
Total average power

$$P_T = P(t)$$

HOMEWORK  
Show that

Δ - Connection:

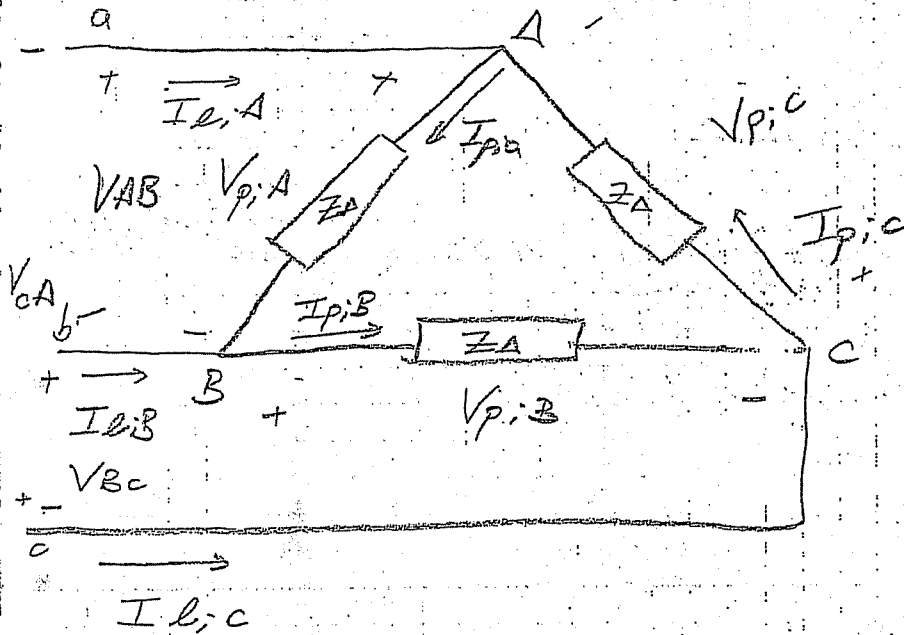

When the load side is balanced

$$Z_A = 3 Z_x$$

$$\left. \begin{aligned} V_{ab} &= V_{p;A} \\ V_{bc} &= V_{p;B} \\ V_{ca} &= V_{p;C} \end{aligned} \right\} \begin{array}{l} \text{line and phase} \\ \text{voltages are} \\ \text{equal} \end{array}$$

The phase currents

$$I_{p;A} = I_\phi \angle 0^\circ$$

$$I_{p;B} = I_\phi \angle -120^\circ$$

$$I_{p;C} = I_\phi \angle +120^\circ$$

The line currents

$$\begin{aligned} I_{L;A} &= I_{p;A} - I_{p;C} \\ &= I_\phi \angle 0^\circ - I_\phi \angle 120^\circ \\ &= \sqrt{3} I_\phi \angle -30^\circ \end{aligned}$$


$$I_{L;B} = \sqrt{3} I_\phi \angle -150^\circ$$

$$I_{L;C} = \sqrt{3} I_\phi \angle 90^\circ$$

$$|I_{e,A}| = |I_{e,B}| = |I_{e,C}| = |I_{line}|$$

$$|I_{p,A}| = |I_{p,B}| = |I_{p,C}| = |I_{phase}|$$

$$|I_{line}| = \sqrt{3} |I_{phase}|$$

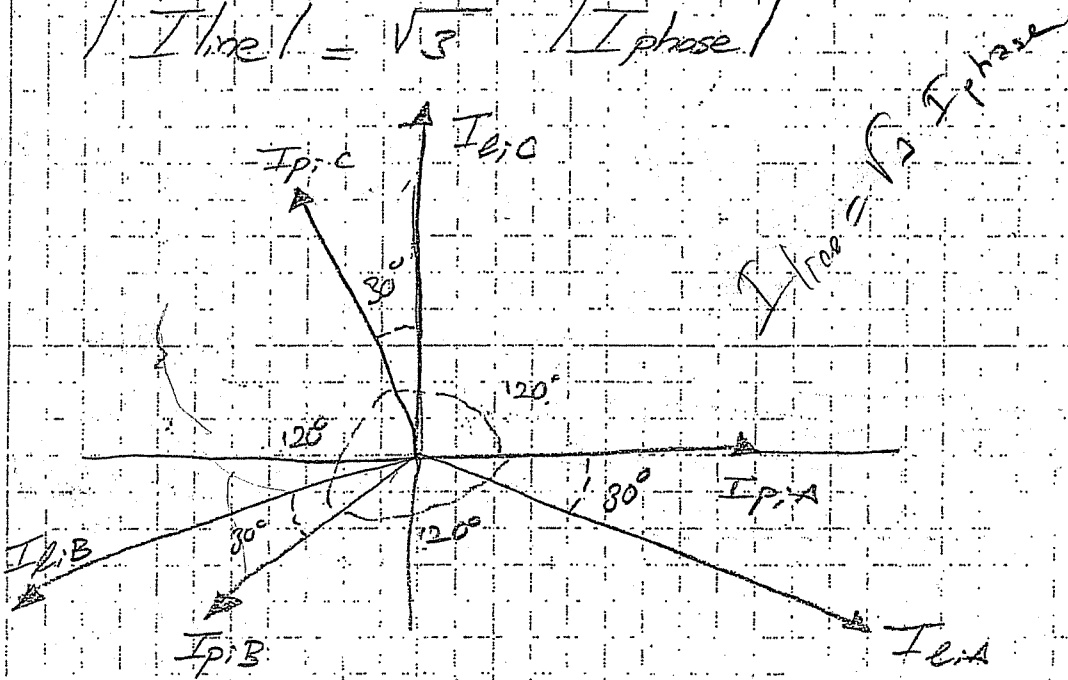

### Complex Power:

$$S_1 = V_{ab} I_{p,A}^*$$

$$= |V_{line}| |I_{phase}| \quad \checkmark \quad \text{rms value}$$

$$S_2 = V_{bc} I_{p,B}^*$$

$$S_3 = V_{ca} I_{p,C}^*$$


$$S_T = S_1 + S_2 + S_3 = 3 |V_{line}| |I_{phase}| \quad \checkmark$$

$$S_{total} = 3 |V_{line}| |I_{phase}| \quad \checkmark$$

$$S_{total} = \sqrt{3} |V_{line}| |I_{line}| \quad \checkmark$$

$$\left. \begin{array}{l} \Delta \text{ Connection} \\ |V_{line}| = |V_{phase}| \\ |I_{phase}| = \frac{|I_{line}|}{\sqrt{3}} \end{array} \right\}$$

$$\begin{aligned}
 S_{\text{total}} &= 3 |V_{\text{phase}}| |I_{\text{line}}| \cos \theta \\
 S_{\text{total}} &= \sqrt{3} |V_{\text{line}}| |I_{\text{line}}| \cos \theta
 \end{aligned}
 \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} \text{Y Connection} \\ \\ |I_{\text{line}}| = |I_{\text{phase}}| \\ |V_{\text{phase}}| = \frac{|V_{\text{line}}|}{\sqrt{3}} \end{array}$$

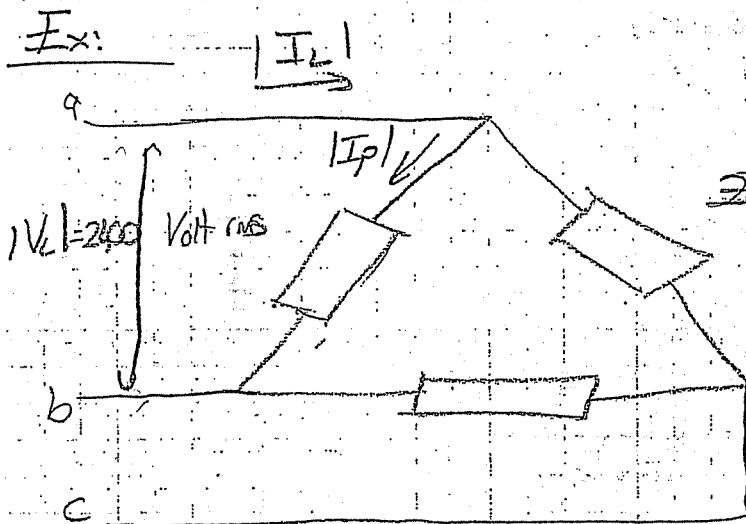

$$|V_L| = 2400$$

$$|I_p| = \frac{2400}{50} = \frac{|V_L|}{|Z_A|} = 48 \text{ Amp}$$

$$\text{pf} = \cos \theta = \frac{\text{Re}\{Z_A\}}{|Z_A|} = \frac{40}{50} = 0.8$$

$$|I_L| = \sqrt{3} |I_p| = \sqrt{3} \cdot 48$$

$$P_\phi = |I_p|^2 \text{Re}\{Z_A\} = 48^2 \cdot 40$$

single phase

$$P_{3\phi} = 3 |I_p|^2 \text{Re}\{Z_A\} = 3 \cdot 48^2 \cdot 40 = 276480 \text{ Watt}$$

$$Q_{3\phi} = 3 * |I_p|^2 * \text{Im}\{Z_A\} = 207360 \text{ VAR}$$

$$S_{3\phi} = P_{3\phi} + j Q_{3\phi} = 276480 + j 207360 \text{ VA}$$


$$|S_{3\phi}| = 345600 \text{ VA}$$

### Complex Power

$$S_{3\phi} = P_{3\phi} + j Q_{3\phi}$$

$$S_{\phi} = P_{\phi} + j Q_{\phi}$$

$$\boxed{\text{pf} = \cos \theta = \frac{P}{|S|}}$$

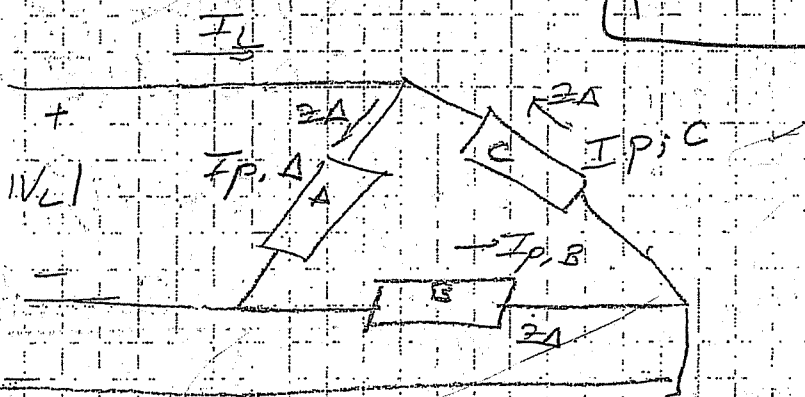


$$S_1 = V_L * I_{p,A}^* = 2\Delta I_{p,A} * I_{p,A}^*$$

$$= 2\Delta |I_{p,A}|^2$$


$$= \left[ \text{Re}\{2\Delta\} + j \text{Im}\{2\Delta\} \right] |I_{p,A}|^2$$



$\Delta - Y$  transformation:

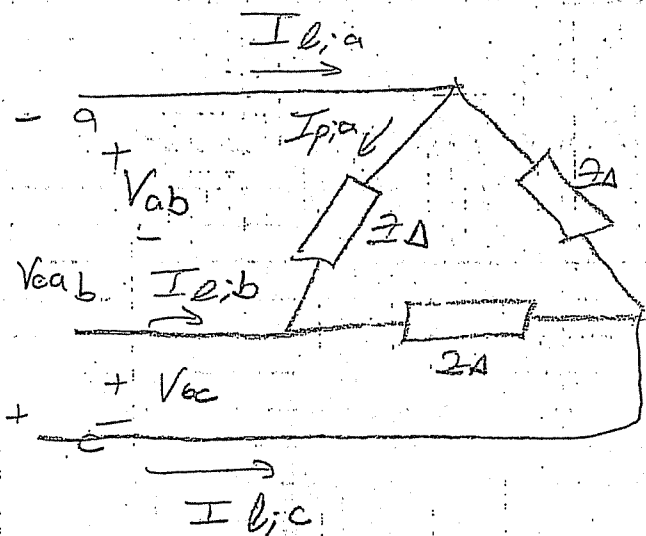

$\equiv V_{ca}$

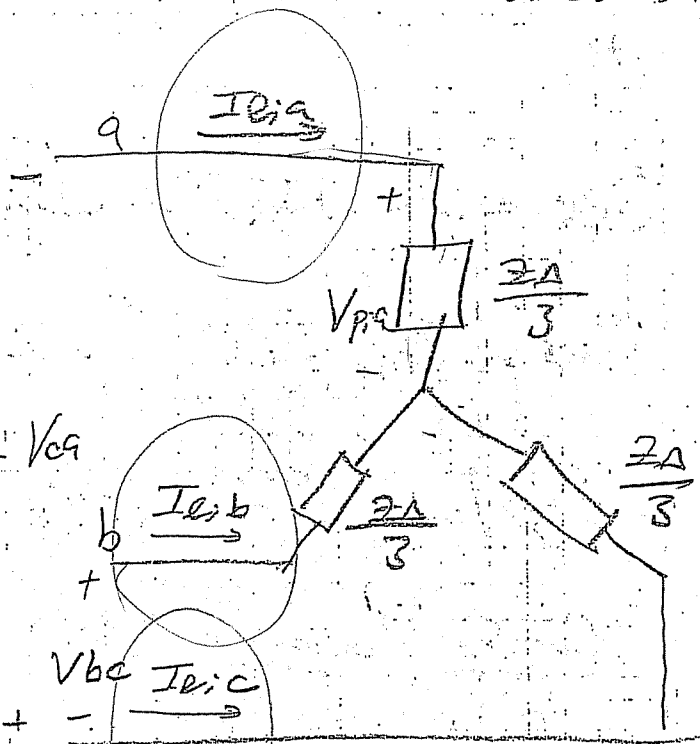

$|I_{l;c}| = |I_{l;a}| = \sqrt{3} |I_{p;a}| = |I_{l;b}|$

$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$

$|S| = \sqrt{3} |V_L| |I_{l;a}|$

$|S| = 3 |V_L| |I_{p;a}|$

Y-connection (load)

$P_\phi = |V_p| |I_p| \cos \theta$

$P_\phi = \frac{|V_L|}{\sqrt{3}} |I_L| \cos \theta$

$P_T = \sqrt{3} |V_L| |I_L| \cos \theta$

$V_L = \sqrt{3} |V_p|$

$Q_T = \sqrt{3} |V_L| |I_L| \sin \theta$

$S_T = P_T + j Q_T$

$|V_{p;a}| = \frac{|V_{l;a}|}{\sqrt{3}} = \frac{|V_L|}{\sqrt{3}}$

$|S| = \sqrt{3} |I_{l;a}| |V_L|$

$= \sqrt{3} |I_{l;a}| \sqrt{3} |V_{p;a}|$

$|S| = 3 |I_{l;a}| |V_{p;a}|$

$\Delta$  - Connection (load)

$P_\phi = |V_p| |I_p| \cos \theta$

$P_\phi = |V_L| \frac{|I_L|}{\sqrt{3}} \cos \theta$

$I_L = |I_p| \sqrt{3}$

$P_T = \sqrt{3} |V_L| |I_L| \cos \theta$

$Q_T = \sqrt{3} |V_L| |I_L| \sin \theta$



$S_T = P_T + j Q_T$



just remember  $\Delta$  connected load


$$|I_{eL}| = \sqrt{3} |I_{pL}|$$

$$|V_{eL}| = |V_{pL}|$$

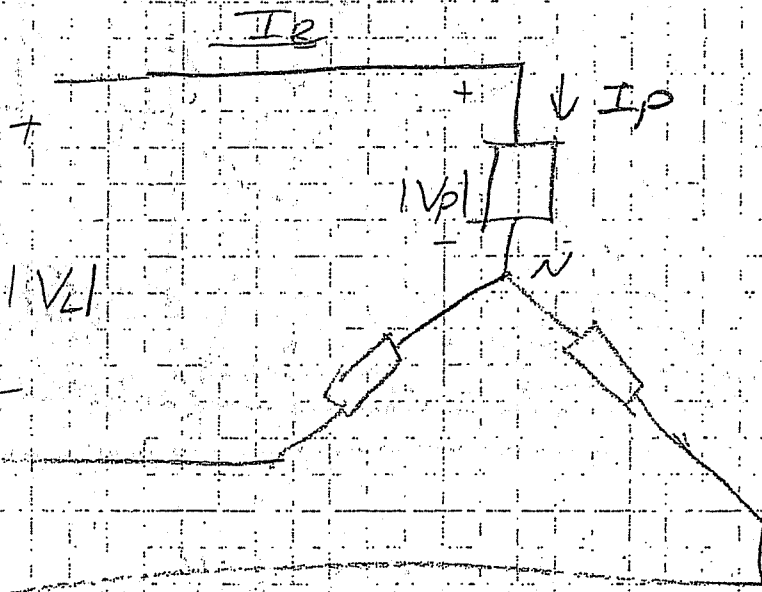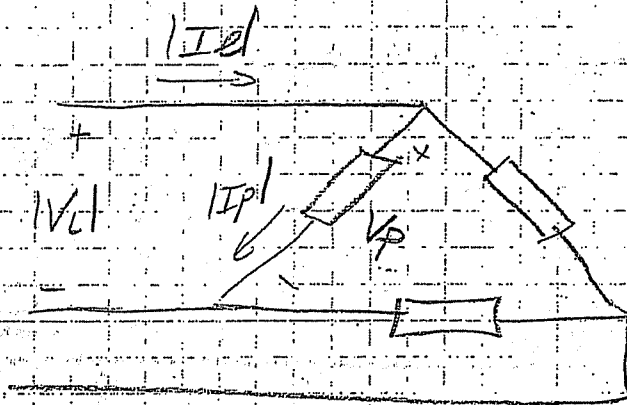


$$|V_{eL}| = \sqrt{3} |V_{pL}|$$

$$|I_{eL}| = |I_{pL}|$$

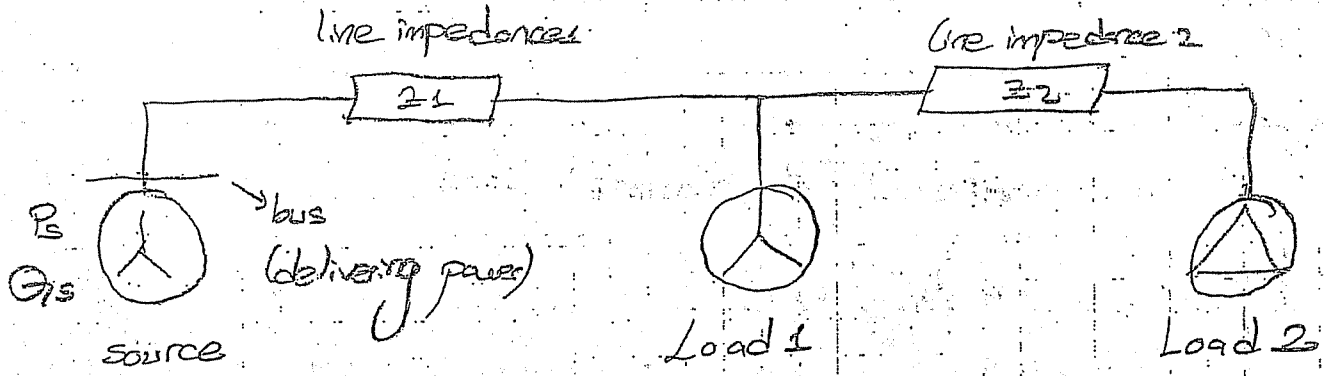

single line representation

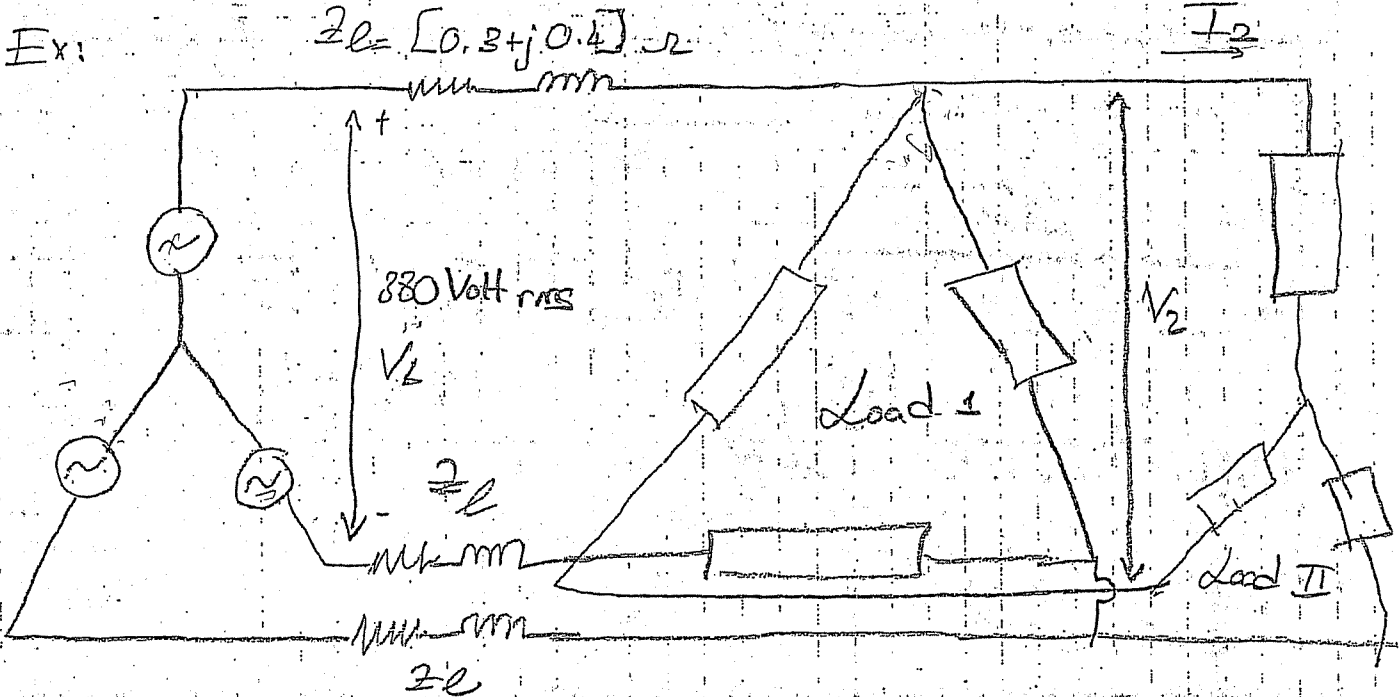- the neutral line is omitted (not shown)
- the currents and voltages associated with different phases are shown only by their magnitude.



\* Source side line voltage =  $V_L = 380$  Volt rms


\* Source delivers a total of 9 kW and 9kVAR

Load I: absorbs 6 kW at a 0.6 pf of lagging

Find  $|V_2|$ ,  $|I_2|$ ,  $[P_2, G_2$  and  $pf_2]$  for load II

1<sup>st</sup> approach:

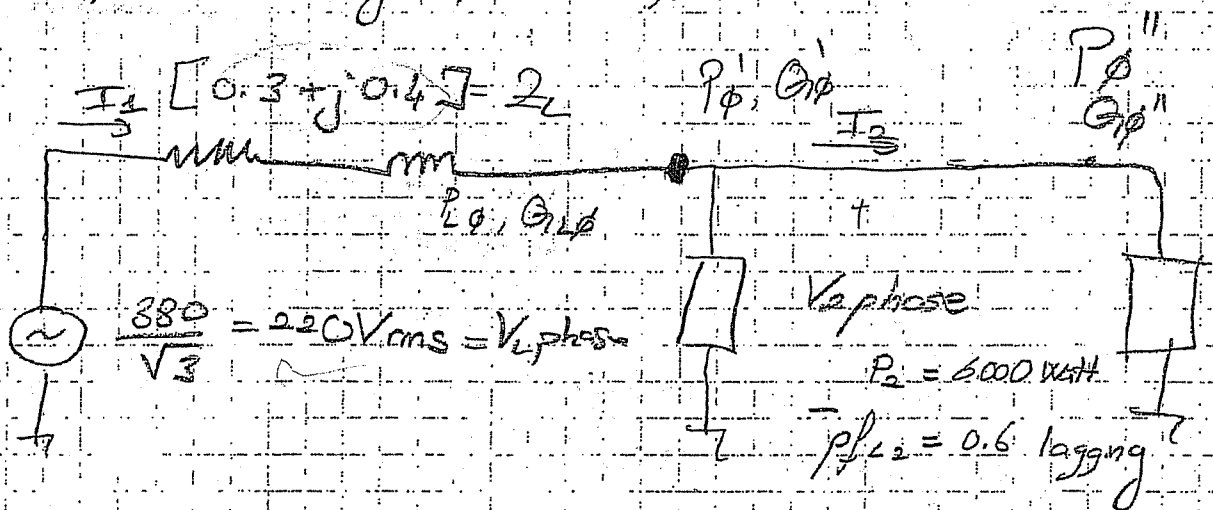1<sup>st</sup> approach: Single-phase approach:



$\frac{9}{8} \text{ kW} + \frac{9}{3} j \text{ kVAR}$  complex power delivered per phase

$$P_{S\phi} = \frac{9}{8} = 3 \text{ kW}$$

$$P_{S\phi} = 3000$$

$$Q_{S\phi} = \frac{9}{3} = 3 \text{ kVAR}$$

$$Q_{S\phi} = 3000$$

$$S_{S\phi} = P_{S\phi} + jQ_{S\phi} = 3000 + 3000j$$

$$|S_{S\phi}| = |V_{L \text{ phase}}| |I_L|$$


$$\sqrt{3000^2 + 3000^2} = 220 |I_L| \Rightarrow |I_L| = 19.3 \text{ A}$$

$$P_{L\phi} = |I_L|^2 \operatorname{Re}\{Z_L\} = |19.3|^2 * 0.3 = 112 \text{ WATTS}$$

$$Q_{L\phi} = |I_L|^2 \operatorname{Im}\{Z_L\} = |19.3|^2 * 0.4 = 149 \text{ VAR}$$

$$P_{\phi'} = 3000 - P_{L\phi} = 3000 - 112 = 2888 \text{ WATT}$$
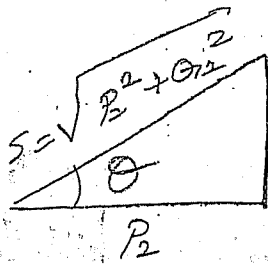
$$Q_{\phi'} = 3000 - Q_{L\phi} = 3000 - 149 = 2851 \text{ VAR}$$



$$pf = \cos \theta = 0.6 = \frac{P_2}{\sqrt{P_2^2 + Q_{12}^2}}$$

$$\cos \theta = \frac{6000}{\sqrt{6000^2 + Q_{12}^2}} = 0.6$$

$$\Rightarrow Q_{12} = 8000$$

$$P_{2\phi} = \frac{6000}{2} = 3000 \text{ Watt}$$

$$Q_{2\phi} = \frac{8000}{3} = 2666 \text{ VAR}$$

$$S_{\phi'} = \sqrt{(2888)^2 + (2851)^2} = 4058 \text{ VA}$$

$$|I_1| |V_{2\text{phase}}| = S_{\phi'}$$

$$19.3 |V_{2\text{phase}}| = 4058 \Rightarrow |V_{2\text{phase}}| = 210.3 \text{ Volts rms}$$

$$V_2 = \sqrt{3} * 210.3 = 364 \text{ Volts}$$

$$P_{\phi''} = P_{\phi'} - P_{2\phi} = 2888 - 2000 = 888 \text{ Watt}$$

$$Q_{\phi''} = Q_{\phi'} - Q_{2\phi} = 2851 - 2666.6 \approx 187 \text{ VAR}$$


$$|S_{\phi''}| = \sqrt{(P_{\phi''})^2 + (Q_{\phi''})^2} = \sqrt{888^2 + 187^2} = 907$$

$$|S_{\phi''}| = |I_2| |V_{2\text{phase}}|$$

$$907 = |I_2| \cdot 210.3 \Rightarrow |I_2| = 4.31 \text{ A}$$

$$PF_{load2} = \frac{P_d''}{|S_d''|} = \frac{888}{907} = 0.98 \text{ lagging}$$

2<sup>nd</sup> approach (Single line)

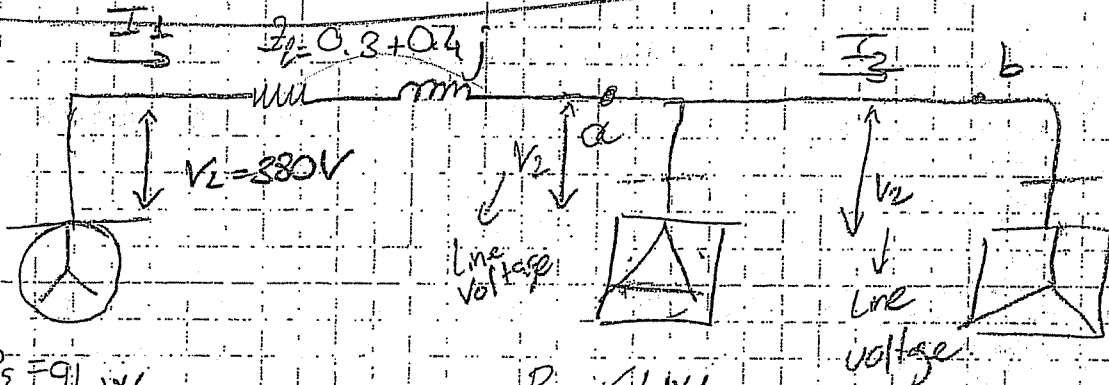

$$P_s = 9 \text{ kW}$$

$$Q_s = 9 \text{ kVAR}$$

$$S_s$$

$$P_e = 6 \text{ kW}$$

$$0.6 \text{ pf lagging}$$

$$Q_e = 6 \tan^{-1} [\cos(0.6)] = 7992 \text{ VAR}$$

Consider the power

$$S_s = \sqrt{P_s^2 + Q_s^2} = \sqrt{9^2 + 9^2} = 12.72 \text{ kVA}$$

$$|I_L| = \frac{|S_s|}{V \sqrt{3}} = \frac{12.72 \cdot 10^3}{\sqrt{3} \cdot 380} = 19.3 \text{ Amp}$$

$$P_{\text{transfer}} = |I_L|^2 \cdot 0.3 \cdot 3 = 336 \text{ Watt}$$

$$Q_{\text{transfer}} = |I_L|^2 \cdot 0.4 \cdot 3 = 447 \text{ VAR}$$

$$P_a = P_s - P_{\text{transfer}} = 9000 - 336 = 8664 \text{ Watt}$$

$$Q_a = Q_s - Q_{\text{transfer}} = 9000 - 447 = 8553 \text{ VAR}$$

$$|S_a| = \sqrt{P_a^2 + Q_a^2} = 12174.5 \text{ VA}$$

$$|V_2| = \frac{|S_a|}{|I_1| \sqrt{3}} = \frac{12174.5}{19.3 \cdot \sqrt{3}} = 364 \text{ Volts}$$

$$P_b = P_a - P_2 = 8664 - 6000 = 2664 \text{ Watts}$$


$$Q_b = Q_a - Q_2 = 8553 - 7992 = 561 \text{ VAR}$$

$$|S_b| = \sqrt{P_b^2 + Q_b^2} = \sqrt{2664^2 + 561^2} = 2722.4 \text{ VA}$$

$$|I_2| = \frac{|S_b|}{\sqrt{3} |V_2|} = 2.31 \text{ A}$$

$\frac{6000 \text{ VA}}{3}$
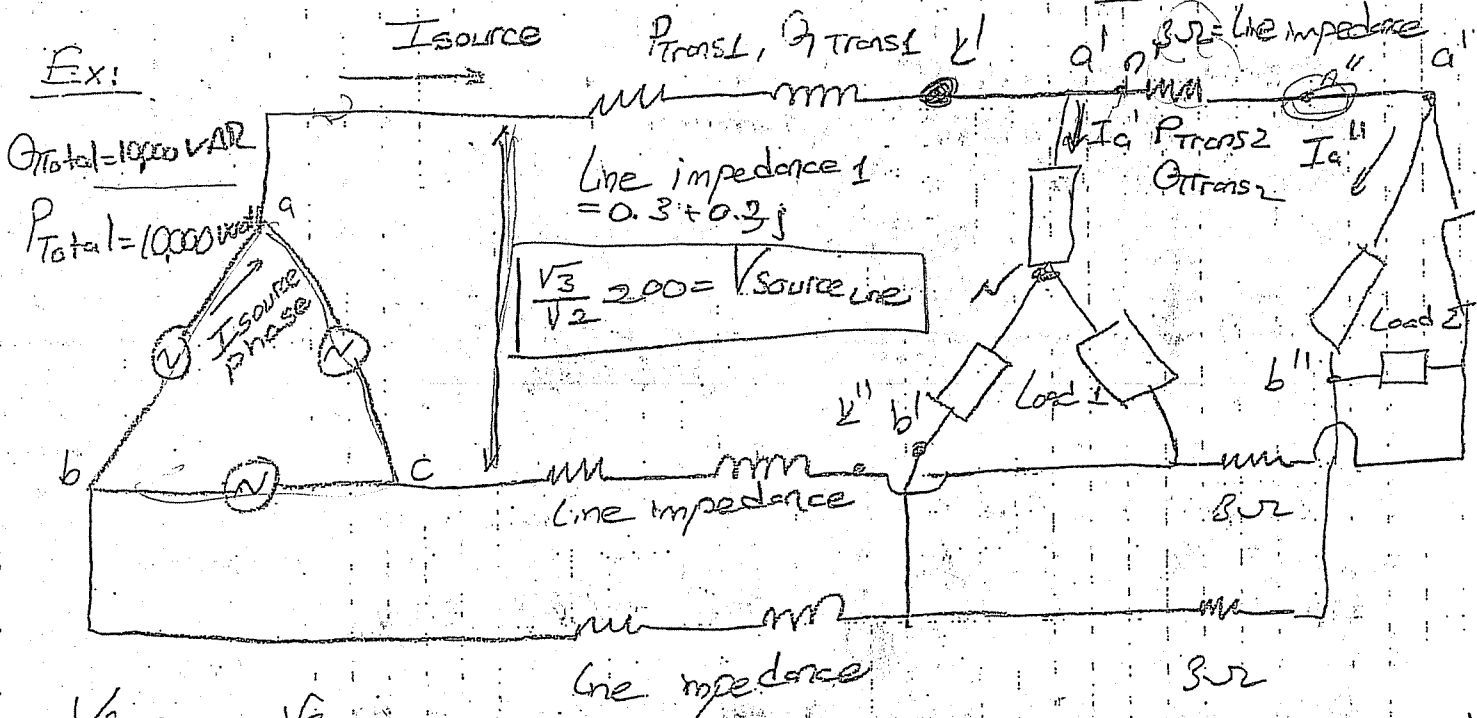
$$P_{f \text{ load } 2} = \frac{P_b}{\sqrt{P_b^2 + Q_b^2}} = \frac{2664}{2722.4} = 0.98 \text{ lagging}$$



$$V_{\text{source line}} = \frac{\sqrt{3}}{\sqrt{2}} 200 \text{ Volt rms}$$

$$P_{\text{load, total}} = 5000 \text{ Watt} = 9000 \text{ Watt}$$

$$Q_{\text{load, total}} = \text{VAR} = 9000 \text{ VA}$$

Find  $|V_{a'N}|$ ;  $|V_{a'b'}|$ ;  $|I_{a'}|$ ;  $|I_{a''}|$ ;  $|V_{a''b''}|$ ;  $|I_{n'}|$

$$S_{\text{Total}} = \sqrt{P_{\text{Total}}^2 + Q_{\text{Total}}^2} = 10000\sqrt{2} \text{ VA}$$

$$|S_{\text{Total}}| = \sqrt{3} |I_{\text{source}}| |V_{\text{source line}}|$$

$$10000\sqrt{2} = \sqrt{3} |I_{\text{source}}| \cdot \frac{200\sqrt{3}}{\sqrt{2}}$$

$$|I_{\text{source}}| = \frac{100}{3}$$

$$|I_{\text{source phase}}| = \frac{100}{3} \cdot \frac{1}{\sqrt{3}} = \frac{100}{3\sqrt{3}} \text{ A}$$

$$P_{\text{Trans L}} = |I_{\text{source}}|^2 * 0.3 * 3 = \left(\frac{100}{3}\right)^2 * 0.3 * 3 = 1000 \text{ W}$$

$$Q_{\text{Trans L}} = |I_{\text{source}}|^2 * 0.2 * 3 = \left(\frac{100}{3}\right)^2 * 0.2 * 3 = 1000 \text{ VAR}$$

$$P_{\text{K}} = P_{\text{S}} - P_{\text{Trans L}} = 10000 - 1000 = 9000 \text{ W}$$

$$Q_{\text{K}} = Q_{\text{S}} - Q_{\text{Trans L}} = 10000 - 1000 = 9000 \text{ VAR}$$

$$|S_{\text{K}}| = \sqrt{P_{\text{K}}^2 + Q_{\text{K}}^2} = 9000\sqrt{2} \text{ VA}$$

$$S_{\text{K}} = \sqrt{3} |I_{\text{source}}| |V_{\text{K}}|$$

$$9000\sqrt{2} = \sqrt{3} \cdot \frac{100}{3} |V_{\text{K}}|$$

$$90\sqrt{6} = |V_{\text{K}}|$$

$$\begin{aligned} 9000\sqrt{2} &= \frac{100}{3} \\ &\downarrow \\ &3 \\ &\downarrow \\ &1 \end{aligned}$$



$$|V_{k'k''}| = |V_{a'b'}| = 90\sqrt{6} \text{ Volt}$$

$$|V_{a'n'}| = \frac{|V_{a'b'}|}{\sqrt{3}} = \frac{90\sqrt{6}}{\sqrt{3}} = 90\sqrt{2} \text{ Volt}$$

$$P_n' = P_k' - P_{\text{load total}} = 9000 - 5000 = 4000 \text{ Watt}$$

$$Q_n' = Q_k' - Q_{\text{load total}} = 9000 - 5000 = 4000 \text{ VAR}$$

$$|S_n'| = \sqrt{(P_n')^2 + (Q_n')^2} = 4000\sqrt{2} \text{ VA}$$

$$|I_n'| \cdot |V_{k'k''}| \sqrt{3} = 4000\sqrt{2}$$

$$|I_n'| \cdot 90\sqrt{6} \sqrt{3} = 4000\sqrt{2} \Rightarrow |I_n'| = \frac{4000}{270} = \frac{400}{27} \text{ A}$$

$$|S_{\text{load total}}| = \sqrt{P_{\text{load total}}^2 + Q_{\text{load total}}^2} = 5000\sqrt{2}$$

$$|S_{\text{load total}}| = |I_a'| \sqrt{3} |V_{a'b'}| = |I_a'| \cdot 3 |V_{a'n'}|$$

$$5000\sqrt{2} = |I_a'| \sqrt{3} \cdot 90\sqrt{6} \Rightarrow |I_a'| = \frac{500}{27} \text{ A}$$

$$P_{\text{trans 2}} = |I_n'|^2 \cdot 3 \cdot 3 = \left(\frac{400}{27}\right)^2 \cdot 9 = \frac{160000}{81}$$

$$Q_{\text{trans 2}} = 0$$

$$P_n'' = P_n' - P_{\text{trans 2}} = 4000 - \frac{160000}{81} = 2024.7 \text{ Watt}$$

$$Q_n'' = Q_n' - Q_{\text{trans 2}} = 4000 - 0 = 4000 \text{ VAR}$$

$$|S_n''| = \sqrt{(P_n'')^2 + (Q_n'')^2}$$

$$|I_a''| = \frac{I_n'}{\sqrt{3}} = \frac{400}{27} \cdot \frac{1}{\sqrt{3}} = \frac{400}{27\sqrt{3}}$$


$$|S_n''| \approx 2000\sqrt{5} \text{ VA}$$

$$|S_n''| = |I_n'| \sqrt{3} |V_{a''b''}|$$

$$2000\sqrt{5} = \frac{400}{27} \sqrt{3} |V_{a''b''}| \Rightarrow$$

$$|V_{a''b''}| = \frac{2000\sqrt{5} \cdot 27}{400\sqrt{3}} = \frac{5\sqrt{5} \cdot 27}{\sqrt{3}} \text{ Volt}$$


Convolution Integral:

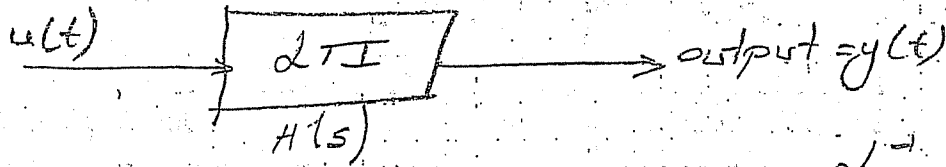


zero-state solution =  $y(s) = H(s)U(s) \xrightarrow{\mathcal{L}^{-1}} y(t) = h(t) * u(t)$   
 ↓  
 Convolution

$$y(t) = h(t) * u(t) = \int_{-\infty}^t h(t-\tau) u(\tau) d\tau$$
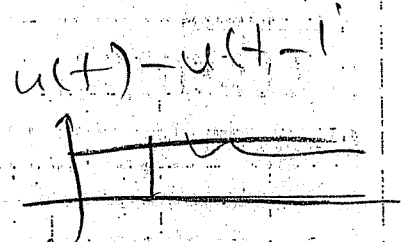
$$= \int_{-\infty}^t u(t-\tau) h(\tau) d\tau$$




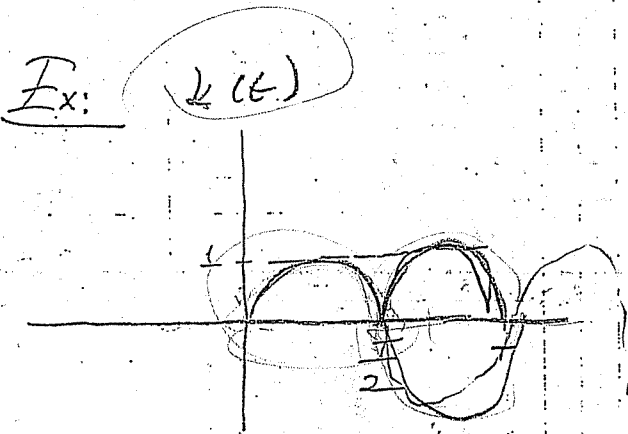Total solution = zero-state solution + add effect of initial states  
 convolution




$$u(t) = \begin{cases} \sin\left(\frac{2\pi}{T}t\right) & 0 < t < \frac{T}{2} \\ -\sin\left(\frac{2\pi}{T}t\right) & \frac{T}{2} < t < \frac{2T}{2} \\ 0 & \text{otherwise} \end{cases}$$
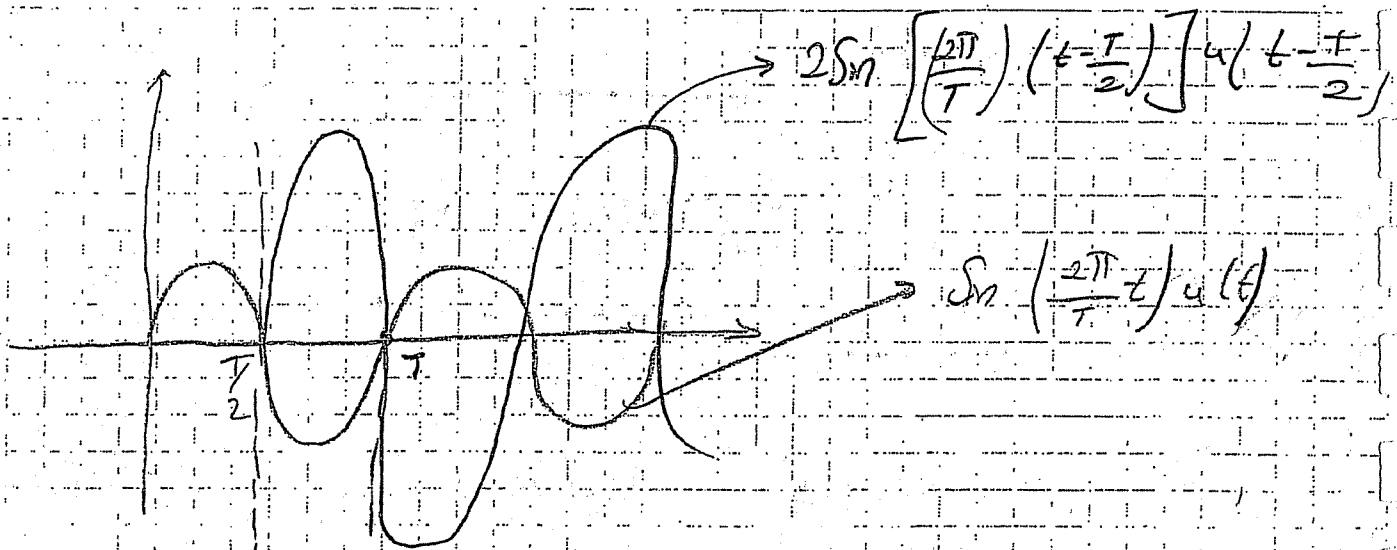
$$u(t) = \sin\left(\frac{2\pi}{T}(t-0)\right) u(t-0) + \frac{2}{T} \sin\left[\left(\frac{2\pi}{T}\right)\left(t-\frac{T}{2}\right)\right] u\left(t-\frac{T}{2}\right) + \sin\left[\left(\frac{2\pi}{T}\right)(t-T)\right] u(t-T)$$


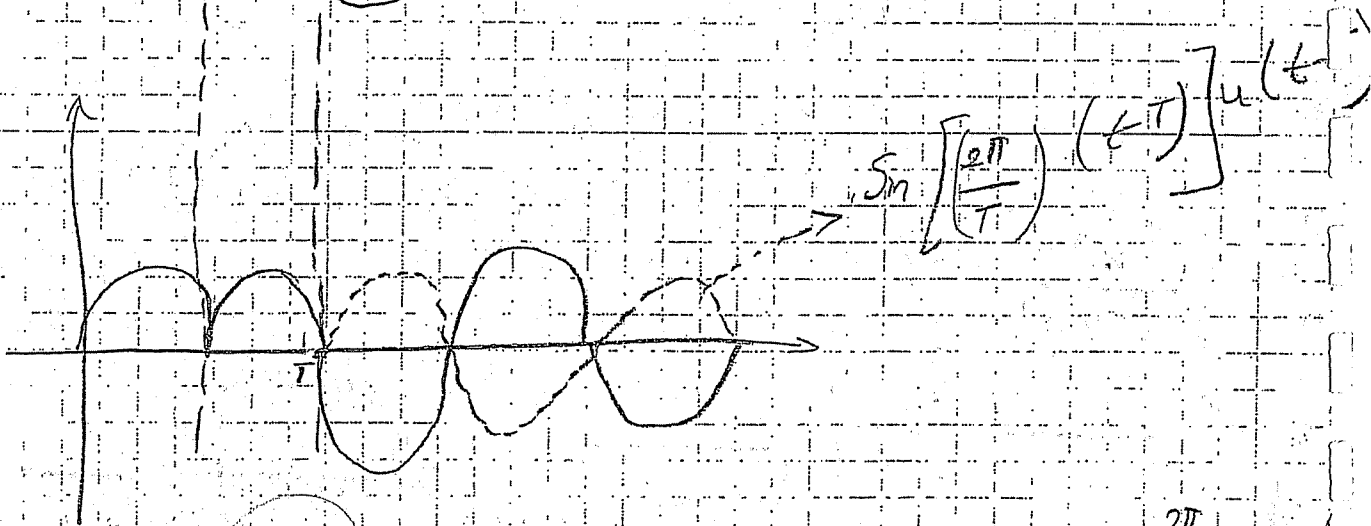
$$\sin\left(\frac{2\pi}{T}t\right) u(t)$$




$$\sin\left[\frac{2\pi}{T}\left(t\right)\right] u(t)$$

$$K(s) = \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} + 2 \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} e^{-\frac{T}{2}s} + \frac{2\pi}{T} \frac{1}{s^2 + \left(\frac{2\pi}{T}\right)^2} e^{-Ts}$$

$$K(s) = \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} \left[ 1 + 2e^{-\frac{T}{2}s} + e^{-Ts} \right]$$

Ex:

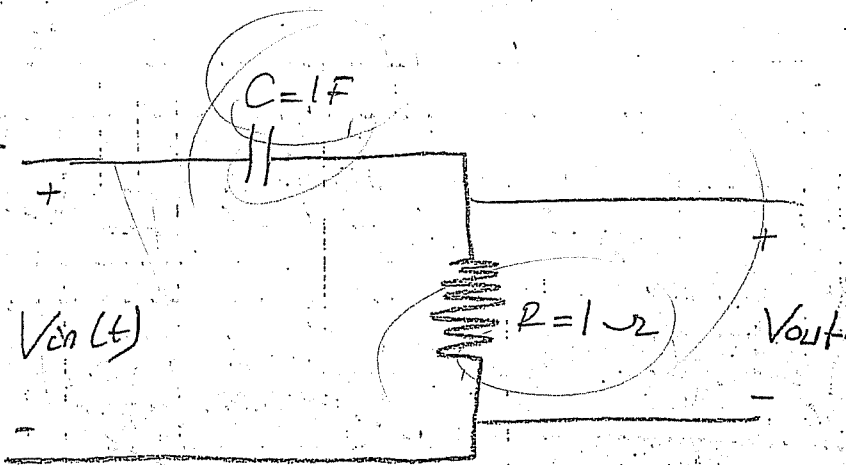

a)  $V_{in}(t) = e^{-t} u(t)$

What is  $V_{out}$ ?

Use Laplace


$$V_{in}(t) = e^{-t} u(t)$$

 $\alpha$ 

$$V_{in}(s) = \frac{1}{s+1}$$

$$V_{out}(s) = ?$$

$$\frac{V_{out}(s)}{V_{in}(s)}$$

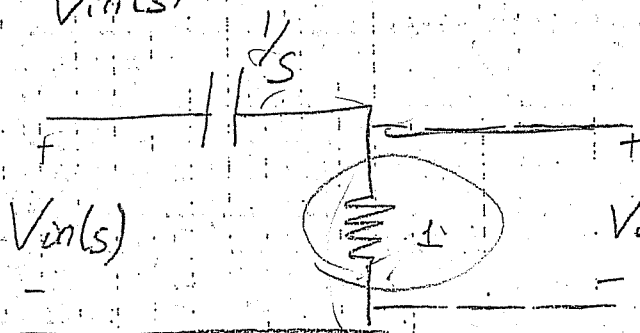

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + \frac{1}{s}} = \frac{s}{s+1}$$

$$V_{out}(s) = V_{in}(s) H(s) = \left( \frac{1}{s+1} \right) \cdot \frac{s}{s+1} = \frac{s}{(s+1)^2} = \frac{A}{s+1} + \frac{B}{(s+1)^2}$$

$$As + A + B = s$$

$$A = 1 \quad A + B = 0 \Rightarrow B = -1$$


$$V_{out}(s) = \frac{1}{s+1} + \frac{-1}{(s+1)^2}$$

 $\alpha$ 

$$V_{out}(t) = e^{-t} u(t) - te^{-t} u(t)$$

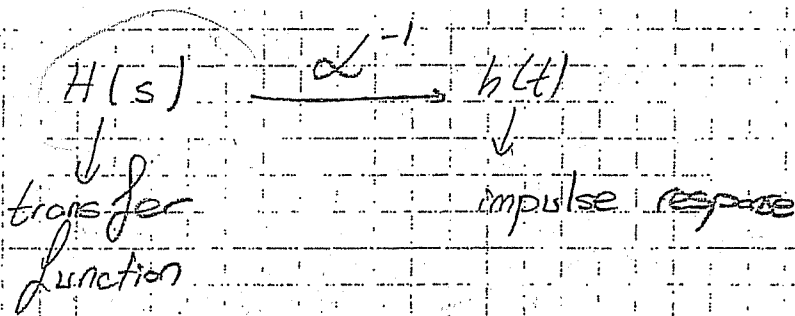(b)  $V_{in}(t) = e^{-t} u(t)$      $V_{out}(t) = ? \rightarrow$  use convolution

$$V_{out}(t) = \int_{-\infty}^t V_{in}(t-\tau) h(\tau) d\tau$$



$$H(s) = \frac{s}{s+1} = \frac{s+1-1}{s+1} = 1 - \frac{1}{s+1}$$


$$h(t) = \delta(t) - e^{-t} u(t)$$

$$V_{in}(t) = e^{-t} u(t)$$


$V_{in}(t)$




$h(t)$

$V_{in}(t)$

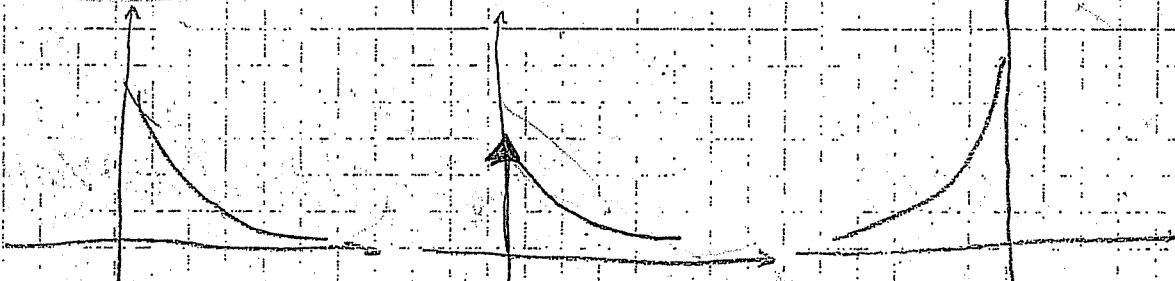

$V_{in}(t-\tau)$

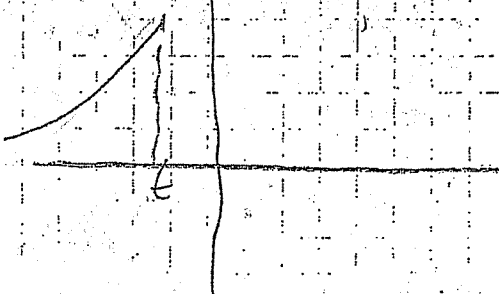

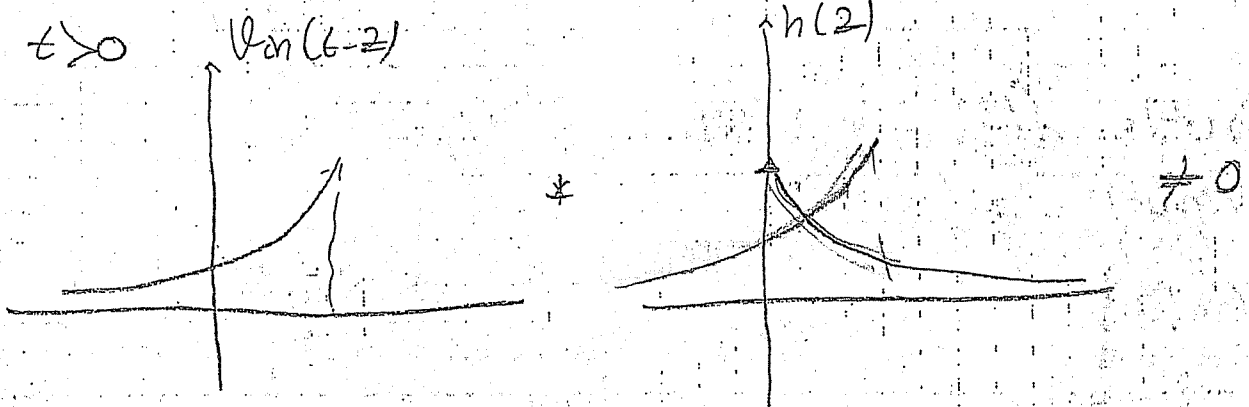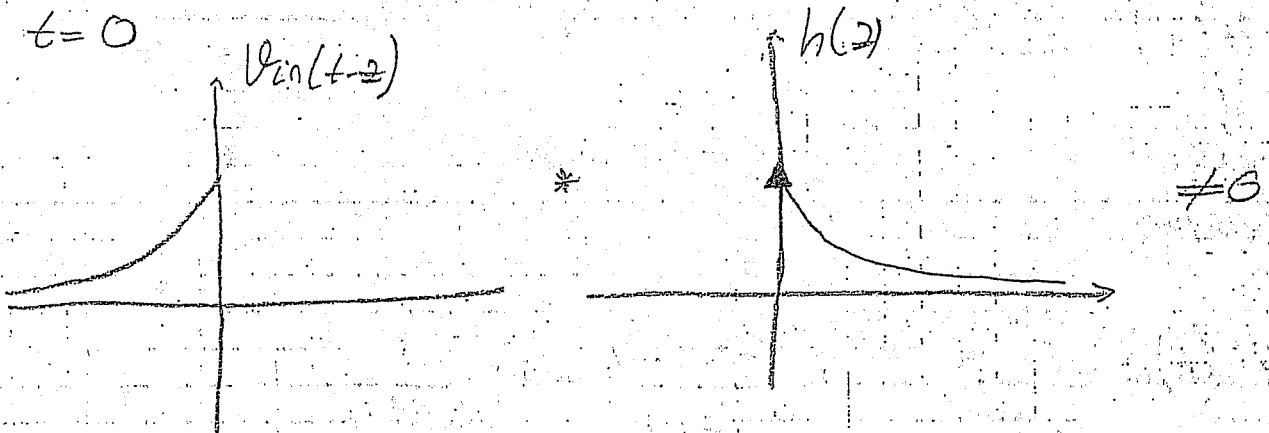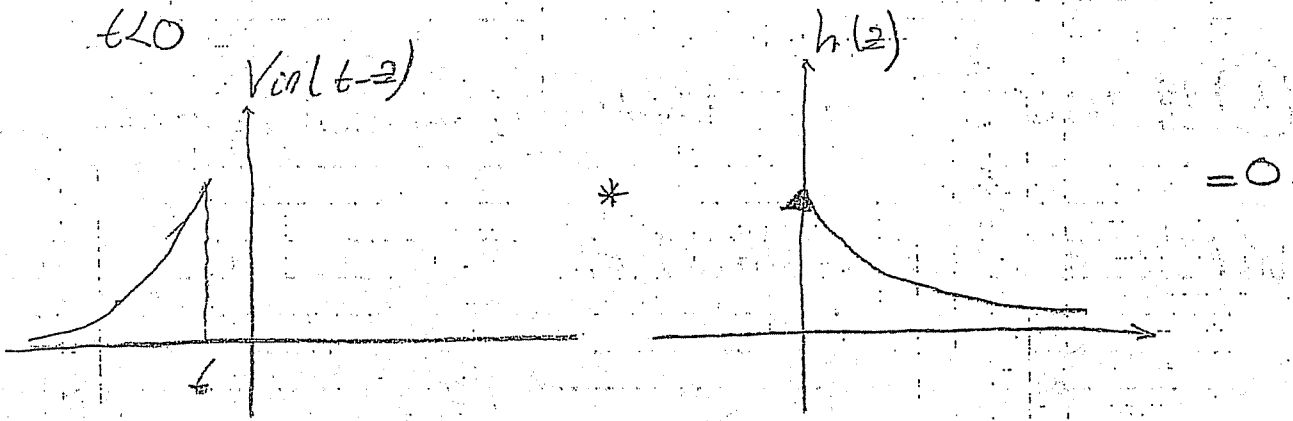

$t < 0$

$V_{out}(t) = 0$

$t = 0$

$V_{out}(t) =$

$$= \int_{-\infty}^{0^-} h(z) V_{in}(t-z) dz + \int_{0^-}^{0^+} h(z) V_{in}(t-z) dz$$

$$= \int_{0^-}^{0^+} \left[ \delta(z) e^{-\frac{z}{\tau}} u(z) \right] e^{-\frac{(t-z)}{\tau}} u(t-z) dz$$

$$V_{out}(t) = 0 + e^{-t} \int_0^t [f(z) e^{-z} u(z)] e^{z} u(t-z) dz$$

$$V_{out}(t) = e^{-t} \int_0^+ f(z) e^{z} u(t-z) dz - \int_0^+ 1 \cdot u(z) u(t-z) dz$$

$$V_{out}(t) = \int_0^+ f(z) e^{z} u(t-z) dz$$

$$f(z) f(z) = f(z) f(0)$$

$t=0$

$$V_{out}(t) = e^{-t} \quad V_{out}(0) = e^{-0} = 1$$

$t > 0$

$$V_{out}(t) = \int_{-\infty}^{0^-} h(z) V_{in}(t-z) dz + \int_0^{0^+} h(z) V_{in}(t-z) dz + \int_0^t h(z) V_{in}(t-z) dz$$

$$V_{out}(t) = 0 + e^{-t} + \int_0^t [f(z) e^{-z} u(z)] e^{-t+z} u(t-z) dz$$



$$V_{out}(t) = e^{-t} + \int_0^t f(z) e^{-z} u(t-z) dz - \int_0^t e^{-z} u(z) u(t-z) dz$$

$$= 0 - \int_0^t e^{-z} u(z) u(t-z) dz = - \int_0^t e^{-z} dz + e^{-t}$$



$$V_{out}(t) = e^{-t} - \int_0^t e^{-z} dz = e^{-t} - e^{-t} t$$

Ex:

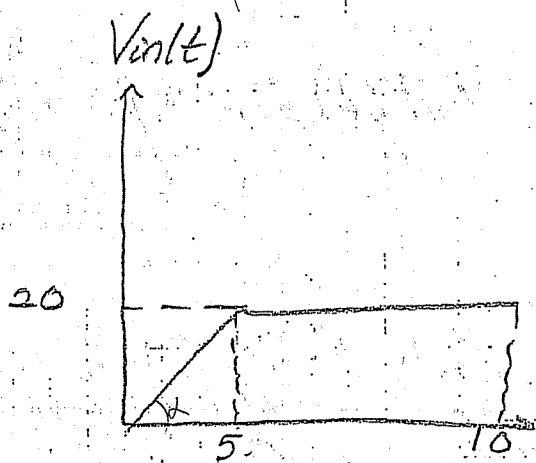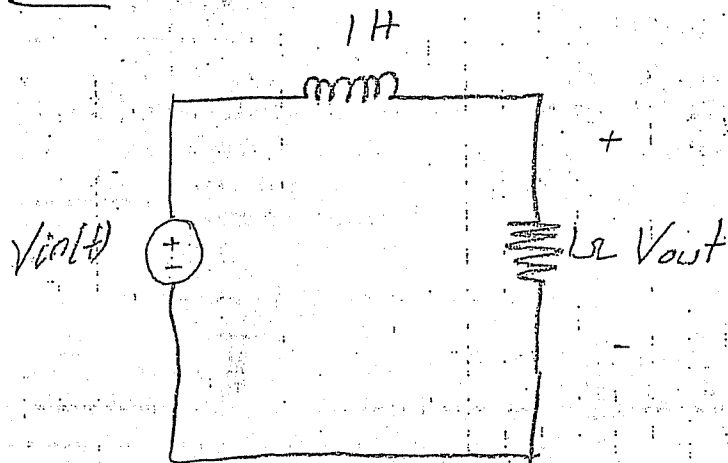


Find  $V_{out}(t) = ?$

Solution:

$$V_{out}(t) = \int_{-\infty}^t h(z) V_{in}(t-z) dz = \int_{-\infty}^t V_{in}(z) h(t-z) dz$$
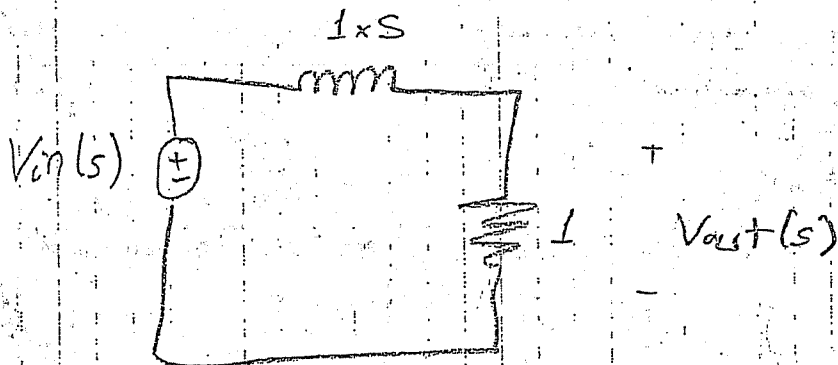
$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{s+1} = \text{Transfer function}$$




$$H(s) = \frac{1}{s+1} \xrightarrow{d^{-1}} h(t) = e^{-t} u(t)$$


↑  
impulse response

$$V_{in}(t) = \begin{cases} 0 & t < 0 \\ 4t & 0 \leq t < 5 \\ 20 & 5 \leq t < 10 \\ 0 & t > 10 \end{cases}$$


$h(z)$

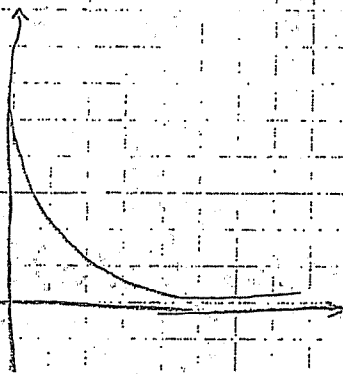

$V_{in}(z)$

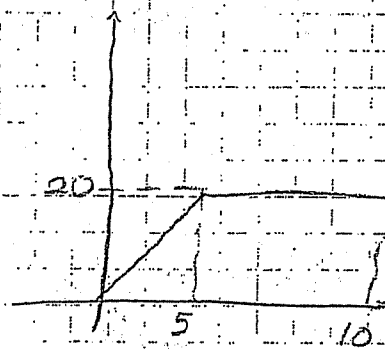


$$h(t-z) = e^{-(t-z)} u(t-z)$$

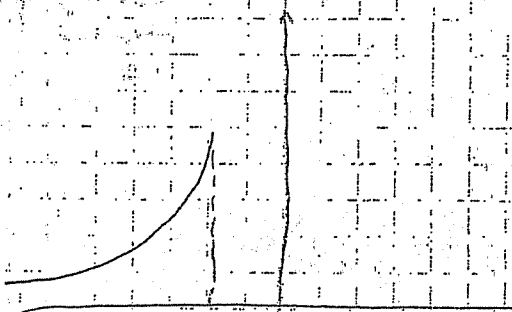


$t$   
parameter

if  $t < 0$

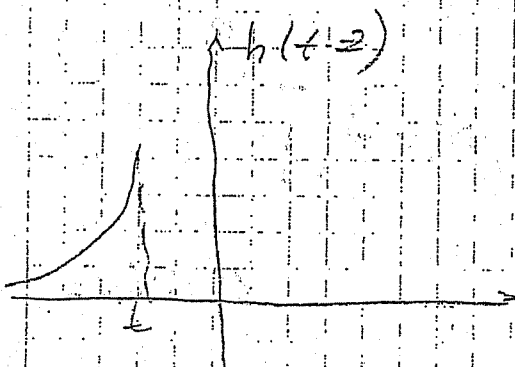

\*



$V_{in}(z)$

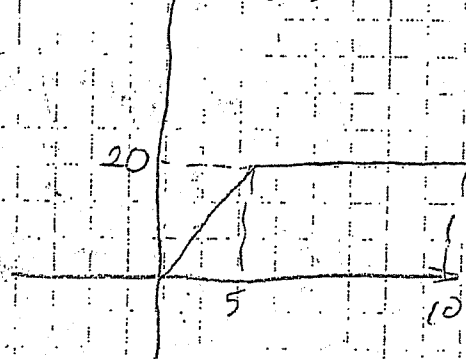


= 0

$$\int_{-\infty}^t h(t-z) V_{in}(z) dz = 0$$

if  $0 < t < 5$

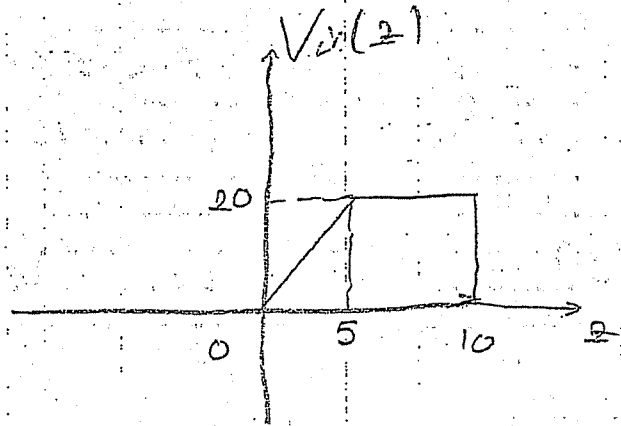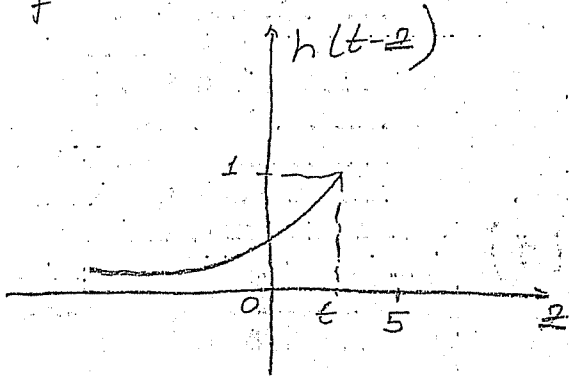
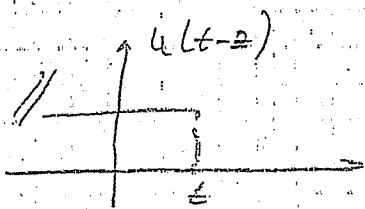
$$\int_{-\infty}^t h(t-z) V_{in}(z) dz = \underbrace{\int_{-\infty}^0 h(t-z) V_{in}(z) dz}_0 + \int_0^t h(t-z) V_{in}(z) dz$$



$$+ \int_0^t e^{-(t-z)} \underbrace{u(t-z)}_1 4 dz dz$$



$$= 0 + \int_0^t e^{-t} e^z 4 dz = 4 e^{-t} \int_0^t e^z dz$$

$$\frac{z}{1} \begin{matrix} \searrow + \\ \swarrow - \end{matrix} \begin{matrix} e^z \\ e^z \\ e^z \end{matrix}$$

$$= 4 e^{-t} \left[ z e^z - e^z \right] \Big|_0^t$$

$$= 4 e^{-t} \left[ t e^t - e^t + 1 \right]$$

$$V_{out}(t) = 4t - 4 + 4e^{-t} \quad 0 \leq t < 5$$

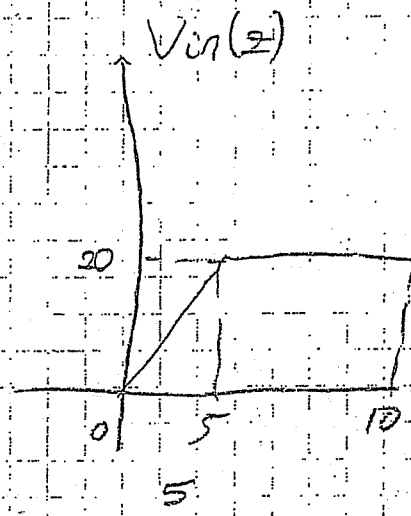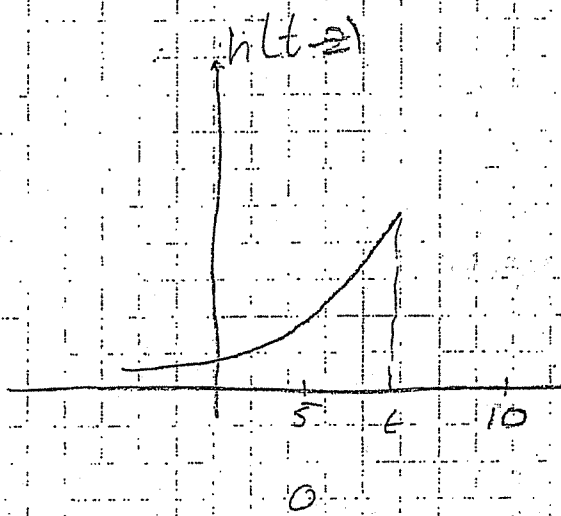if  $5 < t < 10$ 

$$Var_t(t) = \int_{-\infty}^{\infty} h(t-z) v(z) dz + \int_{-\infty}^{\infty} h(t-z) v(z) dz + \int_{-\infty}^{\infty} h(t-z) v(z) dz$$

$$= 0 + \int_0^5 e^{-(t-z)} \underbrace{u(t-z)}_1 4z dz + \int_5^t e^{-(t-z)} \underbrace{u(t-z)}_1 20 dz$$

$$= e^{-t} \int_0^5 e^z 4z dz + e^{-t} \int_5^t e^z 20 dz$$

$$= e^{-t} [4 \cdot 5 e^5 - 4e^5 + 4] + 20e^{-t} (e^t - e^5)$$



$$= e^{-t} [16e^5 + 4] + 20 - 20e^{5-t}$$

$$= e^{-t} [16e^5 + 4 + 20e^t - 20e^5]$$

$$= e^{-t} [-4e^5 + 4] + 20$$

$$V_{out}(t) = e^{-t} [4 - 4e^5] + 20 \quad 5 < t \leq 10$$

if  $t > 10$

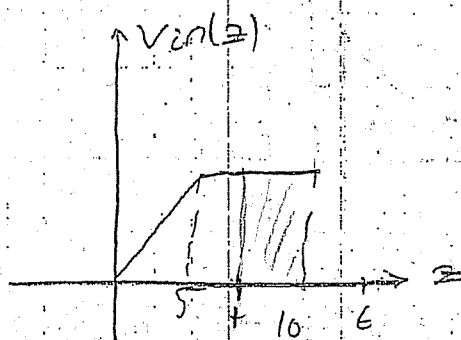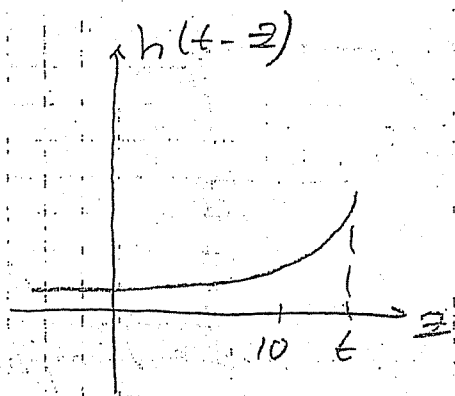


$$V_{out}(t) = \int_{-\infty}^t h(t-z) V_{in}(z) dz = \int_{-\infty}^0 \dots + \int_0^5 \dots + \int_5^{10} \dots + \int_{10}^t \dots$$

$$V_{out}(t) = e^{-t} [16e^5 + 4] + \int_5^{10} e^{-(t-z)} \underbrace{u(t-z)}_1 20 dz$$

$$V_{out}(t) = e^{-t} [16e^5 + 4] + e^{-t} \int_5^{10} e^z 20 dz$$


$$= e^{-t} [16e^5 + 4] + 20e^{-t} [e^{10} - e^5]$$
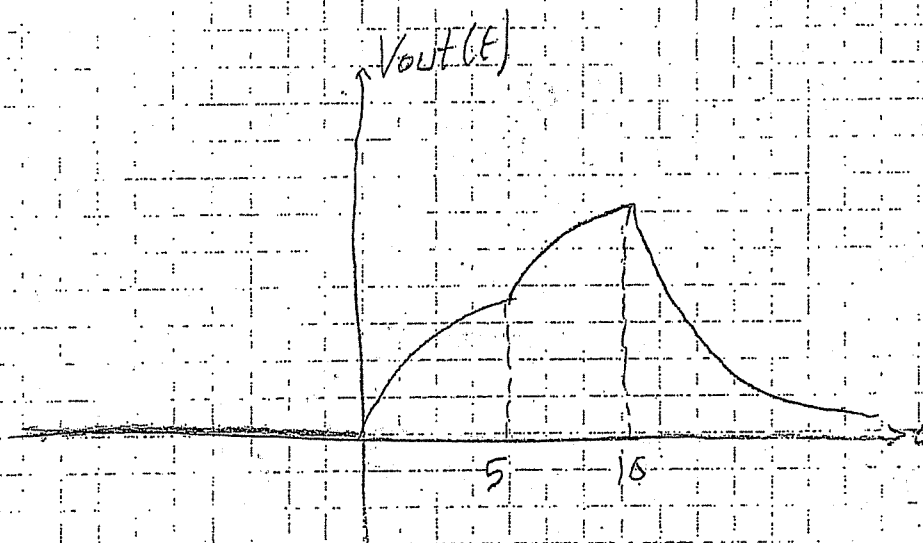
$$V_{out}(t) = e^{-t} [-4e^5 + 4 + 20e^{10}] \quad , \quad t > 10$$





$$V_{out}(t) = \begin{cases} 0 & t < 0 & V_{out}(0) = 0 \\ 4t - 4 + 4e^{-t} & 0 < t < 5 & V_{out}(5) = 16 + 4e^{-5} \\ e^{-t} [4 - 4e^5] + 20 & 5 < t < 10 & V_{out}(5) = 16 + 4e^{-5} \\ & & V_{out}(10) = 4e^{-10} - 4e^{-5} + 20 \\ e^{-t} [4 - 4e^5 + 20e^{10}] & 10 < t & V_{out}(10) = 4e^{-10} - 4e^{-5} + 20 \end{cases}$$

Ex.

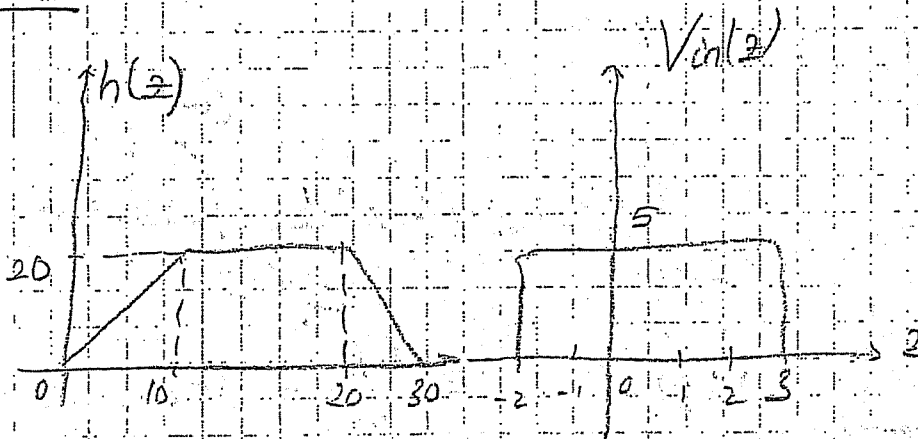


$$V_{out}(t) = h(t) * V_{in}(t)$$

Solution when  $-\infty < t < -2$

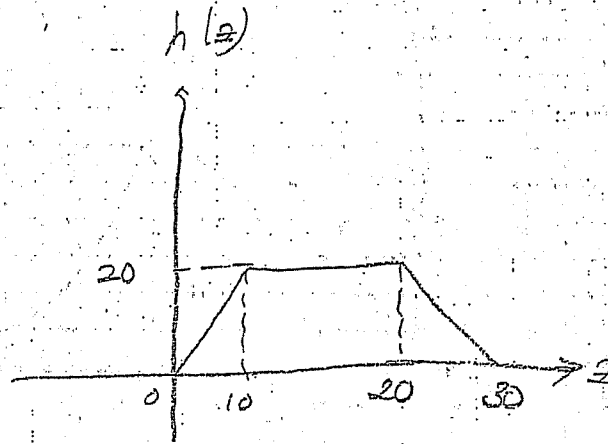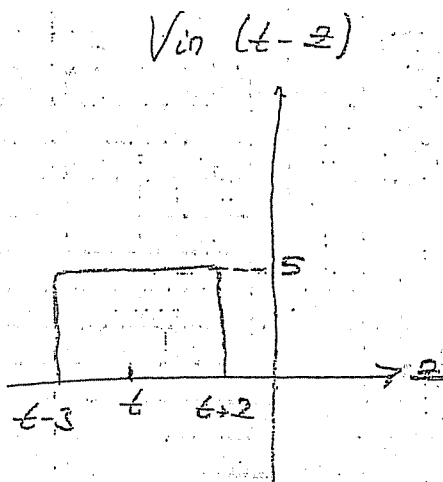

$$V_{out}(t) = \int_{-\infty}^t h(z) V_{in}(t-z) dz = 0$$

when  $-2 < t < 3$

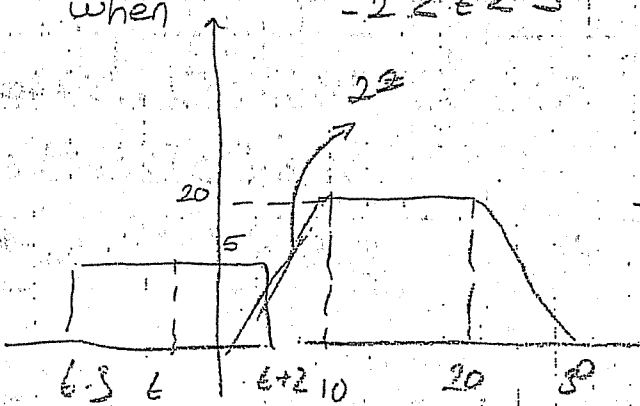


$$\int_{-\infty}^{t+2} h(z) V_{in}(t-z) dz = \int_{-\infty}^0 \dots + \int_0^{t+2} 2z \cdot 5 dz$$

$$V_{out}(t) = 5z^2 \Big|_0^{t+2} = 5(t+2)^2$$


when  $3 < t < 23$

$$\int_{-\infty}^{t+2} h(z) V_{in}(t-z) dz = \int_{t-3}^{t+2} 2z \cdot 5 dz$$

$$V_{out}(t) = 5z^2 \Big|_{t-3}^{t+2} = 50t - 5$$

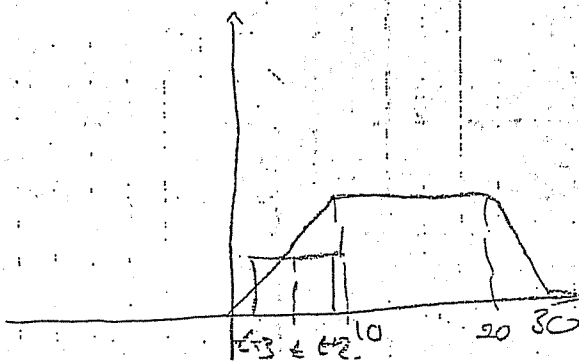

8  $t < 13$

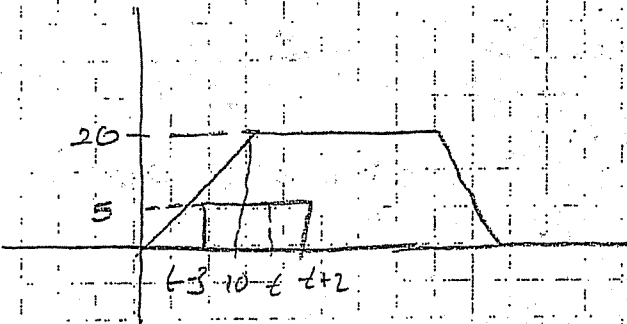


$$\int_{-\infty}^{t+2} \dots = 0 + \int_{t-3}^{10} 5 \, dz + \int_{10}^{t+2} 20 \times 5 \, dz = 10$$

$$V_{out}(t) = \left. 5z^2 \right|_{t-3}^{10} + \left. 100z \right|_{10}^{t+2}$$

$$= 500 - 5t^2 + 30t - 45 + 100t - 800$$

$$= -345 + 130t - 5t^2$$


13  $t < 18$

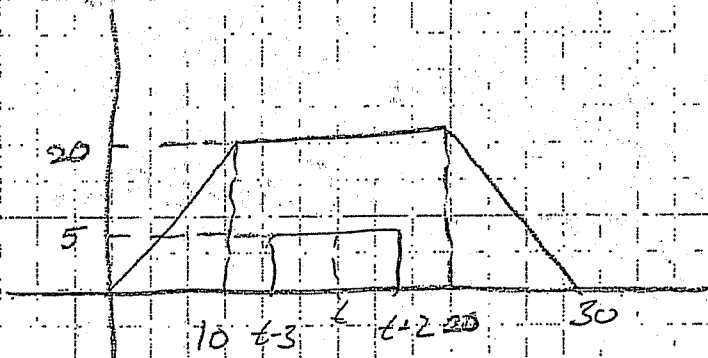

$$\int_{-\infty}^{t+2} \dots = \int_{t-3}^{t+2} 5 \cdot 20 \, dz = 100z \Big|_{t-3}^{t+2} = 500$$




$$18. < t < 23$$

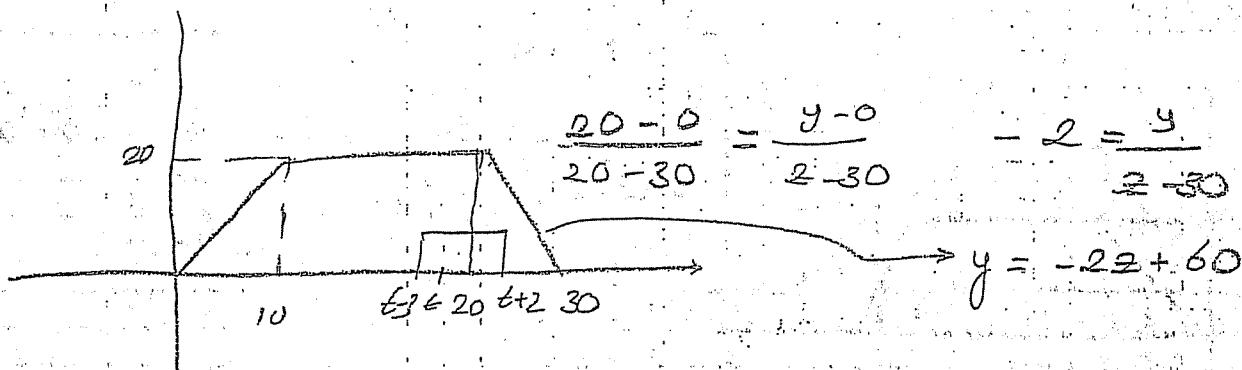


$$\begin{aligned}
 \int_{-\infty}^{t+2} \dots &= \int_{t-3}^{20} 20 \cdot 5 \, dz + \int_{20}^{t+2} 5 \cdot (-2z + 60) \, dz \\
 &= 100z \Big|_{t-3}^{20} + \left[ -5z^2 + 300z \right]_{20}^{t+2} \\
 &= 100[20 - t + 3] - 5[(t+2)^2 - 20^2] + 300[t+2 - 20]
 \end{aligned}$$

$$23 < t < 28$$

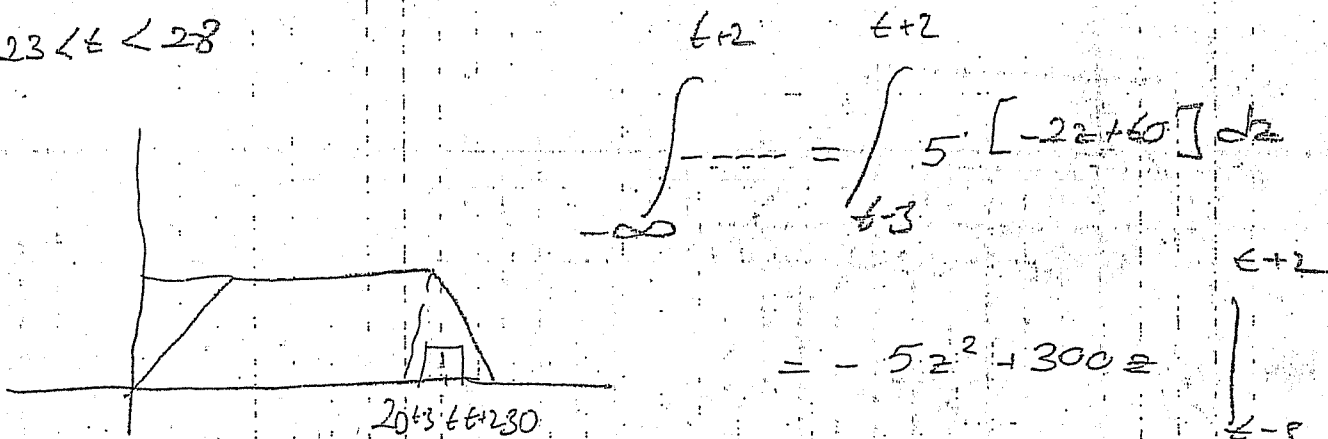
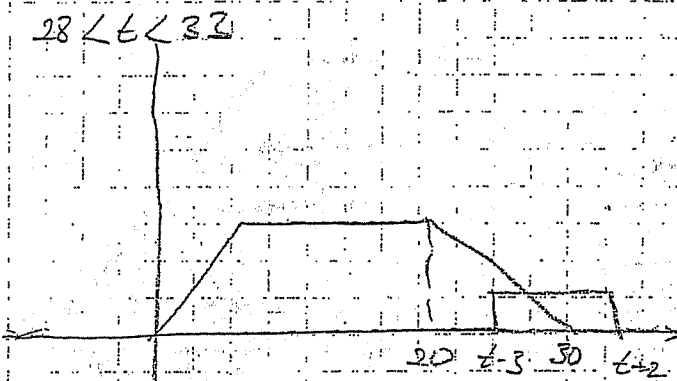
$$\begin{aligned}
 V_{out}(t) &= -5[(t+2)^2 - (t-3)^2] + 300[t+2 - t+3] \\
 &= -5[(2t-1) \cdot 5] + 300 \cdot 5 = -5[10t-5] + 1500
 \end{aligned}$$




$$\int_{-\infty}^{t+2} \dots = \int_{t-3}^{30} 5[-2t+60] = -5t^2 + 300t$$

$$= -5[900 - t^2 + 6t - 9] + 300[33 - t]$$

33 < t

$V_{out}(t) = 0$

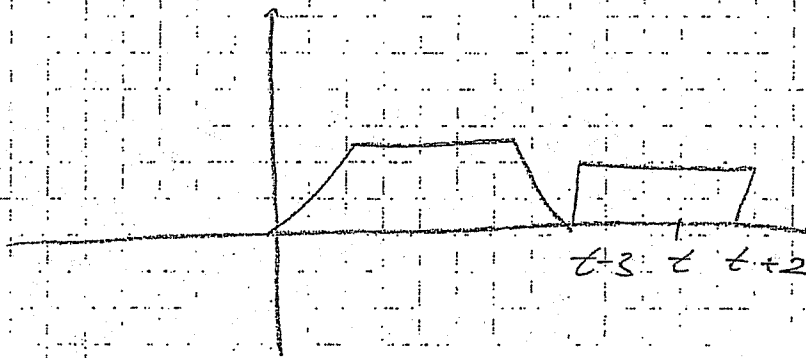

$$V_{out}(t) = \begin{cases} 0 & t < 2 \\ -5(t+2)^2 & 2 < t < 3 \\ 50t - 95 & 3 < t < 8 \\ -5t^2 + 130t - 345 & 8 < t < 13 \\ 500 & 13 < t < 18 \\ -5t^2 - 180t - 1120 & 18 < t < 23 \end{cases}$$

