

## Superposition Theorem

For LTI resistive circuit, if the circuit includes more than one independent source, the response associated with any variable over the circuit can be calculated as follow (variable any current or voltage value over any circuit element)


Step 1- Kill sources 1, ..., n-1, find the effect of n<sup>th</sup> source over the variable:  $Eff_n$

Step 2- Kill sources 1, ..., n-2, n, find the effect of n-1<sup>th</sup> source over the variable:  $Eff_{n-1}$

Step n - Kill sources 2, ..., n find " " " 1<sup>st</sup> " " the variable;  $Eff_1$

$$Eff_{Total} = \text{Algebraic sum } (Eff_1, \dots, Eff_n)$$


Ex:

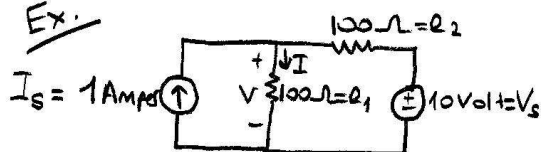

Use superposition to find  $V$  and  $I$ .

S1A:

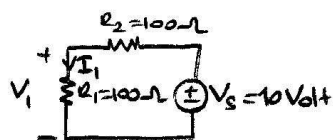
Step 1 → Kill  $I_s$  (open circuit the branch) and see effect of  $V_s$ .



$$V_1 = V_s \frac{R_1}{R_1 + R_2} = 10 \frac{100}{100 + 100} = 5V$$

$$I_1 = \frac{V_s}{R_1 + R_2} = \frac{10}{100 + 100} = 0.05 \text{ Amper}$$

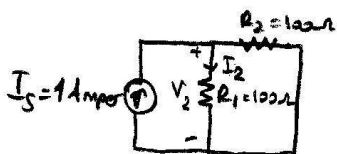Step 2 → Kill  $V_s$  (Short circuit the branch), see effect of  $I_s$



$$I_2 = I_s \frac{R_2}{R_1 + R_2} = 1 \frac{100}{100 + 100} = 0.5 \text{ Amper}$$


$$V_2 = R_1 I_2 = 100 \times 0.5 = 50 \text{ Volt}$$

$$\text{Finally } \rightarrow V = V_1 + V_2 \\ = 5 + 50 = 55 \text{ Volt}$$

$$I = I_1 + I_2 \\ = 0.05 + 0.5 = 0.55 \text{ Amper}$$

⇒ Continues

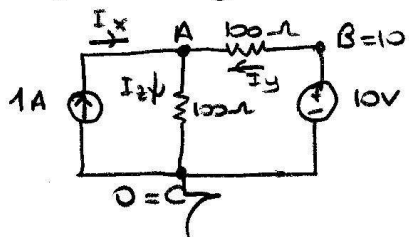Using Node Voltage without Killing the Sources:



$$I_x + I_y = I_z$$

$$I + \frac{B-A}{100} = \frac{A-C}{100}$$

$$100 + B - A = A - C$$

$$100 + B + C = 2A$$

$$110 = 2A$$

$$A = 55 \text{ Volt}$$

$$V = A - C$$



$$= 55 \text{ Volt}$$

$$I_z = \frac{A - C}{100}$$

$$= \frac{55}{100} = 0.55 \text{ A}$$

Same Result!

### Δ (Delta) - Y Connection

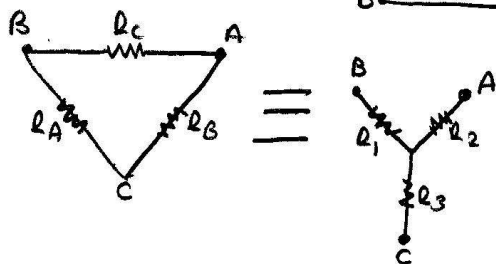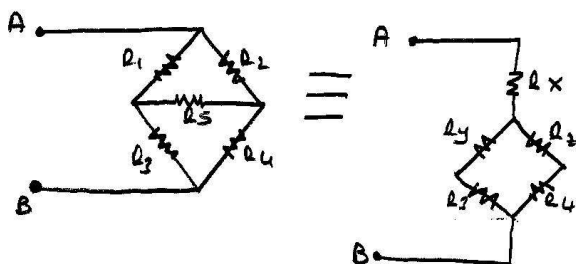


$$R_1 = \frac{R_A R_C}{R_A + R_B + R_C} \quad R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C} \quad R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} \quad R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

### Maximum Power Transfer

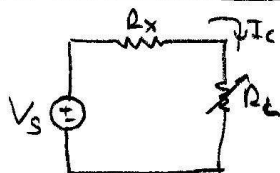

What is the value for  $R_L$  such that  $P_L = I_L^2 R_L$  is maximum.

$$I_L = \frac{V_s}{R_x + R_L}$$

$$P_L = \left( \frac{V_s}{R_x + R_L} \right)^2 R_L = \frac{V_s^2}{(R_x + R_L)^2} R_L$$

To find the  $R_L$  value where  $P_L$  is maximized.

$$\frac{dP_L}{dR_L} = 0 = V_S^2 \left[ \frac{(R_x + R_L)^2 - 2R_L(R_x + R_L)}{(R_x + R_L)^4} \right] = 0$$

$$(R_x + R_L)^2 - 2R_L(R_x + R_L) = 0$$

$$(R_x + R_L) [R_x + R_L - 2R_L] = 0$$

$$(R_x + R_L)(R_x - R_L) = 0$$


$$R_x + R_L = 0 \quad R_x = -R_L \text{ (not valid since } R_L > 0)$$

$$R_x - R_L = 0 \quad R_x = R_L \text{ (valid)}$$

For maximum power transfer to  $R_L$ ,  $R_L = R_x$

$$P_{L \max} \Big|_{R_L = R_x} = \frac{V_S^2 R_x}{(R_x + R_x)^2} = \frac{V_S^2}{4R_x}$$





$$P_{L \max} = \frac{V_S^2}{4R_x}$$

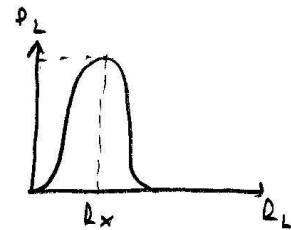


Ex.

Active source  $\rightarrow$  It gives power to it's circuit

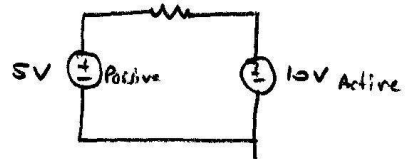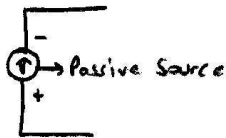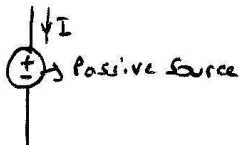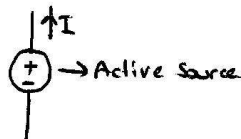Passive source  $\rightarrow$  It takes power from the circuit.



Ex.

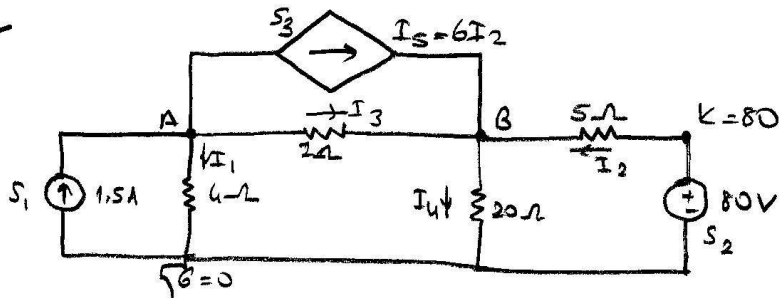

Find the power associated with the sources indicating whether they are active or passive.

Soln.

Node A

$$1.5 = I_1 + I_3 + \frac{I_S}{6I_2}$$

$$1.5 = \frac{A-6}{4} + \frac{A-B}{2} + 6 \frac{K-B}{5} \quad \begin{matrix} K=80 \\ G=0 \end{matrix}$$

Node B

$$I_3 + I_2 + \frac{I_S}{6I_2} = I_4$$

$$\frac{A-B}{2} + 7 \frac{K-B}{5} = \frac{B-6}{20} \quad \begin{matrix} K=80 \\ G=0 \end{matrix}$$

$$I_3 + 7I_2 = I_4$$

$$\begin{aligned} A &= 10 \text{ Volt} \\ B &= 60 \text{ Volt} \end{aligned}$$

For S1

$$V_1 = A - 6 = 10 - 0 = 10 \text{ V } S_1 \text{ is active source}$$

For S2

$$I_2 = \frac{80-60}{5} = 4 \text{ A } S_2 \text{ is active source}$$


For S3

$$I_2 = 4 \text{ A} \rightarrow I_S = 24 \text{ A } (B-A) = V_3 = 50 \text{ V } S_3 \text{ is active source}$$

Total Power Supplied to the Circuit

$$P_T = P_{S_1} + P_{S_2} + P_{S_3} \quad (\text{since all sources are active})$$
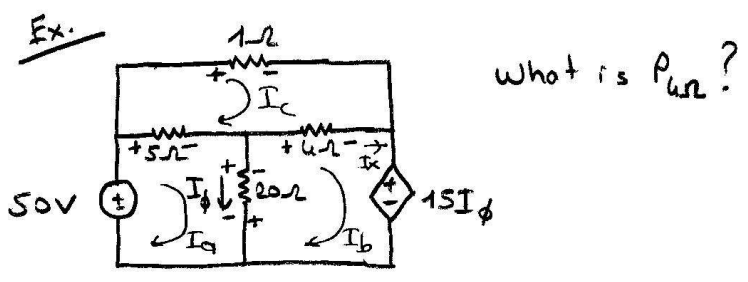
$$\begin{aligned} P_T &= V_1 \cdot 1.5 + 50 I_2 + V_3 6 I_2 \\ &= 10 \times 1.5 + 50 \times 4 + 50 \times 24 \\ &= 1535 \text{ watt} \end{aligned}$$



Soln.

Mesh Ia

$$-50 + 5(I_a - I_c) + 20(I_a - I_b) = 0$$

Mesh Ic

$$1I_c + 4(I_c - I_b) + 5(I_c - I_a) = 0$$

Mesh Ib

$$20(I_b - I_a) + 4(I_b - I_c) + 15I_\phi = 0$$

$(I_a - I_b)$

$$50 = 25I_a - 20I_b - 5I_c$$

$$0 = -5I_a + 9I_b - 4I_c$$


$$0 = -5I_a - 4I_b + 10I_c$$

$$\begin{bmatrix} 25 & -20 & -5 \\ -5 & 9 & -4 \\ -5 & -4 & 10 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix} \quad \begin{matrix} I_b = 28A \\ I_c = 26A \end{matrix}$$

$$I_x = I_b - I_c = 28 - 26 = 2A$$

$$P_{ux} = 4 \times (2)^2 = 16 \text{ Watt.}$$

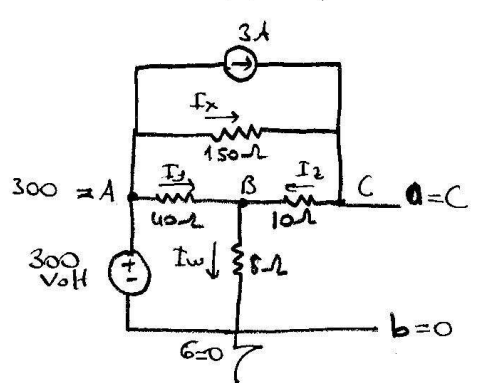Ex. Find thevenin equivalent circuit w.r.t. a-b



Soln.

For  $V_{Th} = V_{ab}$

Node B

$$I_y + I_2 = I_w$$

$$\frac{A-B}{40} + \frac{C-B}{10} = \frac{B-0}{8}$$

Node C



$$3 + I_x = I_2$$

$$3 + \frac{A-C}{150} = \frac{C-B}{10}$$

$$C = 120, \quad V_{ob} = C - b = 120 - 0$$

$$V_{Th} = V_{ob} = 120$$

For  $R_{Th}$ , kill independent sources

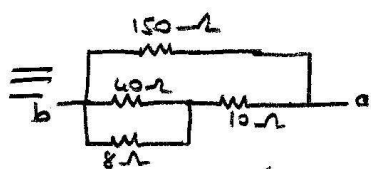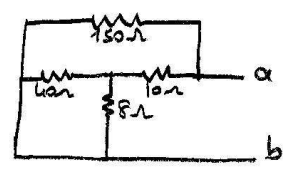


$$R_{ob} = R_{Th} = ((40 \parallel 8) + 10) \parallel 150$$

$$R_{Th} = \left( \frac{40 \times 8}{40 + 8} + 10 \right) \parallel 150$$

$$= \left( \frac{800}{48} \right) \parallel 150 = 15 \Omega \parallel$$

# Basic Concepts About AC Analysis

## Sine Wave

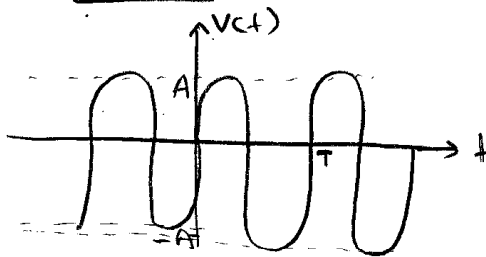

$T =$  Period (seconds)

$$f = \frac{1}{T} \text{ (Hz)}$$


$$V(t) = V_p \sin(2\pi ft)$$

$$V_p = A \rightarrow \text{peak value}$$

$$-V_p = -A$$

$$V_{pp} = 2A \rightarrow \text{peak-to-peak value}$$

## Root-mean-square value (RMS)

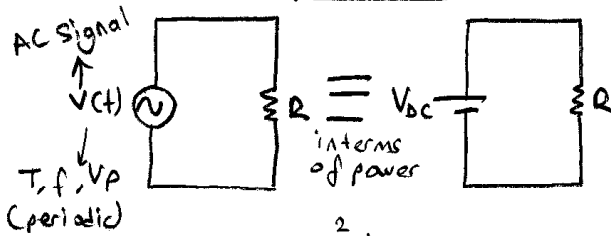

\* what is the value for  $V_{DC}$  such that ( $V_{DC}$  is a DC Value) both circuits produce some amount of energy in the same period of time?

$$P(t) = \frac{V(t)^2}{R}$$

instantaneous power

$$E(t) = \int_0^t P(t') dt' = \int_0^t \frac{V^2(t')}{R} dt'$$

$$E(T) = \int_0^T \frac{V^2(t')}{R} dt'$$

energy produced in a single period for AC circuit

for the DC circuit

$$P = \frac{V_{DC}^2}{R}$$

$$E(T) = \frac{V_{DC}^2}{R} T$$

$$\int_0^T \frac{V^2(t')}{R} dt' = \frac{V_{DC}^2}{R} T$$

$$V_{DC} = \sqrt{\frac{1}{T} \int_0^T V^2(t') dt'}$$

$V_{RMS} \rightarrow$  Root-Mean-Square

Let's find RMS of a sine wave;

$$V(t) = V_p \sin(2\pi ft) = V_p \sin\left(\frac{2\pi t}{T}\right)$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \sin^2\left(\frac{2\pi t}{T}\right) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T V_p^2 \left(1 - \cos\left(\frac{4\pi t}{T}\right)\right) dt}$$

$$= \sqrt{\frac{V_p^2}{2T} \left(t - \frac{T}{4\pi} \sin\left(\frac{4\pi t}{T}\right)\right) \Big|_0^T}$$

$$= \sqrt{\frac{V_p^2}{2T} \left(T - \frac{T}{4\pi} \sin\left(\frac{4\pi T}{T}\right) - \left(0 - \frac{T}{4\pi} \sin(0)\right)\right)}$$

$$= \sqrt{\frac{V_p^2 T}{2T}} = \frac{V_p}{\sqrt{2}}$$

for sine wave  $V(t) = V_p \sin\left(\frac{2\pi t}{T}\right) \rightarrow V_{RMS} = \frac{V_p}{\sqrt{2}}$

### Average Value

$$V_{avg} = \frac{1}{T} \int_0^T V(t') dt'$$

$V_{avg}$  gives the DC content in a signal

in oscilloscope;

DC pressed  $\rightarrow$  DC + DC

AC pressed  $\rightarrow$  AC

$\rightarrow$   $V_{avg}$  formula

Let's calculate average value for a sine wave;

$$V(t) = V_p \sin\left(\frac{2\pi t}{T}\right)$$

$$V_{avg, \text{sine}} = \frac{1}{T} \int_0^T V_p \sin\left(\frac{2\pi t}{T}\right) dt$$

$$= \frac{1}{T} V_p \frac{T}{2\pi} \left(-\cos\left(\frac{2\pi t}{T}\right)\right) \Big|_0^T$$

$$= \frac{-V_p}{2\pi} \left[ \underbrace{\cos(2\pi)}_1 - \underbrace{\cos(0)}_1 \right]$$


$$V_{avg, \text{sine}} = 0$$



Ex.  $v(t) = st \sin\left(\frac{2\pi t}{T}\right)$  What is  $V_{avg}(v(t))$ ?

$$\begin{aligned} V_{avg}(v(t)) &= \frac{1}{T} \int_0^T \left[ st \sin\left(\frac{2\pi t}{T}\right) \right] dt \\ &= \frac{1}{T} \left[ st - \frac{T}{2\pi} \cos\left(\frac{2\pi t}{T}\right) \right] \Big|_0^T \\ &= \frac{1}{T} \left[ s(T-0) - \frac{T}{2\pi} (\cos(2\pi) - \cos(0)) \right] \end{aligned}$$

$$v(t) = s_{II}$$

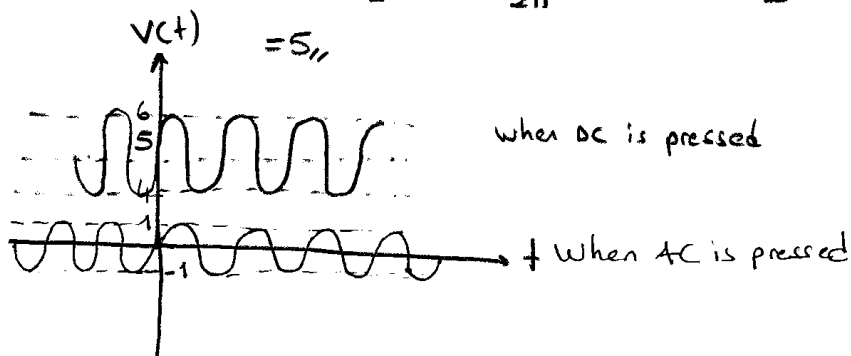

Ex.  $v(t) = \begin{cases} A \sin\left(\frac{2\pi t}{T}\right) & \text{when } 0 < t < T/2 \\ 0 & \text{when } T/2 < t < T \end{cases}$   
 $v(t)$  periodic with  $T$ .  $V_{avg}$  and  $V_{rms}$ ?

$$\begin{aligned} V_{avg}(v(t)) &= \frac{1}{T} \int_0^T v(t) dt \\ &= \frac{1}{T} \left[ \int_0^{T/2} A \sin\left(\frac{2\pi t}{T}\right) dt + \int_{T/2}^T 0 dt \right] \\ &= \frac{1}{T} \left[ A \frac{T}{2\pi} \left[ -\cos\left(\frac{2\pi t}{T}\right) \right] \Big|_0^{T/2} + 0 \right] \\ &= \frac{1}{T} \left[ \frac{-AT}{2\pi} \left[ \cos(\pi) - \cos(0) \right] + 0 \right] \\ &= -\frac{A(-2)T}{T 2\pi} = \frac{A}{\pi} \end{aligned}$$

$$\begin{aligned}
V_{\text{RMS}(v(t))} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \\
&= \sqrt{\frac{1}{T} \left[ \int_0^{T/2} H^2 \sin^2\left(\frac{2\pi t}{T}\right) dt + \int_{T/2}^T 0^2 dt \right]} \\
&= \sqrt{\frac{A^2}{T} \frac{1}{2} \int_0^{T/2} (1 - \cos\left(\frac{4\pi t}{T}\right)) dt} \\
&= \sqrt{\frac{A^2}{T} \frac{1}{2} \left[ t - \frac{T}{4\pi} \sin\left(\frac{4\pi t}{T}\right) \right] \Big|_0^{T/2}} \\
&= \sqrt{\frac{A^2}{T} \frac{1}{2} \left[ \left(\frac{T}{2} - 0\right) - \frac{T}{4\pi} (\sin(2\pi) - \sin(0)) \right]} \\
&= \sqrt{\frac{A^2}{T} \frac{1}{2} \cdot \frac{T}{2}} = \frac{A}{2} \quad V_{\text{RMS}(v(t))} = \frac{A}{2}
\end{aligned}$$