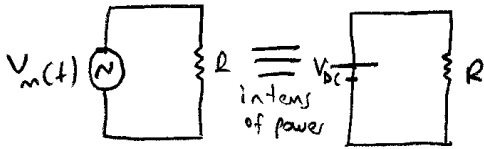


03.07.2010


## Summary

AC circuit



$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

## Square Wave

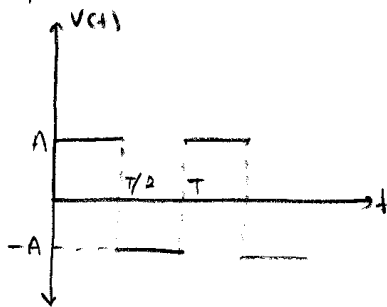

$$v(t) = \begin{cases} A & 0 \leq t < T/2 \\ -A & T/2 \leq t < T \end{cases}$$


$v(t)$  is periodic with  $T$

Let's find average and RMS values for square wave;

$$\begin{aligned} V_{avg, sq} &= \frac{1}{T} \int_0^T v(t) dt \\ &= \frac{1}{T} \left[ \int_0^{T/2} A dt + \int_{T/2}^T -A dt \right] \\ &= \frac{1}{T} \left[ A \left. t \right|_0^{T/2} + (-A) \left. t \right|_{T/2}^T \right] \\ &= \frac{1}{T} \left[ A(T/2 - 0) + (-A)(T - T/2) \right] = 0 \end{aligned}$$

$$\begin{aligned} V_{RMS} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \\ &= \sqrt{\frac{1}{T} \left[ \int_0^{T/2} A^2 dt + \int_{T/2}^T (-A)^2 dt \right]} \\ &= \sqrt{\frac{1}{T} \left[ \int_0^{T/2} A^2 dt + \int_{T/2}^T A^2 dt \right]} \\ &= \sqrt{\frac{1}{T} A^2 \left[ \left. t \right|_0^{T/2} + \left. t \right|_{T/2}^T \right]} = A_{RMS} \end{aligned}$$

### Triangular Wave

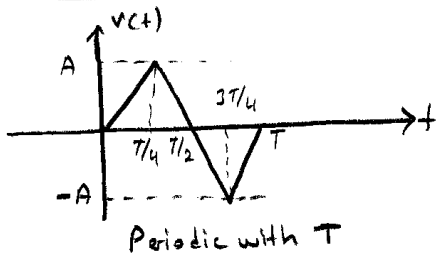

$$v(t) = \begin{cases} \frac{4A}{T} t & 0 \leq t < T/4 \\ -\frac{4A}{T} [t - T/2] & T/4 \leq t < 3T/4 \\ \frac{4A}{T} (t - T) & 3T/4 \leq t < T \end{cases}$$


For triangular wave;

$$V_{avg}(v(t)) = 0$$

$$V_{rms}(v(t)) = \frac{A}{\sqrt{3}}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$v^2(t)$  second order parabolas

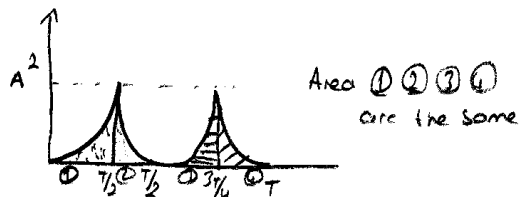

So

$$\sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{T} 4 \int_0^{T/4} v^2(t) dt}$$

for triangular wave


$$= \sqrt{\frac{1}{T} 4 \int_0^{T/4} \left(\frac{4A}{T} t\right)^2 dt}$$

$$= \sqrt{\frac{1}{T} 4 \frac{16A^2}{T^2} \int_0^{T/4} t^2 dt}$$

$$= \sqrt{\frac{64}{T^3} \frac{A^2}{3} \left| \frac{t^3}{3} \right|_0^{T/4}}$$

$$= \sqrt{\frac{64A^2}{T^3 \times 3} \left[ \frac{T^3}{64} - 0 \right]} = \frac{A}{\sqrt{3}}$$

Ex.

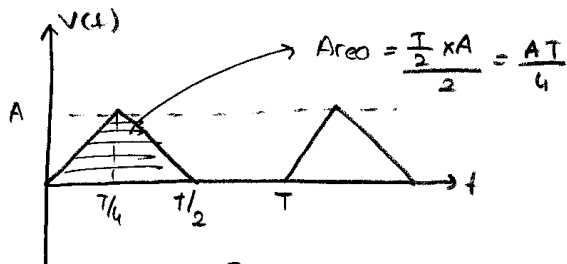


$$V_{\text{avg } v(t)} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \frac{AT}{4} = \frac{A}{4}$$


find the area under this singular up to x-axis

$$v(t) = \begin{cases} \frac{4A}{T} t & 0 \leq t < T/4 \\ -\frac{4A}{T} (t - T/2) & T/4 \leq t < T/2 \\ 0 & T/2 \leq t < T \end{cases}$$

$$\begin{aligned} V_{\text{avg } v(t)} &= \frac{1}{T} \int_0^T v(t) dt \\ &= \frac{1}{T} \left[ \int_0^{T/4} \frac{4A}{T} t dt + \int_{T/4}^{T/2} \left(-\frac{4A}{T}\right) \left(t - \frac{T}{2}\right) dt + \int_{T/2}^T 0 dt \right] \\ &= \frac{1}{T} \left[ \left. \frac{4A}{T} \frac{t^2}{2} \right|_0^{T/4} + \left(-\frac{4A}{T}\right) \left( \frac{t^2}{2} - \frac{T}{2} t \right) \Big|_{T/4}^{T/2} + 0 \right] \\ &= \frac{1}{T} \left[ \frac{2A}{T} \left[ \frac{t^2}{16} - 0 \right] + \left(-\frac{4A}{T}\right) \left[ \frac{1}{2} \left( \frac{T^2}{4} - \frac{T^2}{16} \right) - \frac{T}{2} \left( \frac{T}{4} - \frac{T}{4} \right) \right] \right] \\ &= \frac{1}{T} \left[ \frac{2AT}{16} + \left(-\frac{4A}{T}\right) \left[ \frac{1}{2} \frac{3T^2}{16} - \frac{T^2}{8} \right] \right] \\ &= \frac{1}{T} \left[ \frac{AT}{8} + \left(-\frac{4A}{T}\right) \left[ \frac{3T^2}{32} - \frac{4T^2}{32} \right] \right] = \frac{A}{8} + \frac{4A}{32} = \frac{A}{4} \end{aligned}$$

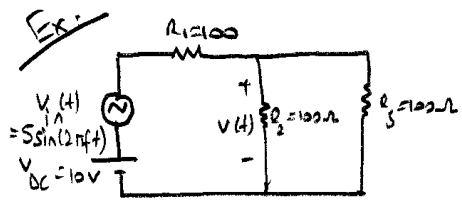


kill  $v_i(t)$  (only DC circuit)

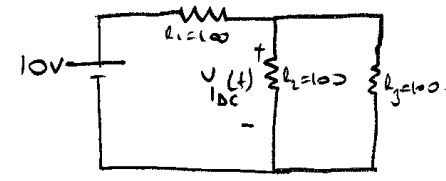

$$V_{DC}(t) = \frac{10}{3}$$

kill  $v_{DC}$  (only AC circuit)

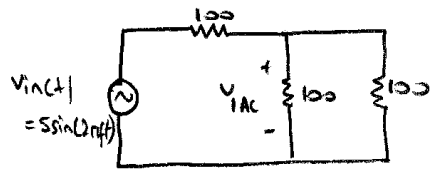

$$V_{AC}(t) = \frac{5}{3} \sin(2\pi ft)$$


$$v(t) = v_{DC} + v_{AC} = \frac{10}{3} + \frac{5}{3} \sin(2\pi ft)$$

### Complex Domain Operations

$$A = a_1 + a_2 j \quad \text{Re}\{A\} = a_1$$

$$\text{Im}\{A\} = a_2$$

Cartesian Representation

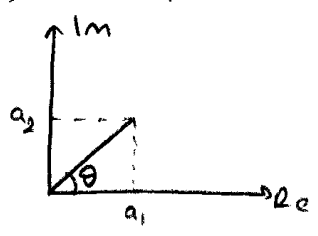

$$A = \underbrace{\sqrt{a_1^2 + a_2^2}}_{\text{magnitude}} e^{j\theta}$$

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$\cos\theta = \frac{a_1}{\sqrt{a_1^2 + a_2^2}}$$

$$A = \underbrace{\sqrt{a_1^2 + a_2^2}}_{\text{polar representation}} e^{j\theta}$$

$$\sin\theta = \frac{a_2}{\sqrt{a_1^2 + a_2^2}}$$

$$\theta = \angle A \text{ phase}$$

$$A = a_1 + a_2j \quad B = b_1 + b_2j$$


$$A + B = (a_1 + b_1) + j(a_2 + b_2)$$

$$A - B = (a_1 - b_1) + j(a_2 - b_2)$$

$$\frac{A}{B} = \frac{a_1 + a_2j}{b_1 + b_2j} \cdot \frac{(b_1 - b_2j)}{(b_1 - b_2j)} = \frac{(a_1 + a_2j)(b_1 - b_2j)}{b_1^2 + b_2^2}$$

$$B = b_1 + b_2j = \sqrt{b_1^2 + b_2^2} e^{j\theta} \quad \angle B = \theta$$
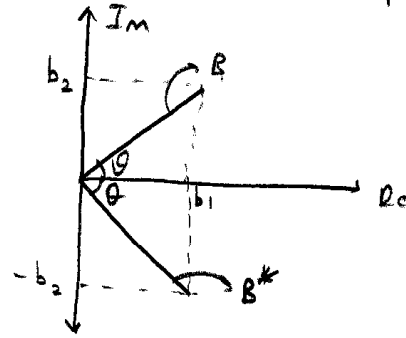
$$B^* = b_1 - b_2j \rightarrow \text{conjugate} = \sqrt{b_1^2 + b_2^2} e^{-j\theta} \quad \angle B^* = -\theta$$



$$A = |A| e^{j\theta} \rightarrow \text{polar}$$


$$B = |B| e^{j\beta} \rightarrow \text{polar}$$

$$A \times B = |A||B| e^{j(\theta + \beta)}$$


$$\frac{A}{B} = \left| \frac{A}{B} \right| e^{j(\theta - \beta)}$$
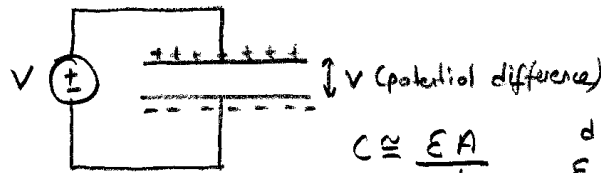
### # Capacitors #

Two terminal element used to store electrical energy.



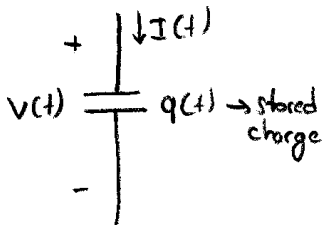
$d \rightarrow$  distance b/w. plates  
 $E \rightarrow$  dielectric constant  
 $A \rightarrow$  active area of the plates



$$I(t) = \frac{dq(t)}{dt} \rightarrow \int_{t_0}^t I(t) dt = \int_{q_0}^{q(t)} dq(t)$$

$$\int_{t_0}^t I(t) dt = q(t) - q_0$$

For LTI Capacitors

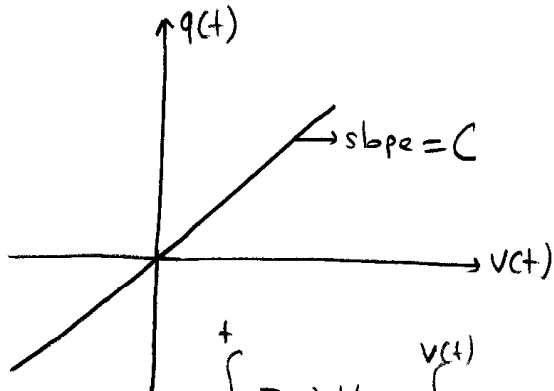

$$q(t) = Cv(t) \text{ (for LTI capacitors)}$$

$$\frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$$

$$I(t) = C \frac{dv(t)}{dt}$$

$$\int_{t_0}^t I(t') dt' = \int_{v_0}^{v(t)} C dv(t')$$

$$\int_{t_0}^t I(t') dt' = C [v(t) - v_0]$$

$$v(t) = v_0 + \frac{1}{C} \int_{t_0}^t I(t') dt'$$

- $v(t)$  depends on  $I(t)$ ,  $v_0$ ,  $C$
- A capacitor has a memory.


\* If  $v(t) = K$  (constant DC value) then

$$I(t) = C \frac{dK}{dt} = 0 //$$


(Capacitor acts as open circuit for DC voltage excitation)

\* If  $I(t)$  is bounded, i.e.  $\|I(t)\| \leq M$  for  $\forall t$  then, Voltage across the capacitor is a continuous function.

$I(t) \rightarrow$  bounded

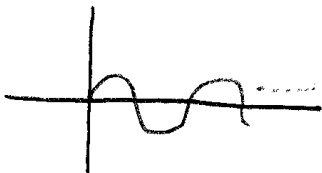


### Series Connection of Capacitors

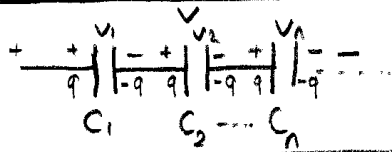

$$\frac{1}{C_{\text{Total}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

### Parallel Connection of Capacitors

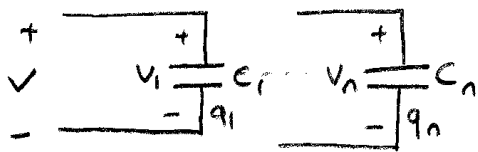

$$V = V_1 = V_2 = \dots = V_n$$

$$q_{\text{Total}} = q_1 + \dots + q_n$$

$$C_{\text{Total}} = C_1 + \dots + C_n$$

### ~ Power and Energy ~

$$P(t) = V(t)I(t) = V(t)C \frac{dV(t)}{dt}$$

$\downarrow$  instantaneous power       $\uparrow$  for LTI capacitors

$$= \frac{1}{2} \frac{d}{dt} [CV^2(t)] = P(t)$$

$$W(t, t_0) = \int_{t_0}^t P(t') dt'$$

The work done depends on initial time and final time.

$$= \int_{t_0}^t \frac{1}{2} C \frac{d}{dt'} [V^2(t')] dt'$$

$$= \int_{V_0}^{V(t)} \frac{1}{2} C dV^2(t)$$

$$= \frac{1}{2} C [V^2(t) - V_0^2]$$


$$W(t, t_0) = \frac{1}{2} CV^2(t) - \frac{1}{2} CV_0^2$$

If  $V_0^2 > V^2(t) \Rightarrow w(t, t_0) < 0 \Rightarrow$  Capacitor is being discharged.  
 $w(t, t_0) > 0 \Rightarrow$  " " " " charged

\* If initially capacitor is uncharged (let  $t_0 = 0$   $q_0 = 0$  and  $V_0 = 0$ )  
 $E(t) = \frac{1}{2} C V^2(t)$

\* If  $P(t) > 0 \Rightarrow$  Capacitor is being charged (storing energy)

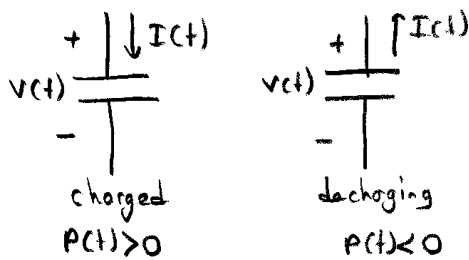
\* If  $P(t) < 0 \Rightarrow$  " " " " discharged (supplying energy to its circuit)



\* Capacitor is a lossless energy storage element.

$E(t) = \frac{1}{2} C V^2(t) \geq 0$  when  $C > 0$   
 Capacitor is a passive element.

### Capacitors in DC Circuits

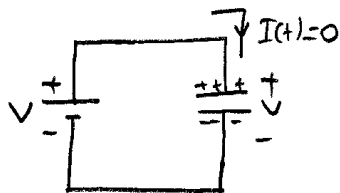

\* A capacitor blocks DC current

\* It acts as open circuit when DC voltage is applied.



## Capacitors in AC Circuits

$$Q = CV \quad I = C \frac{dV}{dt}$$

In Laplace Domain

$$I(s) = Cs V(s)$$

$$\frac{V(s)}{I(s)} = \frac{1}{Cs} \xrightarrow[\text{domain } s=j\omega]{\text{in frequency}} \frac{V(j\omega)}{I(j\omega)} = \frac{1}{j\omega C} = \frac{1}{j2\pi f C}$$

$$\omega = 2\pi f \quad \frac{1}{\text{sec}} = \text{Hertz}$$


angular frequency      frequency

$$\frac{V(j\omega)}{I(j\omega)} = \frac{-j}{\omega C} = -jX_C$$

$X_C \rightarrow$  Complex resistance

$X_C = \frac{1}{2\pi f C} \Rightarrow$  When  $f$  increase  $|X_C|$  decreases and much more current will pass over the capacitor.

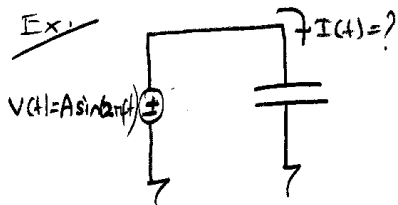\* A capacitor acts as short circuit for AC excitation.




$$I(t) = C \frac{dV(t)}{dt}$$

$$= C \frac{d}{dt} A \sin(2\pi ft)$$

$$= CA 2\pi f \cos(2\pi ft)$$
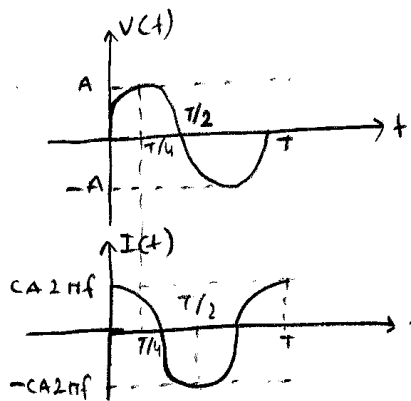
$$I(t) = CA 2\pi f \sin(2\pi ft + 90^\circ)$$



\* Current leads Voltage  $90^\circ$  for capacitor.

## # Inductors #

Any device that stores magnetical energy is called as inductor. For inductors the flux over the inductor, is a function of the current passing through the inductor.

$$\text{webers} \leftarrow \phi(t) = \phi(I(t), t)$$

$$\frac{d\phi}{dt} = V(t) \quad (\text{Faraday's Law})$$

### LTI Inductors

$$\phi = L I$$

constant  $\leftarrow$  Inductance Value (Henry)


$$\frac{d\phi}{dt} = L \frac{dI}{dt} \Rightarrow \boxed{V = L \frac{dI}{dt}} \rightarrow I(t) = I_0 + \frac{1}{L} \int_{t_0}^t V(t') dt'$$

\* The current over the inductor is a continuous function of time if the voltage across the inductor is bounded for  $\forall t$ .

x Assume  $I(t) = K$  (constant DC excitation)  $V = L \frac{dI}{dt} = L \frac{dK}{dt} = 0$


$\hookrightarrow$  An inductor behaves as short circuit for DC current excitation.

### Series Connection of Inductors

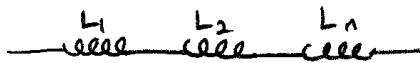

$$\boxed{L_{\text{Total}} = L_1 + L_2 + \dots + L_n}$$

## Parallel Connection of Inductors

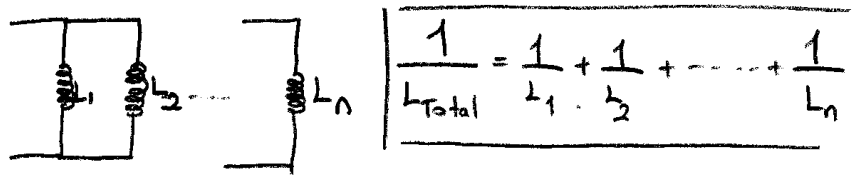

## ~ Power and Energy ~

$$P(t) = V(t)I(t) \stackrel{\text{LTI Inductor}}{=} L \frac{dI(t)}{dt} I(t)$$

↑  
instantaneous  
power

$$P(t) = \frac{1}{2} L \left[ \frac{d}{dt} I^2(t) \right]$$

$$W(t, t_0) = \int_0^t P(t') dt' = \int_0^t \frac{1}{2} L \left[ \frac{d}{dt} I^2(t') \right] dt'$$

$$= \int_{I_0}^{I_t} \frac{1}{2} L dI^2(t) = \frac{1}{2} L [I^2(t) - I_0^2]$$

$$= \frac{1}{2} L I^2(t) - \frac{1}{2} L I_0^2$$

if  $I^2(t) > I_0^2$  inductor is being charged

if  $I^2(t) < I_0^2$  " " " discharging.

