
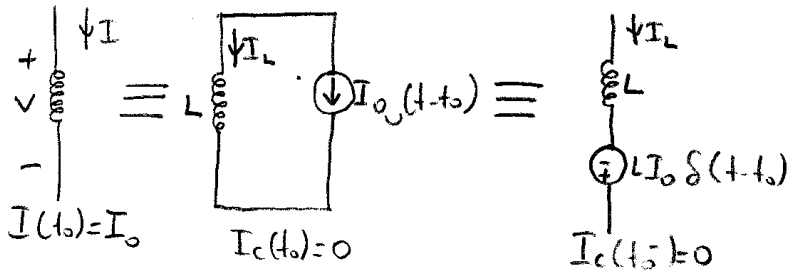


For Inductor

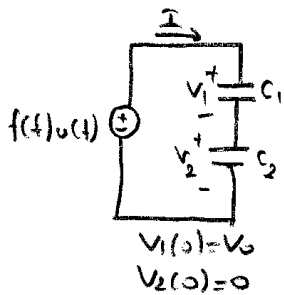


Voltage Division



Find $V_1(t), V_2(t)$

Using initial condition models

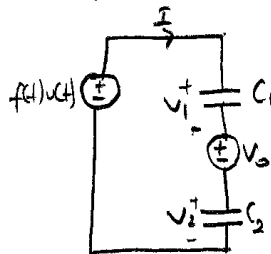

$$I(t) = C_{total} \frac{d}{dt} V_{total}$$

$$I(t) = \frac{C_1 C_2}{C_1 + C_2} \frac{d}{dt} [f(t)u(t) - V_0 u(t)]$$

$$I(t) = \frac{C_1 C_2}{C_1 + C_2} [f'(t)u(t) + f(t)\delta(t) - V_0 \delta(t)]$$

$$I(t) = \frac{C_1 C_2}{C_1 + C_2} [f'(t)u(t) + (f(0) - V_0)\delta(t)]$$

$$V_1(t) = V_1(0) + \frac{1}{C_1} \int_0^t I(t') dt'$$

$$V_1(t) = V_1(0) + \frac{1}{C_1} \int_0^t \frac{C_1 C_2}{C_1 + C_2} [f'(t')u(t') + (f(0) - V_0)\delta(t')] dt'$$

$$V_1(t) = V_1(0) + \frac{C_2}{C_1 + C_2} \left[\int_0^t f'(t')u(t') dt' + \int_0^t (f(0) - V_0)\delta(t') dt' \right]$$

$$= V_1(0) + \frac{C_2}{C_1 + C_2} [f(t) - f(0)]u(t) + \frac{C_1}{C_1 + C_2} [f(0) - V_0]u(t)$$

$$= V_1(0) + \frac{C_2}{C_1 + C_2} [f(t) - V_0]u(t)$$

$$= V_0 + \frac{C_2}{C_1 + C_2} [f(t) - V_0]u(t) \rightarrow \boxed{V_0 + \frac{C_2}{C_1 + C_2} (f(t) - V_0) \text{ when } t > 0}$$

For $v_2(t)$

$$v_2(t) = f(t)u(t) - v_1(t)$$


$$= f(t)u(t) - \left[v_0 + \frac{C_2}{C_1+C_2} [f(t) - v_0] u(t) \right]$$

$$= f(t)u(t) - v_0 - \frac{C_2}{C_1+C_2} f(t)u(t) + v_0 \frac{C_2}{C_1+C_2} u(t)$$

$$= f(t)u(t) \left(\frac{C_1}{C_1+C_2} \right) + v_0 \frac{C_2}{C_1+C_2} u(t) - v_0 \text{ for } t > 0$$

$$\cong \left[f(t) - v_0 \right] \frac{C_1}{C_1+C_2} u(t)$$

Voltage Division 2

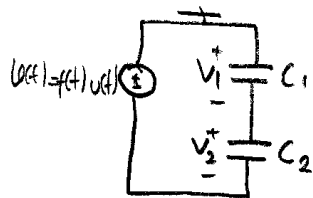


$$v_1(t) = \frac{C_2}{C_1+C_2} u(t)$$

$$v_2(t) = \frac{C_1}{C_1+C_2} u(t)$$

$$v_1(0) = v_2(0) = 0$$

Exⁿ

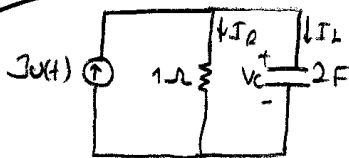

a) $v_C(0^-) = 0$, find $v_C(0^+)$, $I_R(0^-)$, $I_R(0^+)$, $I_C(0^-)$, $I_C(0^+)$

* Impulsive sources might occur when:

- There is really an impulsive current or voltage source.
- Connection of an extra circuit element (like capacitor, inductor) is provided.

$$v_C(0^+) = v_C(0^-) = 0 \text{ (continuous since no impulsive source exists)}$$

$$I_R(0^-) = \frac{v_R(0^-)}{1} = \frac{v_C(0^-)}{1} = \frac{0}{1} = 0$$

$$I_s = 3u(t) = I_R + I_L$$

$$I_s(\bar{0}) = I_R(\bar{0}) + I_L(\bar{0})$$

$$3u(\bar{0}) = 0 + I_L(\bar{0}) \rightarrow I_L(\bar{0}) = 0$$
$$0 = 0 \rightarrow I_L(\bar{0})$$

$$I_R(\bar{0}^+) = \frac{V_R(\bar{0}^+)}{R} = \frac{V_C(\bar{0}^+)}{R} = \frac{0}{R} = 0$$

$$I_s(\bar{0}^+) = I_R(\bar{0}^+) + I_C(\bar{0}^+)$$

$$3u(\bar{0}^+) = 0 + I_C(\bar{0}^+)$$

$$3 = 0 + I_C(\bar{0}^+)$$

$$I_C(\bar{0}^+) = 3$$

b) $I_F V_C(\bar{0}^-) = 4 \text{ Volt}$

$$V_C(\bar{0}^+) = V_C(\bar{0}^-) = 4 \text{ Volt}$$

$$I_R(\bar{0}^-) = \frac{V_C(\bar{0}^-)}{R} = \frac{4}{1} = 4 \text{ Amper}$$

$$I_s(\bar{0}^-) = I_R(\bar{0}^-) + I_C(\bar{0}^-)$$

$$3u(\bar{0}^-) = 4 + I_C(\bar{0}^-)$$

$$0 = 4 + I_C(\bar{0}^-)$$

$$I_C(\bar{0}^-) = -4 \text{ Amper}$$


$$I_R(\bar{0}^+) = \frac{V_C(\bar{0}^+)}{R} = \frac{4}{1} = 4 \text{ Amper}$$

$$I_s(\bar{0}^+) = I_R(\bar{0}^+) + I_C(\bar{0}^+)$$

$$3 = 4 + I_C(\bar{0}^+)$$

$$I_C(\bar{0}^+) = -1 \text{ Amper}$$

Current Division

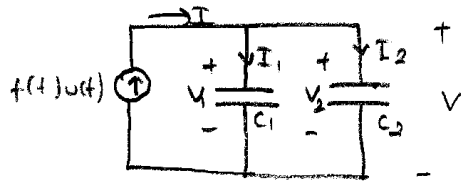

$$V_1(0^-) = V_2(0^-) = 0$$

$$I_1 = C_1 \frac{dV_1}{dt} \quad I_2 = C_2 \frac{dV_2}{dt} \quad C_{\text{Total}} = C_1 + C_2$$

$$V(t) = V(0) + \frac{1}{C_{\text{Total}}} \int_0^t I(t') dt'$$

$$V(t) = V(0) + \frac{1}{C_1 + C_2} \int_0^t f(t') u(t') dt'$$

$$\int f(t) dt = F(t)$$


$$V(t) = 0 + \frac{1}{C_1 + C_2} [F(t) - F(0)] u(t)$$

$$I_1 = C_1 \frac{dV_1}{dt} = C_1 \frac{dV}{dt}$$

$$= C_1 \frac{d}{dt} \frac{1}{C_1 + C_2} [F(t)u(t) - F(0)u(t)]$$

$$= \frac{C_1}{C_1 + C_2} [f(t)u(t) + F(t)\delta(t) - F(0)\delta(t)]$$
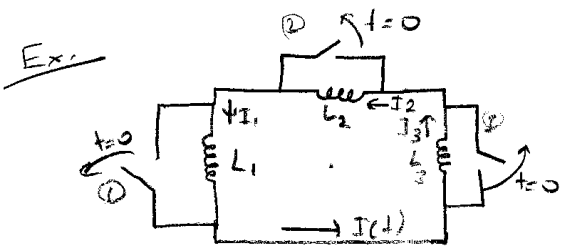
$$I_1(t) = \frac{C_1}{C_1 + C_2} f(t)u(t)$$



When $t=0$ all the three switches ①, ②, ③ are opened



$$I_1(0^-) = I_{10}$$

$$I_2(0^-) = I_{20}$$

$$I_3(0^-) = I_{30}$$

Find $I(t) \ t > 0$

Use initial condition models

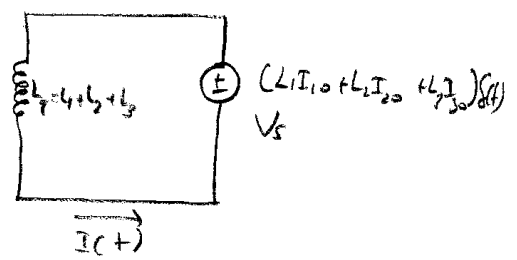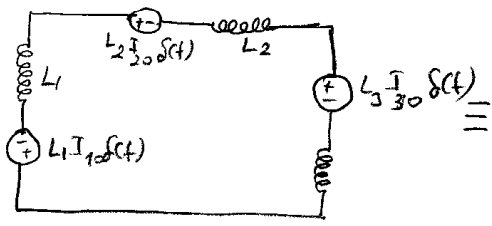


$$I(t) = I(0) + \frac{1}{L_{\text{total}}} \int_0^t v_s(t') dt'$$

$$I(t) = 0 + \frac{1}{L_1 + L_2 + L_3} \int_0^t (L_1 I_{10} + L_2 I_{20} + L_3 I_{30}) \delta(t') dt'$$

$$I(t) = \frac{(L_1 I_{10} + L_2 I_{20} + L_3 I_{30}) u(t)}{L_1 + L_2 + L_3}$$

Ex-

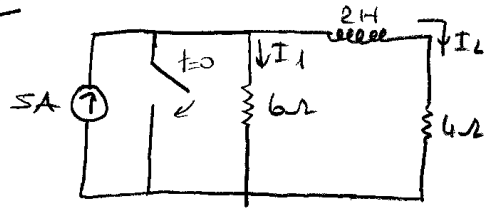


$$I_1(0^-) = 2A$$

Find $I_L(0^-), I_L(0^+), I_1(0^+)$

on $\frac{dI}{dt}(0^+)$ if the switch is closed when $t=0$

Soln:

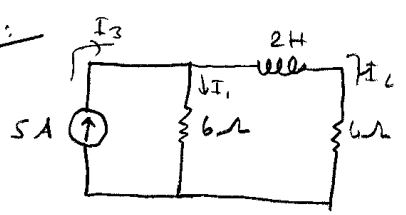

$$I_2 = I_1 + I_L$$

$$I_5(0^-) = I_1(0^-) + I_L(0^-)$$

$$5 = 2 + I_L(0^-)$$

$$I_L(0^-) = 3A$$

$$I_L(0^+) = I_L(0^-) = 3A \text{ (due to continuity property)}$$

$$V_1(0^+) = 0 \text{ (since short-circuit exists)}$$

$$F_1(0^+) = \frac{V_1(0^+)}{6} = 0$$

$$\frac{dI_L}{dt}(0^+) = ?$$

$$V_1 = V_L + V_2$$


$$V_1(0^+) = V_L(0^+) + V_2(0^+)$$

$$0 = L \frac{dI_L(0^+)}{dt} + I_L(0^+) \cdot 4 - 4I_L(0^+) = L \frac{dI_L}{dt}(0^+) - 2I_L(0^+) = \frac{dI_L}{dt}(0^+) = -6$$

First Order Circuits

$C+R \rightarrow$
 $L+R \rightarrow$ First order circuits

RC and RL Circuits

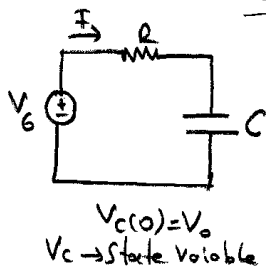

$$I(t) = C \frac{dV_C}{dt}$$


$$-V_s + \underbrace{V_R}_{RI} + V_C = 0$$

$$RC \frac{dV_C}{dt} + V_C = V_s$$

$$\boxed{\frac{dV_C}{dt} + \frac{1}{RC} V_C = \frac{1}{RC} V_s}$$

$$V_C(0) = V_0$$

$\xrightarrow{\text{dual problem}}$

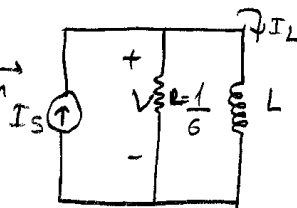

$I_L \rightarrow$ state variable

State variables determine the energy stored in the system.

$$V(t) = L \frac{dI_L}{dt}$$

$$I_s = \underbrace{I_R}_{\frac{V}{R}} + I_L$$

$$I_s = \frac{L}{R} \frac{dI_L}{dt} + I_L$$

$$\boxed{\frac{dI_L}{dt} + \frac{1}{LG} I_L = \frac{1}{LG} I_s}$$

$$I_L(0) = I_0$$

First order linear differential equations with constant coefficients

The response V_C and I_L depends on;

- ① The inputs " V_s ", " I_s "
- ② Circuit parameters; R, C, L
- ③ Initial conditions V_0, I_0

The initially stored energy in the circuit due to I_0 and V_0 will produce a non-zero solution ($V_C(t) \neq 0, I_C \neq 0$) even if there is no input to the system. ($V_0(t)=0$ and $I_C(t)=0$) (Known as zero-input response)