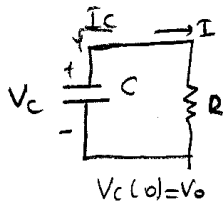


07.07.2010

Zero-Input Response ( $V_s=0, I_s=0$ )




$$I_c = -I$$

$$C \frac{dV_c}{dt} = -\frac{V_c}{R}$$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = 0$$

$$V_c(0) = V_0$$

RC

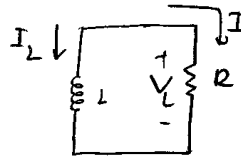

$$L = \frac{1}{G}$$

$$I_L = -I$$

$$I_L = -\frac{V_L}{R}$$

$$I_L = -\frac{L}{R} \frac{dI_L}{dt}$$

$$\frac{dI_L}{dt} + \frac{1}{LG} I_L = 0$$

$$I_L(0) = I_0$$

$$\frac{dI_L}{dt} + \frac{R}{L} I_L = 0$$

$$I_L(0) = I_0$$

RL

First order linear homogeneous constant coefficient diff-eqv.

RHS (The effect of input is zero)

$$V_c(t) = K e^{st}$$

$$I_L(t) = M e^{st}$$

$K$  and  $M$  are determined due to initial conditions.

Put the solution in diff. eqn.

$$\frac{d}{dt} (K e^{st}) + \frac{1}{RC} (K e^{st}) = 0$$

$$\frac{d}{dt} (M e^{st}) + \frac{1}{LG} (M e^{st}) = 0$$

$$K s e^{st} + \frac{1}{RC} K e^{st} = 0$$

$$M s e^{st} + \frac{1}{LG} M e^{st} = 0$$

$$\left(s + \frac{1}{RC}\right) \underbrace{K e^{st}}_{\text{non zero}} = 0$$

$$\left(s + \frac{1}{LG}\right) \underbrace{M e^{st}}_{\text{non zero}} = 0$$

$$s = -\frac{1}{RC} \text{ (natural frequency)}$$

$$s = -\frac{1}{LG} \text{ (natural frequency)}$$

$$V_c(t) = K e^{-\frac{t}{RC}} \quad t \geq 0$$

$$I_L(t) = M e^{-\frac{t}{LG}} \quad t \geq 0$$

$$V_c(0) = V_0 = K e^{-\frac{0}{RC}}$$

$$I_L(0) = I_0 = M e^{-\frac{0}{LG}}$$

$$K = V_0$$

$$M = I_0$$

$$V_c(t) = V_0 e^{-\frac{t}{RC}}$$

$$I_L(t) = I_0 e^{-\frac{t}{LG}}$$


$$\tau = RC$$

$$\tau = LG$$

Time constants.

\* Time constant: The time required for a zero input first order response to reach " $\frac{1}{e}$ " of its initial condition value.

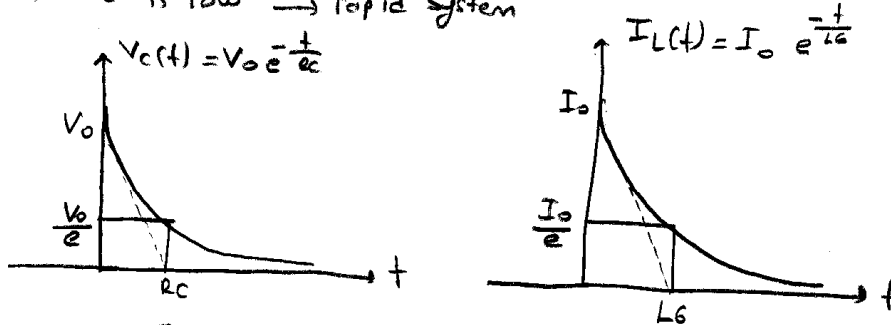if  $\tau$  is high  $\rightarrow$  slow system  
 $\tau$  is low  $\rightarrow$  rapid system




For practical application when  $t = t \gg 5\tau$  we assume that  $V_c(t) \approx 0$   $I_L(t) \approx 0$

$$I_c = C \frac{dV_c}{dt}$$

$$= C \frac{d}{dt} V_0 e^{-\frac{t}{RC}}$$


$$= -\frac{V_0}{RC} e^{-\frac{t}{RC}}$$

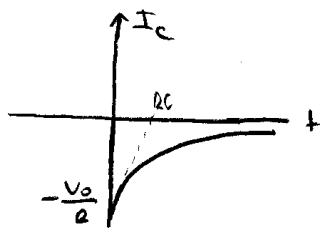

$$V_L = L \frac{dI_L}{dt}$$

$$= L \frac{d}{dt} I_0 e^{-\frac{t}{LG}}$$

$$= -\frac{I_0 L}{G} e^{-\frac{t}{LG}}$$

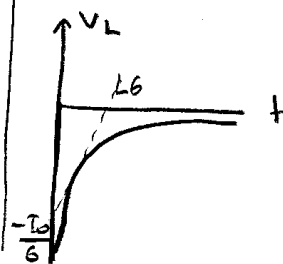

## Complete Response

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_s(t)$$

$$V_c(0) = V_0$$

→ complete response

$$V_c(t) = V_h(t) + V_p(t)$$

$V_h$  = Homogeneous (natural) solution.  
(meaning solution when  $V_s(t) = 0$ )

- It doesn't depend on input.

- It depends on initial condition, and circuit parameters.

$V_p$  = It is the solution due to input.  
(forced response)

Step ① Find  $V_p(t)$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = V_s(t)$$

Generally,  $V_p(t)$  is similar to  $V_s(t)$ .

- If  $V_s(t)$  is sinusoidal,  $V_p(t)$  is also sinusoidal.

- If " " DC, " " " DC.

- " " " exponential, " " " exponential.

Step ② Determine  $V_h(t)$


$$V_h(t) = K e^{-\frac{t}{RC}}$$

Step ③  $V_c = V_p + V_h$

Step ④ Use the initial condition

$$V_c(0) = V_0 \text{ to determine } K$$

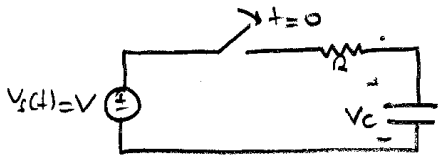Constant Input ( $V_s(t) = V$ ) <sup>constant</sup>



Step ①  $V_p = M \rightarrow \text{constant}$

$$\frac{d}{dt} M + \frac{1}{RC} M = \frac{1}{RC} V$$

$$0 + \frac{1}{RC} M = \frac{1}{RC} V \quad M = V = V_p$$

$$\boxed{V_p = V}$$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V \quad V_c(t) = \frac{1}{RC} V$$

$$V_c(0) = V_0$$


Step ②  $V_h = K e^{-\frac{t}{RC}}$

Step ③  $V_c = V_p + V_h = V + K e^{-\frac{t}{RC}}$

Step ④  $V_c(0) = V_0 = V + K e^{-\frac{0}{RC}}$

$$K = V_0 - V$$

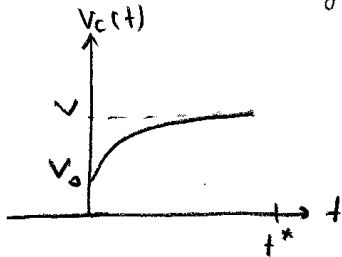Hence;  $V_c(t) = \underbrace{(V_0 - V) e^{-\frac{t}{RC}}}_{\text{homogeneous}} + \underbrace{V}_{\text{forced}}$



$$\tau = RC$$

$$t^* \gg 5RC$$

$$V_c(t) = \underbrace{(V_0 - V) e^{-\frac{t}{RC}}}_{\text{transient response}} + \underbrace{V}_{\text{steady-state response}}$$

Steady state: The response observed when  $t \rightarrow \infty$

transient response: The response that die out as  $t \rightarrow \infty$

\* Transient response is the result of sudden application of the input and the initial conditions.

### Sinusoidal Input ( $V_s = V_m \cos(\omega t)$ )

$$\frac{d}{dt} V_c + \frac{1}{RC} V_c = \frac{1}{RC} V_s(t)$$

$$V_c(0) = V_0$$

Step ①  $V_p = A_1 \cos(\omega t) + A_2 \sin(\omega t)$

$$\begin{aligned} \frac{d}{dt} (A_1 \cos(\omega t) + A_2 \sin(\omega t)) + \frac{1}{RC} (A_1 \cos(\omega t) + A_2 \sin(\omega t)) &= \frac{1}{RC} V_m \cos(\omega t) \\ -\omega A_1 \sin(\omega t) + \omega A_2 \cos(\omega t) + \frac{1}{RC} (A_1 \cos(\omega t) + A_2 \sin(\omega t)) &= \frac{1}{RC} V_m \cos(\omega t) \end{aligned}$$

$$\left[ \omega A_2 + \frac{A_1}{RC} - \frac{V_m}{RC} \right] \cos(\omega t) + \underbrace{\left[ -\omega A_1 + \frac{A_2}{RC} \right]}_0 \sin(\omega t) = 0$$

$$t \geq 0$$

$$A_1 = \frac{V_m}{1 + (\omega RC)^2}$$

$$A_2 = \frac{\omega RC V_m}{1 + (\omega RC)^2}$$

$$V_p = \frac{V_m}{1 + (\omega RC)^2} \cos(\omega t) + \frac{\omega RC V_m}{1 + (\omega RC)^2} \sin(\omega t)$$

Step ②  $V_h = K e^{-\frac{t}{RC}}$

Step ③  $V_c = V_p + V_h$   
 $= K e^{-\frac{t}{RC}} + \frac{V_m}{1 + (\omega RC)^2} \cos(\omega t) + \frac{\omega RC V_m}{1 + (\omega RC)^2} \sin(\omega t)$

Step ④  $V_c(0) = V_0 = K + \frac{V_m}{1 + (\omega RC)^2} + 0$


$$K = V_0 - \frac{V_m}{1 + (\omega RC)^2}$$

$$V_C(t) = \underbrace{\left[ V_0 - \frac{V_m}{1+(\omega RC)^2} \right] e^{-\frac{t}{RC}}}_{\text{homogeneous transient part}} + \underbrace{\frac{V_m}{1+(\omega RC)^2} \left[ \cos(\omega t) + \omega RC \sin(\omega t) \right]}_{\text{forced steady-state}}$$

$$V_L(t) = \left[ V_0 - \frac{V_m}{1+(\omega RC)^2} \right] e^{-\frac{t}{RC}} + \frac{V_m}{\sqrt{1+(\omega RC)^2}} \cos[\omega t - \tan^{-1}(\omega RC)]$$

The forced response has a magnitude and phase shift compared to the input. However, the frequency is same with the input.

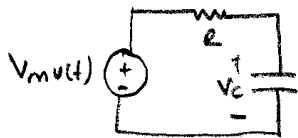
Unit Step Response = Constant Input Response  
(only first order RC or RL circuits)



$$\frac{dV_C}{dt} + \frac{1}{RC} V_C = \frac{V_m u(t)}{RC}$$

$$V_C(0) = V_0$$
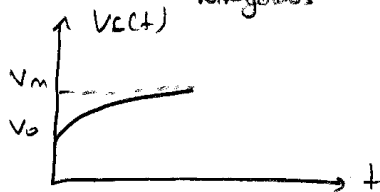
$$V_C(t) = \underbrace{(V_0 - V_m) e^{-\frac{t}{RC}}}_{\text{homogeneous}} + \underbrace{V_m}_{\text{forced}} \quad t \geq 0$$



$$\lim_{t \rightarrow 0} V_C(t) = V_0$$

$$\lim_{t \rightarrow \infty} V_C(t) = V_m$$

$$V_C(t) = \underbrace{V_0 e^{-\frac{t}{RC}}}_{\text{zero input response}} + \underbrace{V_m (1 - e^{-\frac{t}{RC}})}_{\text{zero state response}}$$

zero input response

$$V_C(t) = 0$$


occurs when the input is 0.

zero state response

$$V_C(0) = 0$$

occurs when the initial condition is 0 "V\_C = 0"

For RL Circuit

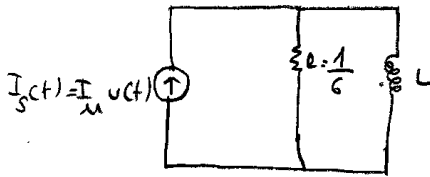

$$\frac{d I_L}{dt} + \frac{1}{LG} I_L = \frac{1}{LG} I_s(t) = \frac{1}{LG} I_m u(t)$$

$$I_L(0) = I_0$$

$$I_L(t) = \underbrace{(I_0 - I_m)}_{\text{homogeneous (natural) response}} e^{-\frac{t}{LG}} + \underbrace{I_m}_{\text{forced response}}$$


$$I_L(t) = \underbrace{I_0 e^{-\frac{t}{LG}}}_{\text{zero-input response}} + \underbrace{I_m (1 - e^{-\frac{t}{LG}})}_{\text{zero state response}}$$

One can think that;

The RC and RL circuits have the INPUTS:

- ① The input that occurred before  $t=0$   
 $\Rightarrow$  zero-input response
- ② The input occurred at  $t=0$   
 $\Rightarrow$  zero-state response

Damp Response

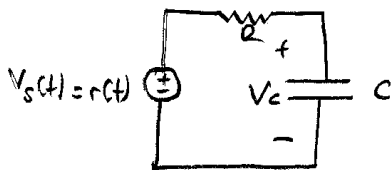

$$V_c(0) = V_0$$

$$r(t) = t u(t)$$

$$\frac{d V_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} r(t) = \frac{1}{RC} t u(t)$$

$t > 0$

$$\frac{d V_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} t$$

$$V_c(0) = V_0$$

Step ①  $V_p = A_1 t + A_2$

$$\frac{d}{dt} (A_1 t + A_2) + \frac{1}{RC} (A_1 t + A_2) = \frac{1}{RC} t$$

$$A_1 + \frac{1}{RC} (A_1 t + A_2) = \frac{1}{RC} t$$

$$\left( \frac{1}{RC} A_1 - \frac{1}{RC} \right) t + \left( A_1 + \frac{A_2}{RC} \right) = 0$$

$$A_1 = 1, \quad A_2 = -RC$$

$$\boxed{V_p = t - RC}$$

Step ②  $V_h = K e^{-\frac{t}{RC}}$


Step ③  $V_c = (t - RC) + K e^{-\frac{t}{RC}}$

Step ④  $V_c(0) = V_0$

$$V_0 = (0 - RC) + K$$

$$K = V_0 + RC$$
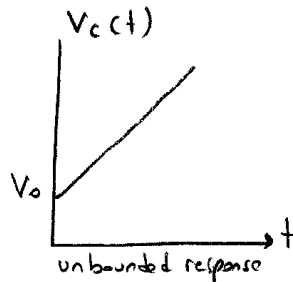
$$V_c(t) = (V_0 + RC) e^{-\frac{t}{RC}} + (t - RC)$$



$$\lim_{t \rightarrow \infty} V_c(t) = \infty$$

Note that, zero state unit step response is the time derivative of zero state unit ramp response.

$$(V_0 = 0)$$


$$V_{c \text{ zero state ramp}} = t - RC (1 - e^{-\frac{t}{RC}})$$

$$\frac{d}{dt} V_{c \text{ zero state ramp}} = 1 - RC \left( 0 - \frac{1}{RC} e^{-\frac{t}{RC}} \right) = 1 - e^{-\frac{t}{RC}}$$

zero state  
unit step  
response



## Exponential Response

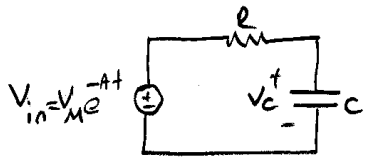

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_m e^{-At}$$

$$V_c(0) = V_0$$

a)  $A \neq \frac{1}{RC}$

b)  $A = \frac{1}{RC}$

a) Step ①  $V_p = M e^{-At}$

$$\frac{d}{dt} M e^{-At} + \frac{1}{RC} M e^{-At} = \frac{1}{RC} V_m e^{-At}$$

$$-AM e^{-At} + \frac{M}{RC} e^{-At} = \frac{V_m}{RC} e^{-At}$$

$$\left(-A + \frac{1}{RC}\right) M = \frac{V_m}{RC}$$

$$M = \frac{V_m}{RC} \left(\frac{RC}{1-ARC}\right)$$

$$M = \frac{V_m}{1-ARC}$$

Step ②  $V_h = K e^{-\frac{t}{RC}}$

Step ③  $V_c = V_p + V_h$   
 $= \frac{V_m}{1-ARC} e^{-At} + K e^{-\frac{t}{RC}}$

Step ④  $V_c(0) = V_0 = \frac{V_m}{1-ARC} + K$

$$K = V_0 - \frac{V_m}{1-ARC}$$

$$V_c(t) = \frac{V_m}{1-ARC} e^{-At} + \left(V_0 - \frac{V_m}{1-ARC}\right) e^{-\frac{t}{RC}}$$

if  $A > 0$  both terms are decaying.

if  $A < 0$  one term decays and the other term is an increasing exponential.

$$b) A = \frac{1}{RC}$$

$$\text{Step ① } V_p = Mte^{-At}$$

$$= Mte^{-\frac{1}{RC}t}$$

$$\frac{d}{dt} (Mte^{-\frac{1}{RC}t}) + \frac{1}{RC} (Mte^{-\frac{1}{RC}t}) = \frac{1}{RC} V_m e^{-At} = \frac{1}{RC} V_m e^{-\frac{1}{RC}t}$$

$$M \left[ e^{-\frac{1}{RC}t} + t \left( -\frac{1}{RC} e^{-\frac{1}{RC}t} \right) \right] + \frac{1}{RC} (Mte^{-\frac{1}{RC}t}) = \frac{1}{RC} V_m e^{-\frac{1}{RC}t}$$

$$M e^{-\frac{1}{RC}t} - M + \frac{1}{RC} M t e^{-\frac{1}{RC}t} + M + \frac{1}{RC} M t e^{-\frac{1}{RC}t} = \frac{1}{RC} V_m e^{-\frac{1}{RC}t}$$

$$M e^{-\frac{1}{RC}t} = \frac{1}{RC} V_m e^{-\frac{1}{RC}t}$$

$$M = \frac{V_m}{RC}$$

$$V_p(t) = \frac{V_m}{RC} t e^{-\frac{t}{RC}}$$


$$\text{Step ② } V_h = K e^{-\frac{t}{RC}}$$

$$\text{Step ③ } V_c = V_h + V_p = \frac{V_m}{RC} t e^{-\frac{t}{RC}} + K e^{-\frac{t}{RC}}$$


$$\text{Step ④ } V_c(0) = V_0 = K$$

$$V_c(t) = \frac{V_m}{RC} t e^{-\frac{t}{RC}} + V_0 e^{-\frac{t}{RC}}$$

### Pulse Response

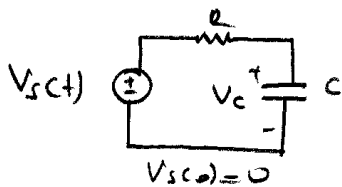

$$V_s(t) = A [u(t) - u(t-T)]$$

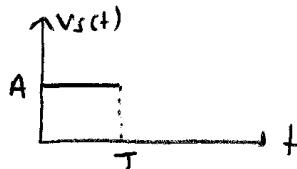


Since the initial condition is zero " $V_c(0) = 0$ ", the total response can be found as the addition (superposition), of the responses caused by step function applied at  $t=0$  and step function applied when  $t=T$ .

$$V_s(t) = \underbrace{Au(t)}_{V_1(t)} - \underbrace{Au(t-T)}_{V_2(t)} = V_1(t) + V_2(t)$$

$$V_1(t) = Au(t) \rightarrow A(1 - e^{-\frac{t}{RC}}) \quad (\text{zero state response } Au(t))$$

$$+ V_2(t) = -Au(t-T) \rightarrow -A(1 - e^{-\frac{(t-T)}{RC}})u(t-T) \quad (\text{ " " " } Au(t-T))$$
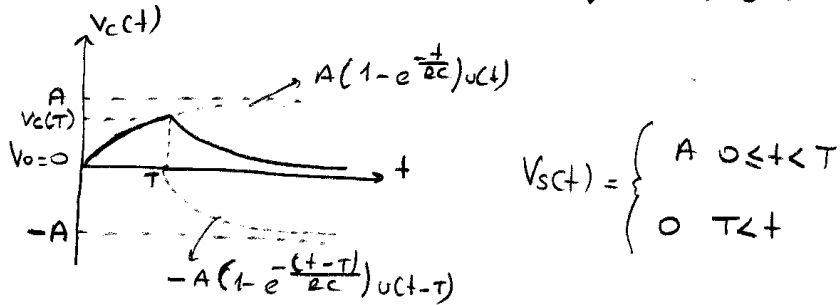
$$V_s(t) \rightarrow A(1 - e^{-\frac{t}{RC}})u(t) - A(1 - e^{-\frac{(t-T)}{RC}})u(t-T)$$



when  $0 \leq t \leq T$ ;

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{A}{RC} \quad V_c(0) = 0$$

$$V_c(t) = A(1 - e^{-\frac{t}{RC}}) \quad 0 \leq t \leq T$$

$$V_c(0) = 0$$

$$V_c(T) = A(1 - e^{-\frac{T}{RC}})$$

when  $T < t$ ;

$V_s(t) = 0$  (in this region)

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = 0 \quad V_c(T) = A(1 - e^{-\frac{T}{RC}})$$

$$V_p = 0$$

$$V_h = K e^{-\frac{t}{RC}}$$

$$= M e^{-\frac{(t-T)}{RC}}$$

$$= M e^{-\frac{t}{RC}} e^{\frac{T}{RC}}$$

$$= M e^{\frac{T}{RC}} e^{-\frac{t}{RC}}$$

$$M e^{\frac{T}{RC}} = K$$

$$V_c = V_p + V_h = 0 + M e^{-\frac{(t-T)}{RC}}$$

$$V_c(T) = A(1 - e^{-\frac{T}{RC}}) = M e^{-\frac{(T-T)}{RC}}$$

$$M = A(1 - e^{-\frac{T}{RC}})$$

$$V_c(t) = \underbrace{A(1 - e^{-\frac{T}{RC}})}_M e^{\frac{(t-T)}{RC}}$$

$$V_c(t) = A(1 - e^{-\frac{T}{RC}}) e^{\frac{T}{RC}} e^{-\frac{t}{RC}}$$

$$= A(e^{\frac{T}{RC}} - 1) e^{-\frac{t}{RC}}$$

What happens if there is non-zero initial condition?

1<sup>st</sup> Method:

$$V_c(t) = V_{\text{due-to-inputs}} + V_{\text{due-to-initial condition}}$$