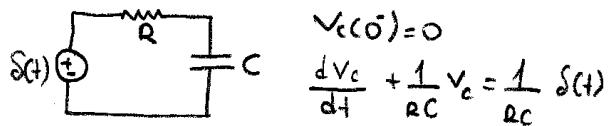


Impulse Response

\* Impulse response is denoted by  $h(t)$ .

$$\text{when } t > 0 \quad \frac{d h(t)}{dt} + \frac{1}{RC} h(t) = 0$$

$$h(t) = K e^{-\frac{t}{RC}} u(t) \rightarrow \text{put } h(t) \text{ in diff. eqn.}$$

$$\frac{d}{dt} (K e^{-\frac{t}{RC}} u(t)) + \frac{1}{RC} (K e^{-\frac{t}{RC}} u(t)) = \frac{1}{RC} S(t)$$


$$K \left( -\frac{1}{RC} \right) e^{-\frac{t}{RC}} u(t) + K e^{-\frac{t}{RC}} \delta(t) + \frac{K}{RC} e^{-\frac{t}{RC}} u(t) = \frac{1}{RC} S(t)$$

$$K e^{-\frac{t}{RC}} \delta(t) = \frac{1}{RC} S(t)$$

$$K \delta(t) = \frac{1}{RC} \delta(t) \quad \boxed{K = \frac{1}{RC}} \quad \boxed{h(t) = \frac{1}{RC} e^{-\frac{t}{RC}} u(t)}$$

\* If  $V_c(0^-) = V_0$
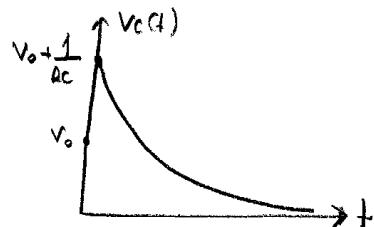
$$\text{input } \delta(t) \rightarrow V_c(t) = \left( V_0 + \frac{1}{RC} \right) e^{-\frac{t}{RC}} u(t)$$




\* The zero state impulse response is the time-derivative of zero state unit step response -

$$g(t)_{\text{zero state}} = (1 - e^{-\frac{t}{RC}}) u(t)$$

$$\frac{d}{dt} g(t)_{\text{zero state}} = ? h(t)_{\text{zero state}}$$

$$\begin{aligned}\frac{d}{dt} \left[ (1 - e^{-\frac{t}{RC}}) u(t) \right] &= -\left(-\frac{1}{RC}\right) e^{-\frac{t}{RC}} u(t) + (1 - e^{-\frac{t}{RC}}) \delta(t) \\ &= \frac{1}{RC} e^{-\frac{t}{RC}} u(t) + \underbrace{(1 - e^{-\frac{t}{RC}})}_0 \delta(t) \\ &= h(t)_{\text{zero state}} = \frac{1}{RC} e^{-\frac{t}{RC}} u(t)\end{aligned}$$

### Parallel RC Circuit

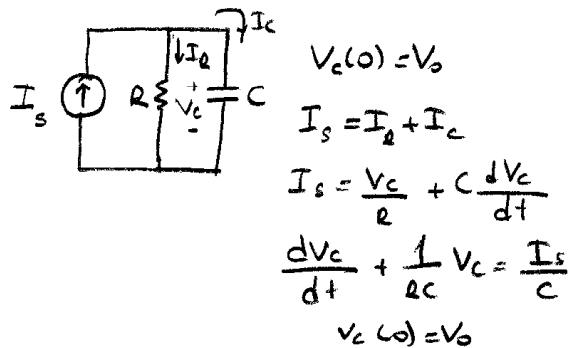

$$\text{Let } I_s(t) = M u(t)$$

+>0

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{M}{C}, V_c(\infty) = V_0$$

$$\textcircled{1} \quad V_{cp} = k$$

$$\frac{d}{dt} (k t) + \frac{1}{RC} k = \frac{M}{C} \quad k = MR$$

$$\textcircled{2} \quad V_{ch} = k_1 e^{-\frac{t}{RC}}$$

$$V_c(t) = (V_0 - MR) e^{-\frac{t}{RC}} + MR$$

$$\textcircled{3} \quad V_c = V_{ch} + V_{cp}$$

$$V_c(t) = k_1 e^{-\frac{t}{RC}} + MR$$

$$\textcircled{4} \quad V_c(0) = V_0 = k_1 + MR$$

$$k_1 = V_0 - MR$$

====>

Let  $I_s(t) = Mv(t)$  where  $M=1$

$$V_c(t) = (V_0 - R) e^{-\frac{t}{RC}} + R$$


if  $V_0 = 0$  (circuit is zero-state)

$$= V_{c_{\text{zero state}}} = R \left[ 1 - e^{-\frac{t}{RC}} \right]$$

zero state response for unit step

$$h(t) = \frac{dV_c(\text{zero state})}{dt} = \frac{1}{C} e^{-\frac{t}{RC}}$$


zero state  
impulse response

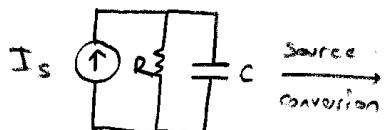

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{I_s}{C}$$

$$g(t) = (1 - e^{-\frac{t}{RC}})$$
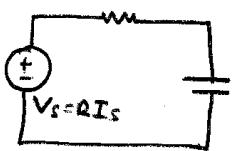
$$h(t) = \frac{1}{RC} e^{-\frac{t}{RC}}$$



$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{V_s}{RC}$$

$$V_s = R I_s$$

$$g(t) = R(1 - e^{-\frac{t}{RC}})$$

$$h(t) = \frac{1}{C} e^{-\frac{t}{RC}}$$

### Linearity

<u>input</u>	<u>output</u>	} if the condition is valid for all k values then the system is linear.
$x(t) \longrightarrow y(t)$	$kx(t) \longrightarrow ky(t)$	

\* The zero-state response of the LTI first order circuit is a linear function of the input.



### Time Invariance

Input      Output  
 $x(t) \rightarrow y(t)$   
 $x(t-t_0) \rightarrow y(t-t_0)$

If the condition is satisfied  
for all  $t_0$  values, then that  
system is time-invariant.

\* The zero-state response of the LTI first order circuit is time-invariant.

Ex.

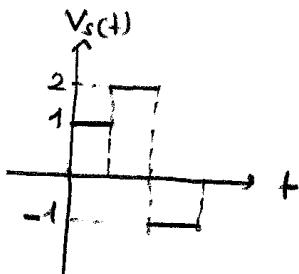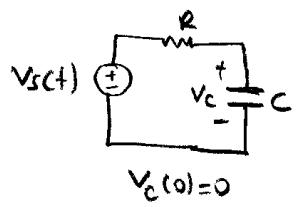

Find  $V_c(t) = ?$

Solt'n.

$$\text{If input } V_s(t) = u(t) \rightarrow V_c(t) = \left(1 - e^{-\frac{t}{RC}}\right) u(t)$$

However;


$$\text{using linearity} \quad V_s(t) = u(t) + u(t-1) - 3u(t-2) + u(t-3)$$

$$\text{and time invariance} \quad V_c(t) = \left(1 - e^{-\frac{t}{RC}}\right) u(t) + \underbrace{\left(1 - e^{-\frac{(t-1)}{RC}}\right) u(t-1)}_{\text{extra term}} + -3 \left(1 - e^{-\frac{(t-2)}{RC}}\right) u(t-2) + \left(1 - e^{-\frac{(t-3)}{RC}}\right) u(t-3)$$

if  $V_c(0) = V_0$ ; there will be an extra term

$$V_0 e^{-\frac{t}{RC}} u(t)$$

### Convolution Integral

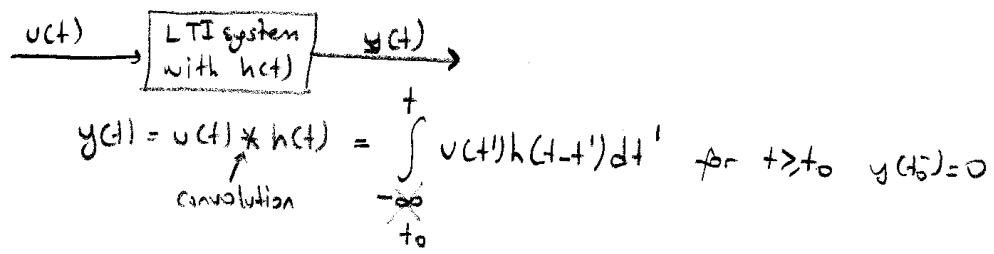

Ex.

Find the zero-state response "Vc(t)" of series RC circuit for the following input:

$$v_s(t) = u(t) - u(t-1)$$


$$\begin{array}{c} 1 \\ \text{---} \\ 0 \end{array} \rightarrow + \quad h(t) = \frac{1}{RC} e^{-\frac{t}{RC}} u(t)$$

for  $t \geq 0$

$$\begin{aligned} V_c(t) &= \int_{-\infty}^{t_0} h(t-t') v_s(t') dt' \\ &= \int_{-\infty}^{t-1} v_s(t-t') h(t') dt' \end{aligned}$$


$$v_s(t') = \begin{cases} 1 & 0 \leq t' < 1 \\ 0 & \text{otherwise} \end{cases}$$
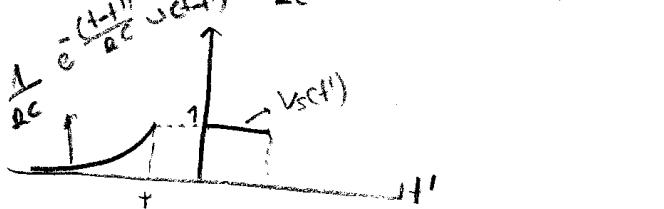
$$h(t-t') = \frac{1}{RC} e^{-\frac{(t-t')}{RC}} u(t-t')$$



$$V_c(t) = \int_{-\infty}^{t-1} h(t-t') v_s(t') dt' = 0$$


$$0 \leq t < 1$$

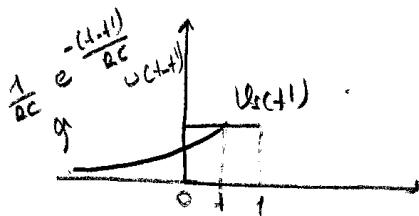

$$V_c(t) = \int_{-\infty}^t h(t-t') u_s(t') dt'$$

$$\begin{aligned} &= \int_{-\infty}^0 0 dt + \int_0^t \frac{1}{ac} e^{-\frac{(t-t')}{ac}} dt' \\ &= \frac{1}{ac} e^{-\frac{t}{ac}} \int_0^t e^{\frac{t'}{ac}} dt' \\ &= \left( \frac{1}{ac} e^{-\frac{t}{ac}} \right) \Big|_0^t = \frac{1}{ac} e^{-\frac{t}{ac}} \end{aligned}$$
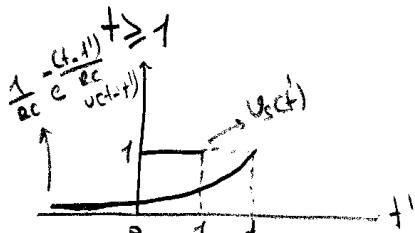
$$V_c(t) = e^{-\frac{t}{ac}} \left[ e^{\frac{t}{ac}} - 1 \right] = 1 - e^{-\frac{t}{ac}}$$




$$V_c(t) = \int_{-\infty}^t h(t-t') u_s(t') dt'$$

$$\begin{aligned} &= \int_{-\infty}^0 0 dt + \int_0^1 \left( \frac{1}{ac} \right) e^{-\frac{(t-t')}{ac}} dt' + \int_1^t 0 dt \\ &= \frac{1}{ac} e^{-\frac{t}{ac}} \int_0^1 e^{\frac{t'}{ac}} dt' \end{aligned}$$

$$\begin{aligned} &= \left( \frac{1}{ac} e^{-\frac{t}{ac}} \right) \Big|_0^1 = \frac{1}{ac} e^{-\frac{t}{ac}} \Big|_0^1 \\ &= e^{-\frac{t}{ac}} \left[ e^{\frac{1}{ac}} - 1 \right] \end{aligned}$$

General solution
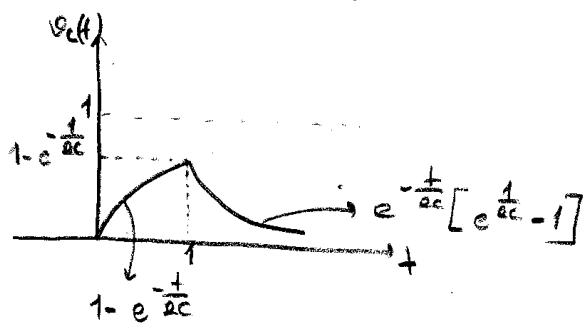
$$V_c(t) = \begin{cases} 0 & 0 \leq t < 0 \\ 1 - e^{-\frac{t}{ac}} & 0 \leq t < 1 \\ (e^{\frac{1}{ac}} - 1)e^{-\frac{t}{ac}} & t \geq 1 \end{cases}$$



### Initial and Final Conditions

If unit step input is applied.

$V_c(0)$ ,  $I_L(0)$   $\rightarrow$  initial conditions

$V_c(\infty)$ ,  $I_L(\infty)$   $\rightarrow$  final conditions  
(steady-state values)

$$V_c(t) = [V_c(0) - V_c(\infty)] e^{-\frac{t}{RC}} + V_c(\infty)$$


$$I_L(t) = [I_L(0) - I_L(\infty)] e^{-\frac{t}{RL}} + I_L(\infty)$$

DC circuit  $\tau = RC$

AC circuit  $\tau = L \cdot G = \frac{L}{R}$


Time Constants

Ex:-

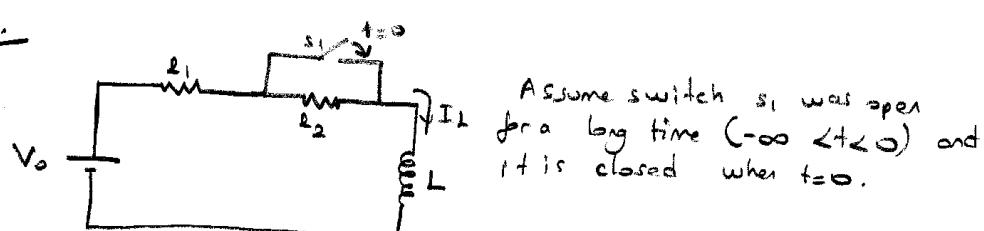


Find  $I_L(t) \rightarrow 0$

$-\infty < t < 0$

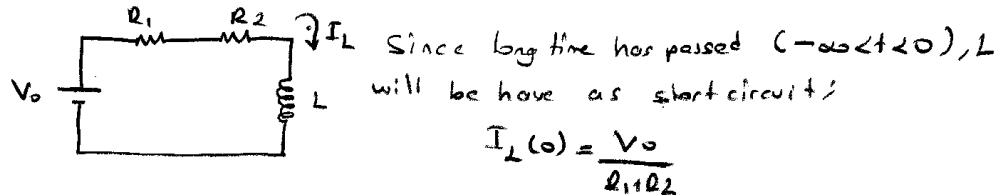

when  $t > 0$

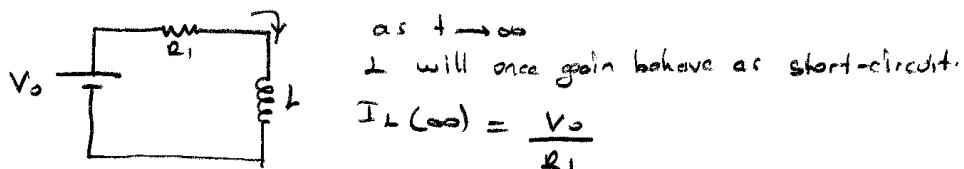


$$I_L(t) = (I_L(0) - I_L(\infty)) e^{\frac{t}{\tau}} + I_L(\infty)$$

$$I_L(t) = \left( \frac{V_o}{R_1 + R_2} - \frac{V_o}{R_1} \right) e^{\frac{-t}{\tau}} + \frac{V_o}{R_1} \quad \boxed{\tau = \frac{L}{R_1}}$$

Midterm Konuları Sona !!!


Ex:
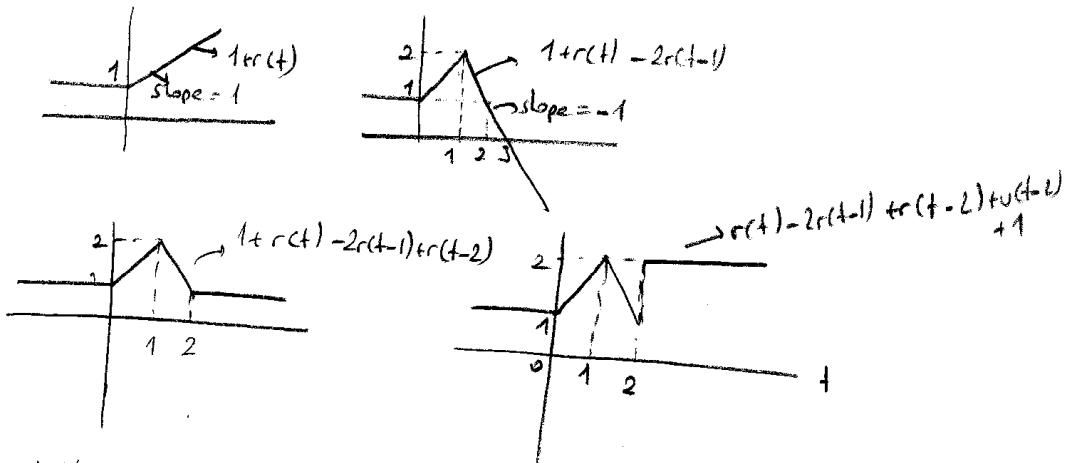
$$x(t) = r(t) - 2r(t-1) + r(t-2) + u(t-2) + 1$$



Let's draw:

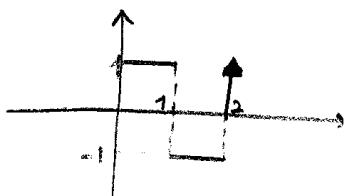
$$\frac{dx(t)}{dt} = u(t) - 2u(t-1) + u(t-2) + \delta(t-2) + 0$$



## # Second Order Circuits #

It includes at least 2 energy storage elements that cannot be decomposed into a single circuit element.

Parallel LTI RLC Circuit

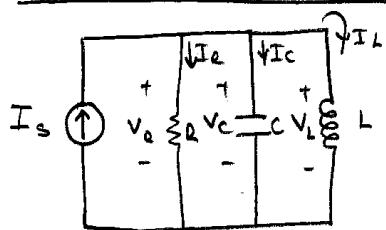

$$V_c(t_0) = V_0, I_L(t_0) = I_0$$

state variables  $I_L, V_c$

$$V_c = V_L = V_R$$

$$I_s = I_L + I_C + I_R$$

$$I_s = \frac{V_R}{R} + C \frac{dV_c}{dt} + I_L$$

$$I_s = \frac{V_c}{L} + C \frac{dV_c}{dt} + I_L$$

$$\textcircled{1} \quad \frac{dV_c}{dt} = \frac{1}{C} I_s - \frac{1}{CR} V_c - \frac{1}{C} I_L$$

$$V_L = V_c = L \frac{dI_L}{dt}$$

$$\textcircled{2} \quad \frac{dI_L}{dt} = \frac{V_c}{L}$$

$$\frac{d}{dt} \begin{bmatrix} V_c \\ I_L \end{bmatrix} = \begin{bmatrix} \frac{1}{C} & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} V_c \\ I_L \end{bmatrix} + \begin{bmatrix} \frac{1}{C} \\ 0 \end{bmatrix} I_s$$

state-space representation.

Take derivative of  $\textcircled{1}$  put  $\textcircled{2}$  inside

$$\frac{d^2V_c}{dt^2} = \frac{1}{C} \frac{dI_s}{dt} - \frac{1}{CR} \frac{dV_c}{dt} - \frac{1}{C} \frac{dI_L}{dt}$$

$$\frac{d^2V_c}{dt^2} = \frac{1}{C} \frac{dI_s}{dt} - \frac{1}{RC} \frac{dV_c}{dt} - \frac{1}{LC} V_L$$

$$\frac{d^2V_c}{dt^2} + \frac{1}{RC} \frac{dV_c}{dt} + \frac{1}{LC} V_L = \frac{1}{C} \frac{dI_s}{dt}$$

$$V_C(t_0) = V_0$$

$$\frac{dV_C}{dt}(t_0) = \frac{I_S(t_0)}{C} - \frac{V_C(t_0)}{CE} - \frac{I_L(t_0)}{C}$$

$$\frac{dV_C}{dt}(t_0) = \frac{I_S(t_0)}{C} - \frac{V_0}{CE} - \frac{I_0}{C}$$

$$\frac{d^2I_L}{dt^2} = \frac{1}{L} \frac{dV_C}{dt}$$

$$= \frac{1}{L} \left[ \frac{1}{C} I_S - \frac{1}{CE} V_0 - \frac{1}{C} I_L \right]$$

$$= \frac{1}{LC} I_S - \frac{1}{LCE} V_0 - \frac{1}{LC} I_L$$

$$\frac{dI_L}{dt}$$

$$\frac{d^2I_L}{dt^2} = \frac{I_S}{LC} - \frac{1}{CE} \frac{dI_C}{dt} - \frac{1}{LC} I_L$$

$$\frac{d^2I_L}{dt^2} + \frac{1}{CE} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{1}{LC} I_S$$

$$I_L(t_0) = I_0 \quad \frac{dI_L}{dt}(t_0) = \frac{V_C(t_0)}{L} = \frac{V_0}{L}$$