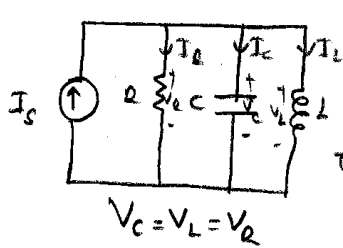


21.07.2010

$$I_S = I_R + I_C + I_L$$



$$I_S = \frac{V_C}{R} + C \frac{dV_C}{dt} + \frac{1}{L} \int_{t_0}^t V_C(t') dt' + I_0$$

(integro-diff equation)

Take derivative divide by C

$$\frac{1}{C} \frac{dI_S}{dt} = \frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{1}{LC} V_C$$

Zero-Input Response (Natural Response)

$I_S(t) = 0$ (response depend on the initial conditions)

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{1}{LC} V_C = 0$$

$$V_C(t_0) = V_0 \quad \frac{dV_C}{dt}(t_0) = -\frac{1}{RC} V_0 - \frac{I_0}{C}$$

$$\frac{dI_L}{dt} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = 0$$

$$I_L(t_0) = I_0 \quad \frac{dI_L}{dt}(t_0) = \frac{V_0}{L}$$

Some parameters similar solutions

Consider a general second order homogenous diff equation.

$$\frac{d^2 x}{dt^2} + a \frac{dx}{dt} + bx = 0$$

$$x = e^{st}$$

$$\frac{d^2}{dt^2} (e^{st}) + a \frac{d}{dt} (e^{st}) + b e^{st} = 0$$

$$s^2 e^{st} + a s e^{st} + b e^{st} = 0$$

$$e^{st} [s^2 + as + b] = 0$$

$$\downarrow$$

$$s^2 + as + b = 0 \text{ (characteristic eqn.)}$$

$$s_{1,2} = \frac{-a}{2} \pm \frac{\sqrt{a^2 - 4b}}{2} \quad \text{natural frequencies.}$$

$$\textcircled{1} \text{ if } s_1 \neq s_2 \quad x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$A_1, A_2 \rightarrow$ coefficients to be determined due to initial conditions.

$$\text{a) if } a^2 > 4b \Rightarrow s_{1,2} \Rightarrow \text{real}$$

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{perfect exponential terms (increasing or decreasing)}$$

$$\text{b) if } a^2 < 4b \quad s_{1,2} \Rightarrow \text{complex conjugate pairs}$$

$$s_1 = c + dj \quad s_2 = c - dj$$

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = A_1 e^{(c+dj)t} + A_2 e^{(c-dj)t}$$

$$= A_1 e^{c+ djt} + A_2 e^{c- djt}$$

$$= e^{ct} [A_1 e^{dj t} + A_2 e^{-dj t}] \quad A_1 \text{ and } A_2 \text{ are also complex conjugate pairs.}$$

$$= e^{ct} [(B_1 + B_2 j) e^{dj t} + (B_1 - B_2 j) e^{-dj t}] \quad \begin{matrix} A_1 = B_1 + B_2 j \\ A_2 = B_1 - B_2 j \end{matrix}$$

$$= e^{ct} [B_1 (e^{dj t} + e^{-dj t}) + B_2 (j e^{dj t} - j e^{-dj t})]$$

$$= e^{ct} \left[2B_1 \frac{e^{dj t} + e^{-dj t}}{2} + B_2 (2j) \frac{e^{dj t} - e^{-dj t}}{2j} \right]$$

$$= e^{ct} [2B_1 \cos(dt) - 2B_2 \sin(dt)]$$

$$= 2e^{ct} [B_1 \cos(dt) - B_2 \sin(dt)]$$

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \rightarrow x(t) = e^{ct} [K_1 \cos(dt) + K_2 \sin(dt)]$$

assume $s_1 \neq s_2^*$

$$s_1 = c + jd$$

$$\begin{matrix} K_1 = 2B_1 \\ K_2 = -2B_2 \end{matrix}$$

(ii) If $s_1 = s_2 = -\frac{a}{2}$ (valid when $a^2 = 4b$)

$e^{s_0 t}$ is a solution $s_0 = s_{1,2} = -\frac{a}{2}$

and $t e^{s_0 t}$ is also the solution of the diff-equation.

$$\frac{d^2 x}{dt^2} + a \frac{dx}{dt} + bx = 0$$

$$\frac{d^2}{dt^2} (t e^{s_0 t}) + a \frac{d}{dt} (t e^{s_0 t}) + b (t e^{s_0 t}) \stackrel{?}{=} 0$$

$$\frac{d}{dt} t e^{s_0 t} = e^{s_0 t} + s_0 t e^{s_0 t}$$

$$\frac{d^2}{dt^2} (t e^{s_0 t}) = \frac{d}{dt} [e^{s_0 t} + s_0 t e^{s_0 t}]$$

$$= s_0 e^{s_0 t} + s_0 e^{s_0 t} + s_0^2 t e^{s_0 t} = 2s_0 e^{s_0 t} + s_0^2 t e^{s_0 t}$$

$$2s_0 e^{s_0 t} + s_0^2 t e^{s_0 t} + a [e^{s_0 t} + s_0 t e^{s_0 t}] + b t e^{s_0 t} \stackrel{?}{=} 0$$

$$(s_0^2 + a s_0 + b) t e^{s_0 t} + (2s_0 + a) e^{s_0 t} \stackrel{?}{=} 0$$

$$s^2 + as + b = 0 \rightarrow \frac{d}{ds} (s^2 + as + b) = 2s + a \Big|_{s=s_0} = 0$$

$$(s - s_0)^2 = 0$$

$$\frac{d}{ds} (s - s_0)^2 \Big|_{s=s_0} = 2(s - s_0) \Big|_{s=s_0} = 0$$

Hence $\Rightarrow e^{s_0 t} \rightarrow$ solution

$t e^{s_0 t} \rightarrow //$

Thus, when $s_1 = s_2 = -\frac{a}{2} = s_0$

$x(t) = (A_1 + A_2 t) e^{s_0 t}$ where $s_0 = -\frac{a}{2}$

When $s_1 \neq s_2$;

* If $\operatorname{Re}\{s_1\} > 0$ and/or $\operatorname{Re}\{s_2\} > 0$

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \lim_{t \rightarrow \infty} |x(t)| \rightarrow \infty \quad \text{unbounded}$$

* If $\operatorname{Re}\{s_1\} \leq 0$ and $\operatorname{Re}\{s_2\} \leq 0$

$$\lim_{t \rightarrow \infty} |x(t)| < M \quad \text{bounded}$$

When $s_1 = s_2 = s_0 = -\frac{a}{2}$

* If $s_0 \geq 0$ ($a \leq 0$)


$$x(t) = (A_1 + A_2 t) e^{s_0 t} \quad \lim_{t \rightarrow \infty} |x(t)| \rightarrow \infty \quad \text{unbounded}$$

* If $s_0 < 0$ ($a > 0$)

$$x(t) = (A_1 + A_2 t) e^{s_0 t} \quad \lim_{t \rightarrow \infty} |x(t)| \rightarrow 0 \quad \text{bounded}$$

Back to zero-input solution of second order parallel circuit

$$I_s(t) = 0$$

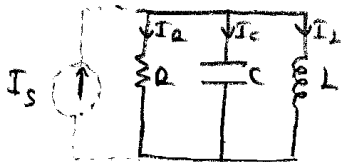

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{1}{LC} V_C = 0$$

$$V_C(t_0) = V_0 \quad \frac{dV_C}{dt}(t_0) = -\frac{1}{RC} V_0 - \frac{1}{C} I_0$$

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = 0$$

$$I_L(t_0) = I_0 \quad \frac{dI_L}{dt}(t_0) = \frac{V_0}{L}$$

Let's define: $C > 0, L > 0, R > 0$

$$2d = \frac{1}{RC} \quad (d \triangleq \text{damping constant (ratio)})$$

$$d \geq 0$$

$$\omega_0^2 \triangleq \frac{1}{LC} \quad \omega_0^2 > 0$$

$$\omega_0 > 0$$

↘ resonant frequency

If $R \rightarrow \infty$ $d = 0$ ← the circuit is lossless and passive (LC circuit)
(open circuit)

$$\frac{d^2 V_C}{dt^2} + 2d \frac{dV_C}{dt} + \omega_0^2 V_C = 0$$

$$V_C(t_0) = V_0 \quad \frac{dV_C}{dt}(t_0) = -\frac{1}{RC} V_0 - \frac{1}{C} I_0 = -2d V_0 - \frac{I_0}{C}$$

$$\frac{d^2 I_L}{dt^2} + 2d \frac{dI_L}{dt} + \omega_0^2 I_L = 0$$

$$I_L(t_0) = I_0 \quad \frac{dI_L}{dt}(t_0) = \frac{V_0}{L}$$

$$s^2 + 2d s + \omega_0^2 = 0$$

char-equation

$$s_{1,2} = -d \pm \sqrt{d^2 - \omega_0^2} \quad \text{natural-frequencies}$$

$$\text{Let } t_0 = 0$$

$$\text{Let } -2d V_0 - \frac{I_0}{C} = \gamma$$

① $\alpha > \omega_0$ (overdamped case)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} < 0 \rightarrow \text{real}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} < 0 \rightarrow \text{negative}$$

$$\alpha_d \triangleq \sqrt{\alpha^2 - \omega_0^2}$$

$$s_{1,2} = -\alpha \pm \alpha_d$$

$$V_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \rightarrow \text{(Both exponentials are decaying)}$$

Let's determine A_1 and A_2 :

$$V_c(0) = V_0 = A_1 + A_2$$

$$\left. \begin{aligned} \frac{dV_c}{dt} \Big|_{t=0} &= s_1 A_1 + s_2 A_2 = \gamma \end{aligned} \right\} \text{Solve for } A_1 \text{ and } A_2$$

② $\alpha = \omega_0$ (critically damped case)

$$s_{1,2} = s_0 = -\alpha$$

$$V_c(t) = (A_1 + A_2 t) e^{-\alpha t}$$

$$V_c(0) = V_0 = A_1$$

$$\frac{dV_c}{dt} \Big|_{t=0} = -\alpha A_1 + A_2 = \gamma$$

$$= -\alpha \underbrace{A_1}_{V_0} + A_2 = \gamma$$

$$A_2 = \gamma + \alpha V_0$$

(ii) $0 < \alpha < \omega_0$ (underdamped).

$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \rightarrow$ frequency of oscillation of damped sinusoids.

$$s_{1,2} = -\alpha \mp j\omega_d$$

$$\operatorname{Re}\{s_1\} = \operatorname{Re}\{s_2\} = -\alpha < 0$$


$$V_c(t) = A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}$$

$$= e^{-\alpha t} [A_1 \cos(\omega_d t) + jA_1 \sin(\omega_d t) + A_2 \cos(\omega_d t) - jA_2 \sin(\omega_d t)]$$

$$= e^{-\alpha t} \left[\underbrace{(A_1 + A_2)}_{B_1 \rightarrow \text{real}} \cos(\omega_d t) + j \underbrace{(A_1 - A_2)}_{B_2 \rightarrow \text{real}} \sin(\omega_d t) \right]$$

$$= e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)]$$
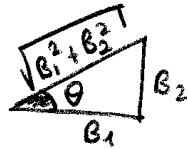
$$= e^{-\alpha t} \sqrt{B_1^2 + B_2^2} \left[\frac{\cos\theta}{\sqrt{B_1^2 + B_2^2}} \cos(\omega_d t) + \frac{\sin\theta}{\sqrt{B_1^2 + B_2^2}} \sin(\omega_d t) \right]$$



$$\cos\theta = \frac{B_1}{\sqrt{B_1^2 + B_2^2}}$$

$$\sin\theta = \frac{B_2}{\sqrt{B_1^2 + B_2^2}}$$

$$= \sqrt{B_1^2 + B_2^2} e^{-\alpha t} \left[\cos[\omega_d t - \theta] \right] \text{ where } \theta = \tan^{-1} \frac{B_2}{B_1}$$

(iv) $d=0$ (Classless case) (LC circuit)

$$s^2 + \omega_0^2 = 0 \text{ char eq.}$$

$$s_{1,2} = \pm j\omega_0$$

$$\operatorname{Re}\{s_{1,2}\} = \operatorname{Re}\{s_{1,2}\} = 0$$

$$V_c(t) = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t} \rightarrow V_c(t) = B_1 \cos(\omega_0 t) + B_2 \sin(\omega_0 t)$$

$$= \sqrt{B_1^2 + B_2^2} \cos(\omega_0 t - \theta)$$


$$\theta = \tan^{-1} \frac{B_2}{B_1}$$

$$V_c(0) = V_0 = B_1$$

$$\frac{dV_c}{dt} = -\omega_0 B_1 \sin(\omega_0 t) + \omega_0 B_2 \cos(\omega_0 t)$$

$$\left. \frac{dV_c}{dt} \right|_{t=0} = \omega_0 B_2 = \gamma \quad B_2 = \frac{\gamma}{\omega_0}$$

Ex.

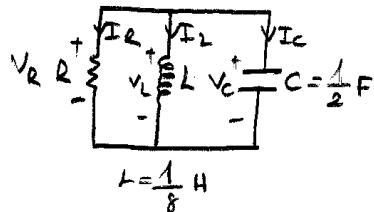

$$I_2(0) = -4 \text{ Amper}$$

$$V_c(0) = 5 \text{ Volt}$$

Soln.

$$2d = \frac{1}{RC} \rightarrow d = \frac{1}{R}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{\frac{1}{8} \cdot \frac{1}{2}} = 16$$

$$\omega_0 = 4 \text{ rad/sec}$$

\Rightarrow

Find $V_C(t), I_L(t)$:

① $R = \frac{1}{5} \Omega$ $d = 5$ $\omega_0 = 4$

$$s_{1,2} = -d \pm \sqrt{d^2 - \omega_0^2}$$

$$= -5 \pm \sqrt{5^2 - 4^2} = -2, -8 \rightarrow \text{real negative (overdamped)}$$

$$V_C(t) = A_1 e^{-8t} + A_2 e^{-2t}$$

$$V_C(0) = \boxed{5 = A_1 + A_2}$$

$$\left. \frac{dV_C}{dt} \right|_{t=0} = -8A_1 - 2A_2 = \frac{V_0}{RC} - \frac{I_0}{C}$$

$$= \frac{-5}{\frac{1}{2} \times \frac{1}{5}} - \frac{(-4)}{\frac{1}{2}} = -42$$

$$\boxed{-8A_1 - 2A_2 = -42}$$

$$A_2 = -\frac{1}{3}, \quad A_1 = \frac{16}{3}$$

$$\boxed{V_C(t) = -\frac{1}{3} e^{-2t} + \frac{16}{3} e^{-8t}}$$

$$I_L(t) = B_1 e^{-8t} + B_2 e^{-2t}$$

$$I_L(0) = \boxed{-4 = B_1 + B_2}$$

$$\left. \frac{dI_L}{dt} \right|_{t=0} = \frac{V_0}{L} = \frac{5}{\frac{1}{8}} = 40 = -8B_1 - 2B_2$$

$$B_1 = -\frac{16}{3}, \quad B_2 = \frac{4}{3}$$

$$\boxed{I_L(t) = \frac{4}{3} e^{-2t} - \frac{16}{3} e^{-8t}}$$

* OR *

$$V_C = V_L = L \frac{dI_L}{dt}$$

$$V_C = L \frac{dI_L}{dt} = \frac{1}{8} \frac{d}{dt} \left[\frac{4}{3} e^{-2t} - \frac{16}{3} e^{-8t} \right]$$

$$= \frac{1}{8} \left[-\frac{8}{3} e^{-2t} + \frac{16 \times 8}{3} e^{-8t} \right]$$

$$= -\frac{1}{3} e^{-2t} + \frac{16}{3} e^{-8t}$$