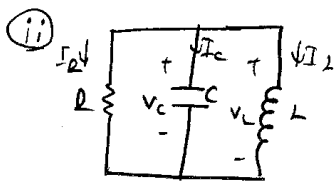


24.07.2010



$$R = \frac{1}{4}$$

$$2\alpha = \frac{1}{RC}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times \frac{1}{4} \times \frac{1}{2}} = 4$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = 4 \text{ rad/sec}$$

$$\alpha = \omega_0 = 4$$

$$s^2 + 2\alpha s + \omega_0^2 = 0 \text{ (char eqn)}$$

$$s^2 + 8s + 16 = 0$$

$$s_{1,2} = -4 = s_0 \text{ (critically damped)}$$

$$V_C(t) = (A_1 + A_2 t) e^{-4t}$$

$$I_2(t) = (B_1 + B_2 t) e^{-4t}$$

$$I_2(0) = -4 = B_1$$

$$\frac{dI_L}{dt} = B_2 e^{-4t} - 4e^{-4t}(B_1 + B_2 t)$$

$$\left. \frac{dI_L}{dt} \right|_{t=0} = B_2 - 4B_1 = 40$$

$$L \frac{dI_L}{dt} = V_L \quad \frac{dI_L}{dt} = \frac{V_L}{L} = \frac{V_C}{L}$$

$$\left. \frac{dI_C}{dt} \right|_{t=0} = \frac{V_C(0)}{L} = \frac{-5}{1/6} = -40$$

$$B_2 - 4B_1 = 40$$

$$B_2 - 4(-4) = 40$$

$$B_2 = 24$$

$$I_2(t) = (-4 + 24t) e^{-4t}$$

$$L \frac{dI_L}{dt} = V_C$$

$$= \frac{1}{8} \left[ \frac{d}{dt} (-4 + 24t) e^{-4t} \right]$$

$$= \frac{1}{8} \left[ 24 e^{-4t} - 4 e^{-4t} (-4 + 24t) \right]$$

$$= \frac{1}{8} \left[ 24 e^{-4t} + 16 e^{-4t} - 96t e^{-4t} \right] = [5 - 12t] e^{-4t}$$

$$V_c(t) = (5 - 12t) e^{-4t}$$

$$V_c(0) = 5$$

$$\lim_{t \rightarrow \infty} V_c(t) = 0$$

$$V_c(t_x) = 0$$


$$(5 - 12t_x) e^{-4t_x} = 0 \Rightarrow t_x = \frac{5}{12}$$

$$\begin{aligned} \frac{dV_c}{dt}(0) &= -\frac{V_0}{RC} - \frac{I_0}{C} \\ &= \frac{5}{\frac{1}{4} \times \frac{1}{2}} - \frac{(-4)}{\frac{1}{2}} = -32 \end{aligned}$$

$$\begin{aligned} \frac{dV_c}{dt} &= -12e^{-4t} + (5 - 12t)(-4)e^{-4t} \\ &= -32e^{-4t} + 48te^{-4t} \\ &= (-32 + 48t)e^{-4t} \end{aligned}$$

$$\begin{aligned} \left. \frac{dV_c}{dt} \right| = 0 &= (-32 + 48t_k) e^{-4t_k} \\ t_k \quad t_k &= \frac{2}{3} \end{aligned}$$
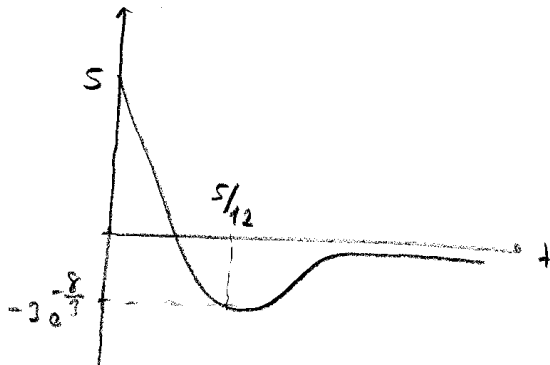
$$\begin{aligned} V_c(t_k) &= \left(5 - 12 \times \frac{2}{3}\right) e^{-4 \times \frac{2}{3}} \\ &= -3e^{-\frac{8}{3}} \end{aligned}$$



$$\textcircled{11} R = \frac{1}{2} \quad s^2 + 2\alpha s + \omega_0^2 = 0 \text{ (char eq)}$$

$$2\alpha = \frac{1}{RC} = \frac{1}{\frac{1}{3} \times \frac{1}{2}} = 6$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{\frac{1}{2} \times \frac{1}{8}} = 16$$

$$\omega_0 = 4 \text{ rad/sec}$$

$$\alpha = 3, \quad \alpha < \omega_0$$

$$s^2 + 6s + 16 = 0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -3 \pm \sqrt{9-16}$$

$$= -3 \pm j\sqrt{7} \text{ (complex conjugate root pairs) (underdamped case)}$$

$$V_C(t) = e^{-3t} [A_1 \cos(\sqrt{7}t) + A_2 \sin(\sqrt{7}t)]$$

$$I_2(t) = e^{-3t} [B_1 \cos(\sqrt{7}t) + B_2 \sin(\sqrt{7}t)]$$

$$I_2(0) = -4 = B_1$$

$$\frac{dI_2}{dt} = -3e^{-3t} [B_1 \cos(\sqrt{7}t) + B_2 \sin(\sqrt{7}t)] + e^{-3t} [-\sqrt{7}B_1 \sin(\sqrt{7}t) + \sqrt{7}B_2 \cos(\sqrt{7}t)]$$

$$\left. \frac{dI_2}{dt} \right|_{t=0} = -3B_1 + \sqrt{7}B_2 \rightarrow -3(-4) + \sqrt{7}B_2 = 40$$

$$\left. \frac{dI_2}{dt} \right|_{t=0} = \frac{V_C(0)}{L} = \frac{5}{\frac{1}{8}} = 40$$


$$\boxed{B_2 = \frac{28}{\sqrt{7}} = 4\sqrt{7}}$$

$$I_2(t) = e^{-3t} [-4\cos(\sqrt{7}t) + 4\sqrt{7}\sin(\sqrt{7}t)]$$

$$L \frac{dI_2}{dt} = V_C(t) \quad \text{HW}$$

(iii-2)

$$|x| = \sqrt{(-4)^2 + (4\sqrt{3})^2} = \sqrt{16 + 48} = 8\sqrt{2}$$

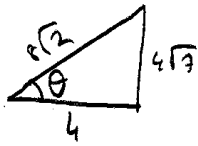


$$I_2(t) = e^{-3t} \left[ \frac{-4}{8\sqrt{2}} \cos(\sqrt{3}t) + \frac{4\sqrt{3}}{8\sqrt{2}} \sin(\sqrt{3}t) \right] 8\sqrt{2}$$

$$= e^{-3t} [\cos(\sqrt{3}t) \cos(\theta) + \sin(\theta) \sin(\sqrt{3}t)]$$


$$= -8\sqrt{2} e^{-3t} [\cos(\sqrt{3}t) \cos(\theta) - \sin(\sqrt{3}t) \sin(\theta)]$$

$$V_C(t) = -8\sqrt{2} e^{-3t} [\cos(\sqrt{3}t + \theta)]$$
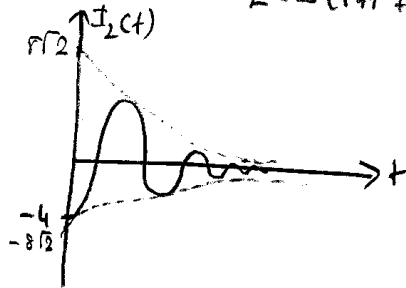
$$= -8\sqrt{2} e^{-3t} [\cos(\sqrt{3}t + \tan^{-1}(\sqrt{3}))]$$



(iv)

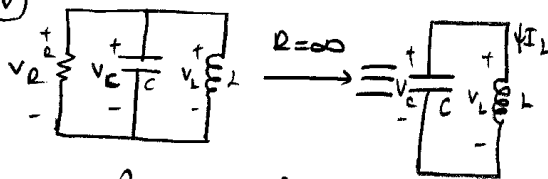

$$s^2 + 2\alpha s + \omega_0^2$$

$$\alpha = \frac{1}{2RC} = 0$$

$$s^2 + 16 = 0 \text{ (char eq)}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = 4$$

$$s_{1,2} = \pm 4j \text{ (natural frequencies)}$$

$$V_C(t) = A_1 \cos(4t) + A_2 \sin(4t)$$

$$I_L(t) = B_1 \cos(4t) + B_2 \sin(4t)$$

$$I_L(0) = -4 = B_1$$

$$\frac{dI_L}{dt} = -4B_1 \sin(4t) + 4B_2 \cos(4t)$$


$$\left. \frac{dI_L}{dt} \right|_{t=0} = 4B_2$$

$$\left. \frac{dI_L}{dt} \right|_{t=0} = \frac{V_C(0)}{L} = \frac{5}{1/8} = 40$$

$$4B_2 = 40$$

$$B_2 = 10$$

$$I_L = -4\cos(4t) + 10\sin(4t)$$

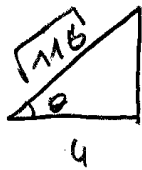


$$I_2(t) = \sqrt{116} \left[ \frac{-4}{\sqrt{116}} \cos(4t) + \frac{10}{\sqrt{116}} \sin(4t) \right]$$

$$= -\sqrt{116} \left[ \cos(\theta) \cos(4t) - \sin(\theta) \sin(4t) \right]$$


$$= \sqrt{-116} \cos(4t + \theta)$$

$$I_2(t) = \sqrt{-116} \cos\left(4t + \tan^{-1}\frac{5}{2}\right)$$
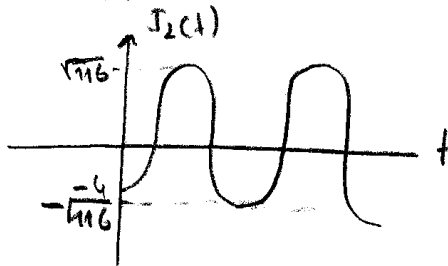
$$2 \frac{dI_L}{dt} = V_C \quad \text{HW}$$



### Complete Response

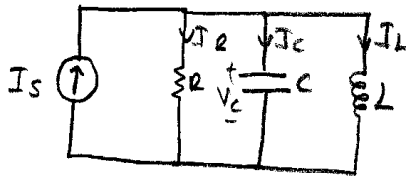

$$\frac{d^2 V_C}{dt^2} + 2 \frac{dV_C}{dt} + \omega_0^2 V_C = \frac{1}{C} \frac{dI_s}{dt}$$

$$V_C(t_0) = V_0 \quad \frac{dV_C}{dt}(t_0) = -2V_0 - \frac{I_0}{C} + \frac{1}{C} I_s(t_0)$$

$$\frac{d^2 I_C}{dt^2} + 2 \frac{dI_C}{dt} + \omega_0^2 I_C = \omega_0^2 I_s$$

$$I_L(t_0) = I_0 \quad \frac{dI_L}{dt}(t_0) = \frac{V_0}{L}$$

$$V_C(t) = V_{ch}(t) + V_{cp}(t)$$

Homogeneous  
solution

Particular  
solution

OR

$$V_C(t) = V_{czi}(t) + V_{czs}(t)$$

zero input  
solution

zero state  
solution

$$t_0 = 0$$

constant input =  $I_s(t) = I_s$   
(DC Input)

$$\frac{d^2 V_c}{dt^2} + 2\alpha \frac{dV_c}{dt} + \omega_0^2 V_c = \frac{1}{C} \frac{dI_s}{dt} = 0$$

$$V_c(t_0) = V_0 \quad \frac{dV_c}{dt}(t_0) = -2\alpha V_0 - \frac{I_0}{C} + \frac{I_s}{C}$$

$$s^2 + 2\alpha s + \omega_0^2 = 0 \begin{cases} \rightarrow \text{critically damped} \\ \rightarrow \text{under damped} \\ \rightarrow \text{over damped} \\ \rightarrow \text{purely sinusoidal} \end{cases} \left. \begin{array}{l} V_{ch} = (A_1 + A_2 t) e^{-\alpha t} \\ V_{ch} = A_1 e^{s_1 t} + A_2 e^{s_2 t} \end{array} \right\}$$

$$\left. \begin{array}{l} \text{overdamped} \\ \text{underdamped} \\ \text{purely sinusoidal} \end{array} \right\} A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{overdamped} \rightarrow A_1 e^{s_1 t} + A_2 e^{s_2 t} = V_{ch}(t)$$

$$\text{underdamped} \rightarrow s_1 = s_2^* \quad s_1 = \alpha_1 + j\alpha_2$$

$$V_{ch}(t) = e^{\alpha_1 t} [B_1 \cos(\alpha_2 t) + B_2 \sin(\alpha_2 t)]$$

$$\text{purely sinusoidal} \rightarrow s_1 = s_2^* \quad s_1 = j\alpha_2$$

$$V_{ch} = [D_1 \cos(\alpha_2 t) + D_2 \sin(\alpha_2 t)]$$

if system overdamped;

$$V_{ch} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\frac{d^2 V_c}{dt^2} + 2\alpha \frac{dV_c}{dt} + \omega_0^2 V_c = \frac{1}{C} \frac{dI_s}{dt}$$

$$\textcircled{1} V_{cp} = 0$$

$$\textcircled{2} V_{ch} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\textcircled{3} V_c = V_{cp} + V_{ch} \\ = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

=)

$$\textcircled{4} V_c(0) = V_0 = A_1 + A_2$$

$$\frac{dV_c}{dt}(0) = s_1 A_1 + s_2 A_2$$

$$\frac{dV_c}{dt}(0) = -2d V_0 - \frac{I_0}{C} + \frac{I_s}{C}$$

$$** s_1 A_1 + s_2 A_2 = -\frac{V_0}{RC} - \frac{I_0}{C} + \frac{I_s}{C}$$

Solve "\*" and "\*\*" to find  $A_1$  and  $A_2$ .

$$V_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad s_1, s_2 \rightarrow \text{real negative (for overdamped)}$$

$$\lim_{t \rightarrow \infty} V_c(t) = 0$$

Steady state value for  $V_c(t) = 0$

$$\frac{d^2 I_L}{dt^2} + 2d \frac{dI_L}{dt} + \omega_0^2 I_L = \omega_0^2 I_s$$

$$\textcircled{1} V_{cp} = k \quad \left( \begin{array}{l} \text{input is } I_s \text{ (DC)} \\ \text{so } V_{cp} \text{ is similar} \\ \text{DC) (} V_{cp} = k \end{array} \right)$$

$$\frac{d^2}{dt^2} k + 2d \frac{d}{dt} k + \omega_0^2 k = \omega_0^2 I_s$$

$$\omega_0^2 k = \omega_0^2 I_s$$

$$I_{cp} = k = I_s$$

$$\textcircled{2} I_{ch} = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$\textcircled{3} I_2 = I_{cp} + I_{ch} \\ = I_s + k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$\textcircled{4} I_2(0) = I_0 = I_s + k_1 + k_2 \quad *$$


$$\frac{dI_2}{dt} \Big|_{t=0} = s_1 k_1 + s_2 k_2 = \frac{V_0(0)}{L} = \frac{V_0}{L} \quad **$$

⇒


$$\left. \begin{aligned} k_1 + k_2 + I_s &= I_0 \\ s_1 k_1 + s_2 k_2 &= \frac{V_0}{L} \end{aligned} \right\} \begin{array}{l} \text{solve} \\ k_1 \text{ and } k_2 \end{array}$$

$$\lim_{t \rightarrow \infty} I_2(t) = \lim_{t \rightarrow \infty} I_s + k_1 e^{s_1 t} + k_2 e^{s_2 t} = I_s$$

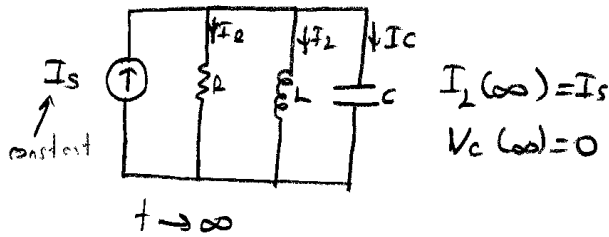(Steady state value for  $I_2(t)$  is  $I_s$ )



Ex.

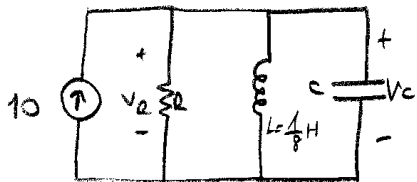

$$C = \frac{1}{2} \text{ F} \quad I_L(0) = -4 \text{ A} \\ V_C(0) = 5 \text{ V}$$

①  $\alpha = \frac{1}{5}$  (overdamped)

$$V_C(t) = 3e^{-2t} + 2e^{-8t}$$

$$I_L(t) = -12e^{-2t} - 2e^{-8t} + 10$$

$$2\alpha = \frac{1}{2.5} = \frac{1}{\frac{1}{2} \times \frac{1}{2}} = 10$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{\frac{1}{8} \times \frac{1}{2}} = 16$$

$$\alpha = 5, \omega_0 = 4 \text{ rad/sec}$$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$s^2 + 10s + 16 = 0$$

$$s_{1,2} = -5 \pm 3$$

$$s_{1,2} = -2, -8$$

$\Rightarrow$



$$\frac{d^2 I_L}{dt^2} + 2\alpha \frac{dI_L}{dt} + \omega_0^2 I_L = \omega_0^2 I_S$$

MS4\_mba tahun  
cibanyilmat abidmal.wmtr.

$$\frac{d^2 I_L}{dt^2} + 10 \frac{dI_L}{dt} + 16 I_L = 16 \times 10$$

$$I_L(0) = -4 \quad \frac{dI_L}{dt}(0) = \frac{V_0}{L} = \frac{5}{1/8} = 40$$

$$\textcircled{1} I_{Lp} = K$$

$$\frac{d^2}{dt^2} K + 10 \frac{d}{dt} K + 16K = 16 \times 10$$

$$16K = 16 \times 10 \rightarrow K = 10$$

$$\textcircled{2} I_{ch} = B_1 e^{-2t} + B_2 e^{-8t}$$

$$\textcircled{3} I_L = I_{cp} + I_{ch} \\ = 10 + B_1 e^{-2t} + B_2 e^{-8t}$$

$$\textcircled{4} I_L(0) = -4 = 10 + B_1 + B_2$$


$$\left. \begin{array}{l} \frac{dI_L}{dt} \Big|_{t=0} = -2B_1 - 8B_2 = 40 \\ B_1 + B_2 = -14 \end{array} \right\} \begin{array}{l} B_2 = -2 \\ B_1 = -12 \end{array}$$

$$I_{Lc}(t) = 10 - 2e^{-8t} - 12e^{-2t}$$

$$L \frac{dI_L}{dt} = V_c = \frac{1}{8} \left[ \frac{d}{dt} [10 - 2e^{-8t} - 12e^{-2t}] \right]$$

$$= \frac{1}{8} [16e^{-8t} + 24e^{-2t}]$$
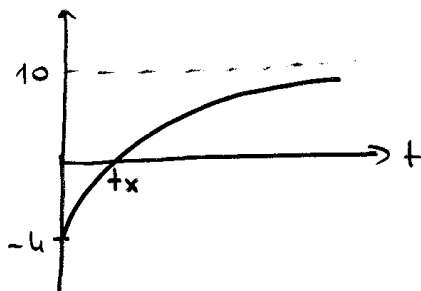
$$I_{Lc}(t) \quad V_c(t) = 2e^{-8t} + 3e^{-2t}$$



## Ramp Response

$$I_S(t) = r(t)$$


$$\frac{d^2 V_C}{dt^2} + 2\alpha \frac{dV_C}{dt} + \omega_0^2 V_C = \frac{1}{C} \frac{d}{dt} \overbrace{I_S(t)}^{r(t)}$$

$$\frac{d^2 I_L}{dt^2} + 2\alpha \frac{dI_L}{dt} + \omega_0^2 I_L = \omega_0^2 \overbrace{I_S(t)}^{r(t)}$$

$$I_L(0^-) = 0$$

$$\begin{aligned} \frac{dV_C}{dt}(0^-) &= -\frac{V_C(0^-)}{RC} - \frac{I_L(0^-)}{C} + \frac{I_S(0^-)}{C} \\ &= -\frac{0}{RC} - \frac{0}{C} + \frac{r(0^-)}{C} \\ &= 0 \end{aligned}$$

$$\left. \frac{dI_L}{dt} \right|_{t=0^-} = \frac{V_C(0^-)}{L} = 0$$


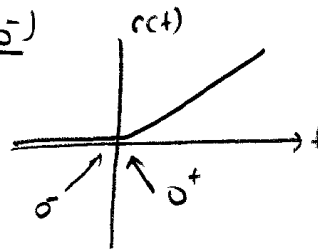


$t > 0$

$$\frac{dV_C}{dt} = -\frac{1}{RC} V_C - \frac{1}{C} I_L + \frac{I_S}{C}$$

$$\int_{V_C(0^-)}^{V_C(0^+)} dV_C = -\frac{1}{RC} \int_{0^-}^{0^+} V_C(t') dt' - \frac{1}{C} \int_{0^-}^{0^+} I_L(t') dt' + \frac{1}{C} \int_{0^-}^{0^+} \overbrace{I_S(t')}^{r(t')} dt'$$
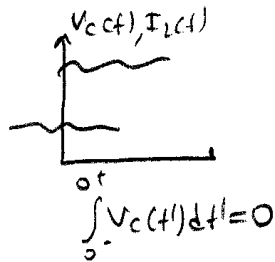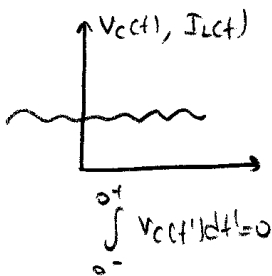
$$V_C(0^+) - V_C(0^-) = 0 - 0 + 0 \rightarrow V_C(0^+) = V_C(0^-) \checkmark$$



$$\frac{dI_L}{dt} = \frac{V_C}{L}$$

$$\int_{I_L(0^-)}^{I_L(0^+)} I_L = \frac{1}{L} \int_0^0 V_C(t') dt'$$

$$I_L(0^+) - I_L(0^-) = 0 \checkmark$$

$$I_L(0^+) = I_L(0^-) = 0 \checkmark$$

$$\frac{dI_L}{dt}(0^+) = \frac{V_C(0^+)}{L} = \frac{0}{L} = 0 \checkmark$$

$$\frac{dV_C}{dt}(0^+) = -\frac{1}{RC} V_C(0^+) - \frac{1}{C} I_L(0^+) + \frac{I_S(0^+)}{C}$$

$$= 0 - 0 + \frac{r(0^+)}{C}$$

$$= 0$$

$t > 0$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{C} \cdot 1$$

$$V_C(0^+) = 0 \quad \frac{dV_C}{dt}(0^+) = 0$$

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{1}{LC} \cdot 1 \quad \swarrow r(t)$$

$$I_L(0^+) = 0 \quad \frac{dI_L}{dt}(0^+) = 0$$

assume system overdamped;

$$\text{char eq} \Rightarrow s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$s_{1,2} \rightarrow$  real negative

For  $I_L$

$$\textcircled{1} I_{Lp} = A_1 t + A_2$$

$$\frac{d^2}{dt^2} (A_1 t + A_2) + \frac{1}{RC} \frac{d}{dt} (A_1 t + A_2) + \frac{1}{LC} (A_1 t + A_2) = \frac{1}{LC} + 0$$

$$\frac{1}{RC} A_1 + \frac{1}{LC} (A_1 t + A_2) = \frac{1}{LC} + 0$$

$\Rightarrow$

$$\underbrace{\left( \frac{1}{RC} + \frac{1}{LC} A_2 \right)}_0 + \underbrace{\left( \frac{A_1}{LC} - \frac{1}{LC} \right)}_0 = 0$$

$$A_1 = 1$$

$$\frac{1}{RC} A_1 = -\frac{1}{LC} A_2$$

$$A_2 = -\frac{L}{R} //$$

$$\textcircled{1} I_{2h} = B_1 e^{s_1 t} + B_2 e^{s_2 t}$$

$$\textcircled{2} I_L = I_{2h} + I_{cp}$$

$$= B_1 e^{s_1 t} + B_2 e^{s_2 t} + 1 - \frac{L}{R}$$

$$\left. \begin{aligned} I_L(0^+) = 0 &= B_1 + B_2 - \frac{L}{R} \\ \frac{dI_L}{dt}(0^+) &= s_1 B_1 + s_2 B_2 + 1 = 0 \end{aligned} \right\} \text{ solve for } B_1 \text{ and } B_2$$

$$B_1 = -\frac{1}{s_1 + s_2} \left( 1 + \frac{s_2 L}{R} \right) \quad B_2 = \frac{1}{s_1 - s_2} \left( 1 + \frac{s_1 L}{R} \right)$$

$$\lim_{t \rightarrow \infty} I_L(t) \cong 1 - \frac{L}{R} \quad (\text{at steady state})$$

$$\lim_{t \rightarrow \infty} I_L(t) = \infty$$

$$L \frac{dI_L}{dt} = V_C = L \left[ \frac{d}{dt} \left[ B_1 e^{s_1 t} + B_2 e^{s_2 t} + 1 - \frac{L}{R} \right] \right]$$

$$V_C(t) = L \left[ s_1 B_1 e^{s_1 t} + s_2 B_2 e^{s_2 t} + 1 \right]$$

$$V_C(t) = \underbrace{\frac{A_1}{s_1 L B_1} e^{s_1 t}}_{V_{ch}} + \underbrace{\frac{A_2}{s_2 L B_2} e^{s_2 t}}_{V_{ch}} + \underbrace{L}_{V_{cp}}$$

$$A_1 = -\frac{s_1 L}{s_1 - s_2} \left( 1 + \frac{s_2 L}{R} \right) \quad A_2 = \frac{s_2 L}{s_1 - s_2} \left( 1 + \frac{s_1 L}{R} \right)$$