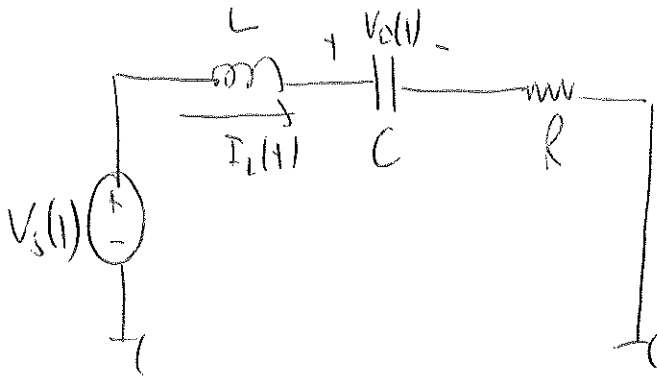


ECE 233

Final

11-01-2013

Q-1-
(a)



$$C \frac{dV_C}{dt} = I_C = I_L$$

$$\boxed{\frac{dV_C}{dt} = \frac{1}{C} I_L} \quad (4)$$

$$V_S = V_L + V_C + V_R$$

$$V_S = L \frac{dI_L}{dt} + V_C + R I_L$$

$$\boxed{\frac{dI_L}{dt} = \frac{V_S}{L} - \frac{V_C}{L} - \frac{R}{L} I_L} \quad (4)$$

$$(2) \begin{bmatrix} \frac{dI_L}{dt} \\ \frac{dV_C}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R}{L} & -\frac{1}{L} \\ 0 & \frac{1}{C} \end{bmatrix} \begin{bmatrix} I_L \\ V_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_S$$

$$(b) \quad \frac{d^2 V_C}{dt^2} = \frac{1}{C} \frac{dI_L}{dt} = \frac{1}{C} \left[\frac{V_S}{L} - \frac{V_C}{L} - \frac{R}{L} I_L \right] \quad (2)$$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{LC} V_C = \frac{1}{LC} V_S - \frac{R}{LC} I_L \rightarrow C \frac{dV_C}{dt}$$

gives (2)

$$(1) \quad \boxed{\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{LC} V_S}$$

$$\frac{d^2 I_c}{dt^2} = \frac{1}{L} \frac{dV_s}{dt} - \frac{1}{L} \frac{dV_c}{dt} - \frac{R}{L} \frac{dI_c}{dt} \quad (2)$$

$$\frac{d^2 I_c}{dt^2} + \frac{R}{L} \frac{dI_c}{dt} = \frac{1}{L} \frac{dV_s}{dt} - \frac{1}{L} \frac{dV_c}{dt} \Rightarrow \frac{I_c}{C} \quad (1)$$

$$\boxed{\frac{d^2 I_c}{dt^2} + \frac{R}{L} \frac{dI_c}{dt} + \frac{1}{LC} I_c = \frac{1}{L} \frac{dV_s}{dt}} \quad (1)$$

$$Q-2- \frac{dV_c}{dt} = 8(t) - 2I_c(t) - V_c(t)$$

$$\int_{I_c(0^-)}^{I_c(0^+)} dV_c = \int_{0^-}^{0^+} 8(t') dt' - 2 \int_{0^-}^{0^+} I_c(t') dt' - \int_{0^-}^{0^+} V_c(t') dt'$$

$$V_c(0^+) - V_c(0^-) = 1 - 0 - 0$$

$$V_c(0^+) = V_c(0^-) + 1$$

$$V_c(0^+) = 1 + 1 = 2V_0$$


$$\frac{dI_c}{dt} = -2V_c \quad \int_{I_c(0^-)}^{I_c(0^+)} dI_c = -2 \int_{0^-}^{0^+} V_c(t') dt' \Rightarrow I_c(0^+) - I_c(0^-) = 0$$

$$I_c(0^+) = I_c(0^-) = 0$$

$$\frac{dI_c}{dt}(0^+) = -2V_c(0^+) = -2 \times 2 = -4 \frac{\text{Ampere}}{\text{sec}} \quad (1.5)$$

$$\frac{dV_c}{dt}(0^+) = 8(0^+) - 2I_c(0^+) - V_c(0^+) = 0 - 2 \times 1 - 2 = -4 \frac{V}{\text{sec}}$$

$$(1.2)$$

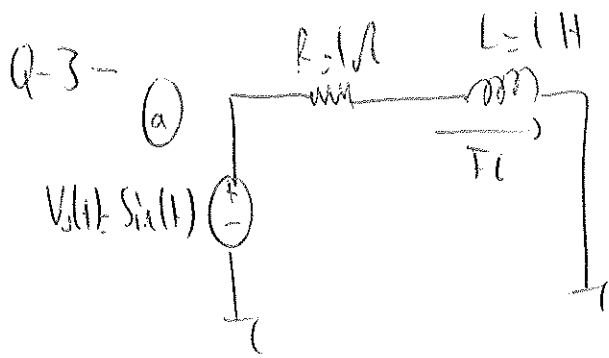

$$V_s = V_R + V_L \quad (2)$$

$$\sin(t) = 1 \cdot I_L + 1 \frac{dI_L}{dt} \quad (1)$$

$$\frac{dI_L}{dt} + I_L = \sin(t) \quad t \geq 0$$

(5) (b) $I_{Lp} = K_1 \sin(t) + K_2 \cos(t) \quad (1)$

$$\frac{d}{dt} (K_1 \sin(t) + K_2 \cos(t)) + K_1 \sin(t) + K_2 \cos(t) = \sin(t) \quad (2)$$

$$K_1 \cos(t) - K_2 \sin(t) + K_1 \sin(t) + K_2 \cos(t) = \sin(t)$$

$$(K_1 - K_2) \sin(t) + (K_1 + K_2) \cos(t) = \sin(t) \quad (1)$$

$$K_1 - K_2 = 1$$


$$K_1 + K_2 = 0$$

$$K_1 = \frac{1}{2} \quad K_2 = -\frac{1}{2}$$

$$I_{Lp} = \frac{1}{2} \sin(t) - \frac{1}{2} \cos(t) \quad (1)$$

Q-4

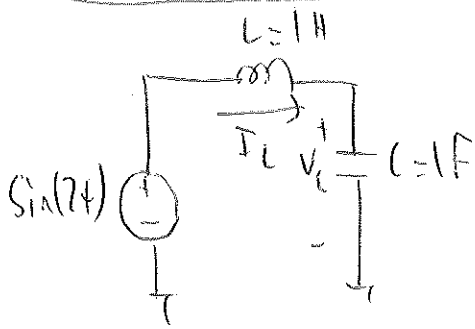$0 \leq t < \pi \rightarrow v_c(t) = \sin(7t)$



$v_{c2}(\pi^-) = v_{c2}(0) = \frac{4}{3}$ Volt
(no change since it is not active when $0 \leq t < \pi$)

$\sin(7t) = V_L + V_C = 1 \frac{dI_C}{dt} + V_C$

$\frac{dI_C}{dt} + V_C = \sin(7t)$ (1)

$\frac{dV_C}{dt} = I_C$ (1)

$\frac{d^2 I_C}{dt^2} + \frac{dV_C}{dt} = 7 \cos(7t) \Rightarrow$

$\frac{d^2 I_C}{dt^2} + I_C = 7 \cos(7t)$ (2)

$\frac{d^2 V_C}{dt^2} = \frac{dI_C}{dt} = \sin(7t) - V_C$

$\frac{d^2 V_C}{dt^2} + V_C = \sin(7t)$ (2)

char-eqn = $s^2 + 1 = 0$ (1) $s_{1,2} = \pm j \rightarrow$ natural frequencies

$V_{ch} = K_1 \sin(t) + K_2 \cos(t)$ (1)

$V_C(0) = 0, I_C(0) = 0$

$V_{cp} = M_1 \sin(7t) + M_2 \cos(7t)$ (1)

$\frac{dV_C}{dt}(0) = I_C(0) = 0$ (1)

$\frac{d^2}{dt^2} (M_1 \sin(7t) + M_2 \cos(7t)) + M_1 \sin(7t) + M_2 \cos(7t) = \sin(7t)$ (1)

$-4M_1 \sin(7t) - 4M_2 \cos(7t) + M_1 \sin(7t) + M_2 \cos(7t) = \sin(7t)$

$-3M_1 \sin(7t) - 3M_2 \cos(7t) = \sin(7t) \quad M_2 = 0 \quad M_1 = -\frac{1}{3}$

$V_{cp} = -\frac{1}{3} \sin(7t)$ (2)

$V_C = V_{cp} + V_{ch} = K_1 \sin(t) + K_2 \cos(t) - \frac{1}{3} \sin(7t)$

$V_C(0) = K_1 \sin(0) + K_2 \cos(0) - \frac{1}{3} \sin(0) = K_2 = 0$ $V_C(\pi) = K_1 \sin(\pi) - \frac{1}{3} \sin(7\pi)$

$\frac{dV_C}{dt} = K_1 \cos(t) - \frac{2}{3} \cos(7t) \quad \frac{dV_C}{dt}(0) = K_1 - \frac{2}{3} = 0 \quad K_1 = \frac{2}{3}$

$$V_c(t) = \frac{2}{3} \sin(t) - \frac{1}{3} \sin(7t) \quad (3) \quad 0 \leq t < \pi$$

$$C \frac{dV_c}{dt} = I_c = \frac{dV_c}{dt} = \frac{2}{3} \cos(t) - \frac{7}{3} \cos(7t) \quad (1) \quad 0 \leq t < \pi$$

$$V_c(\pi^-) = 0 \text{ Volt} \quad (1)$$

$$I_c(\pi^-) = -\frac{2}{3} - \frac{7}{3} = -\frac{9}{3} = -3 \text{ Amper} \quad (1)$$


$$t = \pi \quad (1)$$

$$Q(\pi^-) = Q(\pi^+) \quad C_1 V_{c1}(\pi^-) + C_2 V_{c2}(\pi^-) = (C_1 + C_2) V_c(\pi^+)$$

$$1 \times 0 + 3 \times \frac{4}{3} = 4 V_c(\pi^+)$$

$$V_c(\pi^+) = 1 \text{ Volt} \quad (1)$$

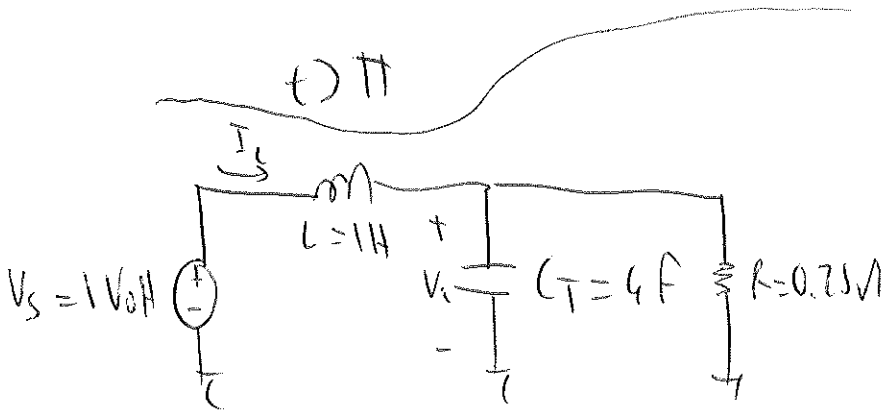No change in I_c hence $I_c(\pi^-) = I_c(\pi^+) = -3 \text{ Amper}$



$$V_S = V_L + V_c \quad \frac{dI_L}{dt} = 1 - V_c \quad (1)$$

$$1 = L \frac{dI_L}{dt} + V_c$$

$$I_L = I_c + I_R$$

$$I_L = C \frac{dV_c}{dt} + \frac{V_c}{R} \quad I_L = 4 \frac{dV_c}{dt} + \frac{4}{0.25} V_c \quad (1)$$

$$\frac{d^2 I_c}{dt^2} = 4 \frac{d^2 V_c}{dt^2} + 4 \frac{dV_c}{dt} = 1 - V_c \Rightarrow$$

$$\frac{d^2 V_c}{dt^2} + \frac{dV_c}{dt} + \frac{1}{4} V_c = \frac{1}{4} \quad (1)$$

char-equation $s^2 + s + \frac{1}{4} = 0$ (1)

natural frequencies $s_{1,2} = -\frac{1}{2}$ (1)

$$V_{ch} = [K_1 + K_2(t - \pi)] e^{-\frac{1}{2}(t - \pi)} \quad (1)$$

$$V_{cp} = M \quad (1)$$

$$\frac{d^2}{dt^2} M + \frac{d}{dt} M + \frac{1}{4} M = \frac{1}{4} \quad M=1 \quad (1)$$

Gedits 8

$$V_c(t) = 1 + [K_1 + K_2(t - \pi)] e^{-\frac{1}{2}(t - \pi)} \quad (1)$$

$$V_c(\pi^+) = 1 = 1 + [K_1 + K_2(\pi - \pi)] e^{-\frac{1}{2}(\pi - \pi)}$$

$$K_1 = 0 //$$

$$V_c(t) = 1 + K_2(t - \pi) e^{-\frac{1}{2}(t - \pi)}$$

$$\frac{dV_c}{dt} = K_2 \left[e^{-\frac{1}{2}(t - \pi)} + (t - \pi) \left(-\frac{1}{2}\right) e^{-\frac{1}{2}(t - \pi)} \right]$$

$$\frac{dV_c}{dt}(\pi^+) = K_2 [1 + 0] = -\frac{4}{3} \quad K_2 = -\frac{4}{3}$$

$$(1) \quad V_c(t) = 1 + \left(-\frac{4}{3}\right) (t - \pi) e^{-\frac{1}{2}(t - \pi)} \quad \frac{dV_c}{dt} = \left(-\frac{4}{3}\right) \left[e^{-\frac{1}{2}(t - \pi)} + (t - \pi) \left(-\frac{1}{2}\right) e^{-\frac{1}{2}(t - \pi)} \right]$$

$$I_c(t) = 4 \frac{dV_c}{dt} + 4V_c = 4 \left[\left(-\frac{4}{3}\right) \left[e^{-\frac{1}{2}(t - \pi)} + (t - \pi) \left(-\frac{1}{2}\right) e^{-\frac{1}{2}(t - \pi)} \right] + 1 + \left(-\frac{4}{3}\right) (t - \pi) e^{-\frac{1}{2}(t - \pi)} \right]$$

Q-5-

$V > V_a$

$$I = \frac{V - V_a}{R_1 + R_3} = \frac{V - 2}{3700 \mu} \quad (5)$$

$V_b < V < V_a$

$$I = 0 \quad (6)$$

$V < V_b$

$$I = - \left[\frac{V_b - V}{R_3 + R_2} \right] = \frac{V - V_b}{2000 \mu} = \frac{V + 2}{2000} \quad (7)$$

