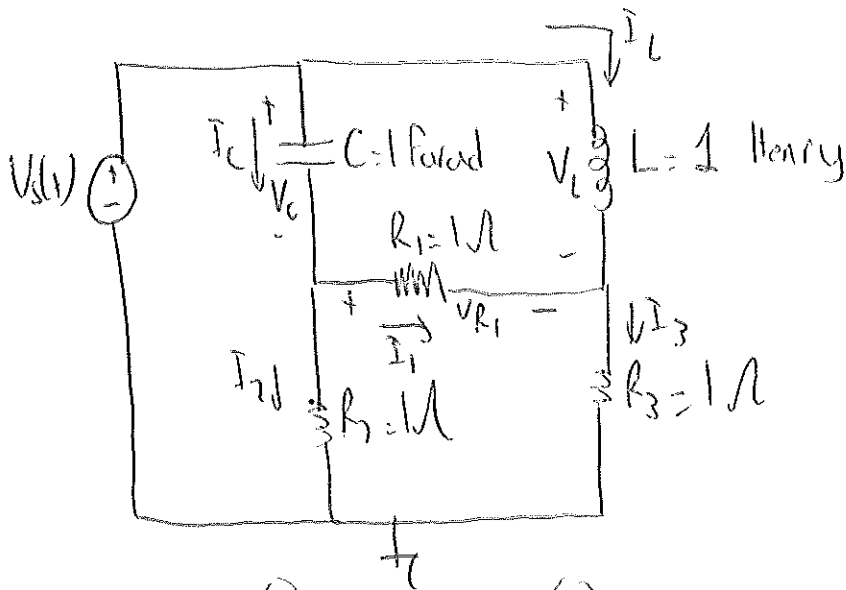


Q-1



$$v_L = L \frac{dI_L}{dt} = \frac{dI_L}{dt} \quad (1)$$

$$C \frac{dv_c}{dt} = I_c = \frac{dv_c}{dt} \quad (1)$$

$$I_c = I_1 + I_2 \quad (1)$$

$$C \frac{dv_c}{dt} = \frac{(v_s - v_c) - (v_s - v_L)}{R_1} + \frac{v_s - v_c - 0}{R_2} \quad (2)$$

$$\frac{dv_c}{dt} = \frac{v_L - v_c}{1} + \frac{v_s - v_c}{1}$$

$$\frac{dv_c}{dt} = \frac{L \frac{dI_L}{dt} - v_c}{1} + \frac{v_s - v_c}{1}$$

$$\frac{dv_c}{dt} = v_s - 2v_c + \frac{dI_L}{dt} \quad (5)$$

$$I_L + I_1 = I_3 \quad (1)$$

$$I_L + \frac{v_s - v_c - (v_s - v_L)}{1} = \frac{v_s - v_L}{1} \quad (2)$$

$$I_L + \frac{v_L - v_c}{1} = \frac{v_s - v_L}{1}$$

$$2v_L = v_s - I_L + v_c$$

$$2 \cdot 1 \cdot \frac{dI_L}{dt} = v_s - I_L + v_c$$

$$\frac{dI_L}{dt} = \frac{1}{2} v_s - \frac{1}{2} I_L + \frac{1}{2} v_c \quad (5) *$$

$$v_c = 2 \frac{dI_L}{dt} + I_L - v_s \quad (2) ***$$

$$\frac{dV_c}{dt} = V_s - 2V_c + \frac{dI_c}{dt} = V_s - 2V_c + \frac{1}{2}V_s - \frac{1}{2}I_c + \frac{1}{2}V_c$$

$$(3) \quad \boxed{\frac{dV_c}{dt} = \frac{3}{2}V_s - \frac{3}{2}V_c - \frac{1}{2}I_c} \quad **$$

Take derivative of * put ** inside

$$\frac{d^2 I_c}{dt^2} = \frac{1}{2} \frac{dV_s}{dt} - \frac{1}{2} \frac{dI_c}{dt} + \frac{1}{2} \frac{dV_c}{dt}$$

$$(3) \quad \frac{d^2 I_c}{dt^2} + \frac{1}{2} \frac{dI_c}{dt} = \frac{1}{2} \frac{dV_s}{dt} + \frac{1}{2} \left[\frac{3}{2} V_s - \frac{3}{2} V_c - \frac{1}{2} I_c \right]$$

$$\frac{d^2 I_c}{dt^2} + \frac{1}{2} \frac{dI_c}{dt} + \frac{1}{4} I_c = \frac{1}{2} \frac{dV_s}{dt} + \frac{3}{4} V_s - \frac{3}{4} V_c \quad \rightarrow (\text{use ***)}$$

$$\frac{d^2 I_c}{dt^2} + \frac{1}{2} \frac{dI_c}{dt} + \frac{1}{4} I_c = \frac{1}{2} \frac{dV_s}{dt} + \frac{3}{4} V_s - \frac{3}{4} \left[2 \frac{dI_c}{dt} + I_c - V_s \right]$$

$$\frac{d^2 I_c}{dt^2} + \left(\frac{1}{2} + \frac{3}{2} \right) \frac{dI_c}{dt} + \left[\frac{1}{4} + \frac{3}{4} \right] I_c = \frac{1}{2} \frac{dV_s}{dt} + \left(\frac{3}{4} + \frac{3}{4} \right) V_s$$

$$\boxed{\frac{d^2 I_c}{dt^2} + 2 \frac{dI_c}{dt} + I_c = \frac{1}{2} \frac{dV_s}{dt} + \frac{3}{2} V_s} \quad (7)$$

(b) Characteristic equation Natural frequencies

$$s^2 + 2s + 1 = 0$$

$$s_{1,2} = -1$$

$$I_{Lh}(t) = [A_1 + A_2 t] e^{-t} \implies I_L \text{ homogeneous solution}$$

Q-2 $s^2 + As + B = 0$ $A \geq 0, B > 0$ roots $= s_{1,2} = \frac{-A \pm \sqrt{A^2 - 4B}}{2}$

(a) Overdamped \implies two real roots, both roots are negative

$$A^2 - 4B > 0 \quad s_1 = \frac{-A + \sqrt{A^2 - 4B}}{2} < 0 \quad s_2 = \frac{-A - \sqrt{A^2 - 4B}}{2} < 0$$

\implies automatically satisfied

(b) Critically-damped \implies two real roots which are equal to each other

$$A^2 - 4B = 0 \quad s_{1,2} = -\frac{A}{2} < 0 \quad (\text{automatically satisfied})$$


(c) Under-damped case \implies two complex conjugate root pairs with Real parts negative

$$s_{1,2} = -\frac{A}{2} \pm j \sqrt{4B - A^2} \quad A^2 - 4B < 0$$

(d) $A = 0$ $4B - A^2 > 0$ $4B > 0$ $B > 0$

purely oscillatory case.

Q-3-

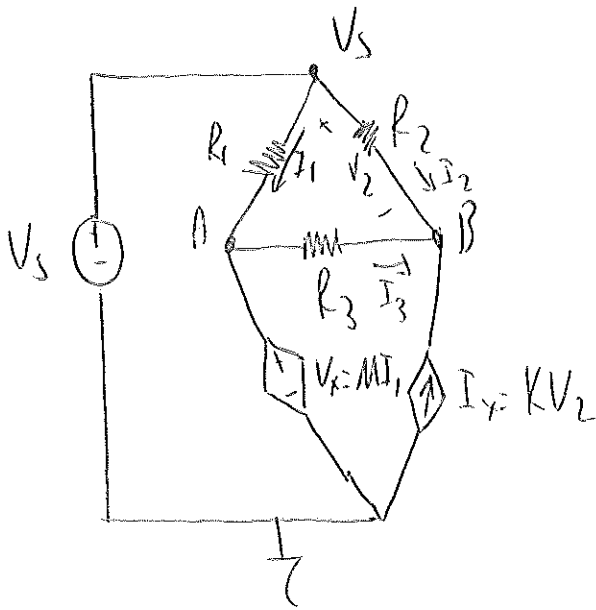

$$I_1 = \frac{V_s - A}{R_1} \quad (2)$$

$$A = V_x = MI_1 = M \frac{V_s - A}{R_1} \quad (2)$$

$$A = M \frac{V_s - A}{R_1}$$

$$A = \frac{V_s M}{R_1 + M} \quad (2) \quad **$$

$$(1) \quad I_2 + I_3 + I_x = 0 \quad V_2 = V_s - B \quad (1)$$

$$(1) \quad \frac{V_s - B}{R_2} + \frac{A - B}{R_3} + KV_2 = 0$$

$$\frac{V_s - B}{R_2} + \frac{A - B}{R_3} + K(V_s - B) = 0 \quad (3)$$

$$\frac{V_s}{R_2} + \frac{A}{R_3} + KV_s = B \left[\frac{1}{R_2} + \frac{1}{R_3} + K \right]$$

$$V_s \left[\frac{1}{R_2} + \frac{M}{(R_1 + M)R_3} + K \right] = B \left[\frac{1}{R_2} + \frac{1}{R_3} + K \right]$$

$$(4) \quad B = \frac{V_s \left[\frac{1}{R_2} + K + \frac{M}{(R_1 + M)R_3} \right]}{\left[\frac{1}{R_2} + \frac{1}{R_3} + K \right]} \quad **$$

Q-4-

$$V_L(t) = \begin{cases} 1 \text{ Volt,} & 0 < t < 1 \\ -1 \text{ Volt,} & 1 < t < 2 \\ 8(t-2) \text{ Volt,} & t > 2 \\ -8(t-3) \text{ Volt,} & t > 3 \\ 0 \text{ Volt,} & \text{otherwise} \end{cases}$$

$$I_L(0) = 0 \text{ Ampere}$$

$$I_L(t) = I_L(0) + \frac{1}{L} \int_{t_0}^t V_L(t') dt'$$

$$0 < t < 1 \quad V_L = 1 \text{ Volt}$$

$$I_L(t) = I_L(0) + \frac{1}{L} \int_0^t 1 dt' = 0 + t' \Big|_0^t = t \quad \text{(2)} \quad I_L(1) = 1 \text{ Ampere}$$

$$1 < t < 2 \quad V_L = -1 \text{ Volt}$$

$$I_L(t) = I_L(1) + \frac{1}{L} \int_1^t -1 dt' = 1 + (-t') \Big|_1^t = 1 + [-(t-1)] = 2 - t \quad \text{(3)}$$

$$I_L(1) = 1 \text{ Ampere}$$

$$I_L(2) = 0 \text{ Ampere}$$

$$t = 2 \quad V_L = 8(t-2) \text{ Volt}$$

$$I_L(t) = I_L(2^-) + \frac{1}{L} \int_{2^-}^t 8(t'-2) dt' = 0 + u(t-2) = u(t-2)$$

$$I_L(2^-) = u(2^- - 2) = 0 \text{ Ampere}$$

$$I_L(2^+) = u(2^+ - 2) = 1 \text{ Ampere}$$

$$2 < t < 3 \quad V_L = 0 \text{ Volt}$$

$$I_L(t) = I_L(2^+) + \frac{1}{L} \int_{2^+}^t 0 dt' = I_L(2^+) = 1 \text{ Ampere} \quad I_L(3^-) = 1 \text{ Ampere}$$

$$t=3 \quad V_L(t) = -\delta(t-3) \text{ Volt}$$

$$I_L(t) = I_L(3^-) + \frac{1}{1} \int_3^t -\delta(t'-3) dt' = 1 - u(t-3)$$

$$I_L(3^-) = 1 - u(3^- - 3) = 1 \text{ Amper}$$

(2)


$$I_L(3^+) = 1 - u(3^+ - 3) = 0 \text{ Amper}$$

$$t > 3 \quad V_L(t) = 0$$

$$I_L(t) = I_L(3^+) + \frac{1}{1} \int_3^t 0 dt' = I_L(3^+) = 0 \text{ Amper}$$


(a)
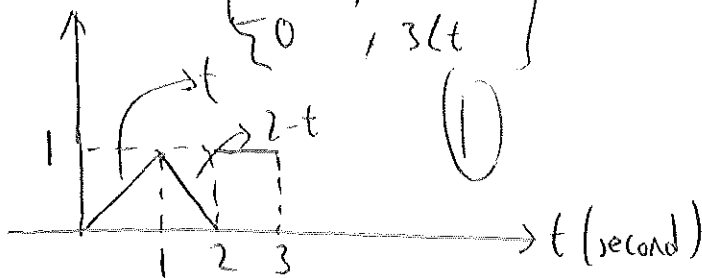
$$I_L(t) = \begin{cases} t & , 0 < t < 1 \\ 2-t & , 1 < t < 2 \\ 1 & , 2 < t < 3 \\ 0 & , 3 < t \end{cases}$$




(b)
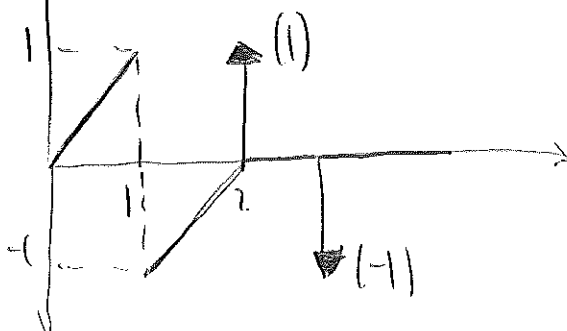
$$P_L(t) = I_L(t) V_L(t) = \begin{cases} 1 \times t \text{ Watt,} & 0 < t < 1 \\ -1 \times (2-t) \text{ Watt,} & 1 < t < 2 \\ \cancel{1.8(t-2)}, & t=2 \\ 0 \text{ Watt,} & 2 < t < 3 \\ \cancel{-1.8(t-3)}, & t=3 \\ 0 \text{ Watt} & t > 3 \end{cases}$$




$$(c) E_{\text{stored}} = \frac{1}{2} L I_L^2(t) - \frac{1}{2} L I_L^2(0) = \frac{1}{2} \times 1 [I_L^2(t) - I_L^2(0)] = \frac{1}{2} \times I_L^2(t)$$
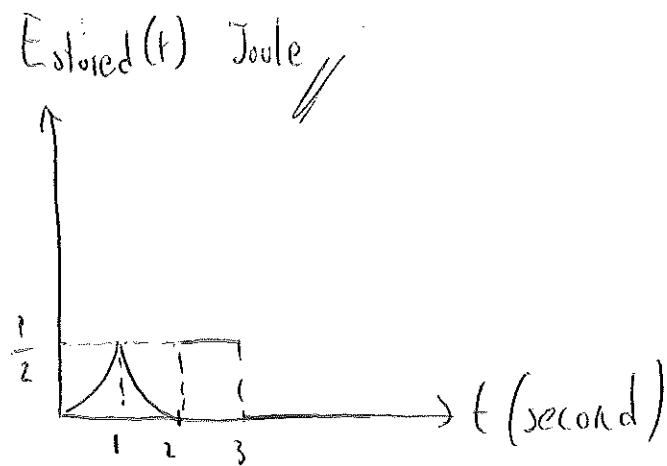
$$E_{\text{stored}} = \begin{cases} \frac{1}{2} t^2, & 0 < t < 1 \\ \frac{1}{2} (2-t)^2, & 1 < t < 2 \\ \frac{1}{2} 1^2, & 2 < t < 3 \\ 0, & t > 3 \end{cases} \quad (2)$$



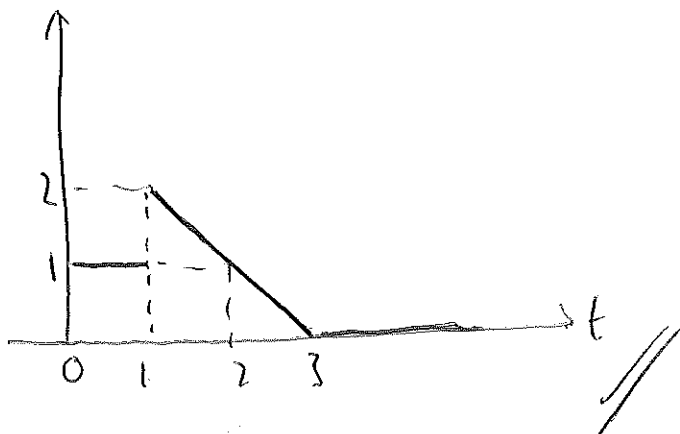Q-5 $k(t) = u(t) + u(t-1) - r(t-1) + r(t-3)$



$$Q-6 \quad x_p(t) = t e^{-t} (k_1 \sin(t) + k_2 \cos(t))$$

$$\begin{aligned} \textcircled{S} \quad \frac{d x_p(t)}{dt} &= e^{-t} [k_1 \sin(t) + k_2 \cos(t)] + t e^{-t} [k_1 \cos(t) - k_2 \sin(t)] - e^{-t} [k_1 \sin(t) + k_2 \cos(t)] \\ &= e^{-t} [k_1 \sin(t) + k_2 \cos(t)] + t e^{-t} [(k_1 - k_2) \cos(t) + (-k_1 - k_2) \sin(t)] \end{aligned}$$

$$\begin{aligned} \frac{d^2 x_p(t)}{dt^2} &= e^{-t} [k_1 \cos(t) - k_2 \sin(t)] - e^{-t} [k_1 \sin(t) + k_2 \cos(t)] \\ &+ e^{-t} [(k_1 - k_2) \cos(t) + (-k_1 - k_2) \sin(t)] \\ &- t e^{-t} [(k_1 - k_2) \cos(t) + (-k_1 - k_2) \sin(t)] \\ &+ t e^{-t} [-(k_1 - k_2) \sin(t) + (-k_1 - k_2) \cos(t)] \end{aligned}$$

$$\begin{aligned} \textcircled{S} &= e^{-t} [(2k_1 - 2k_2) \cos(t) + (-2k_1 - 2k_2) \sin(t)] \\ &+ t e^{-t} [2k_2 \sin(t) - 2k_1 \cos(t)] \end{aligned}$$

put $x_p(t)$ in diff equation

$$\frac{d^2 x_p}{dt^2} + 2 \frac{d x_p}{dt} + 2 x_p = e^{-t} \sin(t)$$

$$\begin{aligned} &e^{-t} [(2k_1 - 2k_2) \cos(t) + (-2k_1 - 2k_2) \sin(t)] + t e^{-t} [2k_2 \sin(t) - 2k_1 \cos(t)] \\ &+ 2 \left[e^{-t} [k_1 \sin(t) + k_2 \cos(t)] + t e^{-t} [(k_1 - k_2) \cos(t) + (-k_1 - k_2) \sin(t)] \right] \\ &+ 2 \left[t e^{-t} [k_1 \sin(t) + k_2 \cos(t)] \right] = e^{-t} \sin(t) \end{aligned}$$

$$x_p(t) = -\frac{1}{2} t e^{-t} \cos(t)$$

$$\frac{dx_p}{dt} = -\frac{1}{2} \left[e^{-t} \cos(t) - t e^{-t} \cos(t) - t e^{-t} \sin(t) \right] = -\frac{1}{2} \left[e^{-t} \cos(t) - t e^{-t} [\cos(t) + \sin(t)] \right]$$

$$\frac{d^2 x_p}{dt^2} = -\frac{1}{2} \left[-e^{-t} \cos(t) - e^{-t} \sin(t) \right] - \left[e^{-t} [\cos(t) + \sin(t)] - t e^{-t} [\cos(t) + \sin(t)] + t e^{-t} [-\sin(t) + \cos(t)] \right]$$

$$= -\frac{1}{2} \left[-e^{-t} [\cos(t) + \sin(t)] - e^{-t} [\cos(t) + \sin(t)] + t e^{-t} 2 \sin(t) \right]$$

$$= -\frac{1}{2} \left[-e^{-t} [2 \cos(t) + 2 \sin(t)] + t e^{-t} 2 \sin(t) \right] = \frac{1}{2} \left[e^{-t} [2 \cos(t) + 2 \sin(t)] - t e^{-t} 2 \sin(t) \right]$$

$$\frac{d^2 x}{dt^2} + 2 \frac{dx}{dt} + 2x = e^{-t} \sin(t)$$

$$\frac{1}{2} \left[e^{-t} [2 \cos(t) + 2 \sin(t)] - t e^{-t} 2 \sin(t) \right] + 2 \left(-\frac{1}{2} \right) \left[e^{-t} \cos(t) - t e^{-t} [\cos(t) + \sin(t)] \right] + 2 \left(-\frac{1}{2} t e^{-t} \cos(t) \right) = e^{-t} \sin(t)$$

$$e^{-t} \left[[\cos(t) + \sin(t) - \cos(t)] \right] + t e^{-t} \left[-\sin(t) + \cos(t) + \sin(t) - \cos(t) \right] = e^{-t} \sin(t)$$

$$e^{-t} \sin(t) = e^{-t} \sin(t) \quad \checkmark \left[\begin{array}{c} 0 \\ \text{what we have found} \\ \text{as } x_p(t) \text{ is correct} \end{array} \right]$$

$$e^{-t} \left[(2K_1 - 2K_2 + 2K_3) \cos(t) + (-2K_1 - 2K_2 + 2K_3) \sin(t) \right]$$

$$+ t e^{-t} \left[\underbrace{(2K_2 - 2K_1 - 2K_3 + 2K_1)}_0 \sin(t) + \underbrace{(-2K_1 + 2K_1 - 2K_2 + 2K_2)}_0 \cos(t) \right] = e^{-t} \sin(t)$$

$$e^{-t} \left[2K_1 \cos(t) + (-2K_2) \sin(t) \right] = e^{-t} \sin(t)$$

$$K_1 = 0$$

$$K_2 = -\frac{1}{2} //$$

(5)

$$x_p(t) = -\frac{1}{2} t e^{-t} \cos(t)$$

$$(1) \quad x_h(t) = e^{-t} [C_1 \sin(t) + C_2 \cos(t)] \rightarrow \text{char equation } s^2 + 2s + 2 = 0 \Rightarrow s_{1,2} = -1 \pm j$$

$$x(t) = x_h(t) + x_p(t) = e^{-t} [C_1 \sin(t) + C_2 \cos(t)] + \left(-\frac{1}{2}\right) t e^{-t} \cos(t)$$

$$x(0) = e^{-0} [C_1 \sin(0) + C_2 \cos(0)] + \left(-\frac{1}{2}\right) (0) e^{-0} \cos(0) = 1$$

$$C_2 = 1 \quad (1)$$

$$\left. \frac{dx}{dt} \right|_{t=0} = 1$$

$$\begin{aligned} \frac{dx}{dt} = & -e^{-t} [C_1 \sin(t) + C_2 \cos(t)] + e^{-t} [C_1 \cos(t) - C_2 \sin(t)] \\ & + \left(-\frac{1}{2}\right) [e^{-t} \cos(t) - t e^{-t} [\cos(t) + \sin(t)]] \end{aligned}$$

$$\begin{aligned} \left. \frac{dx}{dt} \right|_{t=0} = & -e^{-0} [C_1 \sin(0) + C_2 \cos(0)] + e^{-0} [C_1 \cos(0) - C_2 \sin(0)] \\ & + \left(-\frac{1}{2}\right) [e^{-0} \cos(0) - 0 e^{-0} [\cos(0) + \sin(0)]] \\ = & -1 [C_2] + 1 [C_1] + \left(-\frac{1}{2}\right) [1] = 1 \quad \text{put } C_2 = 1 \end{aligned}$$

$$-1 \times 1 + C_1 - \frac{1}{2} = 1 \quad C_1 = \frac{5}{2} \quad (1)$$

$$x(t) = e^{-t} \left[\frac{5}{2} \sin(t) + \cos(t) \right] - \frac{1}{2} t e^{-t} \quad (2)$$