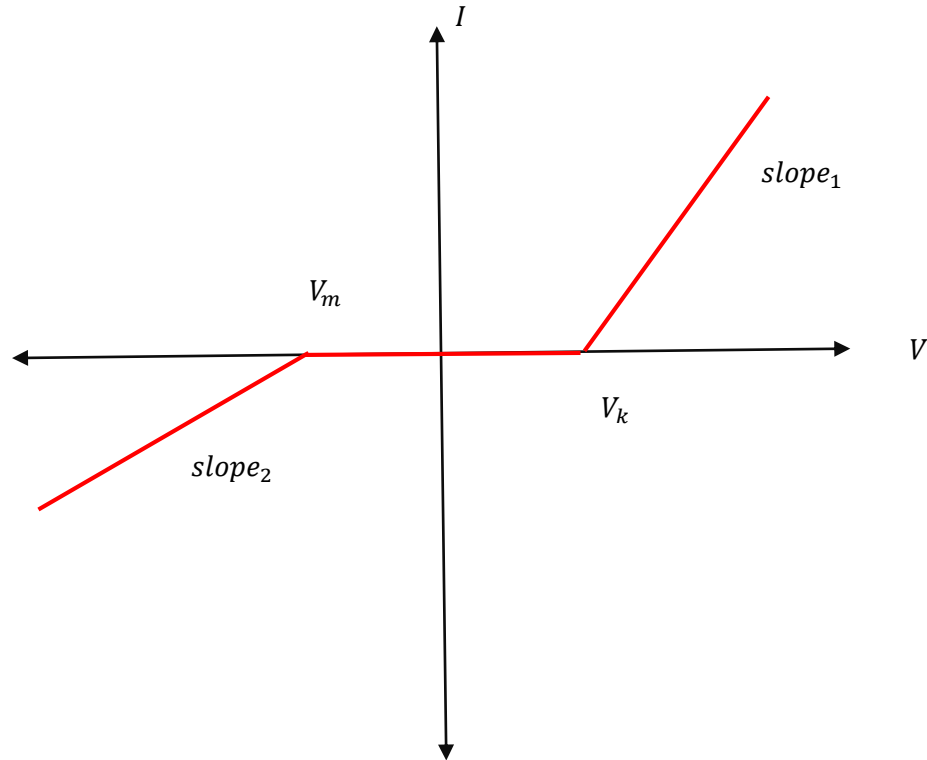


MECE 233 – Electrical Circuit Analysis + Lab


Term Project

1. With using any number of diodes, resistors and batteries construct a circuit that has the I-V characteristic shown in below.



$$\text{slope}_1 \geq 2 * \text{slope}_2, \text{ and } V_m < -1 \text{ V}, V_k > 2 \text{ V}$$

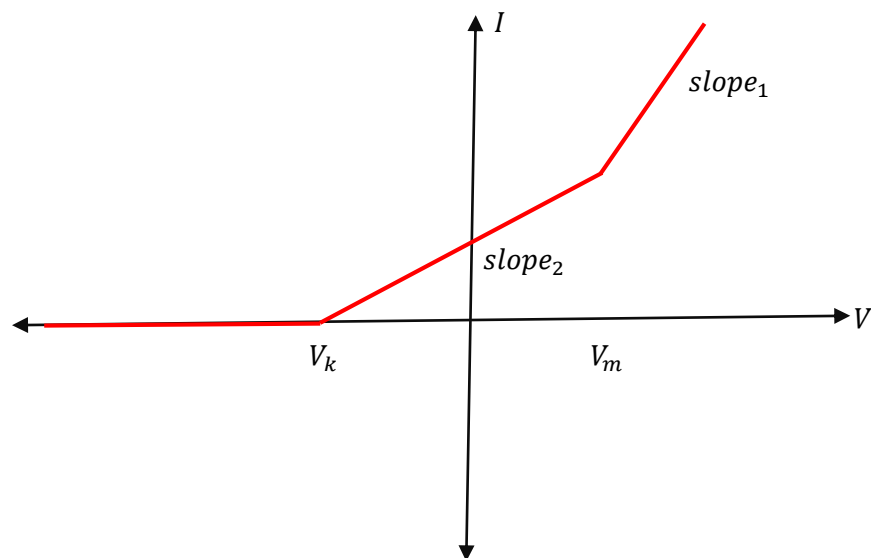2. With using any number of diodes, resistors and batteries construct a circuit that has the I-V characteristic shown in below.



$$\text{slope}_1 \geq 2 * \text{slope}_2, \text{ and } V_m < -1 \text{ V}, V_k > 2 \text{ V}$$

22.11.2019

Note 1 : Students should choose one of these design.

Note 2 : Each group should consist of at least 2 or at most 4 students.

Note 3 : Hard-copy of the 'Project Report' should submit to lab assistant until 10.01.2020.

Project Report should consists of :

- I. Report Cover (Course Name, Student Name/Number)
- II. Introduction
- III. Analysis of the Design Circuit (Mathematical Analysis, Circuit Diagrams, I-V Curve)
- IV. Results