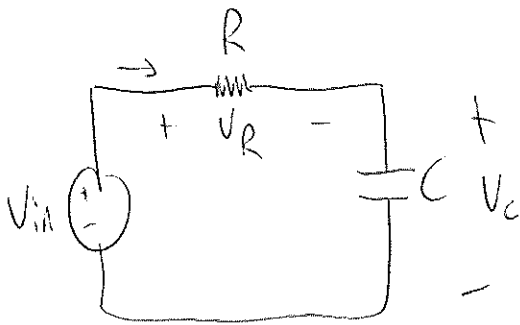


MECE 233 Final

Q1
15 puan



$$i_c = C \frac{dV_c}{dt}$$

$$I_c = I_R =$$

$$C \frac{dV_c}{dt} R + V_c = V_{in}$$

$$V_{in} = V_R + V_c \quad (3)$$

$$V_{in} = R I_R + V_c \quad (3)$$


$$V_{in} = R I_c + V_c \quad (3)$$

$$V_{in} = R C \frac{dV_c}{dt} + V_c \quad (6)$$

Q2

$$V_1 = 20 \text{ Volt}$$

15 puan

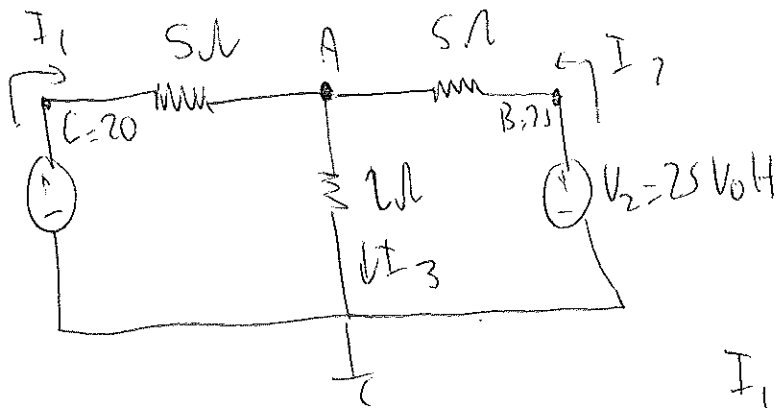

C = 20 = 4
2 puan

R = 25 = 4
2 puan

$$I_1 + I_2 = I_3$$

$$\frac{V_1 - A}{5} + \frac{V_2 - A}{5} = \frac{A}{2}$$

$$\frac{20 - A}{5} + \frac{25 - A}{5} = \frac{A}{2}$$

5 puan

$$2(20 - A + 25 - A) = 5A$$


$$90 = 9A$$

$$A = 10 \text{ Volt}$$

6 puan

25 puan

Q3

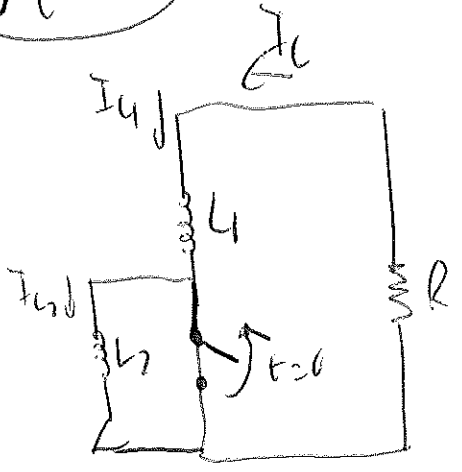

$I_{L_1}(0) = 2 \text{ Ampere}$


$I_{L_2}(0) = \frac{1}{2} \text{ Ampere}$

$L_1 = 1 \text{ H}$

$L_2 = 2 \text{ Henry}$

Gidis 10 puan

0 < t < ln 2

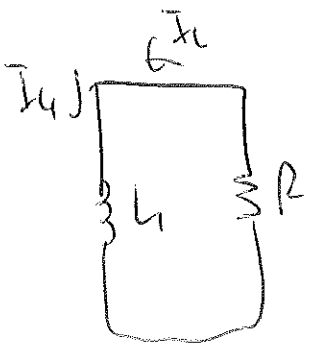

$I_1(0) = 2 \text{ Ampere}$

$L \frac{dI_1}{dt} = V_R = R(-I_1)$

$L \frac{dI_1}{dt} + R I_1 = 0$

$\frac{dI_1}{dt} + \frac{R}{L} I_1 = 0$

$\Rightarrow I_1 = k e^{-t}$

$I_1(0) = 2 e^{-0} = 2$ (2 puan)

$I_1(\ln 2) = 2 e^{-\ln 2}$

$= 2 e^{-\ln 2} = 2 e^{\ln \frac{1}{2}} = 2 \cdot \frac{1}{2} = 1$ (1 puan)

$I_L = I_{L_1}$

= 1 Ampere

at $t = \ln 2$


$L_1 I_{L_1}(\ln 2) + L_2 I_{L_2}(\ln 2) = (L_1 + L_2) I_L(\ln 2)$

$1 + 1 + 2 = \frac{3}{2} = (3) I_L(\ln 2)$

$I_L(\ln 2) = \frac{6}{3} = 2 \text{ Ampere}$

2 puan

$t) \ln 2$

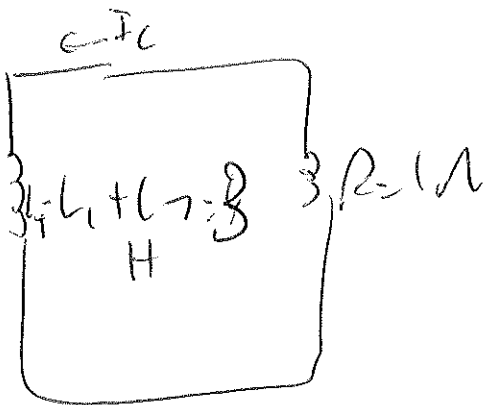

$$\frac{dI_L}{dt} + \frac{R}{L} I_L = 0$$

$$\frac{dI_L}{dt} + \frac{1}{3} I_L = 0$$


3 puan

$$I_L(t) = N e^{-\frac{t}{3}} = N e^{-\frac{1}{3}(t - \ln 2)}$$


$$2 = I_L(\ln 2) = N e^{-\frac{(\ln 2 - \ln 2)}{3}} = N \quad N = 2 \quad \text{2 puan}$$

$$I_L(t) = 2 e^{-\frac{1}{3}(t - \ln 2)}$$
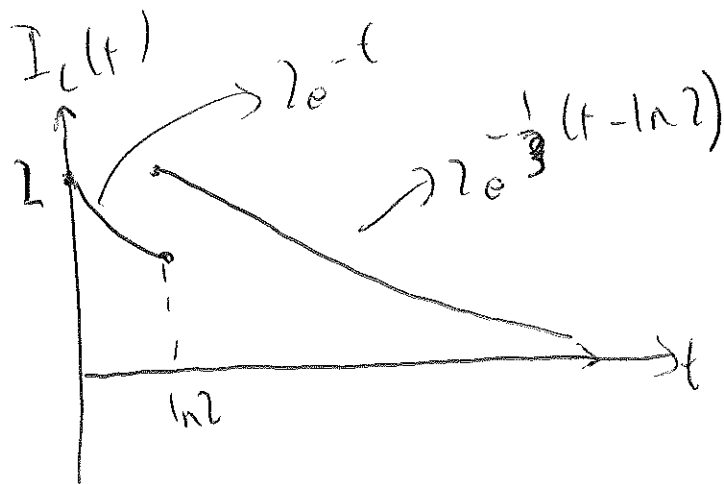
$$I_L(t) = \begin{cases} 2e^{-t} & 0 \leq t < \ln 2 \\ 2e^{-\frac{1}{3}(t - \ln 2)} & \ln 2 \leq t \end{cases}$$



3 puan

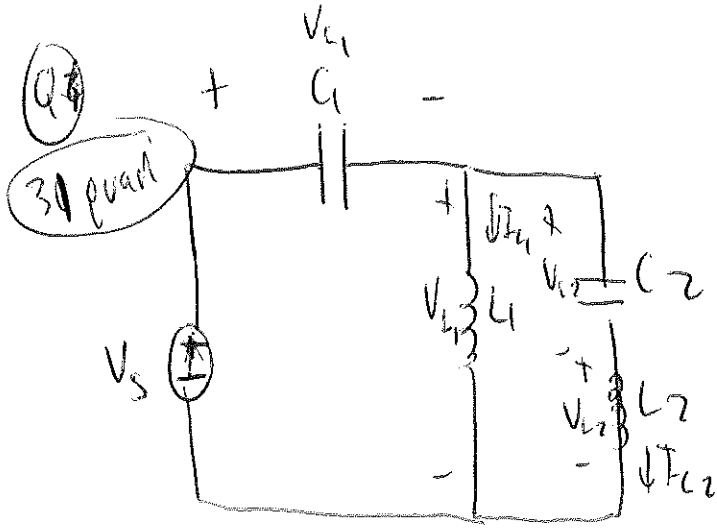

$$V_s = V_{C1} + V_{C2} + V_{C2}$$

$$V_s = V_{C1} + V_{C2} + L_2 \frac{dI_{L2}}{dt}$$

$$\frac{dI_{L1}}{dt} = \frac{V_s}{L_1} - \frac{V_{C1}}{L_1}$$

$$\frac{dI_{L2}}{dt} = \frac{V_s}{L_2} - \frac{V_{C1}}{L_2} - \frac{V_{C2}}{L_2}$$

State equations

$$V_s = V_{C1} + V_{C1}$$

$$V_s = V_{C1} + L_1 \frac{dI_{L1}}{dt}$$

$$V_{L1} = V_{C2} + V_{L2}$$

$$L_1 \frac{dI_{L1}}{dt} = V_{C2} + L_2 \frac{dI_{L2}}{dt}$$

15 puan

$$I_{L2} = C_2 \frac{dV_{C2}}{dt}$$

$$I_{C1} = I_{L1} + I_{L2}$$

$$\frac{dV_{C2}}{dt} = \frac{1}{C_2} I_{L2}$$

$$C_1 \frac{dV_{C1}}{dt} = I_{L1} + I_{L2} \Rightarrow$$

$$\frac{dV_{C1}}{dt} = \frac{1}{C_1} I_{L1} + \frac{1}{C_1} I_{L2}$$

$$\begin{bmatrix} \frac{dV_{C1}}{dt} \\ \frac{dV_{C2}}{dt} \\ \frac{dI_{L1}}{dt} \\ \frac{dI_{L2}}{dt} \end{bmatrix} = \begin{bmatrix} 0 & 0 & \frac{1}{C_1} & \frac{1}{C_1} \\ 0 & 0 & 0 & \frac{1}{C_2} \\ -\frac{1}{L_1} & 0 & 0 & 0 \\ -\frac{1}{L_2} & -\frac{1}{L_2} & 0 & 0 \end{bmatrix} \begin{bmatrix} V_{C1} \\ V_{C2} \\ I_{L1} \\ I_{L2} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \frac{1}{L_1} \\ \frac{1}{L_2} \end{bmatrix} V_s$$

16 puan

$$C_1 = 2$$

$$C_2 = 1$$

$$L_1 = 2$$

$$L_2 = 1$$

mm mm

$$\begin{bmatrix} \frac{dV_{C1}}{dt} \\ \frac{dV_{C2}}{dt} \\ \frac{dI_{L1}}{dt} \\ \frac{dI_{L2}}{dt} \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{2} & \frac{1}{2} & 0 \\ 0 & 0 & 0 & 1 \\ -\frac{1}{2} & 0 & 0 & 0 \\ -1 & -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_{C1} \\ V_{C2} \\ I_{L1} \\ I_{L2} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \frac{1}{4} \\ \frac{1}{2} \end{bmatrix} V_s$$

(Q5) $A(t) = S \cos(5t + 90^\circ) \xrightarrow{\text{phases}} S e^{j90^\circ} = S (\cos 90^\circ + j \sin 90^\circ) = Sj$
 4 point

(Q6) $\frac{d^3x}{dt^3} + \frac{d^2x}{dt^2} + 3\frac{dx}{dt} + 3x = u$

6 point

(a) char - equation $s^3 + s^2 + 3s + 3$

2 point

(b) $s^2(s+1) + 3(s+1) = 0 \quad (s^2+3)(s+1) = 0$

2 point

$s_1 = +\sqrt{3}j \quad s_2 = -\sqrt{3}j \quad s_3 = -1$ natural frequencies

(c) $x_n = k_1 e^{\sqrt{3}j t} + k_2 e^{-\sqrt{3}j t} + k_3 e^{-t}$


$x_n = M_1 \cos(\sqrt{3}t) + M_2 \sin(\sqrt{3}t) + M_3 e^{-t}$

2 point

(d) $x_p = A \cos(3t) + B \sin(3t)$

(e) $x_p = A \cos(\sqrt{3}t) + B \sin(\sqrt{3}t)$

(Q7)

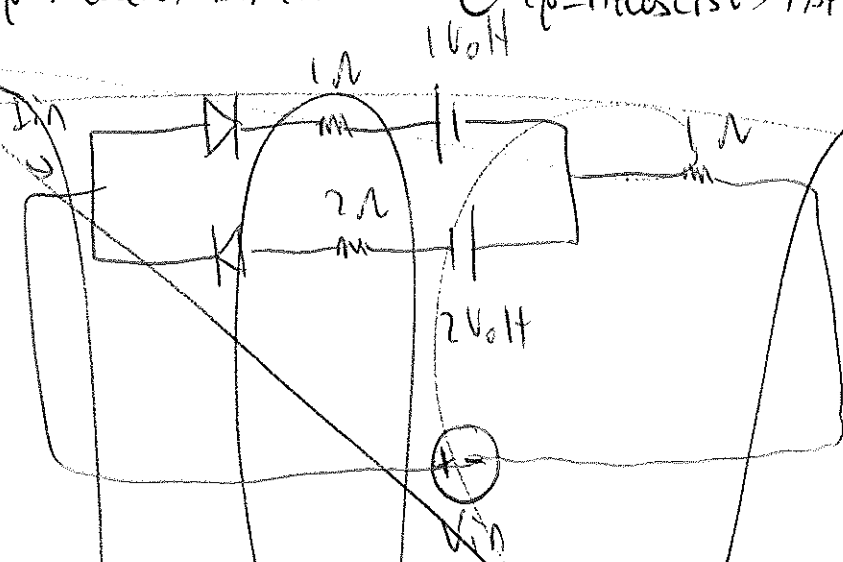

10 point

