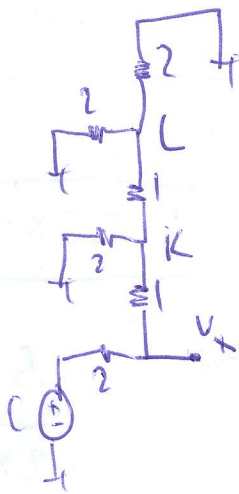


Q-1 - Use superposition theorem

Kill V_1 and V_2



$$\frac{C - V_x}{2} = \frac{V_x - K}{1} \quad (3)$$

$$\frac{C}{2} = 1.5V_x - K$$

$$\frac{V_x - K}{1} = \frac{K}{2} + \frac{K - L}{1} \quad (3)$$

$$V_x = 2.5K - L$$

$$\frac{K - L}{1} = \frac{L}{2} + \frac{L}{2} \quad (3) \rightarrow K = 2L$$


$$\rightarrow V_x = 2.5K - \frac{K}{2}$$

$$V_x = 2K$$

$$\frac{C}{2} = 1.5V_x - \frac{V_x}{2}$$

$$\boxed{\frac{C}{2} = V_x} \quad (4)$$

Kill V_1 and V_3

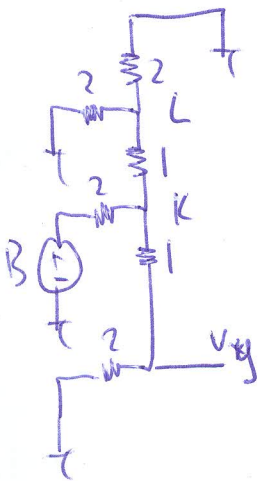

$$(3) \quad \frac{B - K}{2} = \frac{K - V_y}{1} + \frac{K - L}{1}$$

$$\rightarrow B = 2.5K - V_y - L$$

$$(3) \quad \frac{K - V_y}{1} = \frac{V_y}{2} \quad K = 1.5V_y$$

$$(3) \quad \frac{K - L}{1} = \frac{L}{2} + \frac{L}{2} \quad K = 2L$$

$$B = 2.5K - V_y - L = 2.5(1.5V_y) - V_y - \frac{K}{2}$$

$$\frac{B}{2} = 3.75V_y - V_y - \frac{1.5V_y}{2}$$

$$\frac{B}{2} = 2V_y$$

$$\boxed{V_y = \frac{B}{4}} \quad (4)$$



and V_3

② $\frac{A-L}{2} = \frac{L}{2} + \frac{L-K}{1}$

③ $\frac{L-K}{1} = \frac{K}{2} + \frac{K-V_z}{1}$

③ $\frac{K-V_z}{1} = \frac{V_z}{2}$

$\frac{A}{2} = 2L - K \rightarrow \frac{A}{2} = 2[2.5K - V_z] - K$

$L = 2.5K - V_z$

$K = 1.5V_z$

\downarrow
 $\frac{A}{2} = 4K - 2V_z$

\downarrow
 $\frac{A}{2} = 4(1.5V_z) - 2V_z$

\downarrow
 $\frac{A}{2} = 6V_z - 2V_z = 4V_z$

$V_z = \frac{A}{8}$ ④


Due to super-position

$D = V_x + V_y + V_z = \frac{C}{2} + \frac{B}{4} + \frac{A}{8}$

①

Q-2

(a)

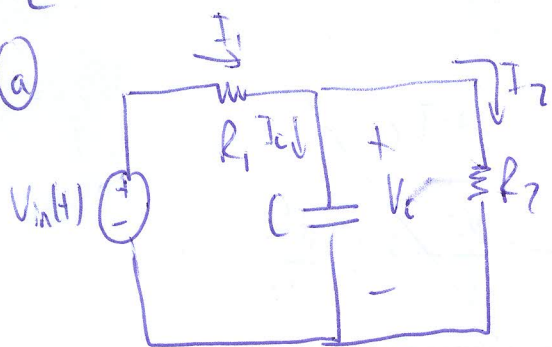

(2)

$$I_1 = I_2 + I_c$$

(3)

$$\frac{V_{in} - V_c}{R_1} = C \frac{dV_c}{dt} + \frac{V_c}{R_2}$$

(5)

$$\frac{dV_c}{dt} + \frac{1}{C} \left[\frac{1}{R_1} + \frac{1}{R_2} \right] V_c = \frac{1}{CR_1} V_{in}$$

(b) $\frac{dx}{dt} + 5x = e^{-5t} + te^{-5t}$

$$x_p(t) = (k_1 t + k_2 t^2) e^{-5t}$$

$$\frac{d}{dt} x_p(t) + 5x_p(t) = e^{-5t} + te^{-5t}$$

$$\frac{d}{dt} \left[(k_1 t + k_2 t^2) e^{-5t} \right] + 5 \left[(k_1 t + k_2 t^2) e^{-5t} \right] = e^{-5t} + te^{-5t}$$

(8)

$$(k_1 + 2k_2 t) e^{-5t} + (-5) e^{-5t} (k_1 t + k_2 t^2) + 5k_1 t e^{-5t} + 5k_2 t^2 e^{-5t} = e^{-5t} + te^{-5t}$$

$$k_1 e^{-5t} + 2k_2 t e^{-5t} - 5k_1 t e^{-5t} - 5k_2 t^2 e^{-5t} + 5k_1 t e^{-5t} + 5k_2 t^2 e^{-5t} = e^{-5t} + te^{-5t}$$

$$k_1 e^{-5t} + (2k_2 - 5k_1 + 5k_1) t e^{-5t} = e^{-5t} + te^{-5t}$$

(1) $k_1 = 1$

(1) $2k_2 = 1 \quad k_2 = \frac{1}{2}$

$$x_p(t) = \left(t + \frac{t^2}{2} \right) e^{-5t}$$


$$x_n(t) = k e^{-5t}$$

(3) $x(t) = x_n(t) + x_p(t) = \left(t + \frac{t^2}{2} \right) e^{-5t} + k e^{-5t}$

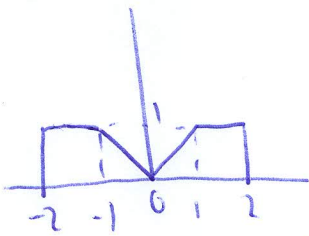(2) $x(0) = k = 2 \quad \longrightarrow \quad x(t) = \left(t - \frac{t^2}{2} \right) e^{-5t} + 2e^{-5t}$

Q-3

⑧ (a) $y(t) = u(t+2) - r(t+1) + r(t) - r(t-1) - u(t-2)$



⑨ (b) $I_c(t) = \begin{cases} 2S(t) & , 0^- < t < 0^+ \\ \sin(\pi t) & , 0^+ < t < 2 \\ 0 & , \text{otherwise} \end{cases}$

result

$$V_c(t) = \begin{cases} 2 & , 0^- < t < 0^+ \\ 2 + \frac{1}{\pi} - \frac{\cos(\pi t)}{\pi} & , 0^+ < t < 2 \\ 2 & , t > 2 \end{cases}$$

$0^- < t < 0^+$

$$V_c(t) = V_c(0^-) + \frac{1}{C} \int_{0^-}^t I_c(t') dt' = 0 + \frac{1}{1} \int_{0^-}^t 2S(t') dt' = 2u(t)$$

$V_c(0^+) = 2$ (4)

$0^+ < t < 2$


$$V_c(t) = V_c(0^+) + \frac{1}{C} \int_{0^+}^t I_c(t') dt' = 2 + \frac{1}{1} \int_{0^+}^t \sin(\pi t') dt'$$

$$= 2 + \frac{1}{\pi} (-\cos(\pi t)) \Big|_{0^+}^t = 2 + \frac{1}{\pi} [-\cos(\pi t) + \cos(0\pi)] \quad (8)$$

$$= 2 + \frac{1}{\pi} [-\cos(\pi t) + 1] = 2 - \frac{1}{\pi} [\cos(\pi t) - 1] = 2 + \frac{1}{\pi} - \frac{\cos(\pi t)}{\pi}$$


$V_c(0^+) = 2$ $V_c(1) = 2 - \frac{1}{\pi} [-1 - 1] = 2 + \frac{2}{\pi}$ $V_c(2) = 2 - \frac{1}{\pi} [1 - 1] = 2$

$2(t) \Rightarrow V_c(t) = 2$

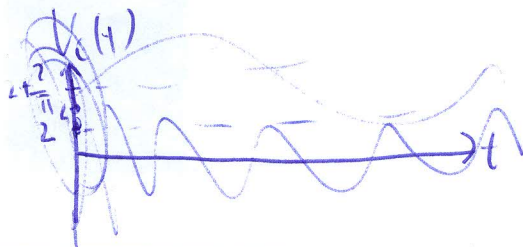


10

Q-4-

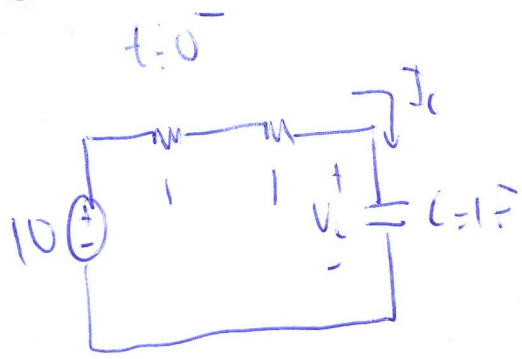

$$V_c(0^-) = 5 \text{ Volt}$$
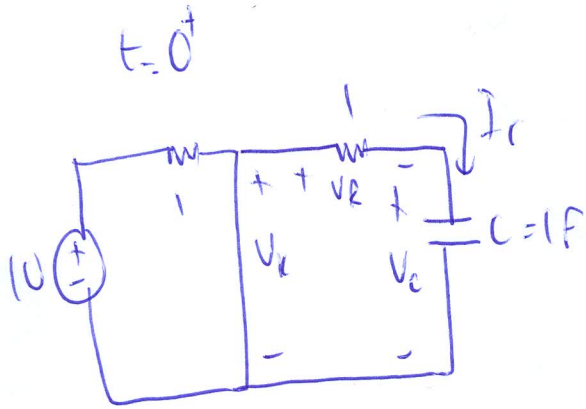
$$I_c(0^-) = \frac{10 - V_c(0^-)}{1} = \frac{10 - 5}{1} = 5 \text{ A} \quad (3)$$



$$V_c(0^+) = V_c(0^-) = 5 \text{ Volt} \quad (3)$$

due to continuity property

$$V_R = V_R + V_c$$

$$0 = V_R(0^+) + V_c(0^+)$$

$$0 = 1 \times I_c(0^+) + V_c(0^+)$$

$$0 = I_c(0^+) + 5 \quad I_c(0^+) = -5 \quad (4)$$