

Sayfa 1

$$1 - f(t) = -\frac{1}{3}e^{-2t} + \frac{1}{8}e^{-8t}$$

$$f(0) = -\frac{1}{3} + \frac{1}{8} = \frac{-5}{24}$$

$$f'(0) = \frac{2}{3} - 1 = -\frac{1}{3}$$

$$f'(t) = \frac{2}{3}e^{-2t} - e^{-8t}$$

$$f'(t^*) = 0 = \frac{2}{3}e^{-2t^*} - e^{-8t^*} = 0 \quad \frac{2}{3}e^{-2t^*} = e^{-8t^*} \quad e^{6t^*} = \frac{3}{2}$$

$$6t^* = \ln\left(\frac{3}{2}\right) \quad t^* = \frac{1}{6} \ln\left(\frac{3}{2}\right) \quad \text{minimum}$$

$$\text{when } t = t^*, f(t^*) = -\frac{1}{3}e^{-2t^*} + \frac{1}{8}e^{-8t^*}$$

$$= -\frac{1}{3}e^{-2 \cdot \frac{1}{6} \ln\left(\frac{3}{2}\right)} + \frac{1}{8}e^{-8 \cdot \frac{1}{6} \ln\left(\frac{3}{2}\right)}$$

$$= -\frac{1}{3}e^{\ln\left(\frac{3}{2}\right)^{-\frac{1}{3}}} + \frac{1}{8}e^{\ln\left(\frac{3}{2}\right)^{-\frac{4}{3}}}$$

$$= -\frac{1}{3}e^{\ln\left(\frac{2}{3}\right)^{\frac{1}{3}}} + \frac{1}{8}e^{\ln\left(\frac{2}{3}\right)^{\frac{4}{3}}}$$

$$= -\frac{1}{3} \left(\frac{2}{3}\right)^{\frac{1}{3}} + \frac{1}{8} \left(\frac{2}{3}\right)^{\frac{4}{3}}$$

$$= \left(\frac{2}{3}\right)^{\frac{1}{3}} \left[-\frac{1}{3} + \frac{1}{8} \left(\frac{2}{3}\right)\right] = \left(\frac{2}{3}\right)^{\frac{1}{3}} \left[-\frac{1}{3} + \frac{1}{12}\right]$$

$$(2) = \left(\frac{2}{3}\right)^{\frac{1}{3}} \left(-\frac{1}{4}\right)$$

$$f(t_x) = 0 = -\frac{1}{3}e^{-2t_x} + \frac{1}{8}e^{-8t_x}$$

$$\frac{1}{3}e^{-2t_x} = \frac{1}{8}e^{-8t_x}$$


$$e^{6t_x} = \frac{3}{8}$$

$$6t_x = \ln(3) - \ln(8)$$

$$t_x = \frac{\ln(3) - \ln(8)}{6}$$

so $t_x < 0$

(2)

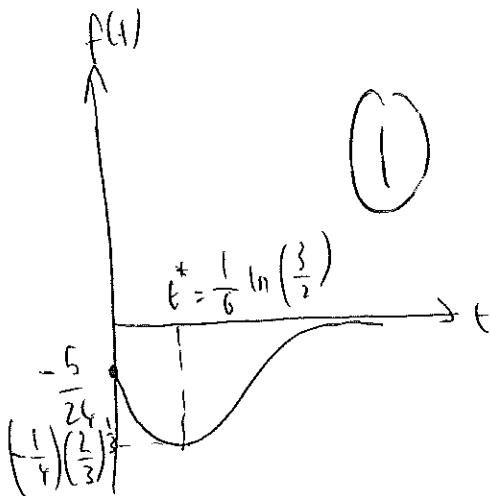

$$\lim_{t \rightarrow \infty} f(t) = 0$$


Sayfa 2

2-

$t=0^-$

$$V_1 \begin{matrix} + \\ | \\ \frac{1}{C_1} \\ | \\ - \end{matrix} \quad E_{\text{initial}-C_1} = \frac{1}{2} C_1 V_1^2(0^-)$$

$$V_2 \begin{matrix} + \\ | \\ \frac{1}{C_2} \\ | \\ - \end{matrix} \quad E_{\text{initial}-C_2} = \frac{1}{2} C_2 V_2^2(0^-)$$

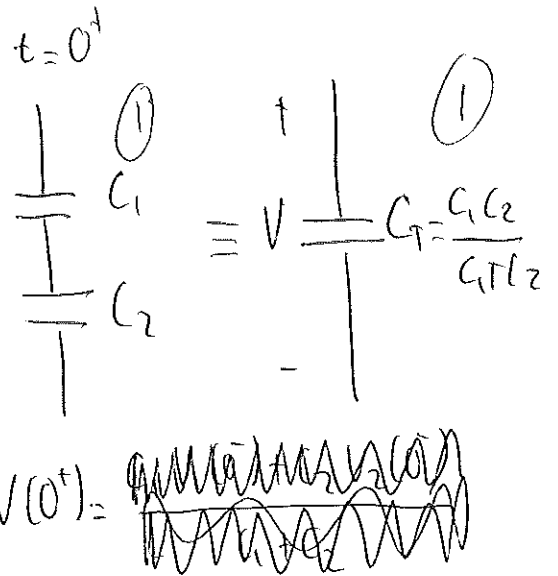

Prove that

$$E_{\text{initial}-C_1} + E_{\text{initial}-C_2} \geq E_{\text{final}}$$

Let $V_1(0^-) = a$ $V_2(0^-) = b$

~~$$\frac{1}{2} C_1 a^2 + \frac{1}{2} C_2 b^2 \geq \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} \left(\frac{C_1 a + C_2 b}{C_1 + C_2} \right)^2$$~~

$$E_{\text{final}} = \frac{1}{2} C_T V^2(0^+)$$

$$= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} \left[\frac{C_1 a + C_2 b}{C_1 + C_2} \right]^2$$

$$\frac{1}{2} C_1 a^2 + \frac{1}{2} C_2 b^2 \geq \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} [a + b]^2 \quad (2) \text{ ifadeyi aynal}$$

$$\frac{1}{2} C_1^2 a^2 + \frac{1}{2} C_1 C_2 a^2 + \frac{1}{2} C_1 C_2 b^2 + \frac{1}{2} C_2^2 b^2 \geq \frac{1}{2} [a^2 C_1 C_2 + 2ab C_1 C_2 + b^2 C_1 C_2]$$

$$\frac{1}{2} C_1^2 a^2 - ab C_1 C_2 + \frac{1}{2} C_2^2 b^2 \geq 0$$

②
bu biçime
getirmek

$$\frac{1}{2} [(C_1 a - C_2 b)^2] \geq 0 \quad \text{always true since}$$

①
tam
kare
ifadesi
 $(C_1 a - C_2 b)^2$ is always positive

Sayfa 3

3- $\frac{d^2x}{dt^2} + 2\frac{dx}{dt} + x = \sin(t)$

- (a) $s^2 + 2s + 1 = 0$ char equation (1)
- (b) $s_{1,2} = -1$ (2)
- (c) $x_h(t) = (A + Bt)e^{-t}$ (2)

4- $\frac{d^2x}{dt^2} + 2x = e^{-t}$

- (a) $s^2 + 2 = 0$ (1)
- (b) $s_{1,2} = \pm j\sqrt{2}$ (2)
- (c) $x_h(t) = A_1 \cos(\sqrt{2}t) + A_2 \sin(\sqrt{2}t)$ (2)

5- $\frac{d^2x}{dt^2} - 2\frac{dx}{dt} + 2 = \frac{1}{t}$

- (a) $s^2 - 2s + 2 = 0$ (1)
- (b) $s_{1,2} = 1 \pm j$ (2)
- (c) $x_h(t) = e^t [A_1 \cos(t) + A_2 \sin(t)]$ (2)

6- $\frac{d^2x}{dt^2} + x = 4 \sin(t)$

char equation $s^2 + 1 = 0$ input $4 \sin(t)$
 $s_{1,2} = \pm j \rightarrow$ natural frequencies \hookrightarrow angular frequency $= \omega = 1 \frac{\text{rad}}{\text{sr}}$
 Hence $s_1 = j = j \cdot \omega = j$

$x_p(t) = t [A_1 \cos(t) + A_2 \sin(t)]$ (2)

$\frac{dx_p}{dt} = [A_1 \cos(t) + A_2 \sin(t)] + t [-A_1 \sin(t) + A_2 \cos(t)]$ (3)

$\frac{d^2x_p}{dt^2} = [-A_1 \sin(t) + A_2 \cos(t)] + [-A_1 \sin(t) + A_2 \cos(t)] + t [-A_1 \cos(t) + A_2 \sin(t)]$
 $= -2A_1 \sin(t) + 2A_2 \cos(t) - t [A_1 \cos(t) + A_2 \sin(t)]$ (5)

$-2A_1 \sin(t) + 2A_2 \cos(t) - t [A_1 \cos(t) + A_2 \sin(t)] + t [A_1 \cos(t) + A_2 \sin(t)] = 4 \sin(t)$


$-2A_1 \sin(t) + 2A_2 \cos(t) = 4 \sin(t)$ $A_2 = 0, A_1 = -2$

$x_p(t) = t [-2 \cos(t)]$ (2)

~~$x_p(t) = t [-2 \cos(t) + A_2 \sin(t)]$~~

~~.....~~

Sayfa 4

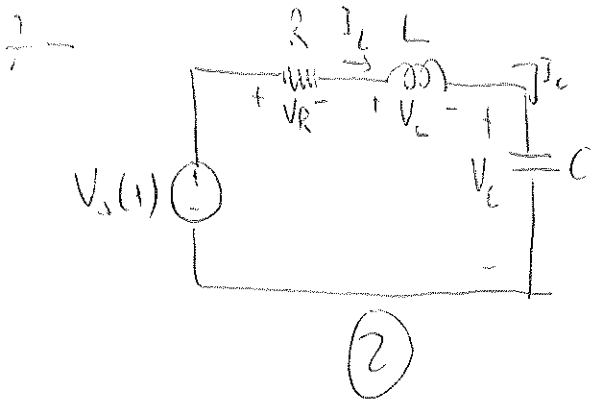

$$C \frac{dV_C}{dt} = I_C = I_L \quad (2)$$

$$\frac{dV_C}{dt} = \frac{I_L}{C}$$

$$V_s = V_R + V_L + V_C$$

$$V_s = RI_L + L \frac{dI_L}{dt} + V_C$$

$$\frac{dI_L}{dt} = \frac{V_C}{L} - \frac{R}{L} I_L - \frac{V_C}{L}$$

$$\# \frac{d^2 V_C}{dt^2} = \frac{1}{C} \frac{dI_L}{dt} = \frac{1}{C} \left[\frac{V_s}{L} - \frac{R}{L} I_L - \frac{1}{L} V_C \right] = \frac{V_C}{LC} - \frac{R}{LC} I_L - \frac{1}{LC} V_C$$

$$\frac{d^2 V_C}{dt^2} + \frac{V_C}{LC} = \frac{V_s}{LC} - \frac{R}{L} \frac{dV_C}{dt}$$

$$\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{LC} V_s$$

$$\# \frac{d^2 I_L}{dt^2} = \frac{1}{L} \frac{dV_s}{dt} - \frac{R}{L} \frac{dI_L}{dt} - \frac{1}{L} \frac{dV_C}{dt}$$


$$\frac{d^2 I_L}{dt^2} + \frac{R}{L} \frac{dI_L}{dt} = \frac{1}{L} \frac{dV_s}{dt} - \frac{I_L}{LC}$$

$$\frac{d^2 I_L}{dt^2} + \frac{R}{L} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{1}{L} \frac{dV_s}{dt}$$

(2)

Sayfa 5


8-

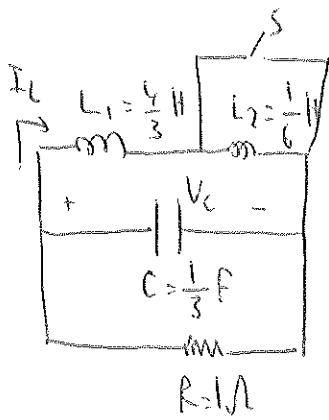

$V_c(0) = 5 \text{ Volt}$
 $I_L(0) = 0 \text{ Amper}$

$0 < t < \ln(2)$ switch open (L_1 and L_2 series)

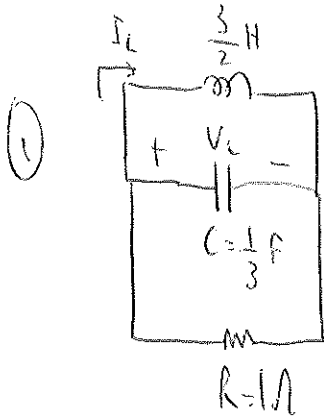$L_T = L_1 + L_2 = \frac{3}{2} \text{ H}$



$V_c(0) = 5 \text{ Volt}$
 $I_L(0) = 0 \text{ Amper}$

$\frac{V_c}{R} + I_L + C \frac{dV_c}{dt} = 0$ $L_T \frac{dI_L}{dt} = V_c$

$V_c + I_L + \frac{1}{3} \frac{dV_c}{dt} = 0$ $\frac{3}{2} \frac{dI_L}{dt} = V_c$

② $\frac{dV_c}{dt} = -3V_c - 3I_L$

② $\frac{dI_L}{dt} = \frac{2}{3} V_c$

* $\frac{d^2 I_L}{dt^2} = \frac{2}{3} \frac{dV_c}{dt} = \frac{2}{3} [-3V_c - 3I_L] = -2V_c - 2I_L = -\frac{3}{2} \times 2 \frac{dI_L}{dt} - 2I_L$

Hence $\frac{d^2 I_L}{dt^2} + 3 \frac{dI_L}{dt} + 2I_L = 0$ $I_L(0) = 0 \text{ Amper}$ (0.5)
 $\frac{dI_L}{dt}(0) = \frac{2}{3} V_c(0) = \frac{10}{3}$ (0.5)

③ char-equation: $s^2 + 3s + 2 = 0$ $s_{1,2} = -1, -2$ (natural frequencies)
 (overdamped case)

① $I_L(t) = A_1 e^{-t} + A_2 e^{-2t}$ $\frac{dI_L}{dt} = -A_1 e^{-t} - 2A_2 e^{-2t}$ $A_1 = \frac{10}{3}$ $A_2 = -\frac{10}{3}$
 $I_L(0) = 0 = A_1 + A_2$ (0.5) $\frac{dI_L}{dt}(0) = \frac{10}{3} = -A_1 - 2A_2$ (0.5) (0.5)

(Sample 6)

$$I_L(t) = \frac{10}{3} e^{-t} - \frac{10}{3} e^{-2t} \quad L_T \frac{dI_L}{dt} = V_L = V_C = \frac{3}{2} \frac{d}{dt} \left[-\frac{10}{3} e^{-2t} + \frac{10}{3} e^{-t} \right]$$

$$\textcircled{1} V_C(t) = -5e^{-t} + 10e^{-2t}$$


Hence when $0 \leq t < \ln(2) \rightarrow \begin{cases} V_C(t) = -5e^{-t} + 10e^{-2t} \\ I_L(t) = \frac{10}{3} e^{-t} - \frac{10}{3} e^{-2t} \end{cases}$

$$V_C(\ln(2)) = -5e^{-\ln(2)} + 10e^{-2\ln(2)} = -5e^{\ln(\frac{1}{2})} + 10e^{\ln(\frac{1}{4})} = -5 \times \frac{1}{2} + 10 \times \frac{1}{4} = 0 \quad \textcircled{0.5}$$

$$V_C(\ln(2)) = 0 \text{ Volt} //$$

$$I_L(\ln(2)) = \frac{10}{3} e^{-\ln(2)} - \frac{10}{3} e^{-2\ln(2)} = \frac{10}{3} e^{\ln(\frac{1}{2})} - \frac{10}{3} e^{\ln(\frac{1}{4})} = \frac{10}{3} \times \frac{1}{2} - \frac{10}{3} \times \frac{1}{4} = \frac{5}{6} \text{ Amper} \quad \textcircled{0.5}$$

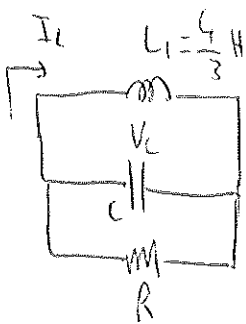when $t > \ln(2)$ switch closed [L_2 shorted]



$$\phi(\ln(2^-)) = \phi(\ln(2^+)) \quad \text{[conserve total flux]}$$

$$I_L(\ln(2^-)) L_T = L_1 I_L(\ln(2^+)) \quad \textcircled{1}$$

$$\frac{5}{6} \times \frac{3}{2} = \frac{4}{3} I_L(\ln(2^+)) \quad I_L(\ln(2^+)) = \frac{15}{16} \text{ Amper} //$$

$$\textcircled{0.5} V_C(\ln(2^+)) = V_C(\ln(2^-)) = 0 \text{ Volt (no change)}$$

(To find the diff equations just put L_1 instead of L_T)
for the diff-equations valid for $t > \ln(2)$

$$\frac{d^2 I_C}{dt^2} + 3 \frac{dI_C}{dt} + \frac{9}{4} I_C = 0$$

$$I_L(\ln(2^+)) = \frac{15}{16} //$$

$$\downarrow s^2 + 3s + \frac{9}{4} = 0$$

(char-equation)

$\textcircled{2}$

$$\textcircled{0.5} s_{1,2} = -\frac{3}{2} //$$

(critically-damped case)
(natural frequencies)

$$\frac{dI_C}{dt}(\ln(2^+)) = \frac{3}{4} V_C(\ln(2^+)) = 0 //$$

$$\text{Hence } I_C(t) = (A + B) e^{-\frac{3}{2}t} \text{ or } I_C(t) = [A(t - \ln(2)) + B] e^{-\frac{3}{2}(t - \ln(2))}$$

$\rightarrow \textcircled{0}$

Sayfa 7

$$\frac{dI_L}{dt} = A e^{-\frac{3}{2}(t-\ln(2))} + \left(-\frac{3}{2}\right) e^{-\frac{3}{2}(t-\ln(2))} \left[A(t-\ln(2)) + B \right] \quad (1)$$

$$I_L(\ln(2)) = B = \frac{15}{16} \quad (0.5)$$

$$\frac{dI_L}{dt}(\ln(2)) = A - \frac{3}{2}B = 0$$

$$\rightarrow A = \frac{45}{32} \quad (0.5)$$

$$I_L(t) = \left[\frac{45}{32}(t-\ln(2)) + \frac{15}{16} \right] e^{-\frac{3}{2}(t-\ln(2))} \quad (1) \rightarrow \text{when } t \rightarrow \ln(2)$$

$$L_1 \frac{dI_L}{dt} = V_0 = \frac{4}{3} \left[\frac{45}{32} e^{-\frac{3}{2}(t-\ln(2))} + \left(-\frac{3}{2}\right) e^{-\frac{3}{2}(t-\ln(2))} \left[\frac{45}{32}(t-\ln(2)) + \frac{15}{16} \right] \right]$$

$$(1) \quad V_L(t) = \frac{45}{8} e^{-\frac{3}{2}(t-\ln(2))} - 2 \left[\frac{45}{32}(t-\ln(2)) + \frac{15}{16} \right] \rightarrow \text{when } t \rightarrow \ln(2)$$

Giris 10 puan