

Q-1-

$$\textcircled{1} X_L = j\omega L = j\omega L = j \cdot 1 \cdot 1 = j \Omega$$

$$X_R = 1 \Omega \textcircled{2}$$


$$\textcircled{2} X_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 1 \cdot 1} = -j \Omega$$

$$V_p = e^{j0} = e^{j0^\circ} = (\cos 0^\circ + j \sin 0^\circ) = 1 \textcircled{2}$$

$$\tilde{I}_{Lp} = \frac{V_p}{X_C + X_L + X_R} = \frac{1}{j(-j) + 1} = 1 \textcircled{5}$$

$$\tilde{I}_{L_{SSS}}(t) = 1 \cos(t) \textcircled{2}$$

2

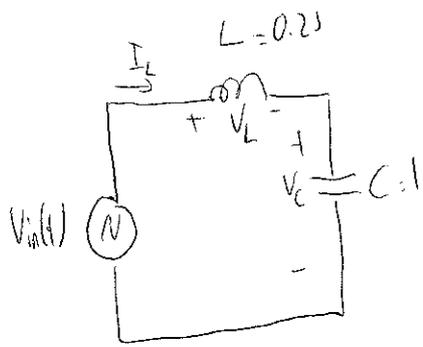

$$V_{in} = V_L + V_C \quad I_L = I_C = C \frac{dV_C}{dt} \quad \boxed{\frac{dV_C}{dt} = \frac{I_L}{1} = I_L}$$

$$V_{in} = L \frac{dI_L}{dt} + V_C$$

$$V_{in} = L \frac{d}{dt} \left[ C \frac{dV_C}{dt} \right] + V_C \rightarrow V_{in} = LC \frac{d^2 V_C}{dt^2} + V_C$$

$$V_{in}(t) = \sin(3t) \Rightarrow \omega = 3 \frac{\text{rad}}{\text{sec}}$$


$$\frac{d^2 V_C}{dt^2} + \frac{1}{LC} V_C = \frac{1}{LC} V_{in} \quad \frac{d^2 V_C}{dt^2} + 4V_C = 4V_{in} \quad \text{2}$$

char-equation  $s^2 + 4 = 0 \quad s_1 = 2j \Rightarrow s_1 \neq j\omega = 3j$  hence  
 $s_2 = -2j \Rightarrow s_2 \neq j\omega = 3j$

(a) Sinusoidal steady state exists  $\Rightarrow$  2

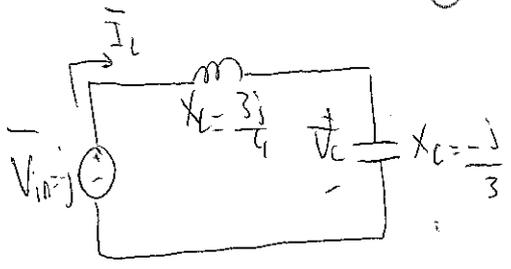(b) Use phasors  $V_{in}(t) = \sin(3t) = \cos(3t - 90^\circ) \rightarrow \bar{V}_{in} = e^{j90} = \cos(-90) + j \sin(-90) = -j$  1

$$X_L = j\omega L = j \cdot 3 \cdot 0.25 = \frac{3j}{4} \quad X_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 3 \cdot 1} = -\frac{j}{3} \quad \text{1}$$



$$\bar{I}_L = \frac{\bar{V}_{in}}{X_L + X_C} = \frac{-j}{\frac{3j}{4} - \frac{j}{3}} = \frac{-j}{\frac{9j - 4j}{12}} = \frac{-j}{\frac{5j}{12}} = \frac{-12j}{5j} = -\frac{12}{5} \quad \text{3}$$

$$\bar{V}_C = \bar{I}_L X_C = -\frac{12}{5} \left(-\frac{j}{3}\right) = \frac{4j}{5} = \frac{4}{5} [0 + j] = \frac{4}{5} [\cos(90) + j \sin(90)] = \frac{4}{5} e^{j90}$$

$$V_{C_{SSS}} = \frac{4}{5} \cos(3t + 90) = -\frac{4}{5} \sin(3t) \quad \text{1}$$

(c)  $\frac{d^2 V_C}{dt^2} + 4V_C = 4 \sin(3t)$

$$V_C(0) = 1 \text{ Volt}$$

$$\frac{dV_C}{dt}(0) = \frac{I_C(0)}{C} = \frac{0}{1} = 0 \text{ Volt/sec} \quad \text{1}$$

$$V_{cp} = K_1 \sin(3t) + K_2 \cos(3t)$$

$$\boxed{\frac{d^2 V_{cp}}{dt^2} = -9K_1 \sin(3t) - 9K_2 \cos(3t)} \quad \text{1}$$

$$\frac{dV_{cp}}{dt} = 3K_1 \cos(3t) - 3K_2 \sin(3t)$$

$$\begin{aligned} & -9K_1 \sin(3t) - 9K_2 \cos(3t) + 4K_1 \sin(3t) + 4K_2 \cos(3t) = 4 \sin(3t) \\ & \text{1) } -5K_1 \sin(3t) - 5K_2 \cos(3t) = 4 \sin(3t) \end{aligned}$$

$$k_1 = -\frac{4}{5} \quad k_2 = 0$$

$$V_{cp} = -\frac{4}{5} \sin(3t) \quad (1)$$

$$s^2 + 4 = 0 \rightarrow \text{char-equation}$$
$$V_{ch} = M_1 \cos(2t) + M_2 \sin(2t)$$

$$V_c = V_{cp} + V_{ch} = -\frac{4}{5} \sin(3t) + M_1 \cos(2t) + M_2 \sin(2t) \quad (1)$$


$$V_c(0) = 1 = M_1$$

$$\frac{dV_c}{dt} = -\frac{12}{5} \cos(3t) - 2M_1 \sin(2t) + 2M_2 \cos(2t) \quad (1)$$

$$\left. \frac{dV_c}{dt} \right|_{t=0} = 0 = -\frac{12}{5} + 2M_2 \quad M_2 = \frac{6}{5} \quad (2)$$

$$V_c(t) = -\frac{4}{5} \sin(3t) + \cos(2t) + \frac{6}{5} \sin(2t)$$

Q-3

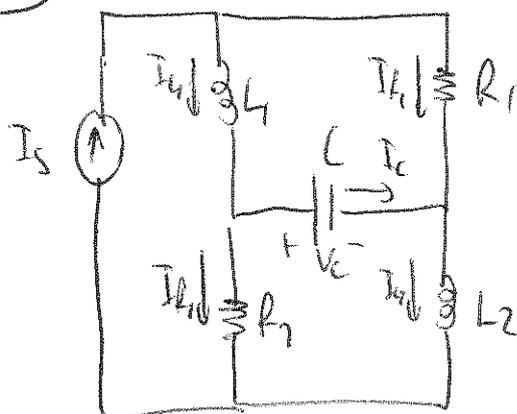

~~Multiple choice~~

~~Multiple choice~~

$$(I_{L1} - I_c) = I_{R2} \quad (1)$$

$$I_{R2} + I_{L2} = I_s \quad (1)$$

$$\rightarrow I_{L1} - I_c + I_{L2} = I_s \quad I_{L1} + I_{L2} - I_s = I_c = C \frac{dV_c}{dt}$$

$$\frac{dV_c}{dt} = \frac{I_{L1}}{C} + \frac{I_{L2}}{C} - \frac{I_s}{C} \quad (3)$$

$$I_c = I_{L1} + I_{L2} - I_s \quad (1)$$

$$V_{R2} = V_c + V_{L2} = V_c + L_2 \frac{dI_{L2}}{dt} = R_2 I_{R2} = R_2 (I_{L1} + I_{L2} - I_s) = R_2 (I_s - I_{L2})$$

you can use KVL

$$V_c + L_2 \frac{dI_{L2}}{dt} = R_2 I_{L1} + R_2 I_{L2} - R_2 I_s$$

$$\frac{dI_{L2}}{dt} = \frac{R_2}{L_2} I_{L1} + \frac{R_2}{L_2} I_{L2} - \frac{V_c}{L_2} - \frac{R_2 I_s}{L_2}$$

$$\frac{dI_{L2}}{dt} = \frac{R_2}{L_2} I_s - \frac{R_2}{L_2} I_{L2} - \frac{V_c}{L_2}$$

(3)


~~Multiple choice~~

$$L_1 \frac{dI_{L1}}{dt} + V_c = V_{R1} = I_{R1} R_1 = R_1 (I_s - I_{L1})$$

$$\frac{dI_{L1}}{dt} = \frac{R_1}{L_1} I_s - \frac{R_1}{L_1} I_{L1} - \frac{V_c}{L_1} \quad (3)$$

$$\begin{pmatrix} V_c \\ I_{L1} \\ I_{L2} \end{pmatrix} = \begin{bmatrix} 0 & \frac{1}{C} & \frac{1}{C} \\ -\frac{1}{L_1} & -\frac{R_1}{L_1} & 0 \\ \frac{1}{L_2} & 0 & -\frac{R_2}{L_2} \end{bmatrix} \begin{pmatrix} V_c \\ I_{L1} \\ I_{L2} \end{pmatrix} + \begin{pmatrix} \frac{1}{C} \\ \frac{R_1}{L_1} \\ \frac{R_2}{L_2} \end{pmatrix} I_s$$

Q-4

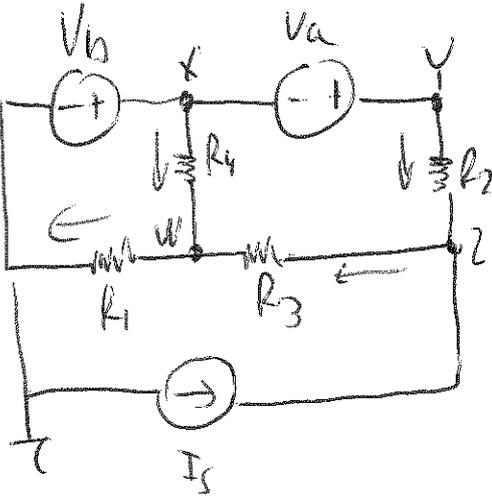

(a)  $X = V_b$ ,  $Y = V_a + V_b$

(b)  $I_s + \frac{Y-Z}{R_2} = \frac{Z-W}{R_3}$


$$I_s + \frac{V_a V_b - Z}{R_2} = \frac{Z - W}{R_3}$$

$$\frac{Z-W}{R_3} + \frac{X-W}{R_4} = \frac{W}{R_1}$$

$$\frac{Z-W}{R_3} + \frac{V_b - W}{R_4} = \frac{W}{R_1}$$

Q-5

Gidis 4

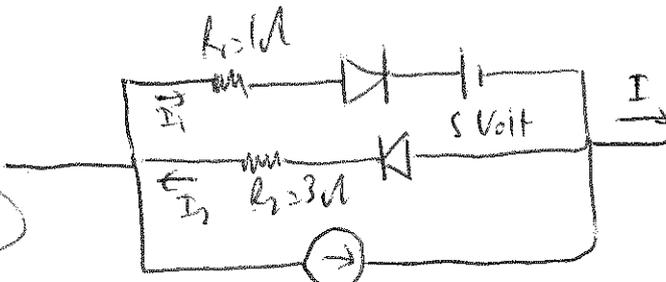

$$I = I_1 + I_x - I_2$$

$I_s = 3 \text{ Amperes}$

Critical points 0, 5 Volt

\* if  $V > 5 \text{ Volt}$   $I_1$  ✓  $I_x$  ✓  $I_2$  ✗

$$I_1 = I_x - I_2 = I_1 + 3 \quad I_1 = (I - 3)$$

$$V = R_1 I_1 + 5 = 1(I - 3) + 5$$

$$V = I + 2 \rightarrow I = V - 2$$

\* if  $0 < V < 5 \text{ Volt}$   $I_1$  ✗  $I_2$  ✗  $I_x$  ✓

$$I = I_x = 3$$


\* if  $V < 0$   $I_1$  ✗  $I_2$  ✓  $I_x$  ✓

$$I = I_x - I_2 \quad V = -I_2 R_3$$

$$I_2 = I_x - I = 3 - I$$

$$V = -(3 - I) \cdot 3 = 3I - 9$$
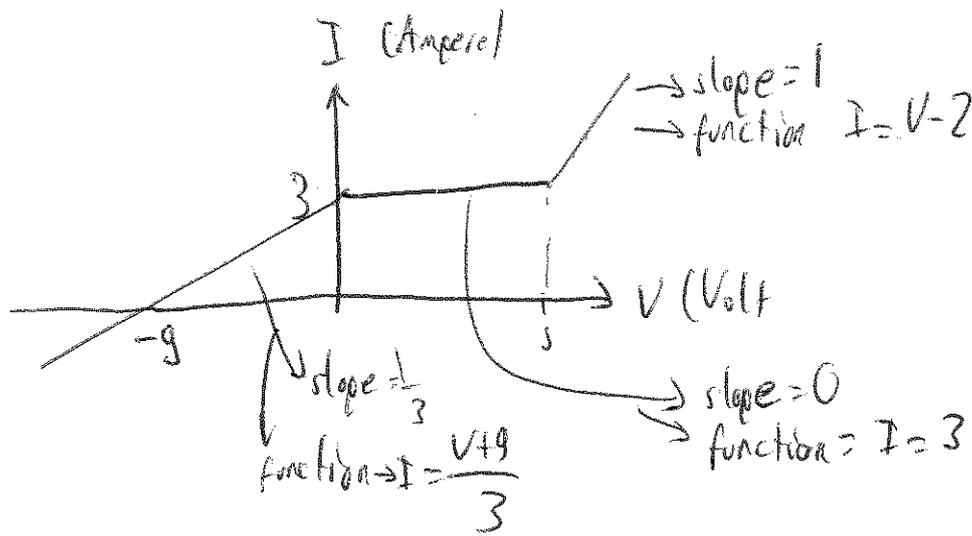
$$V = 3I - 9 \rightarrow I = \frac{V+9}{3}$$



①


Q-6

0 < t < ln 2

Second capacitor is inactive hence  $V_2(\ln 2^-) = V_2(0) = 2.5 \text{ Volt}$  ①

The functioning circuit

Gids  
6

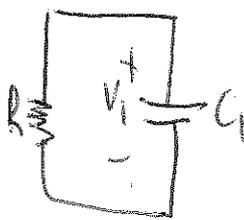

$V_1(0) = 1 \text{ Volt}$  ②

$C_1 \frac{dV_1}{dt} + \frac{V_1}{R} = 0$

$\frac{dV_1}{dt} + \frac{1}{C_1 R} V_1 = 0$

$\frac{dV_1}{dt} + V_1 = 0$  (only homogeneous solution)

$V_1(t) = K e^{-t}$  ③

$V_1(0) = 1 = K \quad V_1(t) = e^{-t}$

$V_1(\ln 2^-) = e^{-\ln 2} = e^{\ln(1/2)} = \frac{1}{2} \text{ Volt}$  ④


$t \geq \ln 2$  (preserve the amount of charges)

$Q(\ln 2^-) = Q(\ln 2^+)$

$C_1 V_1(\ln 2^-) + C_2 V_2(\ln 2^-) = (C_1 + C_2) V_c(\ln 2^+)$  ⑤

$1 \times \frac{1}{2} + 3 \times \frac{5}{2} = (1+3) V_c(\ln 2^+) \quad V_c(\ln 2^+) = 2 \text{ Volt}$

new functioning circuit

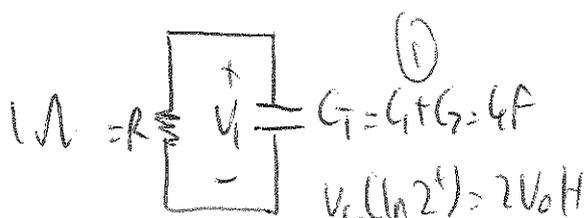

$C_T \frac{dV_1}{dt} + \frac{V_1}{R} = 0$

$\frac{dV_1}{dt} + \frac{V_1}{4} = 0$

(only homogeneous solution)

$V_1(t) = M e^{-\frac{(t-\ln 2)}{4}}$  ⑥

$V_1(\ln 2^+) = 2 = M$

$V_1(t) = 2 e^{-\frac{(t-\ln 2)}{4}}$

$$0 < t < \ln 2 \quad V_1(t) = e^{-t} - \frac{(t - \ln 2)}{4}$$

$$t > \ln 2 \quad V_1(t) = 2e^{-\frac{(t - \ln 2)}{4}}$$

