
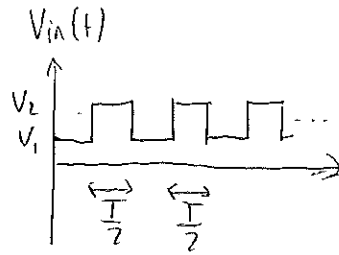


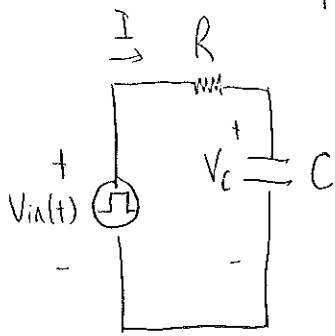First Order Circuits (Preliminary Work) ①



$$V_{in} = RI + V_c$$

$$I = C \frac{dV_c}{dt}$$

$$V_{in} = RC \frac{dV_c}{dt} + V_c$$

~~$$I = C \frac{dV_c}{dt}$$~~

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_{in}$$

$V_0 \rightarrow$ initial condition

Solution to the differential equation

$$V_c(t) = V_0 e^{-(t-t_0)/\tau} + V_s (1 - e^{-(t-t_0)/\tau})$$

where $\tau = RC$ (time constant), $V_0 \rightarrow$ initial condition, $V_s \rightarrow$ input (either V_1 or V_2)

For $0 < t < \frac{T}{2} \Rightarrow V_{in}(t) = V_2, V_c(t) = V_2 (1 - e^{-\frac{t}{\tau}})$ $V_c(\frac{T}{2}) = V_2 (1 - e^{-\frac{T}{2\tau}})$

For $\frac{T}{2} < t < T \Rightarrow V_0 = V_c(\frac{T}{2}), V_{in}(t) = V_1$

$$V_c(t) = V_2 (1 - e^{-\frac{T}{2\tau}}) e^{-(t-\frac{T}{2})/\tau} + V_1 (1 - e^{-(t-\frac{T}{2})/\tau})$$

For $T < t < \frac{3T}{2} \Rightarrow V_0 = V_c(T), V_{in}(t) = V_2$

$$V_c(t) = V_0 e^{-(t-T)/\tau} + V_2 (1 - e^{-(t-T)/\tau})$$

⋮
And so on for other time intervals

② if $T \gg \tau$ [the period of the square waveform is much greater than the time constant of RC circuit]

then, For $0 < t < \frac{T}{2}$, $V_{in}(t) = V_2$
 $V_c(t) = V_2 (1 - e^{-\frac{t}{\tau}})$, $V_c(\frac{T}{2}) = V_2 (1 - e^{-\frac{T}{2\tau}}) \approx V_2$

For $\frac{T}{2} < t < T$, $V_{in}(t) = V_1$
 $V_c(\frac{T}{2}) \approx V_2 = V_0$ [new initial condition when $\frac{T}{2} < t < T$] and ~~scribbled out~~

$$V_c(t) \approx V_2 e^{-(t-\frac{T}{2})/\tau} + V_1 (1 - e^{-\frac{(t-\frac{T}{2})}{\tau}})$$



$$V_c(\frac{T}{2}) \approx V_2 \quad V_c(T) \approx V_1$$

For $T < t < \frac{3T}{2}$, $V_{in}(t) = V_2$, initial condition = $V_c(T) \approx V_1 = V_0$

$$V_c(t) = V_1 e^{-(t-T)/\tau} + V_2 (1 - e^{-(t-T)/\tau})$$

Hence when $f = 2 \text{ kHz}$, $R = 3.3 \text{ k}\Omega$, $C = 4.7 \text{ nF}$

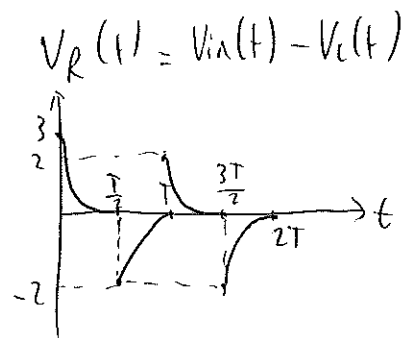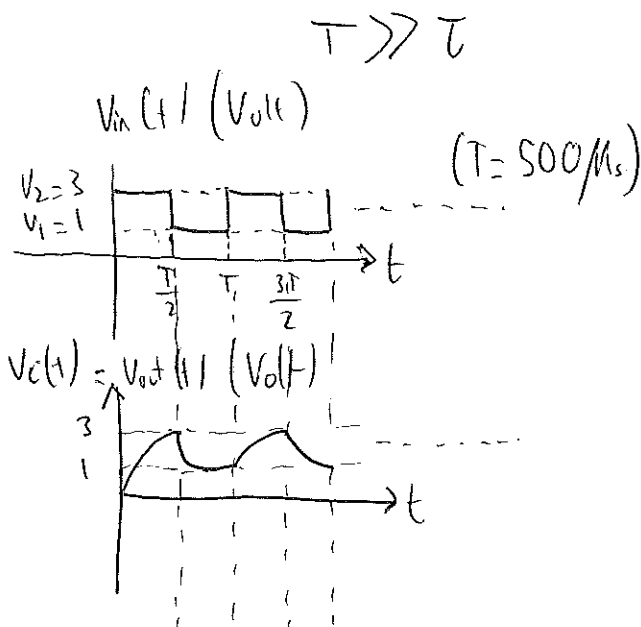when $f = 2 \text{ kHz} \rightarrow T = \frac{1}{2000} = 0.5 \text{ ms} = 500 \mu\text{s}$
 $\tau = 3.3 \times 10^3 \times 4.7 \times 10^{-9} = 15.51 \mu\text{s}$



3

** when $f = 2\text{kHz}$, $R = 3.3\text{k}\Omega$, $C = 10\text{nF}$

$$T = \frac{1}{2000} = 0.5\text{ms} = 500\mu\text{s}$$

$$\tau = 3.3 \times 10^3 \times 10 \times 10^{-9} = 33 \times 10^{-6}\text{sec}$$

$$= 33\mu\text{sec}$$

$$T \gg \tau$$


when we compare * and **, we can see that $T = 15.51\mu\text{s}$ for * but $T = 33\mu\text{s}$ for ** this means The first RC circuit "*" has a faster response. But the waveforms obtained for V_C and V_R will be similar for "**"

*** when $f = 2\text{kHz}$, $R = 68\text{k}\Omega$, $C = 10\text{nF}$

$$T = \frac{1}{2000} = 500\mu\text{s}$$


$$\tau = 68 \times 10^3 \times 10 \times 10^{-9} = 680\mu\text{sec}$$

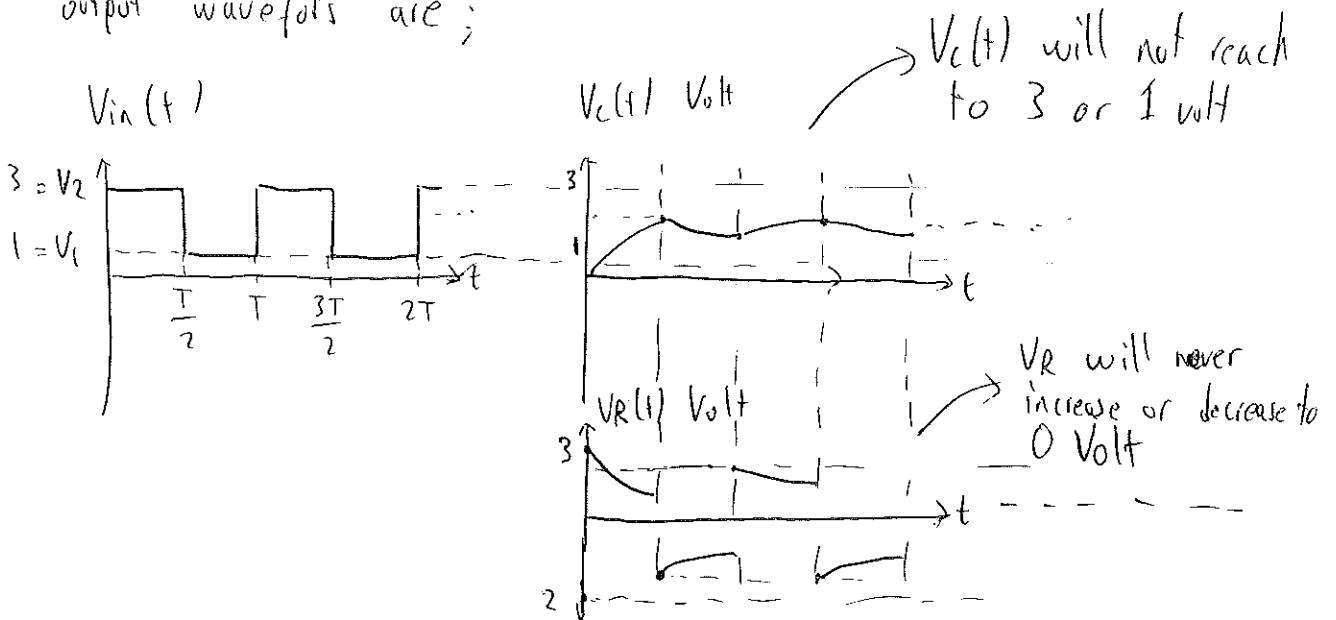we cannot say that $T \gg \tau$, so this circuit has a very slow response. The positive and negative cycles of input waveform (square wave) will change suddenly before the capacitor is fully charged ($V_0 \approx V_2$) or discharged ($V_0 \approx V_1$). Hence the output waveforms are;



(4)

1-b

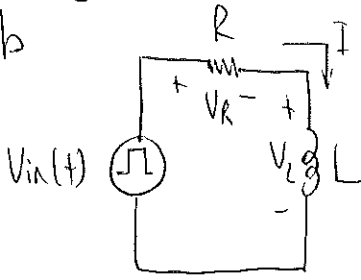

$$V_{in} = V_R + V_L \rightarrow V_{in} = RI + L \frac{dI}{dt}$$

$$V_L = L \frac{dI}{dt} \rightarrow \frac{dI}{dt} + \frac{R}{L} I = \frac{V_{in}}{L}$$

$$V_{in} \rightarrow V_2 \text{ or } V_1$$

$$\tau = \frac{L}{R} \begin{matrix} \text{time} \\ \text{constant} \end{matrix}$$

— if $0 < t < \frac{T}{2}$, $I(0) = 0 = I_0$, $V_{in} = V_2$

$$I(t) = \underset{0}{I_0} e^{-\frac{t}{\tau}} + \frac{V_2}{R} \left[1 - e^{-\frac{t}{\tau}} \right] = \frac{V_2}{R} \left[1 - e^{-\frac{t}{\tau}} \right]$$

$$V_R(t) = RI(t) = R \underset{0}{I_0} e^{-\frac{t}{\tau}} + V_2 \left[1 - e^{-\frac{t}{\tau}} \right] = V_2 \left[1 - e^{-\frac{t}{\tau}} \right]$$

$$V_L = L \frac{dI_L}{dt} = L \frac{V_2}{R} \frac{d}{dt} \left[1 - e^{-\frac{t}{\tau}} \right] = \frac{V_2 L}{R} \frac{1}{\tau} e^{-\frac{t}{\tau}} = V_2 e^{-\frac{t}{\tau}}$$

$$I\left(\frac{T}{2}\right) = \frac{V_2}{R} \left[1 - e^{-\frac{T}{2\tau}} \right]$$

— if $\frac{T}{2} < t < T$, $I_0 = I\left(\frac{T}{2}\right) = \frac{V_2}{R} \left[1 - e^{-\frac{T}{2\tau}} \right]$, $V_{in} = V_1$

$$I(t) = \underset{0}{I_0} e^{-\frac{(t-\frac{T}{2})}{\tau}} + \frac{V_1}{R} \left[1 - e^{-\frac{(t-\frac{T}{2})}{\tau}} \right]$$

$$V_R(t) = RI(t) = R \underset{0}{I_0} e^{-\frac{(t-\frac{T}{2})}{\tau}} + \cancel{V_1} \left[1 - e^{-\frac{(t-\frac{T}{2})}{\tau}} \right]$$

$$V_L(t) = L \frac{dI(t)}{dt} = L \left[\underset{0}{I_0} \left(-\frac{1}{\tau} \right) e^{-\frac{(t-\frac{T}{2})}{\tau}} \right] + L \frac{V_1}{R} \left(\frac{1}{\tau} \right) e^{-\frac{(t-\frac{T}{2})}{\tau}}$$

$$= -R \underset{0}{I_0} e^{-\frac{(t-\frac{T}{2})}{\tau}} + V_1 e^{-\frac{(t-\frac{T}{2})}{\tau}}$$

— if $T < t < \frac{3T}{2}$, $I_0 = I(T)$, $V_{in} = V_2$

$$I(t) = \underset{0}{I_0} e^{-\frac{(t-T)}{\tau}} + \frac{V_2}{R} \left[1 - e^{-\frac{(t-T)}{\tau}} \right]$$

$$V_R(t) = R I_0 = R \underset{0}{I_0} e^{-\frac{(t-T)}{\tau}} + \frac{V_2}{R} \left[1 - e^{-\frac{(t-T)}{\tau}} \right]$$

(5)

$$V_L = L \frac{dI}{dt} = -I_0 R e^{-\frac{(t-T)}{\tau}} + V_2 \left[\cancel{e^{-\frac{(t-T)}{\tau}}} e^{-\frac{(t-T)}{\tau}} \right]$$

and so on for other time intervals

Hence if $T \gg \tau$ (the period of the input waveform is much greater than the time constant of RL circuit $\tau = \frac{L}{R}$)

then For $0 < t < \frac{T}{2}$, $V_{in}(t) = V_2$, $I_0 = 0$

$$V_R(t) = V_2 \left[1 - e^{-\frac{t}{\tau}} \right], \quad V_L(t) = V_2 e^{-\frac{t}{\tau}} \quad \text{and} \quad I\left(\frac{T}{2}\right) \approx \frac{V_2}{R} = I_0$$

For $\frac{T}{2} < t < T$, $V_{in}(t) = V_1$, $I_0 = \frac{V_2}{R} //$

$$V_R(t) = V_2 e^{-\frac{(t-\frac{T}{2})}{\tau}} + V_1 \left[1 - e^{-\frac{(t-\frac{T}{2})}{\tau}} \right]$$

$$V_L(t) = -V_2 e^{-\frac{(t-\frac{T}{2})}{\tau}} + V_1 e^{-\frac{(t-\frac{T}{2})}{\tau}} = [V_1 - V_2] e^{-\frac{(t-\frac{T}{2})}{\tau}}$$

For $T < t < \frac{3T}{2}$, $V_{in}(t) = V_2$, $I_0 = I(t) = \frac{V_1}{R} //$

$$V_R(t) = V_1 e^{-\frac{(t-T)}{\tau}} + V_2 \left[1 - e^{-\frac{(t-T)}{\tau}} \right]$$




$$V_L(t) = -V_1 e^{-\frac{(t-T)}{\tau}} + V_2 e^{-\frac{(t-T)}{\tau}} = [V_2 - V_1] e^{-\frac{(t-T)}{\tau}}$$

* when $f = 2 \text{ kHz}$, $R = 3.3 \text{ k}\Omega$, $L = 0.1 \text{ H}$, $\tau = \frac{L}{R} = \frac{0.1}{3.3 \times 10^3} = 3.03 \times 10^{-5} \text{ sec} = 30.3 \mu\text{sec}$

$$T = \frac{1}{2000} = 0.5 \text{ msec} = 500 \mu\text{sec}$$

$$T \gg \tau //$$

$V_{in}(t) (V_{o1})$

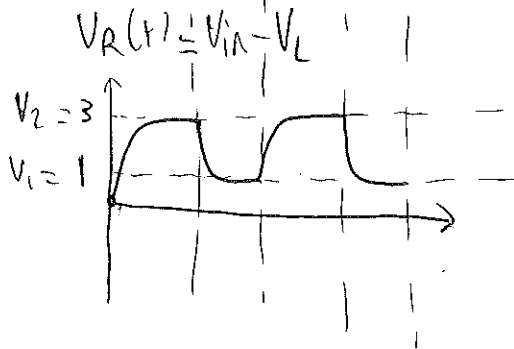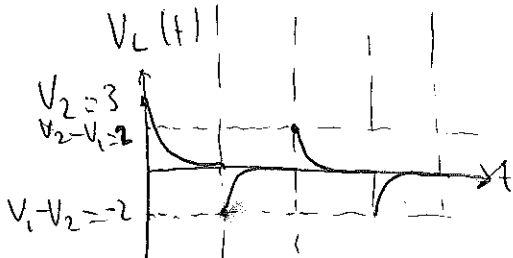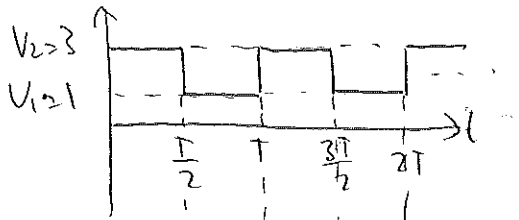

(6)

**When $f = 2\text{kHz}$ $R = 1.8\text{k}\Omega$

$$L = 0.1\text{H}, \tau = \frac{L}{R} = \frac{0.1}{1.8\text{k}\Omega} = 55.5\text{Msec}$$

$T \gg \tau$

where

$$T = \frac{1}{2000} = 500\text{Msec}$$

Both * and ** are very fast RL circuits but * is faster. Hence V_L and V_R plots will be similar while * reaches to steady-state situation more rapidly.

*** $f = 10\text{kHz}$ [a very rapid input waveform]


$$T = \frac{1}{10\text{kHz}} = 100\text{Ms}$$

$$R = 3.3$$



$$L = 0.1$$

$$\tau = \frac{L}{R} = 30.3\text{Ms}$$


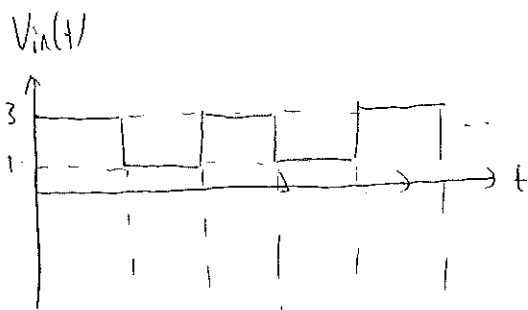
For this circuit we can say that T and τ values are close to each other. Hence the inductor will always have some potential for positive and negative cycles of the input, it will never reach to steady-state short circuit position



(7)

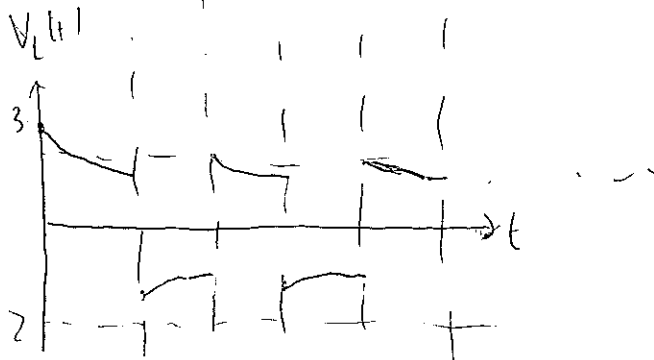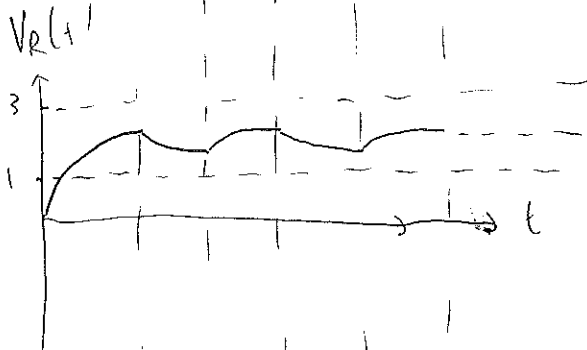

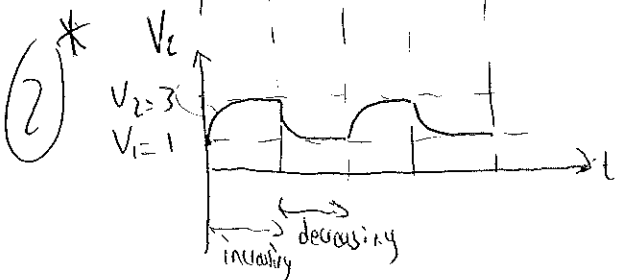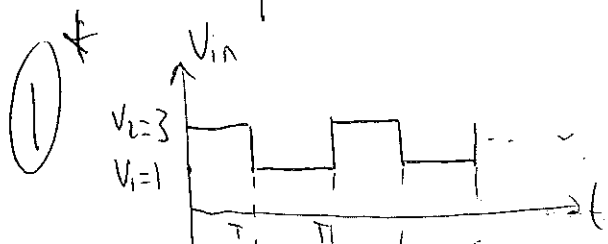(c) The voltage waveform for RC circuit (Voltage over capacitor, V_C) is as follows (if the RC circuit is fast, or τ is small)




The V_C waveform can be written as

$$V_C(t) = V_2 + (V_A - V_C) e^{-\frac{t}{\tau}} \quad \left(\text{for increasing mode} \right)$$

$$V_C(t) = V_1 + (V_C - V_1) e^{-\frac{t}{\tau}} \quad \left(\text{for decreasing mode} \right)$$

Assuming that we see in oscilloscope in AC mode (for V_c) (8)

(3)* $V_c(t)$ [in AC mode]

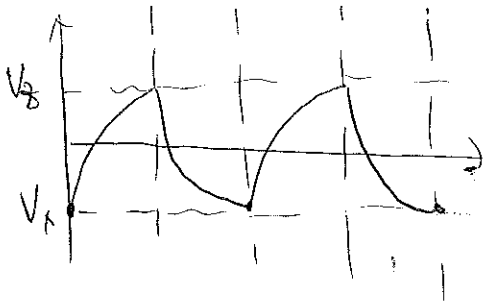


$$\left. \begin{aligned} V_A &= V_x + V_y \\ V_B &= V_z + V_y \end{aligned} \right\} \begin{array}{l} \text{where } V_y \text{ is} \\ \text{the (DC) component} \\ \text{in } V_c. \end{array}$$

Then taking a point on graph (2)* in the increasing mode

$$\left[V_c(t) = V_2 + (V_A - V_2) e^{-\frac{t}{\tau}} \right] \text{ we can find } \tau \text{ directly,}$$

for RL circuit, the voltage waveform " V_L " is as follows

$V_L(t)$ [in DC mode]

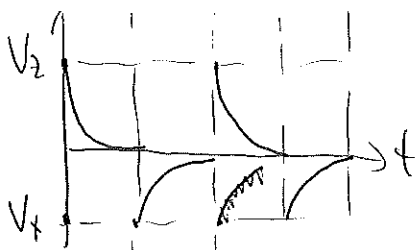

Generally the DC level over the inductor decreases very rapidly to zero so $V_y = 0$

$$V_L(t) = K_1 e^{-\frac{t}{\tau}} \quad \text{[for increasing mode]}$$

$$V_L(t) = K_2 e^{-\frac{t}{\tau}} \quad \text{[for decreasing mode]}$$

$$K_2 < 0 < K_1$$

$$K_1 = V_2 + V_y \approx V_2$$

$$K_2 = V_1 + V_y \approx V_1$$

Then taking a point for $V_L(t)$ graph in the increasing mode, we can find τ directly