

Q-1- $r(t)$ is the ramp function. Draw $k(t)=r(t)+r(t-1)-2r(t-2)-2r(t-3)+r(t-4)+r(t-5)$ with full details. (20 points)


Q-2- The differential equation governing the circuit variable $I_L(t)$ is given by

$$\frac{d^4 I_L}{dt^4} - I_L = \sin(2t)$$

Find the particular solution of this differential equation. (30 points)

Q-3- Design a second order circuit with two resistors and two capacitors and a voltage source V_s which has the following state space representation. (50 points)
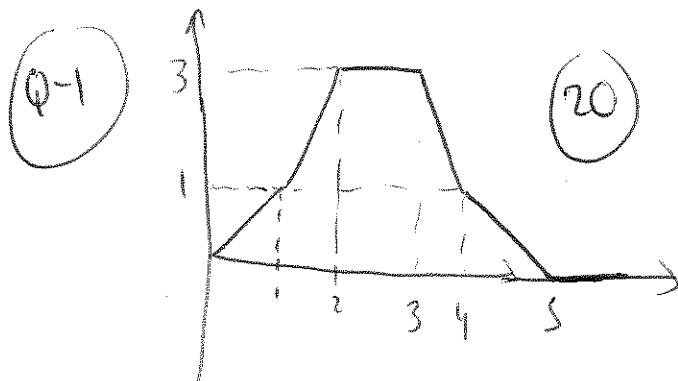
$$k(t) \begin{bmatrix} \frac{dV_{C_1}}{dt} \\ \frac{dV_{C_2}}{dt} \end{bmatrix} = \begin{bmatrix} -2 & -1 \\ 0.5 & -0.5 \end{bmatrix} \begin{bmatrix} V_{C_1} \\ V_{C_2} \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} V_s$$



(Q-2) $\frac{d^4 I_L}{dt^4} - I_L = \sin(2t)$ characteristic equation $s^4 - 1 = 0$
 $(s^2 + 1)(s^2 - 1)$

$$s_1 = j \quad s_2 = -j \quad s_3 = 1 \quad s_4 = -1 \quad (5)$$

$$s_1 \neq j\omega \quad \omega = 2 \frac{\text{rad}}{\text{sec}} \quad \text{hence } I_{lp} = K_1 \sin(2t) + K_2 \cos(2t)$$

$$s_3 \neq j\omega \quad (3)$$

$$s_4 = j\omega$$

$$\frac{dI_{lp}}{dt} = 2K_1 \cos(2t) - 2K_2 \sin(2t) \quad (4)$$

$$\frac{d^2 I_{lp}}{dt^2} = -4K_1 \sin(2t) - 4K_2 \cos(2t) \quad (5)$$

$$\frac{d^3 I_{cp}}{dt^3} = -8K_1 \cos(2t) + 8K_2 \sin(2t) \quad (4)$$

$$\frac{d^4 I_{cp}}{dt^4} = 16K_1 \sin(2t) + 16K_2 \cos(2t) \quad (5)$$

$$\frac{d^4 I_{cp}}{dt^4} - I_{cp} = \sin(2t) \quad 16K_1 \sin(2t) + 16K_2 \cos(2t) - [K_1 \sin(2t) + K_2 \cos(2t)] = \sin(2t)$$



(5) $15K_1 \sin(2t) + 15K_2 \cos(2t) = \sin(2t)$

(0)


$$K_2 = 0 \quad K_1 = \frac{1}{15}$$

$$I_{cp} = \frac{1}{15} \sin(2t)$$

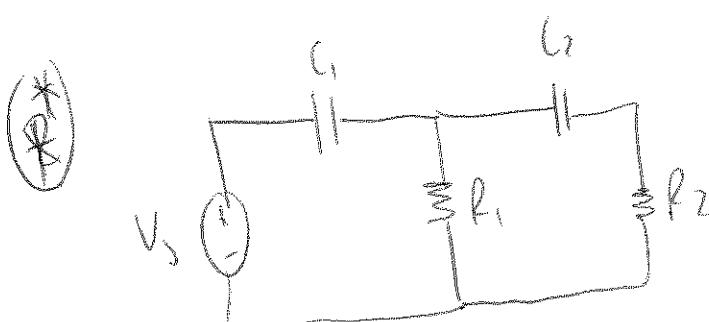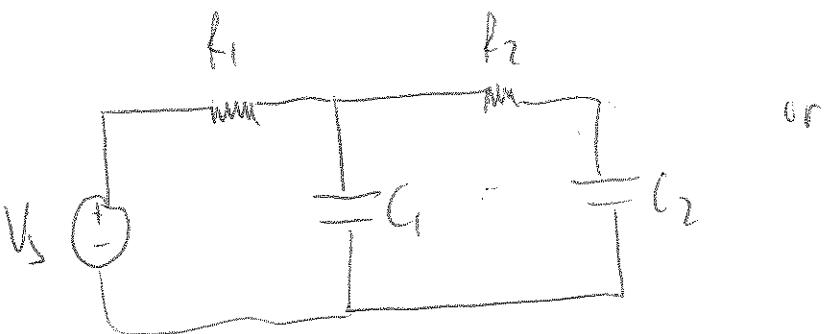Q3 - We have a voltage source so the circuit configuration can be



V_{C2} *

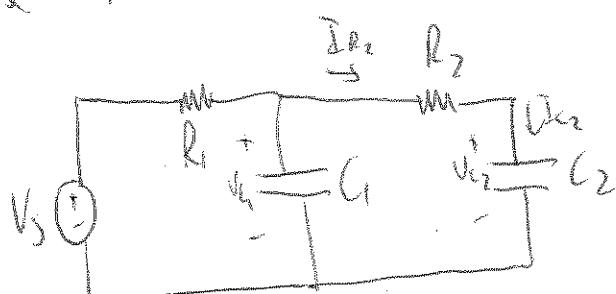

$$V_s = V_{R_1} + V_{C_1}$$

$$I_{C_2} = I_{C_1} = C_2 \frac{dV_{C_2}}{dt}$$

$$V_{C_1} = V_{R_2} + V_{C_2}$$

$$V_{C_1} = R_2 \left(C_2 \frac{dV_{C_2}}{dt} \right) + V_{C_2}$$

$$\frac{dV_{C_2}}{dt} = \frac{1}{R_1 C_2} V_{C_1} - \frac{1}{R_2 C_2} V_{C_2}$$

Hence $\frac{1}{R_2 C_2} = 0.5$ // $V_s = V_{R_1} + V_{C_1}$ $V_s = R_1 [I_{C_1} + I_{C_2}] + V_{C_1}$

$$V_s = R_1 \left[C_1 \frac{dV_{C_1}}{dt} + C_2 \frac{dV_{C_2}}{dt} \right] + V_{C_1}$$

$$V_s = R_1 \left[C_1 \frac{dV_{C_1}}{dt} + C_2 \left(\frac{V_{C_1}}{R_1 C_2} - \frac{V_{C_2}}{R_2 C_2} \right) \right] + V_{C_1}$$

$$V_s = R_1 \left(\frac{dV_{C_1}}{dt} + \left(\frac{R_1}{C_2} - \frac{R_2}{C_2} \right) V_{C_1} \right) + \frac{R_1}{C_2} V_{C_1}$$

$$\frac{dV_{C_1}}{dt} = \frac{V_s}{R_1 C_1} + \frac{1}{C_2} V_{C_2} - \frac{R_1 + R_2}{R_1 R_2} V_{C_1}$$

Hence

$$\frac{1}{R_1 C_1} = 1$$

$$\frac{1}{G_1 R_2} = 1$$

$$\frac{R_1 + R_2}{R_1 R_2} = 2$$

$$\frac{1}{L C_2} = 0.5$$

$$R_1 = 1 \quad R_2 = 1 \Rightarrow \begin{matrix} \text{All conditions} \\ \text{are satisfied} \end{matrix}$$

$$C_1 = 1 \quad G_2 = 2$$

Hence circuit

