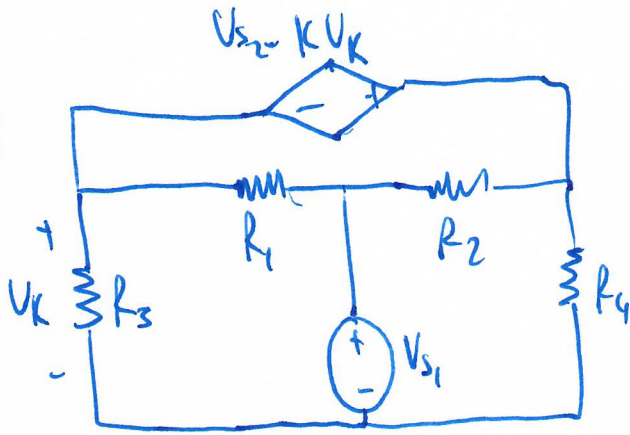


Q1




$R_1 = R_2 = R_3 = R_4 = 1 \Omega$

$K = 5$

$V_{s1} = 10 \text{ Volt}$

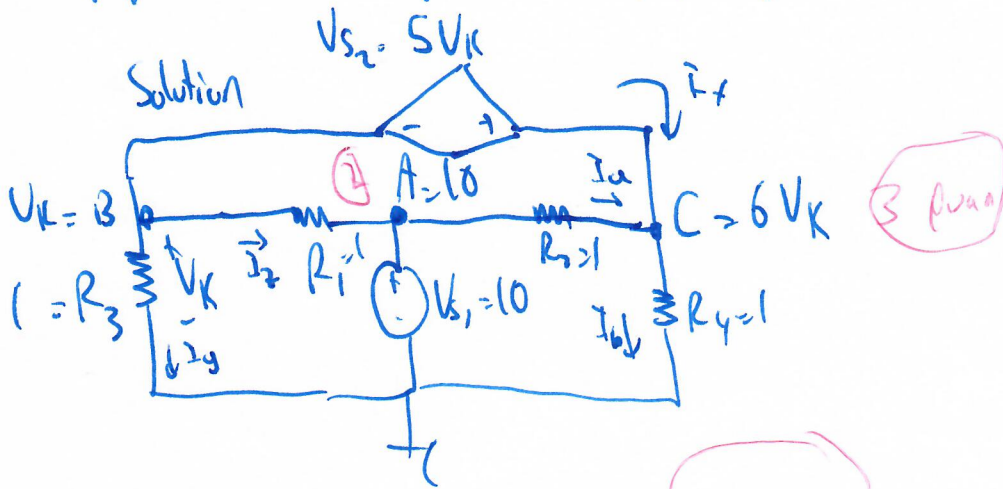What is the power dissipated over V_K , what is the power of V_{s2}



$I_x = -(I_y + I_z) = I_b - I_a$

$-\left(\frac{V_K}{1} + \frac{V_K - A}{1}\right) = \frac{6V_K}{1} \Rightarrow \frac{A - 6V_K}{1}$

$-V_K - V_K + A = 12V_K - A$


$2A = 14V_K$

$20 = 14V_K \Rightarrow V_K = \frac{20}{14} = \frac{10}{7} \text{ Volt}$

$I_x = I_b - I_a = \frac{6V_K}{1} - \frac{10 - 6V_K}{1} = 6 \times \frac{10}{7} - \frac{10 - 6 \times \frac{10}{7}}{1} = \frac{12 \times 10}{7} - 10 = \frac{50}{7} \text{ Ampere}$

$V_{s2} = 5V_K = 5 \times \frac{10}{7} = \frac{50}{7}$

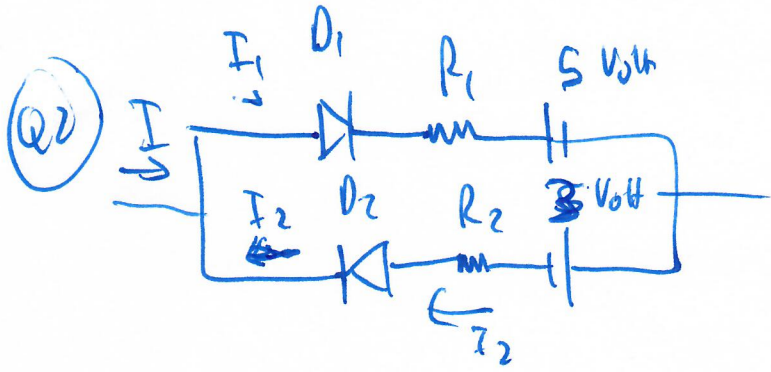$P_{V_{s2}} = V_{s2} \times I_x = \frac{2500}{49} \text{ Watt}$



$$R_1 = 1 \Omega$$

$$R_2 = 1 \Omega$$


$$I = I_1 - I_2$$

$$I_1 = \frac{V - 5}{R_1} \quad I_2 = \frac{-3 - V}{R_2}$$

if $V > 5$ $I = I_1 = \frac{V - 5}{1}$ (3)

if $-3 < V < 5$ $I = 0$ (4)

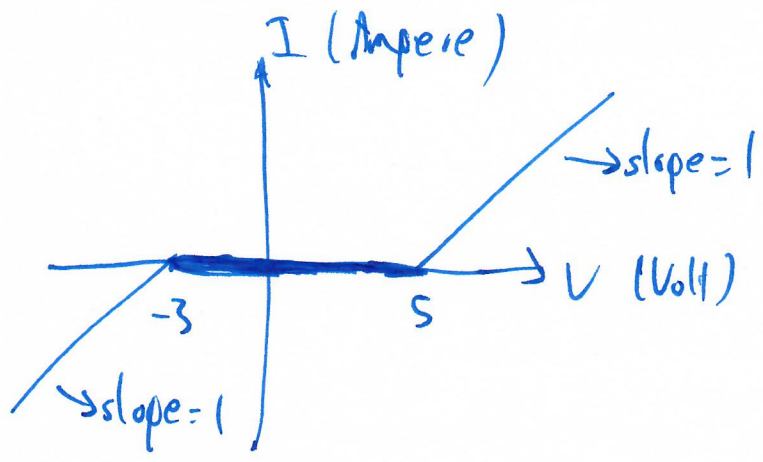if $V < -3$ $I = -I_2 = \frac{V + 3}{1}$ (3)




5 point

Q2

Q3

(a)

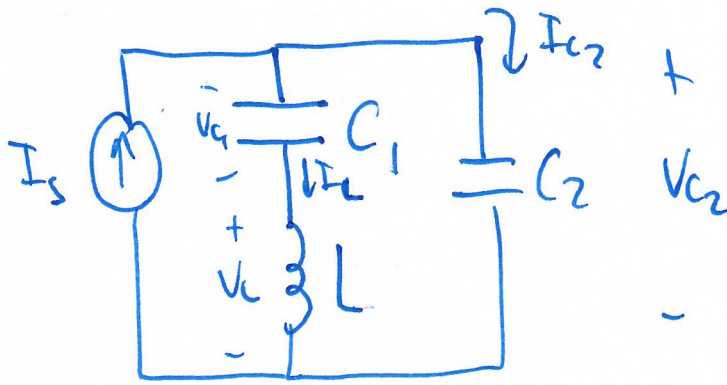

1 puan

1 puan

$$I_s = I_L + I_{C2}$$

$$I_s = I_L + C_2 \frac{dV_{C2}}{dt}$$

$$I_L = I_{C1} = C_1 \frac{dV_{C1}}{dt}$$

$$\frac{dV_{C2}}{dt} = \frac{I_s}{C_2} - \frac{I_L}{C_2}$$

1 puan

$$\frac{dV_{C1}}{dt} = \frac{I_L}{C_1}$$

$$V_{C1} + V_L = V_{C2}$$

1 puan

$$V_{C2} = L \frac{dI_L}{dt} + V_{C1}$$

$$\frac{dI_L}{dt} = \frac{V_{C2}}{L} - \frac{V_{C1}}{L}$$

1 puan

3 puan

$$\begin{bmatrix} \frac{dV_{C1}}{dt} \\ \frac{dV_{C2}}{dt} \\ \frac{dI_L}{dt} \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 0 & \frac{1}{C_1} \\ 0 & 0 & -\frac{1}{C_2} \\ -\frac{1}{L} & \frac{1}{L} & 0 \end{bmatrix}}_A \begin{bmatrix} V_{C1} \\ V_{C2} \\ I_L \end{bmatrix} + \underbrace{\begin{bmatrix} 0 \\ \frac{1}{C_2} I_s \\ 0 \end{bmatrix}}_B$$

(b) $C_1 = C_2 = 1 \text{ F}$

$L = 2 \text{ Henry}$

$$A = \begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & -1 \\ -\frac{1}{2} & \frac{1}{2} & 0 \end{bmatrix}$$

$$(sI - A) = \begin{bmatrix} s & 0 & -1 \\ 0 & s & 1 \\ +\frac{1}{2} & -\frac{1}{2} & s \end{bmatrix}$$

2 puan

$$\det(sI - A) = (-1)^{1+1} s \begin{vmatrix} s & 1 \\ -\frac{1}{2} & s \end{vmatrix} +$$

$$(-1)^{1+2} 0 \begin{vmatrix} 0 & 1 \\ -\frac{1}{2} & s \end{vmatrix} +$$

$$(-1)^{1+3} (-1) \begin{vmatrix} 0 & s \\ +\frac{1}{2} & -\frac{1}{2} \end{vmatrix}$$

4 puan

$$\det(sI - A) = s \left(s^2 + \frac{1}{2} \right) + 0 + (-1) \left(0 - \left(+\frac{1}{2} \right) s \right)$$

$$= s \left(s^2 - \frac{1}{2} \right) + \left(+\frac{s}{2} \right) = s \left(s^2 + \frac{1}{2} \right) + \frac{s}{2}$$

$$= s^3 + \frac{s}{2} + \frac{s}{2} = s^3 + s = s(s^2 + 1)$$

$s_1 = 0$ $s_{2,3} = \pm j$

2 puan

birdisat 10

(c) $\frac{dV_{C1}}{dt} = I_C$ $\frac{dV_{C2}}{dt} = I_S - I_C$ $\frac{dI_C}{dt} = \frac{V_{C2}}{2} - \frac{V_{C1}}{2}$

$$\frac{d^2 V_{C1}}{dt^2} = \frac{dI_C}{dt} \rightarrow \frac{d^3 V_{C1}}{dt^3} = \frac{d^2 I_C}{dt^2} = \frac{d}{dt} \left[\frac{dI_C}{dt} \right] = \frac{d}{dt} \left[\frac{V_{C2}}{2} - \frac{V_{C1}}{2} \right]$$

$$\frac{d^3 V_{C1}}{dt^3} = \frac{1}{2} \frac{dV_{C2}}{dt} - \frac{1}{2} \frac{dV_{C1}}{dt} \rightarrow \frac{d^3 V_{C1}}{dt^3} + \frac{1}{2} \frac{dV_{C1}}{dt} = +\frac{1}{2} (I_S - I_C)$$

$$\frac{d^3 V_{C1}}{dt^3} + \frac{1}{2} \frac{dV_{C1}}{dt} = +\frac{1}{2} I_S - \frac{1}{2} I_C$$

$$\frac{d^3 V_{C1}}{dt^3} + \frac{dV_{C1}}{dt} = +\frac{1}{2} I_s \rightarrow 4 \text{ puan}$$

Q4 (2) $\ddot{x} + \dot{x} = 5t \quad x(0) = 0 \quad \dot{x}(0) = 1 \quad \ddot{x}(0) = 1$

(a) char equation $s^3 + s = 0$ (2)

(b) natural frequencies $s(s^2 + 1) = 0 \quad s_1 = 0 \quad s_{2,3} = \pm j$ (2)

(c) $x_h = K_1 + K_2 \cos(t) + K_3 \sin(t)$ (2)

(d) $x_p = Mt + N$ (2)

$$\frac{d^3}{dt^3} x_p + \frac{d}{dt} x_p = 5t$$

hence

$$\frac{d^3}{dt^3} Mt^2 + \frac{d}{dt} Mt^2 = 5t$$

$$0 + M = 5t$$

not possible

$$x_p = Mt^2$$

$$0 + 2Mt = 5t \quad M = \frac{5}{2}$$

(e) $x = K_1 + K_2 \cos(t) + K_3 \sin(t) + \frac{5}{2} t^2$

$$x(0) = K_1 + K_2 = 1$$

$$\dot{x} = -K_2 \sin(t) + K_3 \cos(t) + 5t$$

$$\dot{x}(0) = K_3 = 1$$

$$\ddot{x} = -K_2 \cos(t) - K_3 \sin(t) + 5$$

$$\ddot{x}(0) = -K_2 + 5 = 1 \quad K_2 = 4$$

$$x(t) = -1 + 4 \cos(t) + \sin(t) + \frac{5}{2} t^2$$

8 puan

$$K_3 = 1$$


$$K_2 = 4$$

$$K_1 = 1 - K_2$$

$$K_1 = 1 - 4 = -3$$

(Q5)


$V_{s1} =$

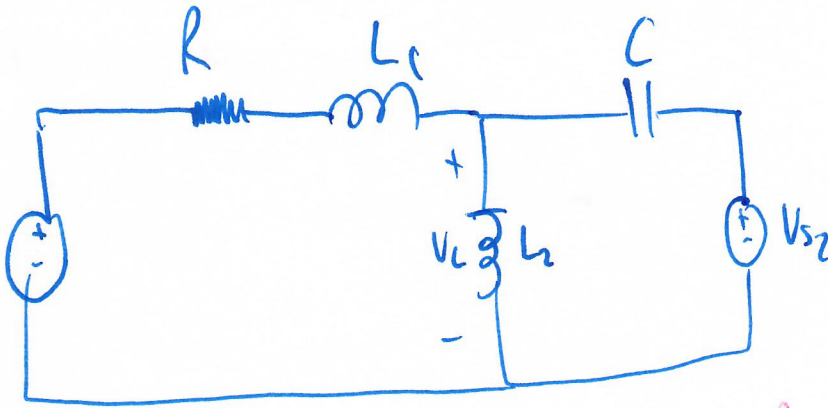

$V_{s1} = 2 \cos(t) \rightarrow \omega = 1 \frac{\text{rad}}{\text{sec}}$
 $V_{s2} = 3 \cos(t + 90^\circ)$
 $\bar{V}_{s1} = 2 \angle 0^\circ \text{ V}$
 $\bar{V}_{s2} = 3 e^{-90^\circ j} = -3j \text{ V}$

$X_{L1} = j\omega L_1$ $X_{L2} = j\omega L_2$ $X_C = \frac{1}{j\omega C} = -j$

phasor

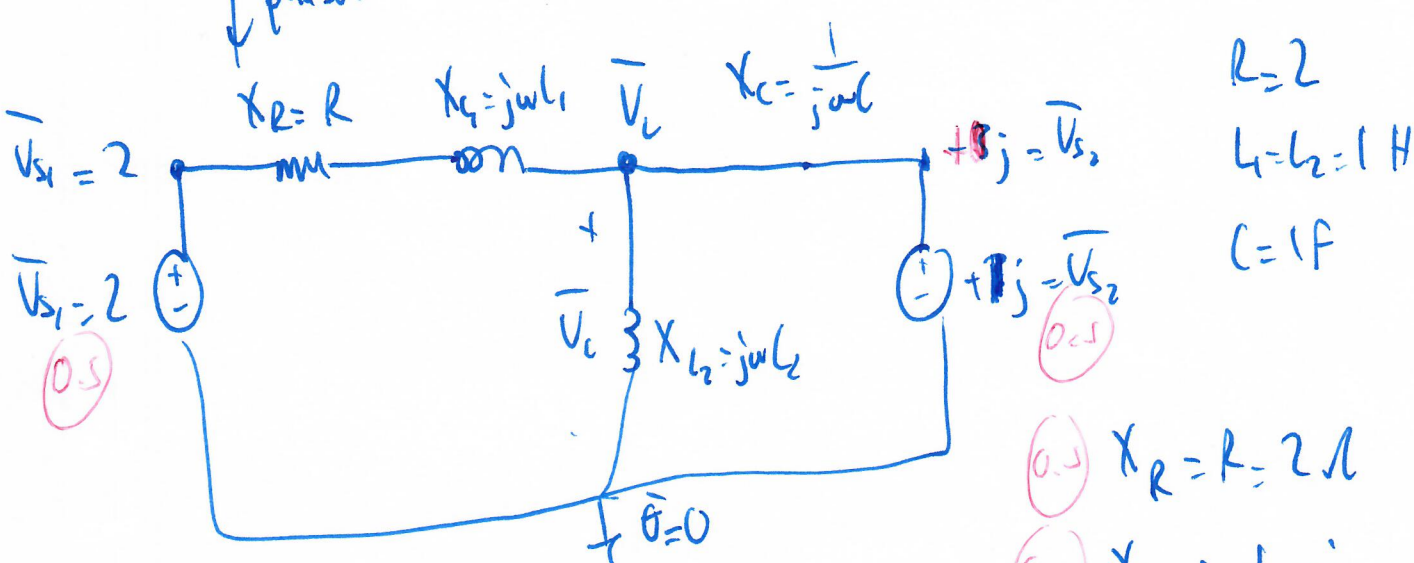

$$\frac{\bar{V}_{s1} - \bar{V}_c}{R + j\omega L_1} + \frac{\bar{V}_{s2} - \bar{V}_c}{\frac{1}{j\omega C}} = \frac{\bar{V}_c}{j\omega L_2}$$

- (0.5) $X_R = R = 2 \Omega$
- (0.5) $X_{L1} = j\omega L_1 = j$
- (0.5) $X_{L2} = j\omega L_2 = j$
- (0.5) $X_C = \frac{1}{j\omega C} = -j$

$$\frac{2 - \bar{V}_c}{2 + j} + \frac{j - \bar{V}_c}{-j} = \frac{\bar{V}_c}{j} \quad (4)$$


$$\frac{2 - \bar{V}_c}{2 + j} + \frac{\bar{V}_c}{j} = \frac{\bar{V}_c}{j}$$

$$\frac{2 - \bar{V}_c}{2 + j} = 0$$


$2 - \bar{V}_c = 0 \Rightarrow \bar{V}_c = 2$
 $V_c = 2 \cos(t) \text{ Volt}$

(1) $V_{s1} = \cos(t - 90^\circ)$
 $V_{s2} = \sin(t) \text{ Volt}$
 $V_c = 2 \cos(t) \text{ Volt}$

$$\bar{V}_L = \dots j$$

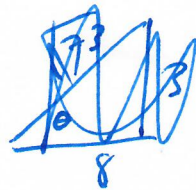

ω
 v

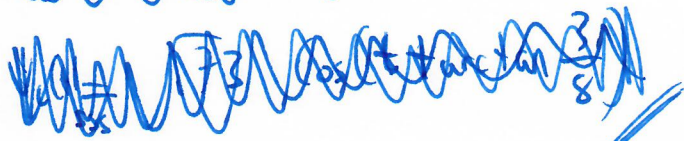


$$\bar{V}_L = -j = e^{-j90}$$

$$V_L(t) = \cos(t - 90^\circ)$$

$$V_{L_{SS}} = \sin(t) \text{ Volt}$$

Q6

R=2 C=1F L=1H

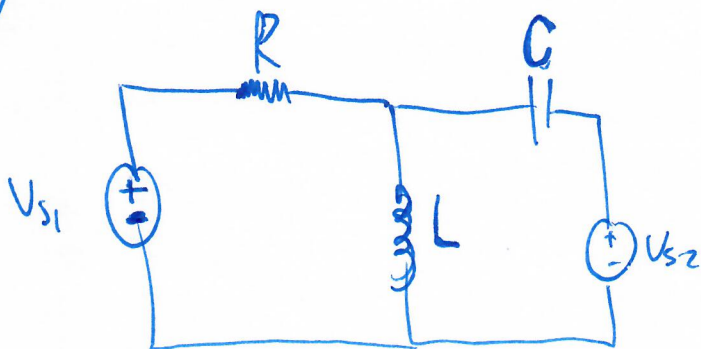

$$V_{s1} = \cos(t) \text{ Volt}$$



$$V_{s2} = \sin(2t) \text{ Volt}$$

$$X_R = R = 2 \Omega$$

$$X_L = j\omega L = j \Omega$$

$$X_C = \frac{1}{j\omega C} = -j \Omega$$

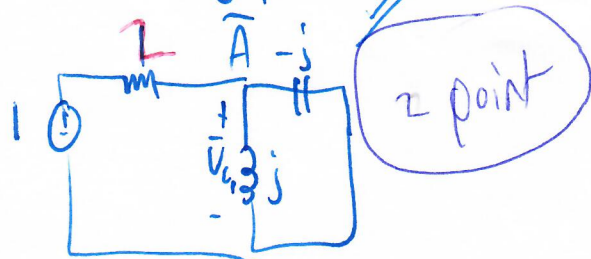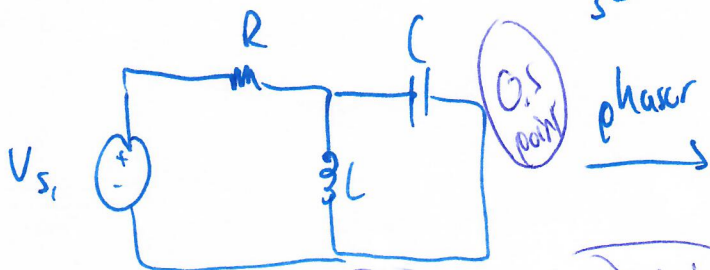Kill V_{s2} ($V_{s1} = \cos(t)$ Volt)
 $\omega_1 = 1 \text{ rad/s}$



2 point

0.5 point

$$\frac{1-A}{2} = \frac{A}{j} + \frac{A}{-j}$$

$$A=1$$


$$\bar{V}_L = A=1$$

$$V_L = \cos(t)$$


1 point

Kill V_{s1} ($V_{s2} = \sin(2t)$)

$\omega = 2 \text{ rad/sec}$

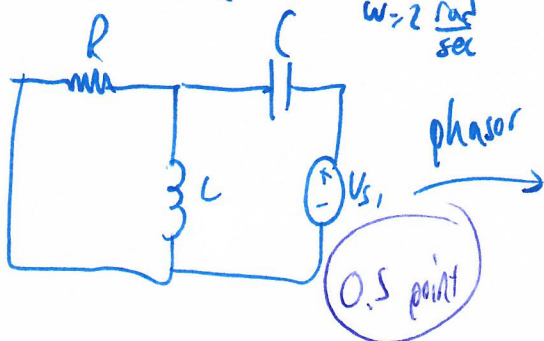
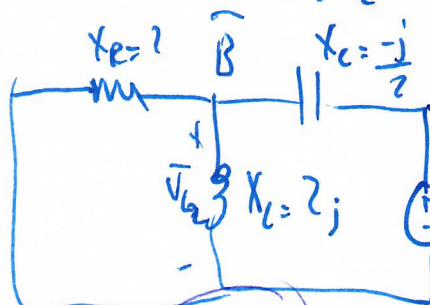
$$X_R = 2 \Omega = R \quad X_C = j\omega C = 2j \quad X_C = \frac{1}{j\omega_2 C} = \frac{1}{j \cdot 2 \cdot 1} = \frac{1}{j2}$$



2 point

$$\bar{B} \rightarrow \bar{V}_{L_2}$$

$$\frac{\bar{V}_{L_1} - \bar{B}}{X_C} = \frac{\bar{B}}{X_C} + \frac{\bar{B}}{X_R}$$

$$\frac{-j - \bar{B}}{\frac{1}{2j}} = \frac{\bar{B}}{2j} + \frac{\bar{B}}{2}$$

2 point

$$\downarrow$$

$$+ 2 - 2j \bar{B} = \frac{\bar{B} (1 + j)}{2j}$$

$$4j + 4\bar{B} = \bar{B} + \bar{B}j$$

$$4j = \bar{B}(j - 3)$$


~~$$4 - 4j \bar{B} = \bar{B} + \bar{B}j$$~~
~~$$4 = \bar{B} + 5\bar{B}j$$~~

~~$$\frac{4}{1 + 5j} = \bar{B}$$~~

$$\bar{B} = \frac{4j}{j - 3}$$
~~$$\frac{4(1 - 5j)}{26} = \bar{B}$$~~
~~$$\frac{4}{\sqrt{26}} \left(\frac{1}{\sqrt{26}} - \frac{5j}{\sqrt{26}} \right) = \bar{B}$$~~

$$\bar{B} = \frac{-4j}{3 - j} = \frac{-4j(3 + j)}{10} = \frac{4 - 12j}{10} = \frac{4}{10}(1 - 3j) = \frac{4}{10} \left(\frac{1 - 3j}{\sqrt{10}} \right) = \bar{B}$$

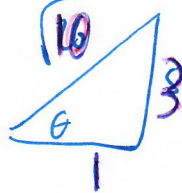~~$$\bar{B} = \frac{4}{\sqrt{26}} (\cos \theta - j \sin \theta)$$~~



$$\theta = \arctan \frac{3}{1}$$

$$\bar{B} = \frac{4}{\sqrt{10}} e^{-j\theta}$$

$$\rightarrow B = V_{L_2}(t) = \frac{4}{\sqrt{10}} \cos(2t - \arctan \frac{3}{1})$$

0.5 point

1 point

1 point

$$V_L(t) = V_{L_1} + V_{L_2}$$

$$V_L(t) = \cos(t) + \frac{4}{\sqrt{10}} \cos(2t - \arctan \frac{3}{1}) \text{ Volt}$$

1 point