
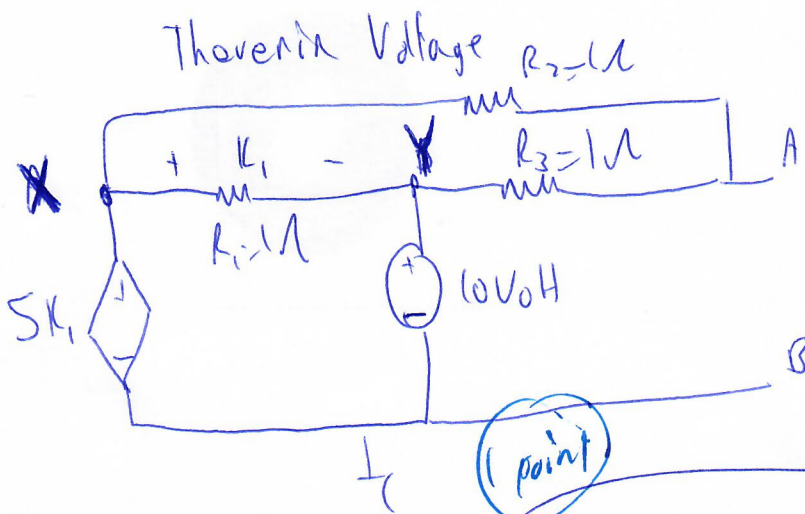


Q1

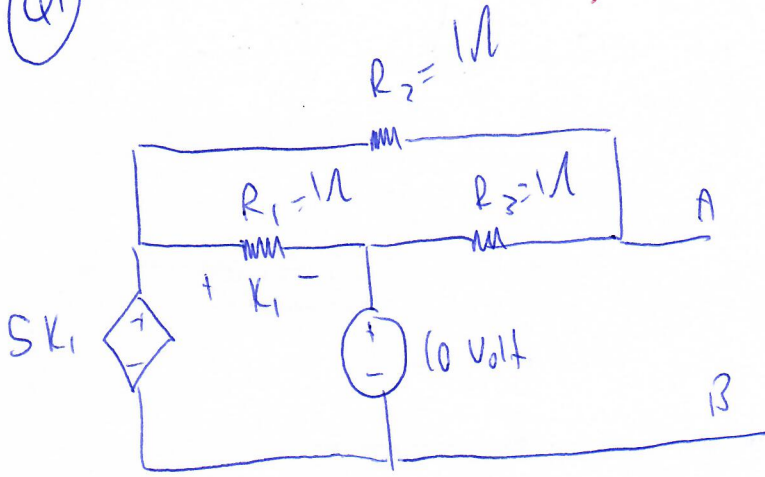

1 point

$V = 10 \text{ Volt}$ $X = SK_1$ $K_1 = X - Y \rightarrow K_1 = SK_1 - Y$
 $Y = 4K_1$ (2 point)


~~scribble~~ $\frac{X - A}{R_2} = \frac{A - Y}{R_3}$ (3 point)

$Y = 10 = 4K_1$
 (point) $K_1 = 2.5 \text{ Volt}$
 $X = 12.5 \text{ Volt}$

$X + Y = 2A$
 $12.5 + 10 = 2A$

$A = \frac{22.5}{2} = 11.25$ (2 point)

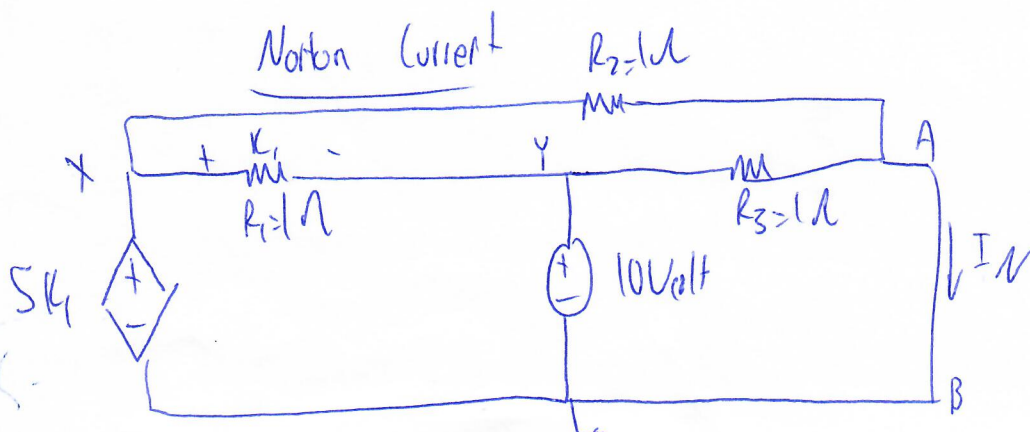$A = 11.25 \text{ Volt}$
 $A - B = V_{TH} = 11.25 \text{ Volt}$



1 point

$$V_1 = 10 \text{ Volt} \quad A = B = 0 \text{ Volt}$$

3 point

$$X = 5k_1 \quad X - Y = k_1 \quad 5k_1 - Y = k_1 \quad Y = 4k_1 = 10 \quad k_1 = 2.5$$

$$X = 12.5 \quad Y = 10$$

4 point

1 point

$$I_N = \frac{Y - A}{R_3} + \frac{X - A}{R_2} = \frac{10 - 0}{1} + \frac{12.5 - 0}{1} = 22.5 \text{ Ampere}$$

$$V_{TH} = 11.25 \text{ Volt}$$


$$R_{TH} = \frac{11.25}{22.5} = 0.5 \Omega$$

$$I_N = 22.5 \text{ Ampere}$$


1 point

$$R_{TH} = 0.5 \Omega$$

$$11.25 = V_{TH} \text{ Volt}$$

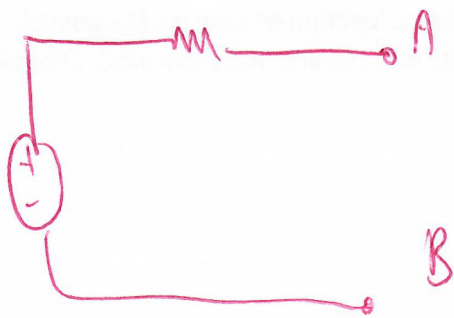

(Q2)

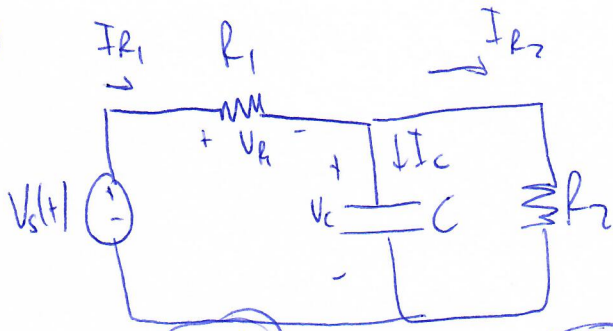

$V_s = V_{R_1} + V_C$ (2 point)

$V_C = V_{R_2}$ (2 point)

$V_s = I_{R_1} R_1 + V_C$ (2 point)

$V_s = (I_C + I_{R_2}) R_1 + V_C$ (2 point)

$V_s = \left[C \frac{dV_C}{dt} + \frac{V_C}{R_2} \right] R_1 + V_C$ (2 point)


$V_s = C R_1 \frac{dV_C}{dt} + \frac{R_1}{R_2} V_C + V_C \quad \left(R_1 \frac{dV_C}{dt} + \left[\frac{R_1 R_2}{R_2} \right] V_C = V_s \right)$

$\frac{dV_C}{dt} + \frac{(R_1 R_2)}{C R_1 R_2} V_C = \frac{1}{C R_1} V_s$

5 point

(Q3)

$y(t) = r(t) - r(t-1) + r(t-2) + u(t-2)$

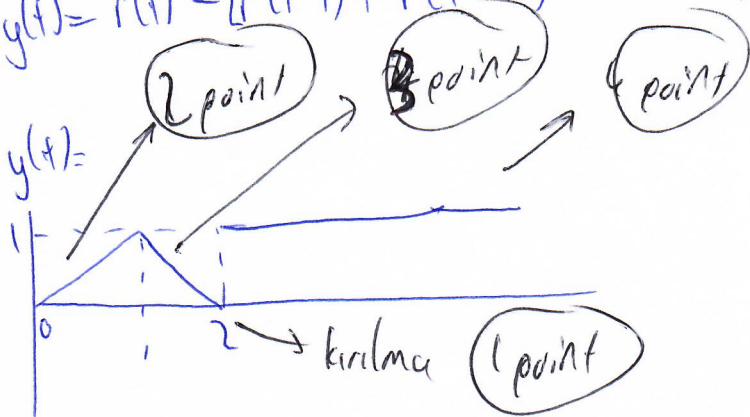


10 point

(Q4)

$\delta(t) f(t) = \delta(t) f(0) = \delta(t) \cdot 1 = \delta(t)$
 $f(t) = 5t^2 + 1$
 $f(0) = 1$

3 point

Q5

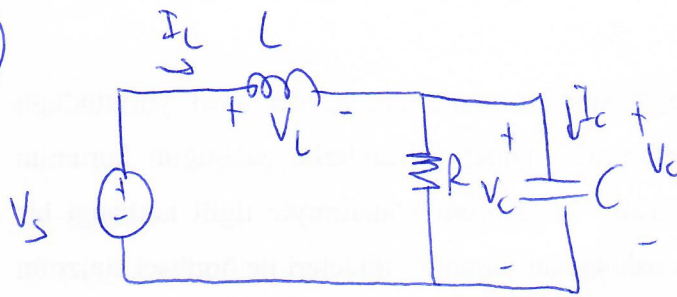

1 point

a

$$V_s = V_L + V_c$$

2 point

$$V_s = L \frac{dI_c}{dt} + V_c$$

2 point

$$\frac{dI_c}{dt} = \frac{V_s}{L} - \frac{V_c}{L}$$

$$I_L = I_R + I_c$$

2 point

$$I_L = \frac{V_c}{R} + C \frac{dV_c}{dt}$$

2 point

$$\frac{dV_c}{dt} = \frac{I_c}{C} - \frac{V_c}{CR}$$

1 point

$$\begin{bmatrix} \frac{dI_c}{dt} \\ \frac{dV_c}{dt} \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{CR} \end{bmatrix} \begin{bmatrix} I_c \\ V_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_s$$

b

$$\frac{d^2 V_c}{dt^2} = \frac{1}{C} \frac{dI_c}{dt} - \frac{1}{CR} \frac{dV_c}{dt}$$

5

$$\frac{d^2 V_c}{dt^2} + \frac{1}{CR} \frac{dV_c}{dt} = \frac{1}{C} \left[\frac{V_s}{L} - \frac{V_c}{L} \right]$$

$$\frac{d^2 V_c}{dt^2} + \frac{1}{CR} \frac{dV_c}{dt} + \frac{1}{LC} V_c = \frac{1}{LC} V_s$$

5

Q6

$$\frac{d^2 V_c}{dt^2} + 7 \frac{dV_c}{dt} + 10V_c = 10$$

Step ① $V_{cp} = K$

3 point

$$\frac{d^2}{dt^2} K + 7 \frac{d}{dt} K + 10K = 10$$

$$K = 1 \quad V_{cp} = 1 \text{ Volt}$$

1 point

1 point

Step ② char-equation $s^2 + 7s + 10 = 0 = (s+2)(s+5) = 0$

$s_1 = -2$ natural frequency
 $s_2 = -5$

$$V_{ch} = K_1 e^{-2t} + K_2 e^{-5t}$$

1 point

Step ③

$$V_c = V_{cp} + V_{ch} = 1 + K_1 e^{-2t} + K_2 e^{-5t}$$

1 point

Step ④

$$V_c(0) = 0 \quad 1 + K_1 + K_2 = 0$$

1 point

$$\frac{dV_c}{dt} = -2K_1 e^{-2t} - 5K_2 e^{-5t}$$

$$\frac{dV_c}{dt}(0) = -2K_1 - 5K_2 = 0$$

$$K_1 + K_2 = -1$$

$$2K_1 + 5K_2 = 0$$

$$K_1 = \frac{-5K_2}{2}$$

2 point

$$-\frac{5}{2}K_2 + K_2 = -1$$

$$K_2 = \frac{2}{3}$$

$$K_1 = -\frac{5}{3}$$

$$-5K_2 + 2K_2 = -2$$

$$-3K_2 = -2$$

$$V_c(t) = 1 - \frac{5}{3} e^{-2t} + \frac{2}{3} e^{-5t}$$

2 point


Q6

$$\frac{d^2 V_c}{dt^2} + A \frac{dV_c}{dt} + B V_c = 10$$

$$s_{1,2} = \frac{-A \pm \sqrt{A^2 - 4B}}{2}$$

- (a) Overdamped $A^2 - 4B > 0$
- (b) Critically - damped $A^2 - 4B = 0 \quad A^2 = 4B$
- (c) Underdamped $A^2 - 4B < 0$
- (d) Purely sinusoidal $A = 0, B > 0$


Q7

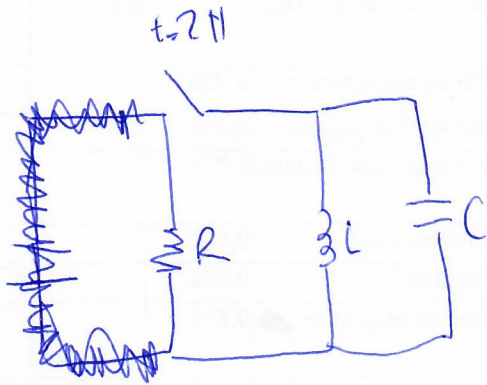

$v_c(t) = 1 \text{ Volt}$
 $i_c(t) = 0 \text{ Ampere}$

$L = 1 \text{ Henry}$
 $C = 1 \text{ Farad}$

$$0 < t < 2 \pi$$

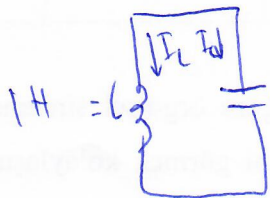

$I_L + I_C = 0$
 $I_C + C \frac{dv_c}{dt} = 0$

$v_L = v_c = L \frac{dI_L}{dt}$
 $I_L + C L \frac{d^2 I_L}{dt^2} = 0$

$\rightarrow s^2 H = 0$
 $s_{1,2} = \pm j$

$\frac{dI_L}{dt} + \frac{1}{LC} I_L = 0$
 $\frac{d^2 I_L}{dt^2} + I_C = 0$
 $L \frac{dI_L}{dt} = v_c \quad \frac{dI_L}{dt} = \frac{v_c}{L}$

$$I_L(t) = K_1 \sin(t) + K_2 \cos(t)$$

$\frac{dI_L}{dt}(0) = \frac{v_c(0)}{L} = \frac{1}{1} = 1$ (1)

$$I_L(0) = 0 \text{ Ampere}$$

$I_L(0) = 0 = K_1 \sin(0) + K_2 \cos(0)$
 $0 = K_2 \cos(0) \rightarrow K_2 = 0$

$$\Rightarrow I_L = K_1 \sin(t)$$

$\frac{dI_L}{dt}(0) = K_1 \cos(0) = 1$

$$K_1 = 1$$

$I_L(t) = \sin(t)$ (2)

$$I_L(2\pi) = \sin(2\pi) = 0 \text{ Ampere}$$


$$V_C = L \frac{dI_L}{dt} = 1 \frac{d}{dt} \sin(t) = \cos(t)$$

$$V_C(2\pi) = \cos(2\pi) = 1 \text{ Volt}$$

$$t > 2\pi$$

$$V_C(t) = L \frac{dI_C}{dt} = 1 \frac{d}{dt} \sin(t) = \cos(t)$$

(1)

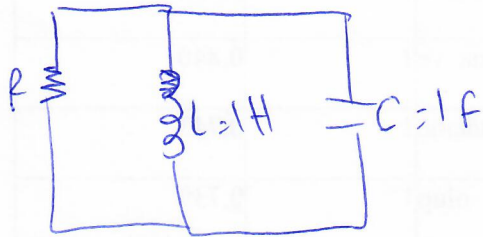

$$\frac{V_C}{R} + C \frac{dV_C}{dt} + I_C = 0$$

$$\frac{1}{R} \frac{dV_C}{dt} + C \frac{d^2V_C}{dt^2} + \frac{dI_C}{dt} = 0$$

$$R = \frac{1}{2} \Omega$$

(3)

$$\frac{1}{R} \frac{dV_C}{dt} + C \frac{d^2V_C}{dt^2} + \frac{V_C}{L} = 0$$

$$L = 1 \text{ H}$$

$$C = 1 \text{ F}$$


$$\frac{d^2V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{1}{LC} V_C = 0$$

homogeneous equations

$$\frac{d^2V_C}{dt^2} + 2 \frac{dV_C}{dt} + V_C = 0$$

$$\text{similarly } \frac{d^2I_C}{dt^2} + 2 \frac{dI_C}{dt} + I_C = 0$$

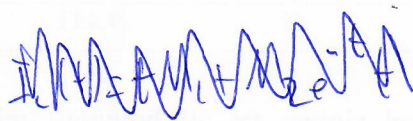(1) char-equation = $(s^2 + 2s + 1) = (s+1)^2 \rightarrow s_1 = -1 \rightarrow$ critically damped
 $\rightarrow s_2 = -1$



$$I_C(t) = M_1 e^{-t} + M_2 t e^{-t}$$

$$I_C(2\pi) = \sin(2\pi) = 0$$

$$I_C(2\pi) = M_1 e^{-2\pi} + M_2 2\pi e^{-2\pi}$$

(1)

$$I_C(t) = M_1 e^{-(t-2\pi)} + M_2 (t-2\pi) e^{-(t-2\pi)}$$

$$I_C(2\pi^+) = I_C(2\pi^-) = 0 \text{ Ampere}$$

$$L \frac{dI_C}{dt} = V_C \quad \left. \frac{dI_C}{dt} \right|_{t=2\pi^+} = \frac{V_C(2\pi^+)}{L} = \frac{1}{1}$$

$$0 = I_c(2\pi^+) = M_1 = 0$$

$$\text{then } I_c(t) = M_2 (t - 2\pi) e^{-(t-2\pi)} = M_2 e^{2\pi} (t - 2\pi) e^{-t}$$

~~$$\frac{dI_c}{dt} = M_2 e^{-(t-2\pi)} + (-1)(t-2\pi) e^{-(t-2\pi)} M_2$$~~

$$\frac{dI_c}{dt} = M_2 e^{2\pi} [1 e^{-t} + (t-2\pi)(-1) e^{-t}]$$

$$\left. \frac{dI_c}{dt} \right|_{t=2\pi} = M_2 = 1$$

$$I_c(t) = (t - 2\pi) e^{-(t-2\pi)} = (t - 2\pi) e^{2\pi} e^{-t}$$

~~$$L \frac{dI_c}{dt} = V_c = e^{-(t-2\pi)} + (-1)(t-2\pi) e^{-(t-2\pi)}$$~~

$$= e^{2\pi} [1 e^{-t} + (-1) e^{-t} (t-2\pi)]$$

$$V_c(t) = e^{-(t-2\pi)} - (t-2\pi) e^{-(t-2\pi)}$$

$$V_c(t) = \begin{cases} \cos(t), & 0 \leq t < 2\pi \\ e^{-(t-2\pi)} - (t-2\pi) e^{-(t-2\pi)}, & 2\pi \leq t \end{cases}$$

$$I_c(t) = \begin{cases} \sin(t), & 0 \leq t < 2\pi \\ (t-2\pi) e^{-(t-2\pi)}, & 2\pi \leq t \end{cases}$$