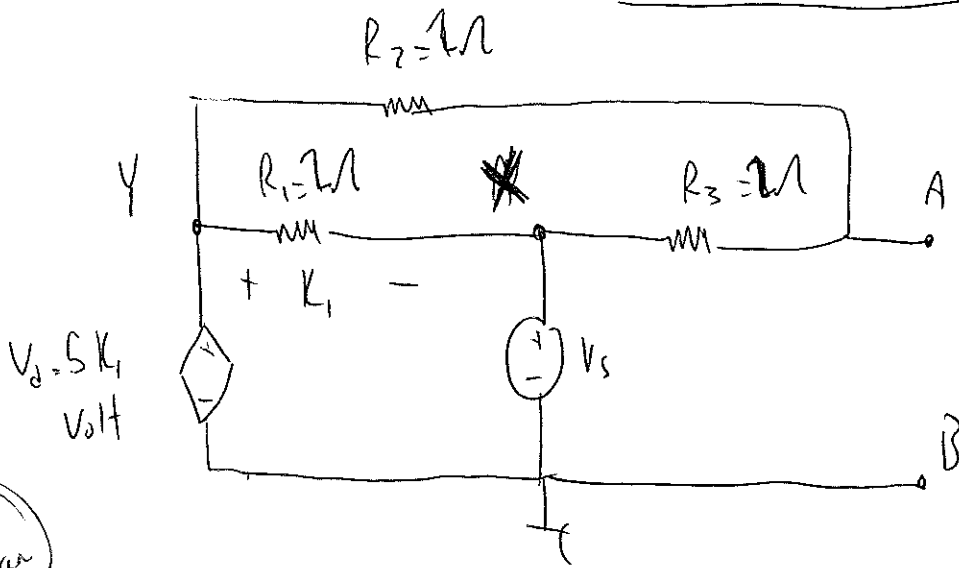


(Q1)



10 pvar

For  $V_{TH}$  use the same circuit and find  $V_{AB} = V_{open-circuit} = V_{TH}$

$X = V_s = 10 \text{ Volt}$  (2)

$Y = 5K_1 = V_d$

$V_1 - X = K_1$   
 $5K_1 - 10 = K_1$

$4K_1 = 10$

$K_1 = 2.5$

$V_1 = 5K_1 = 12.5$


$\frac{V_1 - A}{R_2} = \frac{A - X}{R_3}$

(2)  $\frac{12.5 - A}{2} = \frac{A - 10}{2}$

$2A = 22.5 \quad A = 11.25 \text{ Volt}$

$B = 0 \quad V_{TH} = V_{AB} = V_{open-circuit} = 11.75 \text{ Volt}$

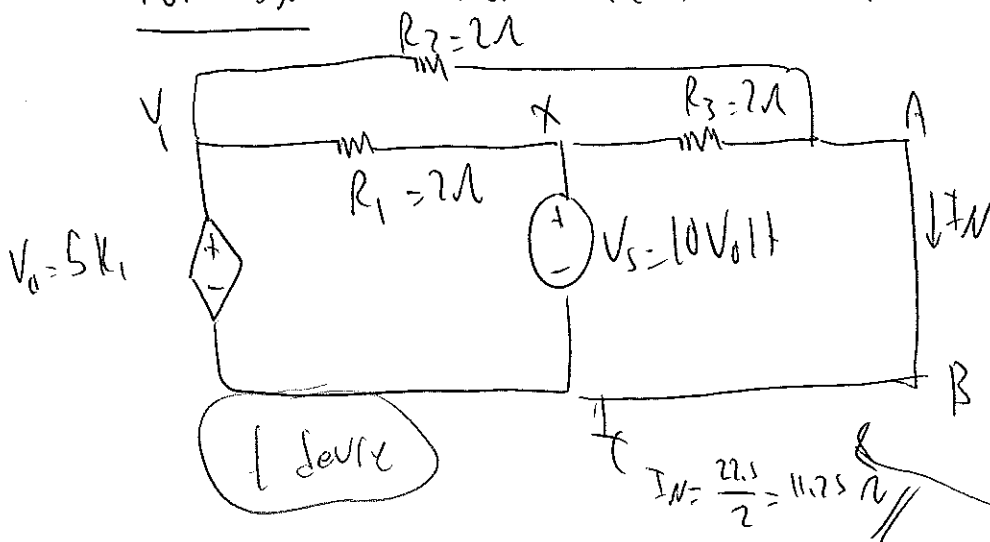For  $I_N$  short circuit A and B terminals  $I_N = I_{short-circuit}$



$X = 10 \text{ Volt}$

$Y = 5K_1$

$V_1 - X = K_1$  (3)  $4K_1 = 10$

$5K_1 - 10 = K_1 \quad K_1 = 2.5$

$Y = 12.5$


$A = B = 0$  (4)  
 $I_N = \frac{Y - A}{R_2} + \frac{X - A}{R_3} = \frac{12.5 - 0}{2} + \frac{10 - 0}{2}$

$I_N = \frac{22.5}{2} = 11.25 \text{ A}$

(Q1)  $I_N = 11.75$        $V_{TH} = 11.75$  (1)

$R_{TH} = \frac{V_{TH}}{I_N} = \frac{11.75}{11.75} = 1 \Omega$  (1)

Thevenin Circuit

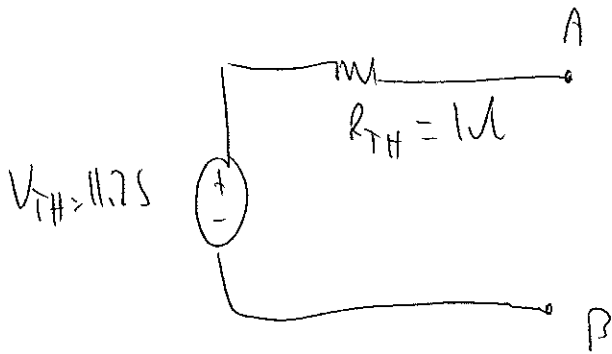

(Q2)  $x'' + 4x = \sin(t)$  → char equation  $s^2 + 4 = 0$  (1)

(1) natural frequencies  
 $s_{1,2} = \pm 2j$

(a)  $x_n(t) = K_1 \sin(2t) + K_2 \cos(2t)$  (2)

(b)  $x_p(t) = M_1 \cos(t) + M_2 \sin(t)$  (2)

$\frac{d^2}{dt^2} x_p(t) + 4x_p(t) = \sin(t)$  (2)

$-M_1 \cos(2t) - M_2 \sin(2t) = \sin(t)$        $M_1 = 0$        $M_2 = -1$

$x_p(t) = -\sin(t)$  (1)

(c)  $x(t) = x_n(t) + x_p(t) = K_1 (\sin(2t)) + K_2 (\cos(2t)) - \sin(t)$  (1)

(d)  $x(0) = 5$        $x(0) = K_1 \times 0 + K_2 \times 1 + 0 = 5$        $K_2 = 5$

$x(t) = K_1 \sin(2t) + 5 \cos(2t) - \sin(t)$  (4)

$x'(t) = 2K_1 \cos(2t) - 5 \times 2 \sin(2t) - \cos(t)$

$x'(0) = 2K_1 - 1 = 2$

$K_1 = \frac{3}{2}$

$x(t) = \frac{3}{2} \sin(2t) + 5 \cos(2t) - \sin(t)$  (1)

Prosedür (S)

(Q2)  $x'' + 4x = \sin(t)$   $s^2 + 4 = 0 \quad s_{1,2} = \pm 2j$  (2)

(a)  $x_h = K_1 \sin(2t) + K_2 \cos(2t)$  (2)

(b)  $x_p = M_1 \cos(t) + M_2 \sin(t)$  (2)  $x_p' = -M_1 \sin(t) + M_2 \cos(t)$

$\frac{d^2}{dt^2} x_p + 4x_p = \sin(t)$   $x_p'' = -M_1 \cos(t) - M_2 \sin(t)$

$[-M_1 \cos(t) + (-M_2) \sin(t)] + 4[M_1 \cos(t) + M_2 \sin(t)] = \sin(t)$

$3M_1 \cos(t) + 3M_2 \sin(t) = \sin(t)$   $M_1 = 0$   
 $M_2 = \frac{1}{3}$  (2)

$x_p = \frac{1}{3} \sin(t)$  (1)

(c)  $x(t) = x_h(t) + x_p(t) = K_1 \sin(2t) + K_2 \cos(2t) - \frac{1}{3} \sin(t)$  (4)

(d)  $2 = x(0) = K_1 \sin(0) + K_2 \cos(0) - \frac{1}{3} \sin(0)$

$K_2 = 5$   
 $x'(t) = 2K_1 \cos(2t) - 2K_2 \sin(2t) - \frac{1}{3} \cos(t)$


prosedur 5

$2 = x'(0) = 2K_1 - \frac{1}{3}$   $2K_1 = 2 + \frac{1}{3}$   $2K_1 = \frac{7}{3}$   $K_1 = \frac{7}{6}$

$x(t) = \frac{7}{6} \sin(2t) + 5 \cos(2t) - \frac{1}{3} \sin(t)$

S pwan

Q3

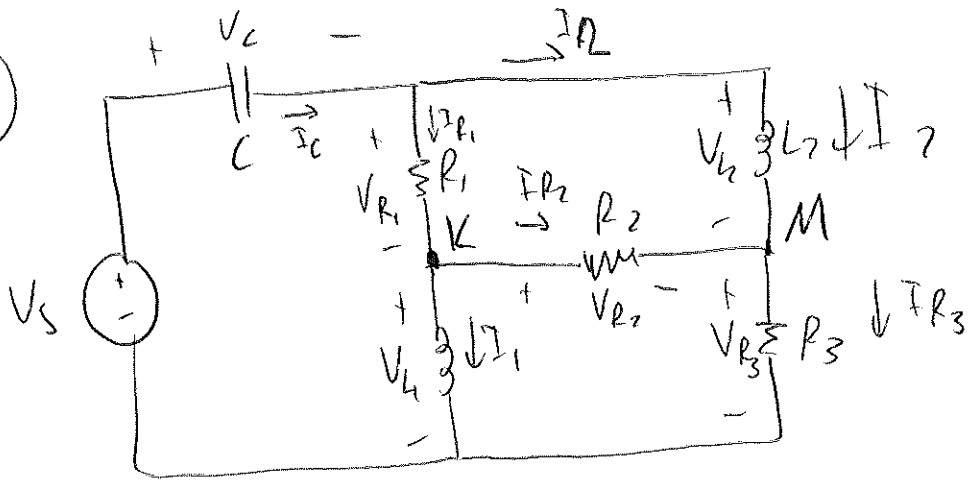

$$R_1 = R_2 = R_3 = 1 \Omega$$

$$L_1 = L_2 = 1 \text{ H}$$

$$C = 2 \text{ F}$$

$$V_s = V_c + V_{R_1} + V_{L_1}$$

$$V_s = V_c + V_{L_2} + V_{R_3}$$

$$V_s = V_c + I_{R_1} R_1 + L_1 \frac{dI_1}{dt}$$

$$V_s = V_c + L_2 \frac{dI_2}{dt} + I_{R_3} R_3$$

$$I_{R_1} = I_c - I_2$$

$$I_{R_3} = I_c - I_1$$

$$V_s = V_c + (I_c - I_2) R_1 + L_1 \frac{dI_1}{dt}$$

$$V_s = V_c + L_2 \frac{dI_2}{dt} + R_3 (I_c - I_1)$$

$$V_s = V_c + \left( C \frac{dV_c}{dt} - I_2 \right) R_1 + L_1 \frac{dI_1}{dt}$$

$$V_s = V_c + L_2 \frac{dI_2}{dt} + R_3 \left[ C \frac{dV_c}{dt} - I_1 \right]$$

$$V_s = V_c + \left[ 2 \frac{dV_c}{dt} - I_2 \right] \times 1 + \frac{dI_1}{dt}$$

$$V_s = V_c + \frac{dI_2}{dt} + 1 \times \left[ 2 \frac{dV_c}{dt} - I_1 \right]$$

$$I_c = I_{R_1} + I_2 = I_1 + I_{R_2} + I_2$$

$$I_{R_2} = \frac{K - M}{R_2} = \frac{V_{L_1} - M}{R_2}$$

$$I_c = I_1 + I_2 + I_{R_2}$$

$$M = V_s - V_c - V_{L_2}$$

$$C \frac{dV_c}{dt} = I_1 + I_2 + \frac{V_{L_1} - (V_s - V_c + V_{L_2})}{R_2}$$

$$\rightarrow 2 \frac{dV_c}{dt} = I_1 + I_2 + \frac{dI_1}{dt} + \frac{dI_2}{dt} + V_c - V_s$$

$$\boxed{2 \frac{dV_c}{dt} = I_1 + I_2 + \frac{L_1 \frac{dI_1}{dt}}{1} + \frac{L_2 \frac{dI_2}{dt}}{1} + V_c - V_s}$$

$C = 2 \text{ Farad}$


$L_1 = 1 \text{ H}, L_2 = 1 \text{ H}$

$R_1 = 1 \Omega, R_2 = 1 \Omega, R_3 = 1 \Omega$

$R_3 = 1 \Omega$

$C = 2 \text{ Farad}$

(a)

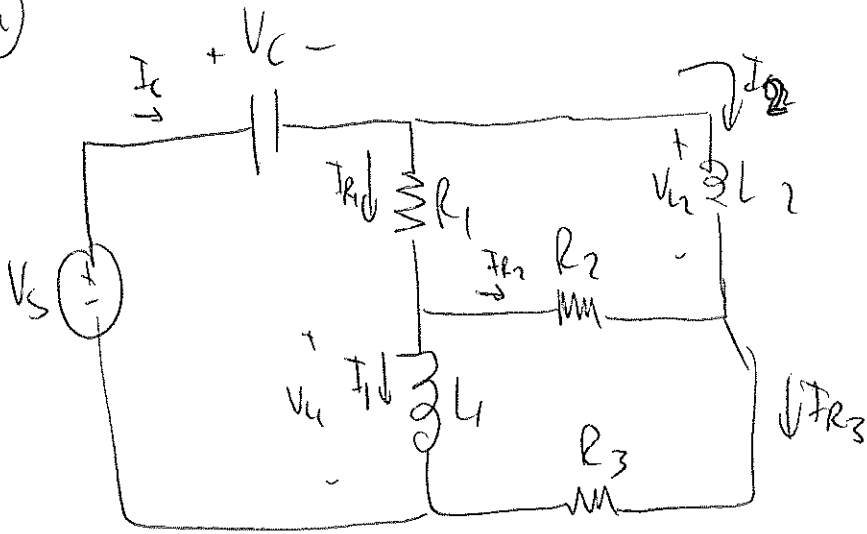

$$I_{R_1} = \frac{V_s - V_c - V_{L_1}}{R_1} = \frac{V_s - V_c - L_1 \frac{dI_1}{dt}}{R_1} = \frac{V_s - V_c - \frac{dI_1}{dt}}{1} = V_s - V_c - \frac{dI_1}{dt} = I_{R_1}$$

1 puan

$$I_c = I_{R_1} + I_{L_2} \quad (1 \text{ puan})$$

$$\frac{V_{L_2} - (V_s - V_c - V_{L_2})}{R_2} = I_{R_2} \quad (1 \text{ puan})$$

$$C \frac{dV_c}{dt} = V_s - V_c - \frac{dI_1}{dt} + I_{L_2}$$

$$2 \frac{dV_c}{dt} = V_s - V_c - \frac{dI_1}{dt} + I_{L_2} \quad *$$

2 puan

$$\frac{L_1 \frac{dI_1}{dt} - (V_s - V_c - L_2 \frac{dI_2}{dt})}{R_2} = I_{R_2}$$

$$\frac{dI_1}{dt} + \frac{dI_2}{dt} - V_s + V_c = I_{R_2} \quad (2 \text{ puan})$$

$$I_{R_1} = I_1 + I_{R_2} \quad (1 \text{ puan})$$

$$I_{R_3} = \frac{V_s - V_c - V_{L_2}}{R_3} = \frac{V_s - V_c - L_2 \frac{dI_2}{dt}}{R_3}$$

$$V_s - V_c - \frac{dI_1}{dt} = I_1 + \frac{dI_1}{dt} + \frac{dI_2}{dt} - V_s + V_c$$

$$I_{R_3} = \frac{V_s - V_c - \frac{dI_2}{dt}}{1} \quad (1 \text{ puan})$$

$$2V_s = 2 \frac{dI_1}{dt} + I_1 + \frac{dI_2}{dt} + I_{R_2} \quad **$$

2 puan

$$I_1 + I_{R_3} = I_c \quad (1 \text{ puan})$$

$$I_1 + V_s - V_c - \frac{dI_2}{dt} = C \frac{dV_c}{dt}$$

$$2 \frac{dV_c}{dt} = V_s - V_c - \frac{dI_2}{dt} + I_1$$

2 puan

güçler 8

\*\*\*

\* and \*\*\*

$$V_s - V_c - \frac{dI_2}{dt} + I_1 = V_c - V_c - \frac{dI_1}{dt} + I_2 \Rightarrow \frac{dI_1}{dt} + I_1 = \frac{dI_2}{dt} + I_2$$

$$\frac{dI_1}{dt} = \frac{dI_2}{dt} + I_2 - I_1 \quad \text{and} \quad \frac{dI_2}{dt} = \frac{dI_1}{dt} + I_1 - I_2$$

↓ put in \*\*

$$2V_s = 2 \left[ \frac{dI_2}{dt} + I_2 - I_1 \right] + I_1 + \frac{dI_2}{dt} + 2V_c$$

$$2V_s = 2 \frac{dI_1}{dt} + I_1 + \left[ \frac{dI_1}{dt} + I_1 - I_2 \right] + 2V_c$$

$$2V_s = 3 \frac{dI_2}{dt} + 2I_2 - I_1 + 2V_c$$

$$2V_s = 3 \frac{dI_1}{dt} + 2I_1 - I_2 + 2V_c$$

$$\frac{dI_2}{dt} = \frac{2}{3} V_s - \frac{2}{3} I_2 + \frac{1}{3} I_1 - \frac{2}{3} V_c$$

$$\frac{dI_1}{dt} = \frac{2}{3} V_s - \frac{2}{3} I_1 + \frac{1}{3} I_2 - \frac{2}{3} V_c$$

$$2 \frac{dV_c}{dt} = V_s - V_c - \frac{dI_1}{dt} + I_2 = V_s - V_c - \left[ \frac{2}{3} V_s - \frac{2}{3} I_1 + \frac{1}{3} I_2 - \frac{2}{3} V_c \right] + I_2$$

$$2 \frac{dV_c}{dt} = \frac{1}{3} V_s - \frac{1}{3} V_c + \frac{2}{3} I_1 + \frac{2}{3} I_2$$

2 puan

$$\frac{dV_c}{dt} = \frac{1}{6} V_s - \frac{1}{6} V_c + \frac{1}{3} I_1 + \frac{1}{3} I_2$$

$$\begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \\ \frac{dV_c}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{2}{3} & \frac{1}{3} & -\frac{2}{3} \\ \frac{1}{3} & -\frac{2}{3} & -\frac{2}{3} \\ \frac{1}{6} & \frac{1}{6} & -\frac{1}{6} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_c \end{bmatrix} + \begin{bmatrix} \frac{2}{3} \\ \frac{2}{3} \\ \frac{1}{6} \end{bmatrix} V_s$$

2 puan

(b)

$$\frac{dV_c}{dt} = \frac{1}{3} I_1 + \frac{1}{3} I_2 - \frac{1}{6} V_c + \frac{1}{6} V_s$$

$$\frac{d^2 V_c}{dt^2} = \frac{1}{3} \frac{dI_1}{dt} + \frac{1}{3} \frac{dI_2}{dt} - \frac{1}{6} \frac{dV_c}{dt} + \frac{1}{6} \frac{dV_s}{dt}$$

$$\frac{d^3 V_c}{dt^3} = \frac{1}{3} \frac{d^2 I_1}{dt^2} + \frac{1}{3} \frac{d^2 I_2}{dt^2} - \frac{1}{6} \frac{d^2 V_c}{dt^2} + \frac{1}{6} \frac{d^2 V_s}{dt^2}$$

$$\frac{d^3 V_c}{dt^3} + \frac{1}{6} \frac{d^2 V_c}{dt^2} = \frac{1}{3} \left[ \frac{d^2 I_1}{dt^2} + \frac{d^2 I_2}{dt^2} \right] + \frac{1}{6} \frac{d^2 V_s}{dt^2}$$

$$\frac{d^3 V_c}{dt^3} + \frac{1}{6} \frac{d^2 V_c}{dt^2} = \frac{1}{3} \left[ -\frac{1}{3} \frac{dI_1}{dt} - \frac{1}{3} \frac{dI_2}{dt} - \frac{4}{3} \frac{dV_c}{dt} + \frac{4}{3} \frac{dV_s}{dt} \right] + \frac{1}{6} \frac{d^2 V_s}{dt^2}$$

$$\frac{d^3 V_c}{dt^3} + \frac{1}{6} \frac{d^2 V_c}{dt^2} + \frac{4}{9} \frac{dV_c}{dt} = -\frac{1}{9} \left[ \frac{dI_1}{dt} + \frac{dI_2}{dt} \right] + \frac{4}{9} \frac{dV_s}{dt} + \frac{1}{6} \frac{d^2 V_s}{dt^2}$$

$$\frac{d^2 I_1}{dt^2} = -\frac{2}{3} \frac{dI_1}{dt} + \frac{1}{3} \frac{dI_2}{dt} - \frac{2}{3} \frac{dV_c}{dt} + \frac{2}{3} \frac{dV_s}{dt}$$

$$\frac{d^2 I_2}{dt^2} = \frac{1}{3} \frac{dI_1}{dt} - \frac{2}{3} \frac{dI_2}{dt} - \frac{2}{3} \frac{dV_c}{dt} + \frac{2}{3} \frac{dV_s}{dt}$$

$$\frac{d^2 I_1}{dt^2} + \frac{d^2 I_2}{dt^2} = -\frac{1}{3} \frac{dI_1}{dt} - \frac{1}{3} \frac{dI_2}{dt} - \frac{4}{3} \frac{dV_c}{dt} + \frac{4}{3} \frac{dV_s}{dt}$$

$$L_1 \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt} = V_{L_1} + V_{L_2} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$V_s - V_c = V_{L_2} - V_{R_2} + V_{L_1} \quad V_s - V_c + V_{R_2} = V_{L_1} + V_{L_2} = L_1 \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$

$$V_s - V_c + R_2 [I_c - I_2 - I_1] = V_{L_1} + V_{L_2} = \frac{dI_1}{dt} + \frac{dI_c}{dt}$$

$$\frac{d^2 V_c}{dt^2} + \frac{1}{6} \frac{d^2 V_c}{dt^2} + \frac{4}{9} \frac{dV_c}{dt} = -\frac{1}{9} \left[ V_s - V_c + 1 \left[ C \frac{dV_c}{dt} - I_2 - I_1 \right] \right] + \frac{4}{9} \frac{dV_s}{dt} + \frac{1}{6} \frac{d^2 V_s}{dt^2}$$

$$\frac{d^3V_C}{dt^3} + \frac{1}{6} \frac{d^2V_C}{dt^2} + \frac{4}{9} \frac{dV_C}{dt} - \frac{1}{9} V_C = -\frac{1}{9} V_S - \frac{2}{9} \frac{dV_C}{dt} + \frac{1}{9} [I_1 + I_2] + \frac{4}{9} \frac{dV_S}{dt} + \frac{1}{6} \frac{d^2V_S}{dt^2}$$

$$\frac{d^3V_C}{dt^3} + \frac{1}{6} \frac{d^2V_C}{dt^2} + \frac{6}{9} \frac{dV_C}{dt} - \frac{1}{9} V_C = -\frac{1}{9} V_S + \frac{1}{9} [I_1 + I_2] + \frac{4}{9} \frac{dV_S}{dt} + \frac{1}{6} \frac{d^2V_S}{dt^2}$$

$$\frac{dV_C}{dt} = \frac{1}{3} [I_1 + I_2] - \frac{1}{6} \frac{dV_C}{dt} + \frac{1}{6} V_S$$

$$I_1 + I_2 = 3 \frac{dV_C}{dt} + \frac{1}{2} V_C - \frac{1}{2} V_S$$

$$\frac{d^3V_C}{dt^3} + \frac{1}{6} \frac{d^2V_C}{dt^2} + \frac{6}{9} \frac{dV_C}{dt} - \frac{1}{9} V_C = -\frac{1}{9} V_S + \frac{1}{9} \left[ 3 \frac{dV_C}{dt} + \frac{1}{2} V_C - \frac{1}{2} V_S \right] + \frac{4}{9} \frac{dV_S}{dt} + \frac{1}{6} \frac{d^2V_S}{dt^2}$$

$$\frac{d^3V_C}{dt^3} + \frac{1}{6} \frac{d^2V_C}{dt^2} + \frac{dV_C}{3 dt} - \frac{1}{9} V_C = -\frac{1}{6} V_S + \frac{4}{9} \frac{dV_S}{dt} + \frac{1}{6} \frac{d^2V_S}{dt^2}$$